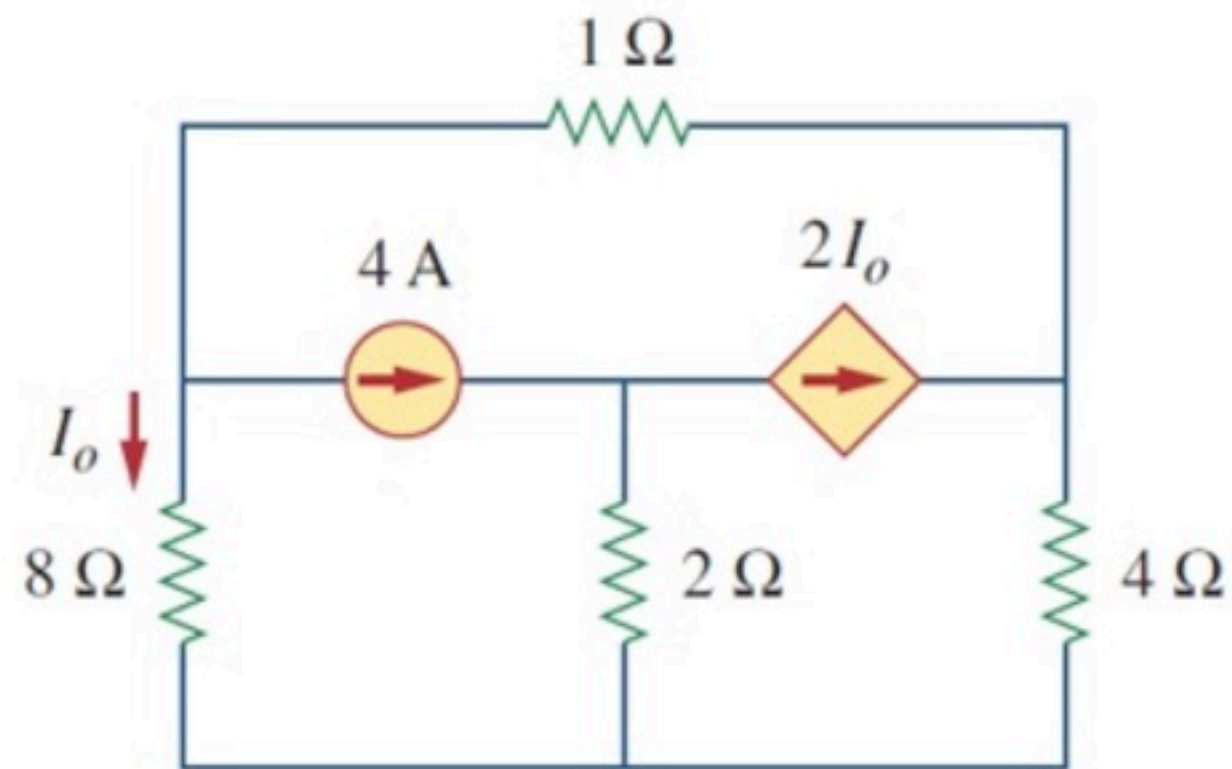


# PP - Nodal Mesh 002

Problem has been graded.

Find  $I_o$ . Solve using nodal analysis.

For extra practice: Afterwards solve again using mesh analysis.



Given Variables:

...

Calculate the following:

$I_o$  (A) :

-4



Hint: Write  $I_o$  as a function of the node voltages