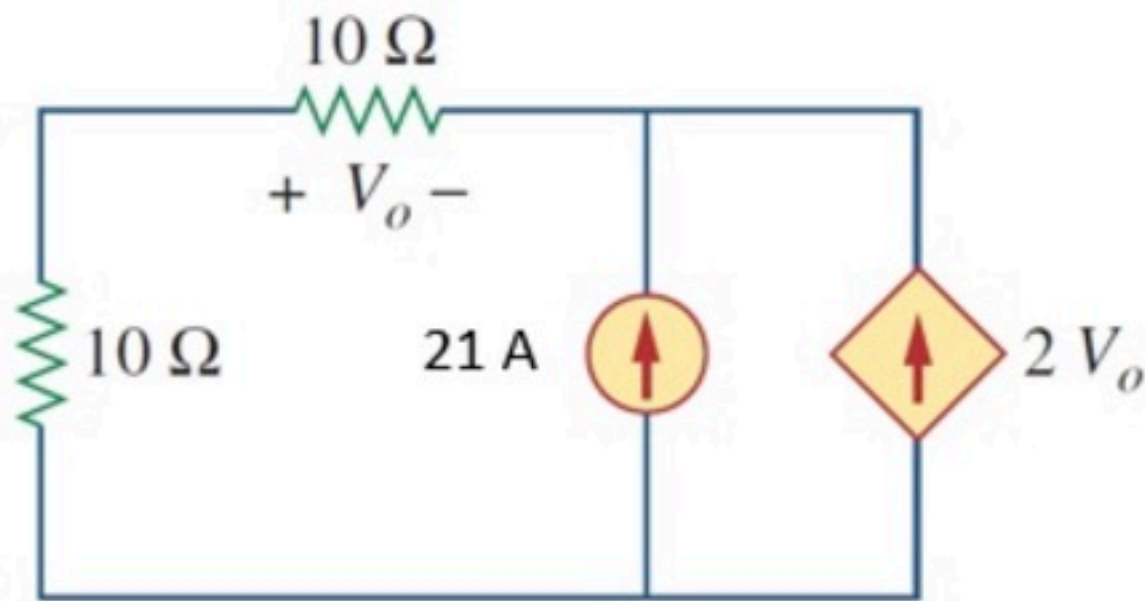


PP - Basic analysis 009

Problem has been graded.

Find the power P supplied by the dependent source.



Given Variables:

...

Calculate the following:

P (W) :

-400



Hint: Use KCL to find the current through the resistors