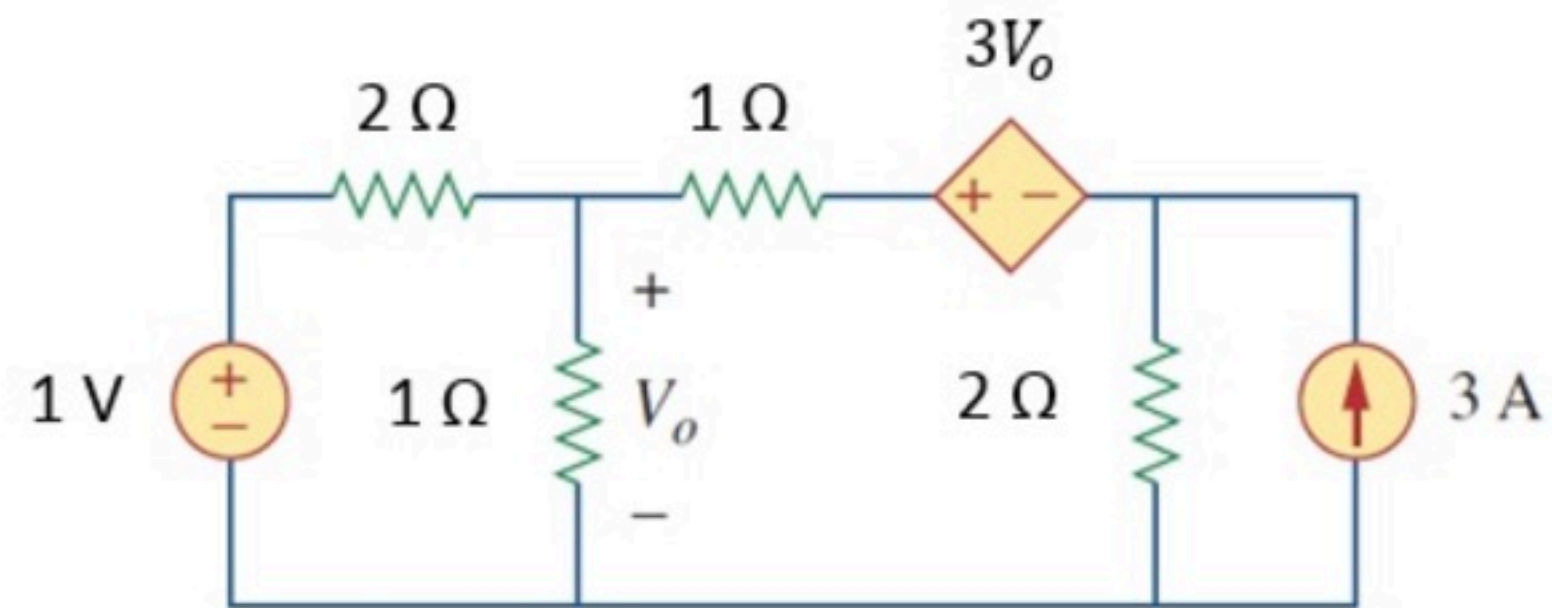


# PP - Nodal Mesh 008

Problem has been graded.

Find  $V_o$ . Solve using nodal analysis.

For extra practice: Afterwards solve again using mesh analysis.



Given Variables:

...

Calculate the following:

$V_o$  (V) :

3



Hint: Use supernode