
## PP Nodal Mesh 017
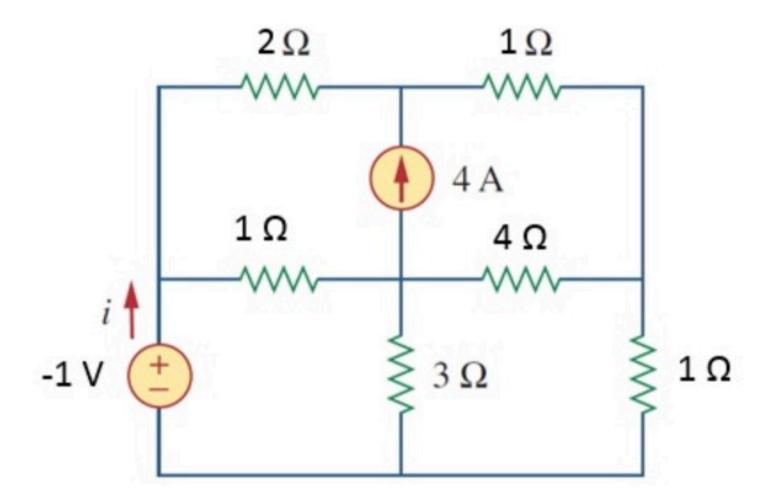
## Unlimited Attempts.

Find the current i. Solve using mesh analysis.

For extra practice: Afterwards solve again using nodal analysis.



Given Variables:

. : . .

Calculate the following:

i (A):

U