Phasors 009


0 of 5 attempts made

$$i_s(t) = A_1 \cdot \cos\left(1000t + \frac{\pi}{2}\right) + A_2 \cdot \cos\left(2000t - \frac{\pi}{2}\right)$$

Assume the system is in steady state. Find the current i_a at times

 $t_1 = 4\pi \text{ ms}: \quad i_a(t_1) = B_1$

 $t_2 = 5\pi \text{ ms}: i_a(t_2) = B_2$

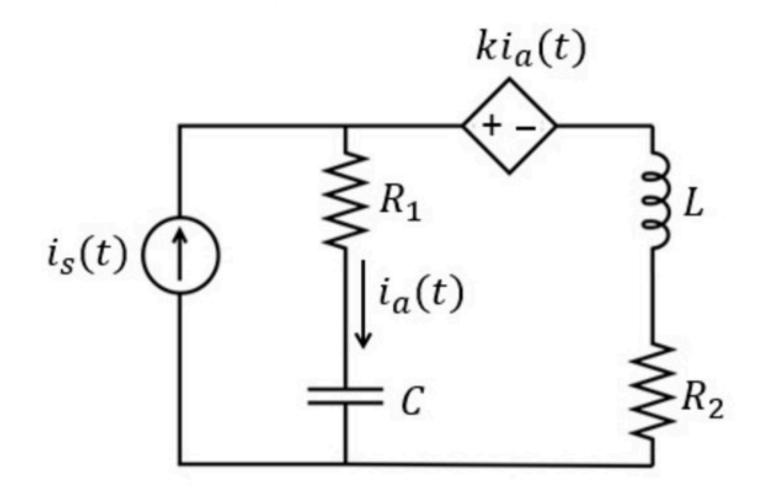

Given Variables:

A1:1A

A2:1A

L:1 mH

C: 250 uF

R1:1 ohm

R2:2 ohm

k:4 V/A

Calculate the following:

B1 (A):

-2.5

B2 (A):

-1.5

 $i_s(t) = A_1 \cdot \cos(1000t + 90) + A_2 \cdot \cos(2000t - 90)$ A1:6 A Assume the system is in steady state. Find the current i_a at times A2:9A $t_1 = 4\pi \text{ ms}: \ \ i_a(t_1) = B_1$ L: 1 mH $t_2 = 5\pi \text{ ms}: \ i_{\pi}(t_2) = B_2$ C: 250 uF $ki_a(t)$ 2 DIFFERENT W! R1:8 ohm R2:2 ohm SUPER POSITION USE k:1 V/A w=1000 . Z, = j. 1000 L = j Zc = 1 = -4 Is= 6 2 = 6 ; $\omega = 2000$. $Z_L = j2000L = 2j$ Zc = 12000 = -2 j Ic= se= = -9; $I_1 = I_3 - I_a \Rightarrow I_a \left(8 + Z_c \right) = 1 \cdot I_a + \left(I_3 - I_a \right) \left(2 + Z_c \right)$ $\Rightarrow \exists_{\alpha} = \exists_{1} \frac{2 + Z_{L}}{\alpha + Z_{L} + Z_{L}}$ (1) $\omega = 1000$: $I_{\alpha} = 6j \frac{(2+j)}{(3-4j+i)} = \frac{6(-1+2j)}{3(3-j)} \frac{(3+j)}{(3+j)} = \frac{2}{10}(-5+5j) = -1+j$ in(t) = 12 cos (1000 t + 1350) (2) $\underline{\omega} = 2000$: $I_{\alpha} = (-9j) \frac{2+2j}{9+2j-21} = 2(1-j) \implies i_{\alpha_1}(t) = 2\sqrt{2} \cos(2\cos t - 45^{\circ})$ (3) ia(t)=ia(t)+ia(t)= V2 cos(1000t+3)+2V2 cos(2000t-4) E = 411.10-3 ia = VI cos(41+3里) +2VI cos(817-里) = VI cos(里) +2VI cos(里) (9) $= l_{1}(-\overline{n}) + 7 l_{1}(\overline{n}) = -1 + 5 = 1$ B,= (A) E= 5TT-10-3. ia=V2 cos(5TT+亞)+2V2 cos(10T-亞)=V2 cos(-亞)+2V2 cos(亚) = 位(症) +7亿(症)=1+7=3 B₂ = 3 A