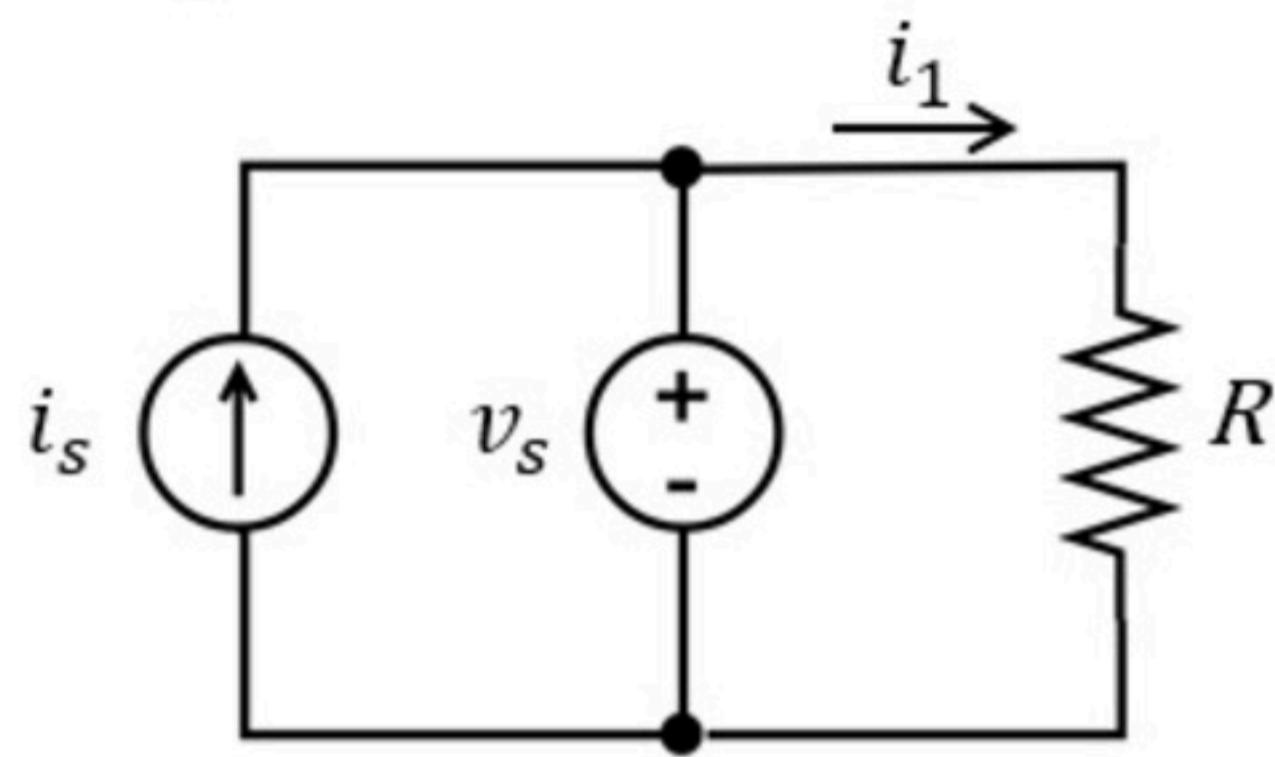


Basic concepts 006

Problem has been graded.

Find the current i_1 and the power P_1 received by the resistor.

Then change the current source to 5A. Recalculate the current i_1 (renaming it to i_2) and the power P_2 received by the resistor.



Given Variables:

v_s : 16 V

i_s : 4 A

R : 8 ohm

Calculate the following:

i_1 (A) :

P_1 (W) :

i_2 (A) :

P_2 (W) :


Find the current i_1 and the power P_1 received by the resistor.

$$V_s = 16 \text{ V}$$

Then change the current source to 5A. Recalculate the current i_1 (renaming it to i_2) and the power P_2 received by the resistor.

$$I_s = 4 \text{ A}$$

$$R = 16 \Omega$$

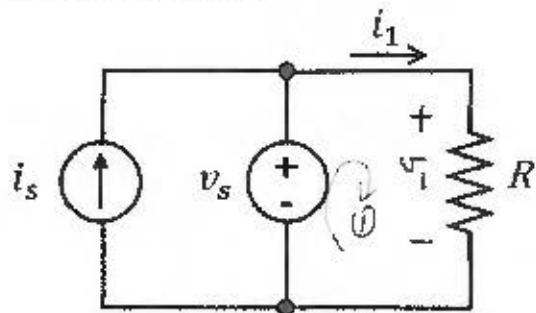

$$\text{KVL} \Rightarrow V_s = V_1 \Rightarrow V_1 = 16 \text{ V}$$

$$i_1 = \frac{V_1}{R} = \frac{16}{16} \Rightarrow i_1 = 1 \text{ A}$$

$$P_1 = i_1^2 \cdot R = 1 \cdot 16 \Rightarrow P_1 = 16 \text{ W}$$

received

When $i_s = 5 \text{ A}$

$$V_1 \text{ still the same. } V_1 = 16 \text{ V} \Rightarrow i_2 = \frac{V_1}{R}$$

$$i_2 = 1 \text{ A}$$

$$P_2 = i_2^2 R$$


$$P_2 = 16 \text{ W}$$

received

Basic analysis 002

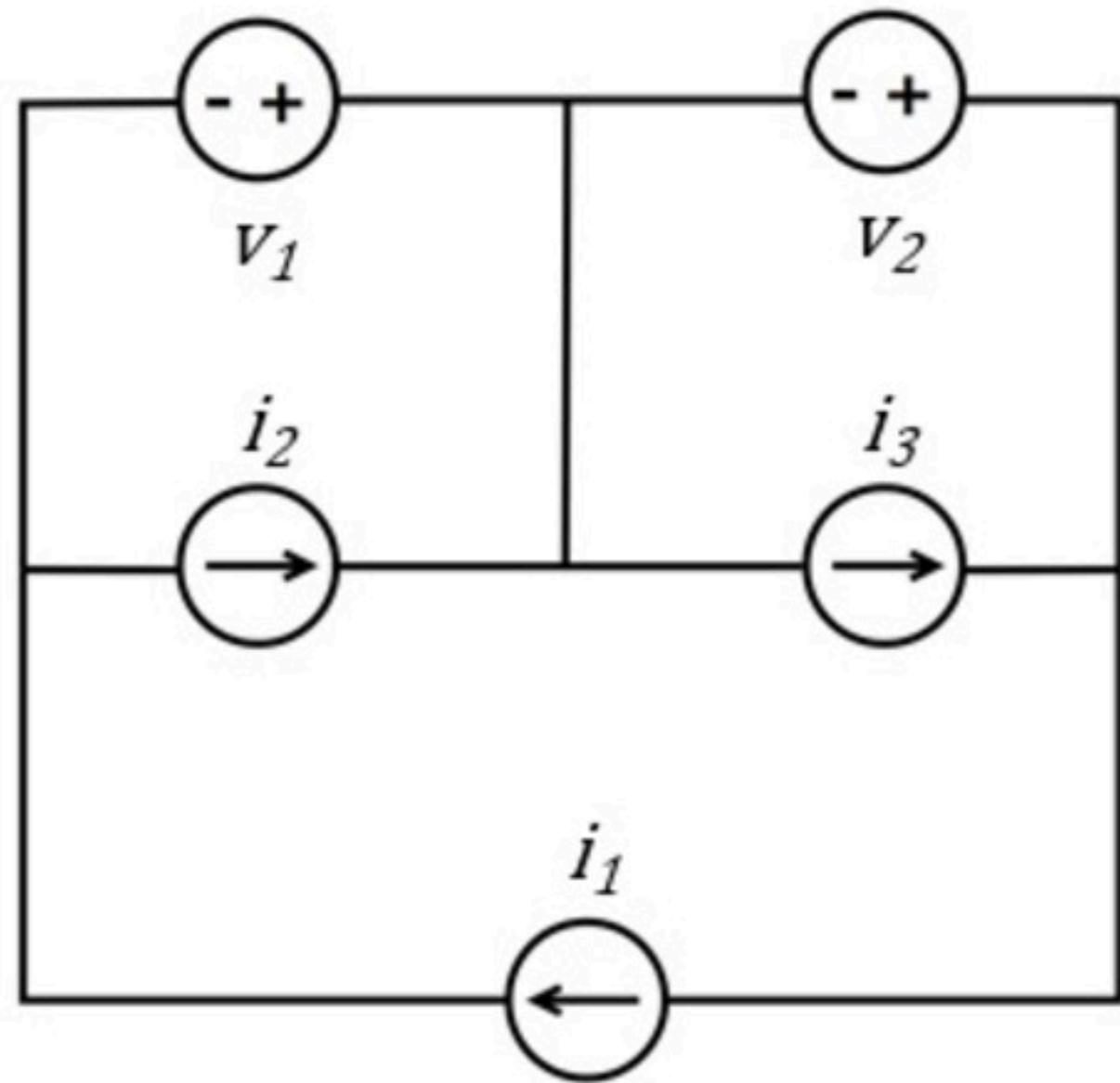Problem has been graded.

Determine the power P_1 supplied by voltage source v_1 and the power P_2 supplied by voltage source v_2 .



Given Variables:

i1 : 4 A

i2 : 2 A

i3 : 3 A

v1 : 3 V

v2 : 4 V

Calculate the following:

P1 (W) :

P2 (W) :

Determine the power P_1 supplied by voltage source v_1
and the power P_2 supplied by voltage source v_2 .


$$i_1 = 4 \text{ A}$$

$$i_2 = 2 \text{ A}$$

$$i_3 = 3 \text{ A}$$

$$v_1 = 3 \text{ V}$$

$$v_2 = 4 \text{ V}$$

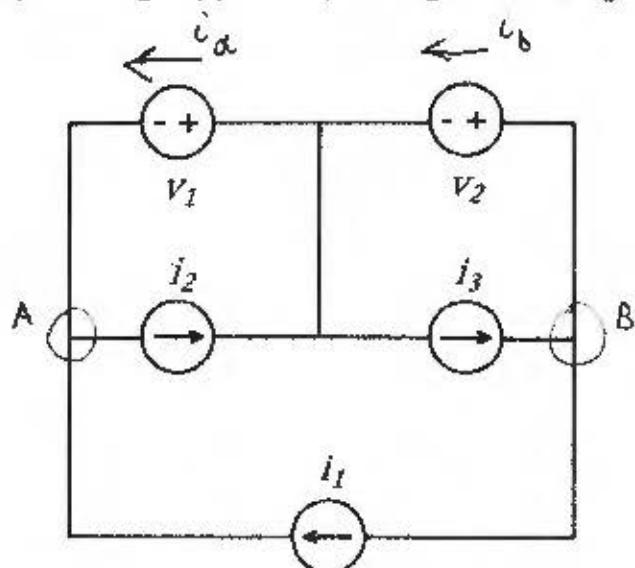

$$\text{KCL @ A} : i_1 + i_a = i_2 \Rightarrow i_a = 2 - 4 = -2 \text{ A}$$

$$P_1 = v_1 \cdot i_a = -6 \text{ W} \quad \text{RECEIVED} \quad \begin{matrix} (\text{PASSIVE SIGN}) \\ \text{CONVENTION} \end{matrix}$$

$$P_1 = 6 \text{ W} \quad \text{SUPPLIED}$$

$$\text{KCL @ B} : i_3 = i_b + i_1 \Rightarrow i_b = 3 - 4 = -1 \text{ A}$$


$$P_2 = v_2 \cdot i_b = -4 \text{ W} \quad \text{RECEIVED}$$

$$P_2 = 4 \text{ W} \quad \text{SUPPLIED}$$

Basic analysis 003

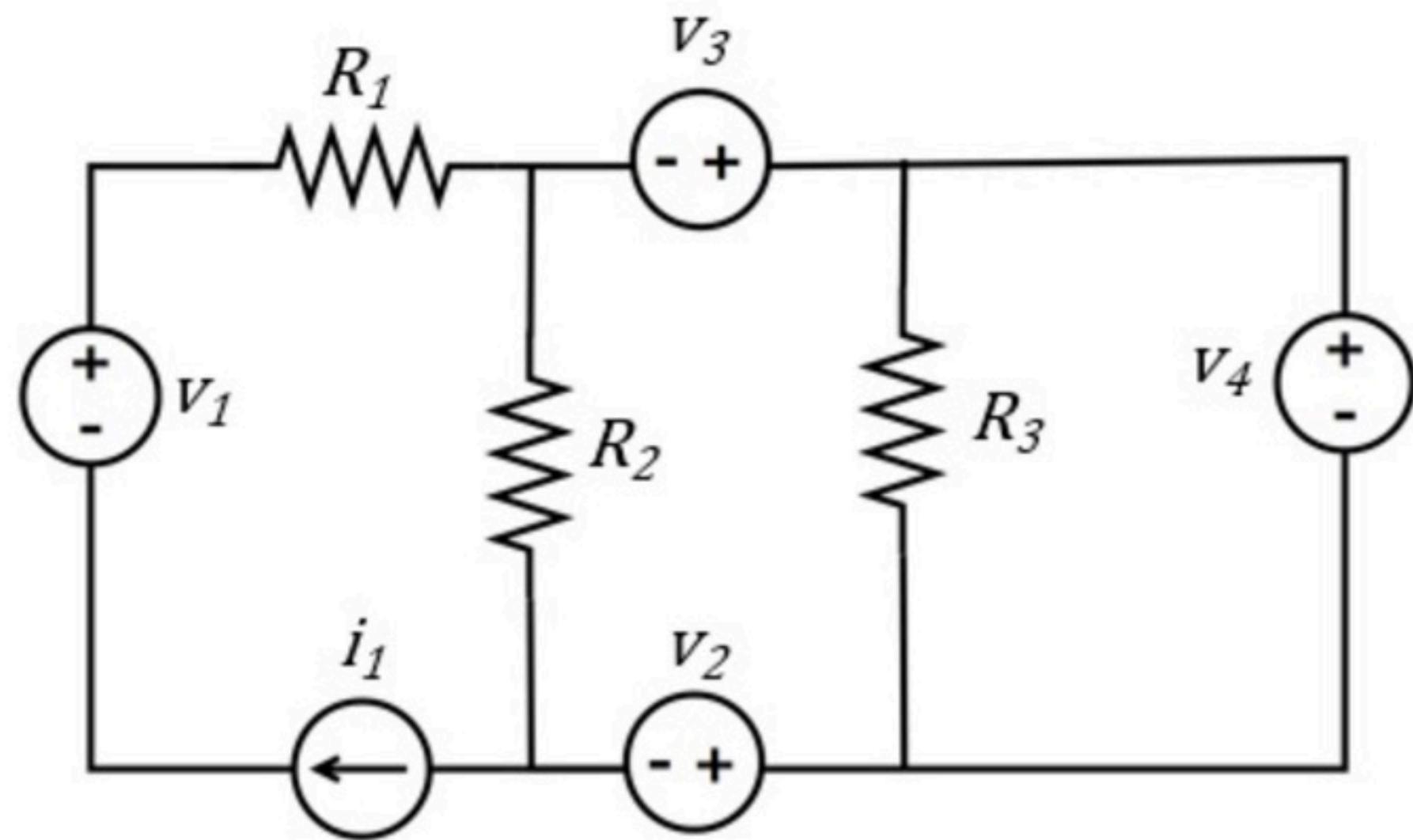Problem has been graded.

Determine the power received by each of the three resistors.



Given Variables:

v1 : 3 V

v2 : 5 V

v3 : 1 V

v4 : 2 V

i1 : 1 A

R1 : 2 ohm

R2 : 3 ohm

R3 : 4 ohm

Calculate the following:

P1 (W) :

P2 (W) :

P3 (W) :

Determine the power received by each of the three resistors.

$$v_1 = 2 \text{ V}$$

$$v_2 = 3 \text{ V}$$

$$v_3 = 4 \text{ V}$$


$$v_4 = 2 \text{ V}$$

$$i_1 = 4 \text{ A}$$

$$R_1 = 2 \Omega$$

$$R_2 = 1 \Omega$$

$$R_3 = 4 \Omega$$

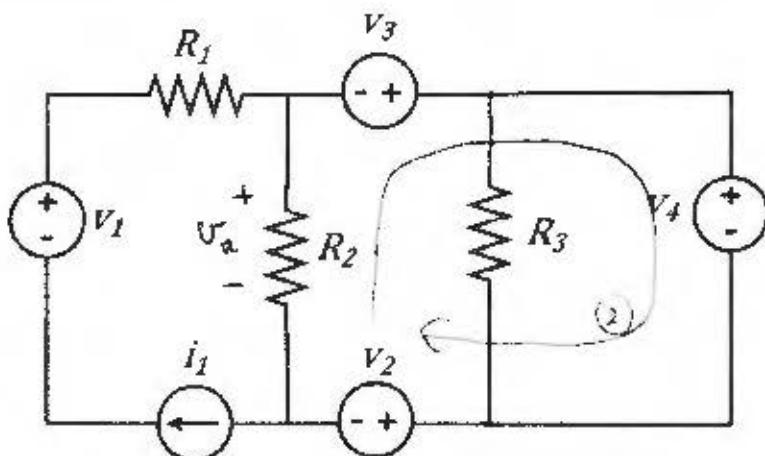

(a) $R_1 : P = R_1 \cdot i_1^2 = 2 \cdot 4^2$

$$P_{R_1} = 32 \text{ W}$$

(b) $R_3 : P = \frac{v_4^2}{R_3} = \frac{4}{4}$

$$P_{R_3} = 1 \text{ W}$$

(c) KVL in (2) : $v_a + v_3 - v_4 - v_2 = 0$

$$v_a = -4 + 2 + 3 = 1 \text{ V}$$

$$P = \frac{v_a^2}{R_2} = \frac{1}{1}$$

$$P_{R_2} = 1 \text{ W}$$

Basic analysis 011

Problem has been graded.


This circuit contains a capacitor (which we will cover in detail later in this course) with a voltage v_C across it.

Voltage v_2 and current i_1 will satisfy the equations shown below (as we will also see later).

Find the coefficients A , D and E .

$$v_C = 10 - 10 \cdot e^{-20t} \text{ V}$$
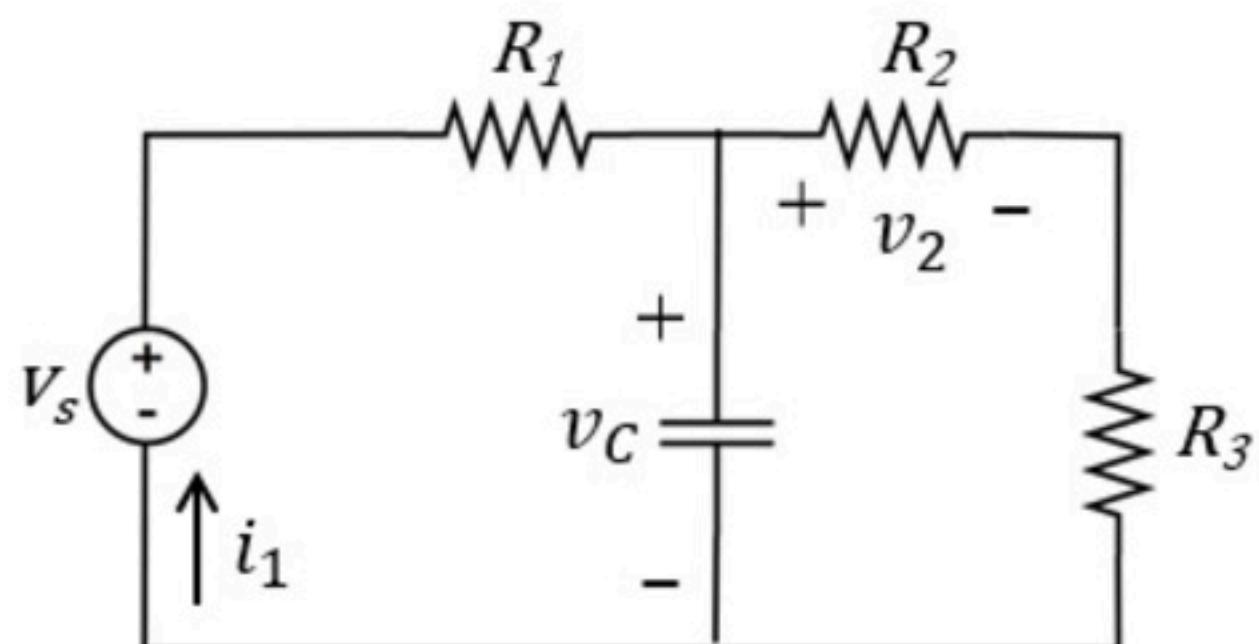
$$v_2 = A + B \cdot e^{-20t} \text{ V} \quad i_1 = D + E \cdot e^{-20t} \text{ A}$$



Given Variables:

$V_s : 20 \text{ V}$

$R_1 : 20 \text{ ohm}$

$R_2 : 7 \text{ ohm}$

$R_3 : 13 \text{ ohm}$

Calculate the following:

$A(.) :$

$B(.) :$

$D(.) :$

$E(.) :$

This circuit contains a capacitor (which we will cover in detail later in this course) with a voltage v_C across it. Voltage v_2 and current i_1 will satisfy the equations shown below (as we will also see later). Find the coefficients A, D and E .

$$V_s = 15 \text{ V}$$


$$R_1 = 10 \Omega$$

$$R_2 = 15 \Omega$$

$$R_3 = 5 \Omega$$

$$v_C = 10 - 10 \cdot e^{-20t} \text{ V}$$
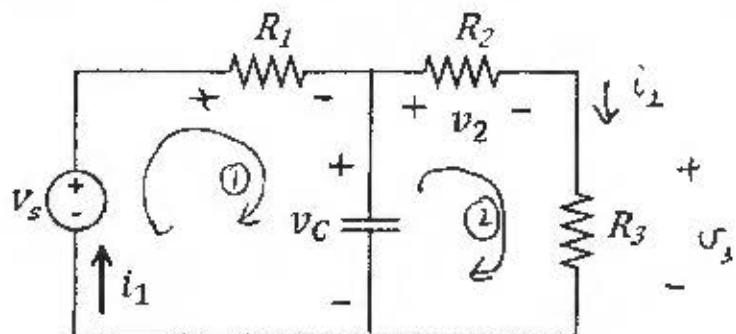
$$v_2 = A + B \cdot e^{-20t} \text{ V} \quad i_1 = D + E \cdot e^{-20t} \text{ A}$$



$$\text{KVL in } \textcircled{1} : V_s - V_{R_1} - V_C = 0 \quad V_{R_1} = i_1 \cdot R_1$$

$$\Rightarrow i_1 = \frac{1}{R_1} \cdot (V_s - V_C) = \frac{1}{10} (15 - 10 + 10 e^{-20t})$$

$$= \frac{1}{10} (5 + 10 e^{-20t})$$

$$D = 0.5$$

$$E = 1$$

$$\text{KVL in } \textcircled{2} : V_C - V_2 - V_3 = 0 \quad V_2 = i_2 \cdot R_2$$

$$V_3 = i_2 \cdot R_3$$

$$\Rightarrow V_C = V_2 + V_3 = i_2 (R_2 + R_3)$$

$$\Rightarrow V_2 = R_2 \cdot i_2 = V_C \cdot \frac{R_2}{R_2 + R_3} \Rightarrow V_2 = V_C \cdot \frac{15}{20}$$

THIS COULD ALSO
BE FOUND DIRECTLY
WITH VOLTAGE DIVIDER

$$\Rightarrow V_2 = 7.5 - 7.5 e^{-20t}$$

$$A = 7.5$$


$$B = -7.5$$

Basic analysis 013

No more attempts left.

Find v_a .

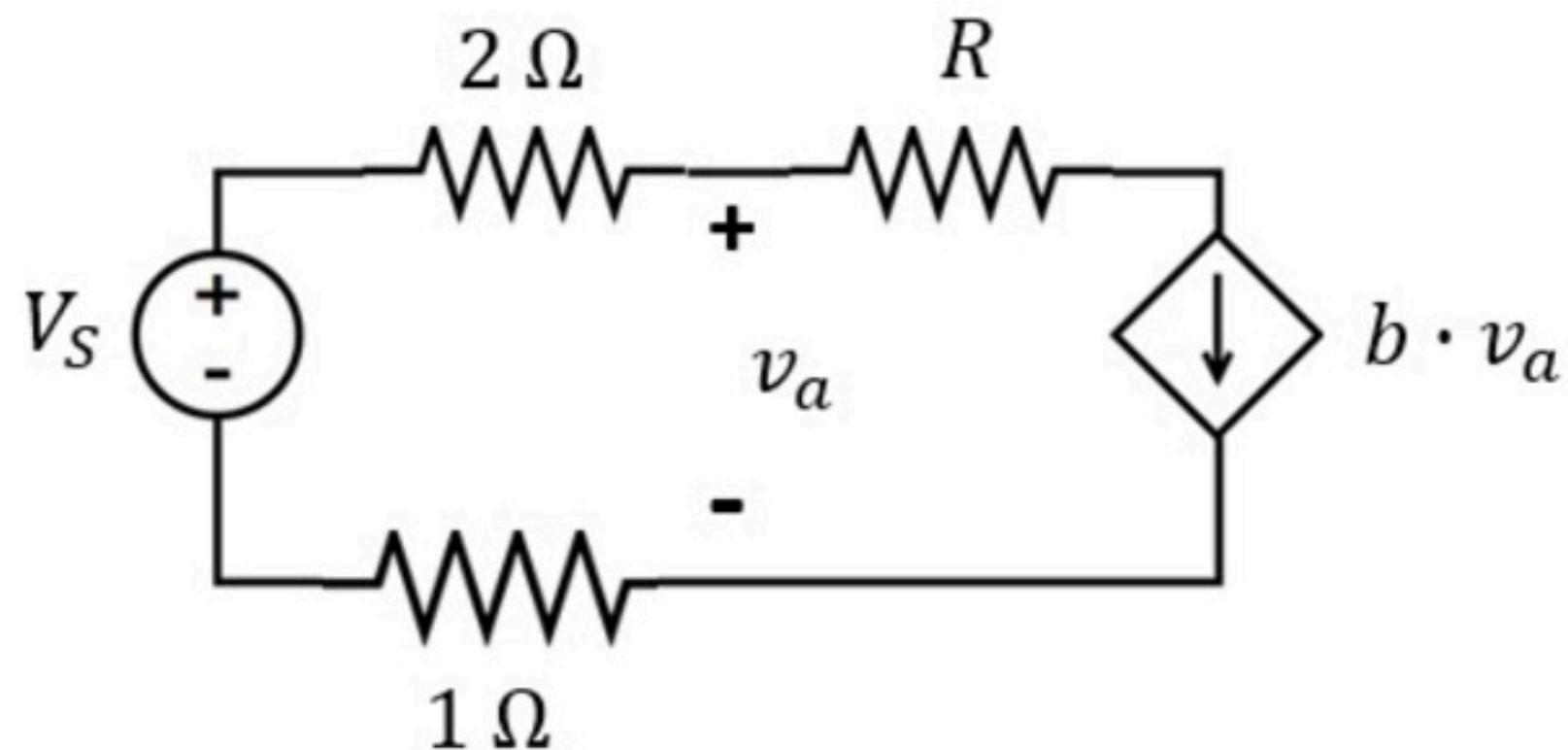What is the power P received by the dependent source?



Given Variables:

$V_s : 7 \text{ V}$

$R : 2 \text{ ohm}$

$b : 2 \text{ A/V}$

Calculate the following:

$v_a (\text{V}) :$

$P (\text{W}) :$

Hint: KVL also works when the voltage drop is not across an element.


Find v_a .

$$V_s = 7 \text{ V}$$

What is the power P received by the dependent source?

$$R = 2 \Omega$$

$$b = 2 \text{ A/V}$$

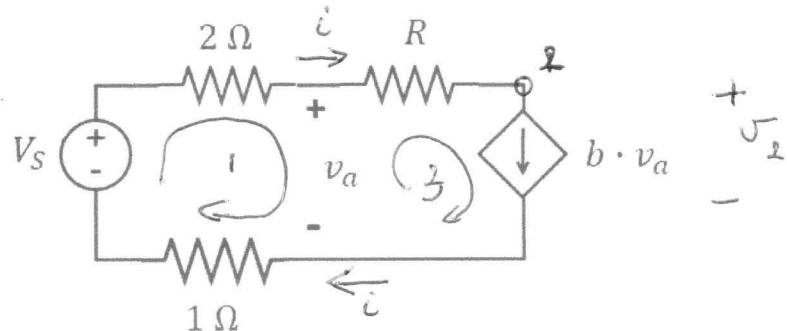


$$\text{KVL 1 : } V_s = 2 \cdot i + v_a + 1 \cdot i \Rightarrow V_s = 3i + v_a \quad (1)$$

$$\text{KCL 2 : } i = b v_a \quad (2)$$

$$(2) \text{ in (1)} : V_s = 3b v_a + v_a = 7v_a \Rightarrow \boxed{v_a = 1 \text{ V}} \\ \stackrel{(2)}{\Rightarrow} i = 2v_a = 2 \text{ A}$$
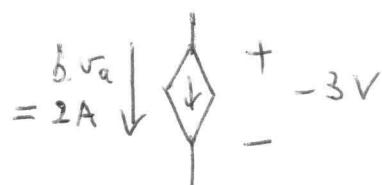
$$\text{KVL 3 : } v_a = R \cdot i + v_2 \Rightarrow v_2 = 1 - 2 \cdot i = -3 \text{ V}$$



PASSIVE SIGN CONVENTION

$$P = (-3) \cdot 2 = -6$$

$$\boxed{P = -6 \text{ W RECEIVED}}$$

Basic concepts 009


Problem has been graded.

The reading of the voltmeter is x and that of the ammeter is y .

What is the power P supplied by the VCVS?

What is the value of the current source i_s ?

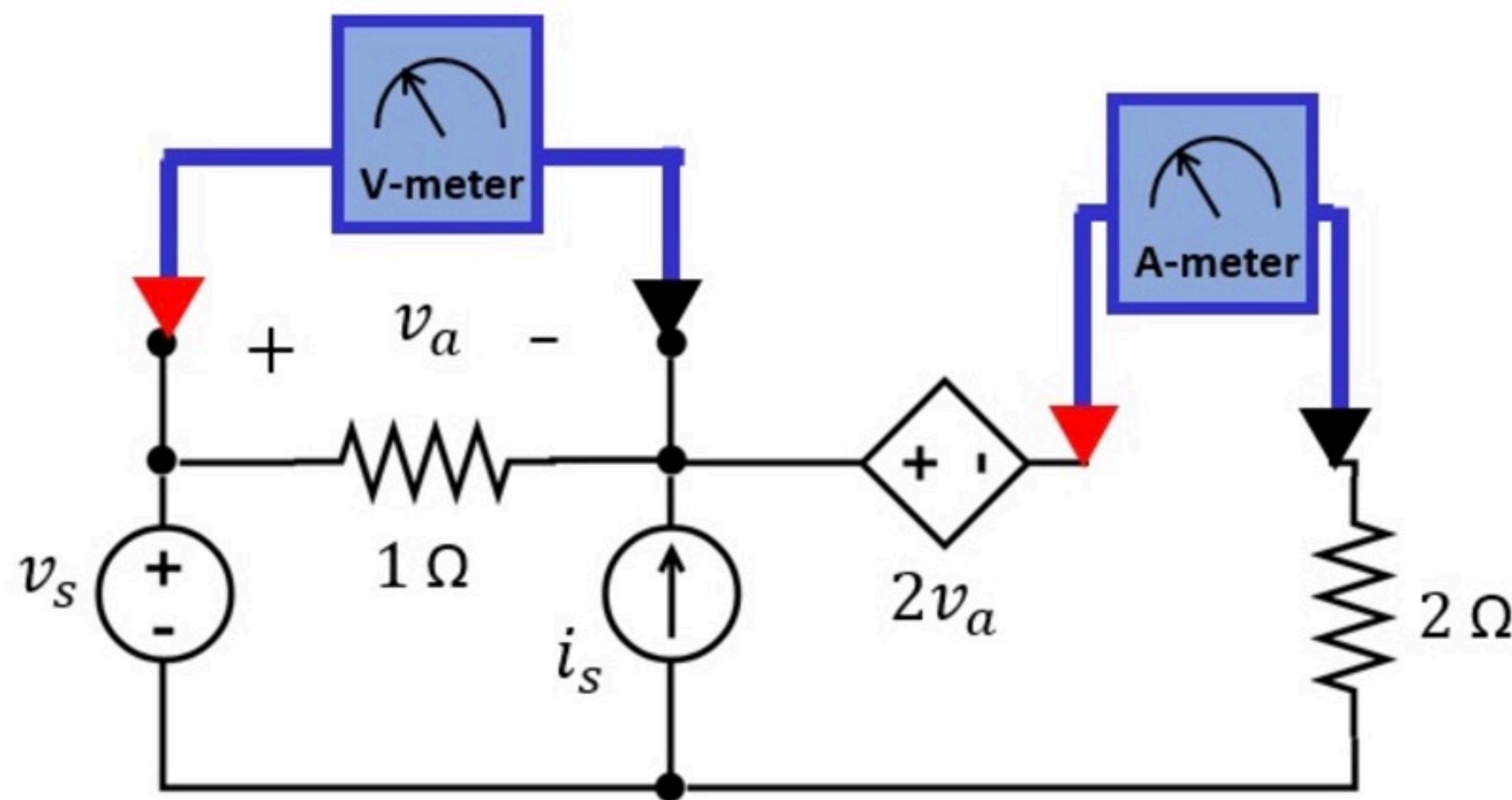What is the value of the voltage source v_s ?



Given Variables:

$x : 3 \text{ V}$

$y : 5 \text{ A}$

Calculate the following:

$P (\text{W}) :$

$i_s (\text{A}) :$

$v_s (\text{V}) :$

The reading of the voltmeter is x and that of the ammeter is y .


What is the power P supplied by the VCVS?

$$X = 6 \text{ V}$$


What is the value of the current source i_s ?

$$Y = 3 \text{ A}$$

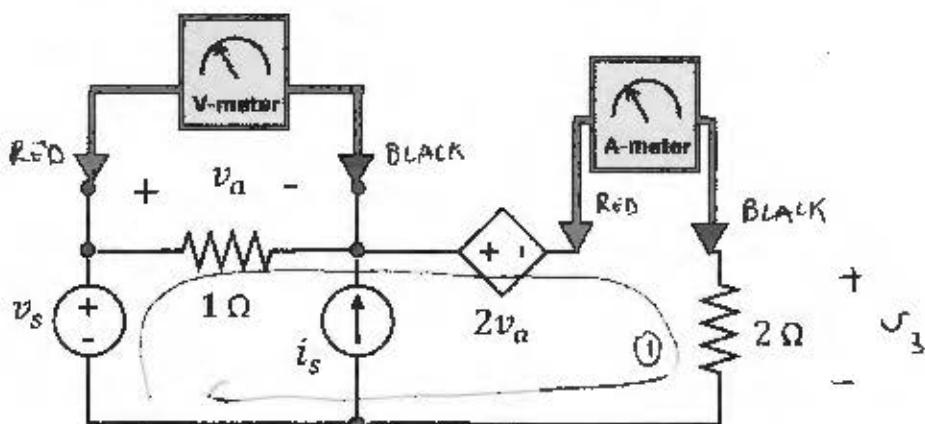What is the value of the voltage source v_s ?



(a) $v_a = X = 6$

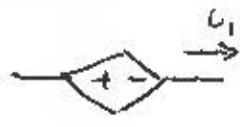


$$P = v_1 \cdot i_1 = 36 \text{ W}$$

RECEIVED

$$i_1 = Y = 3$$

$$v_1 = 2v_a = 12$$

$$P = -36 \text{ W SUPPLIED}$$

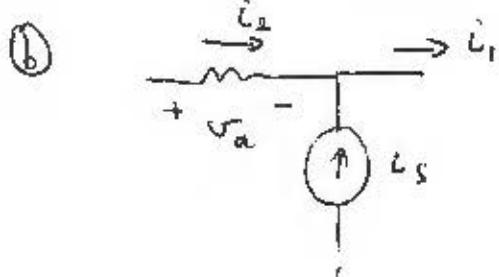

$$i_1 = \frac{v_a}{1} = 6 \text{ A}$$

$$\text{KCL: } i_2 + i_s = i_1 \Rightarrow i_s = 3 - 6 = -3$$

$$i_s = -3 \text{ A}$$

(c) KVL in ①:

$$\begin{aligned} v_s &= v_a + 2v_a + v_3 \\ &= 3 \cdot 6 + 6 \\ &= 24 \end{aligned}$$

$$v_3 = i_1 \cdot 2 = 6 \text{ V}$$



$$v_s = 24 \text{ V}$$

Basic analysis 007

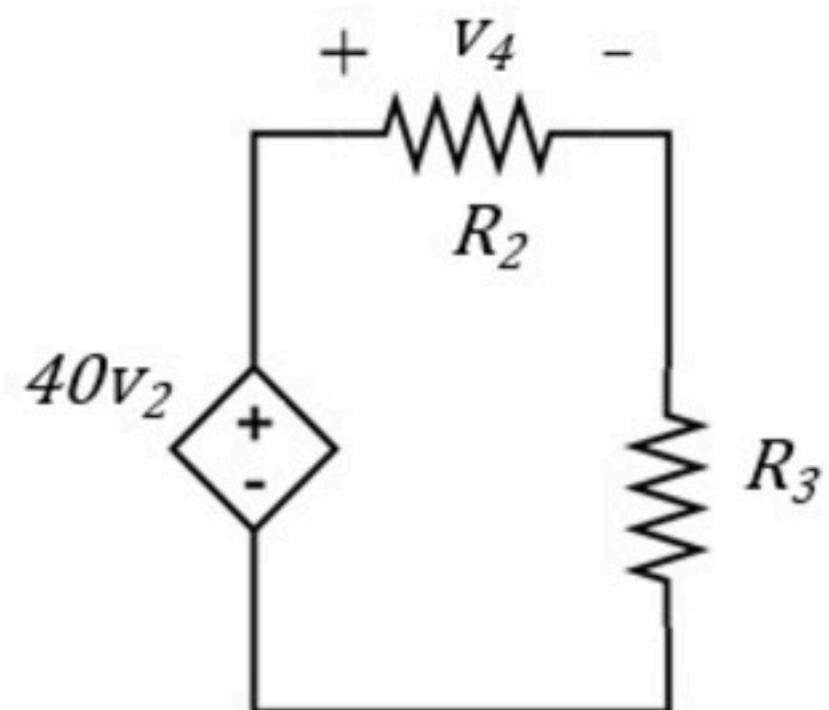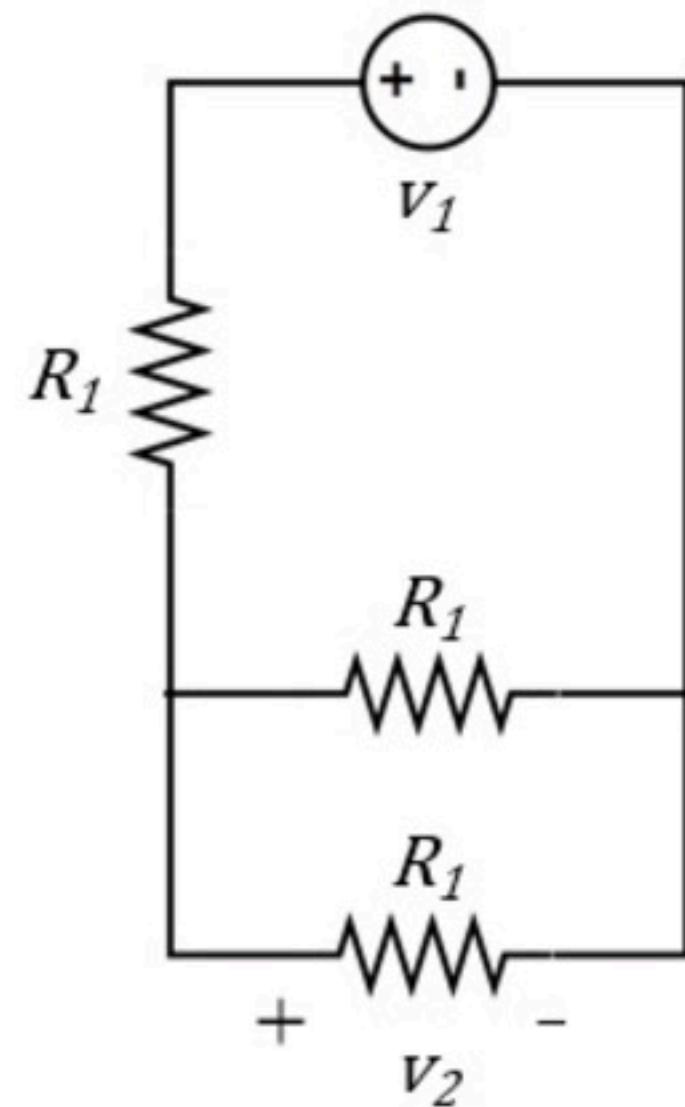Problem has been graded.

In this circuit, v_1 is an input, but you don't know what its value is. Find v_4 as a function of v_1 .

More specifically, find $X = \frac{v_4}{v_1}$.



Given Variables:

$R_1 : 10 \text{ ohm}$

$R_2 : 3 \text{ ohm}$

$R_3 : 5 \text{ ohm}$

Calculate the following:

$X (\text{V/V}) :$



In this circuit, v_I is an input, but you don't know what its value is. Find v_4 as a function of v_I .

More specifically, find $X = \frac{v_4}{v_I}$.


$$R_1 = 20 \Omega$$

$$R_2 = 12 \Omega$$

$$R_3 = 20 \Omega$$

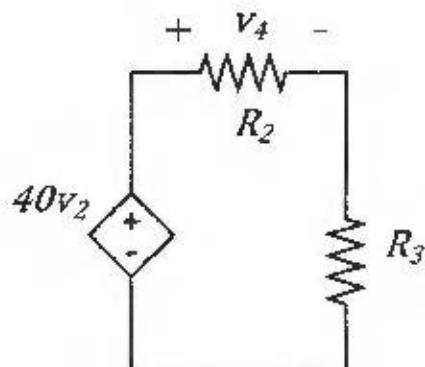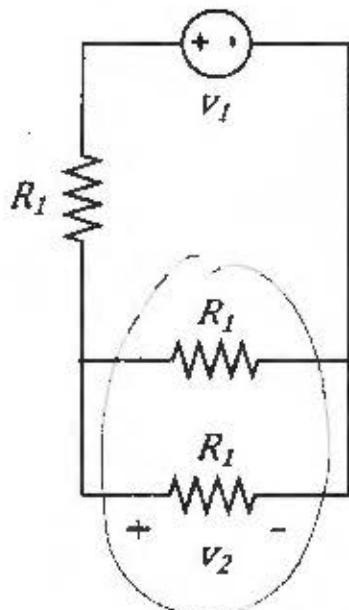

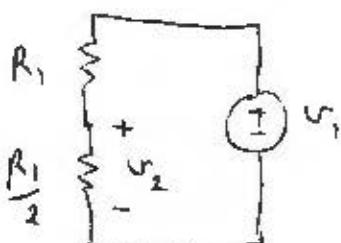
$$\hookrightarrow R_1 \parallel R_1 = \left(\frac{1}{R_1} + \frac{1}{R_1} \right)^{-1} = \left(\frac{2}{R_1} \right)^{-1} = \frac{R_1}{2}$$



VOLTAGE DIVIDER
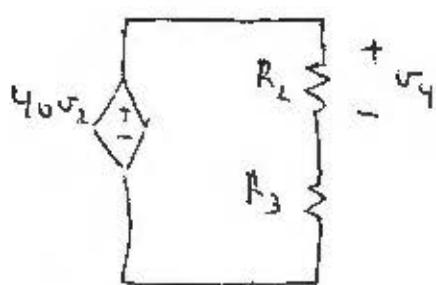
$$v_2 = v_I \cdot \frac{\frac{R_1}{2}}{R_1 + \frac{R_1}{2}} = v_I \cdot \frac{\frac{1}{2}}{1 + \frac{1}{2}} = \frac{v_I}{3}$$



VOLTAGE DIVIDER


$$v_4 = 40 v_2 \cdot \frac{R_2}{R_2 + R_3} = 40 \cdot \frac{v_I}{3} \cdot \frac{12}{3+12} = 5 v_I$$

$$X = \frac{v_4}{v_I} \approx 5$$

Basic analysis 009

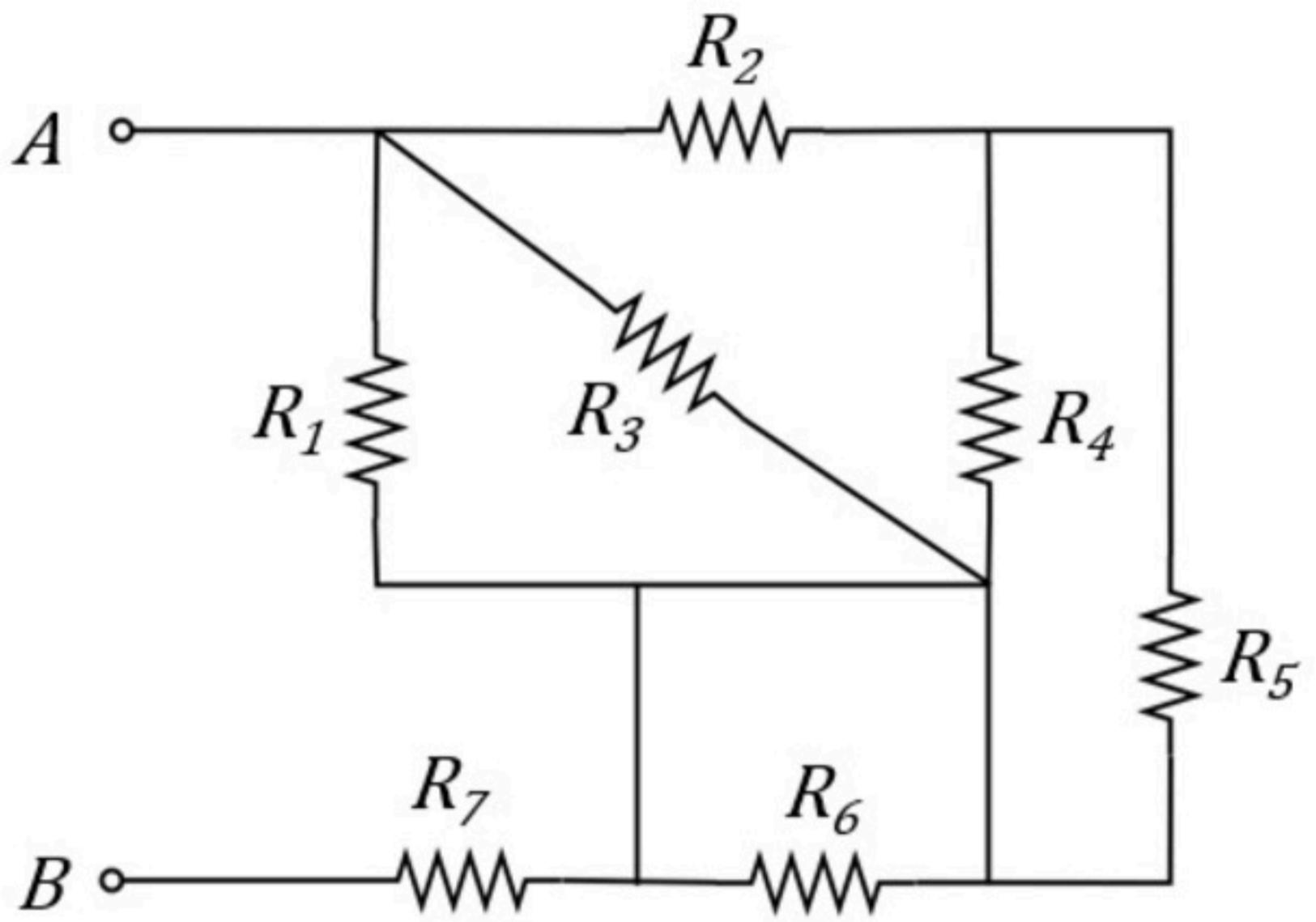Problem has been graded.

You are given that the equivalent resistance between A and B is R_{eq} .
Find the value of R_3 .



Given Variables:

$R_{eq} : 8 \text{ ohm}$

$R_1 : 3 \text{ ohm}$

$R_2 : 4 \text{ ohm}$

$R_4 : 24 \text{ ohm}$

$R_5 : 12 \text{ ohm}$

$R_6 : 12 \text{ ohm}$

$R_7 : 6 \text{ ohm}$

Calculate the following:

$R_3 (\text{ohm}) :$

You are given that the equivalent resistance between A and B is R_{eq} .
Find the value of R_3 .

$$R_{eq} = 8 \Omega$$

$$R_1 = 6 \Omega$$



$$R_2 = 4 \Omega$$

$$R_4 = 40 \Omega$$

$$R_5 = 10 \Omega$$

$$R_6 = 12 \Omega$$

$$R_7 = 5 \Omega$$

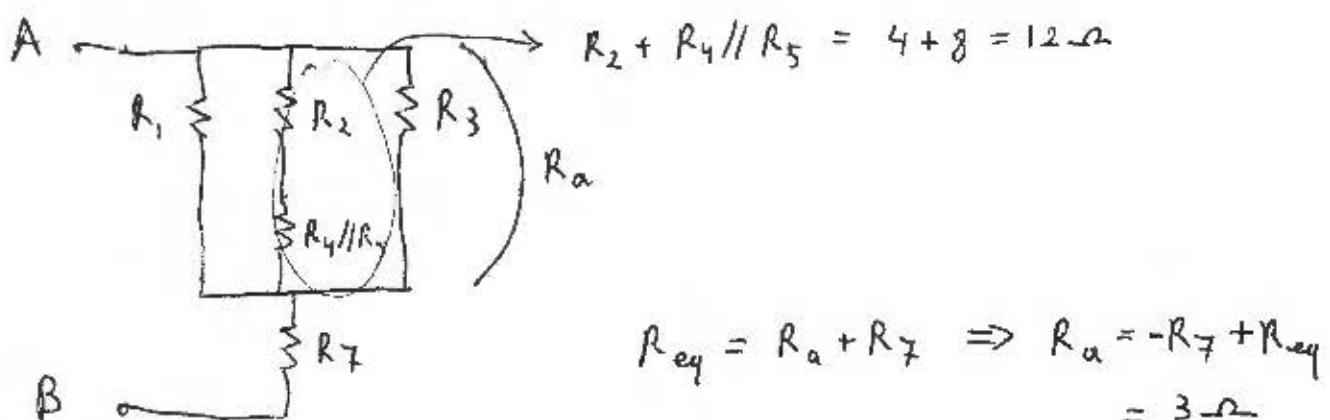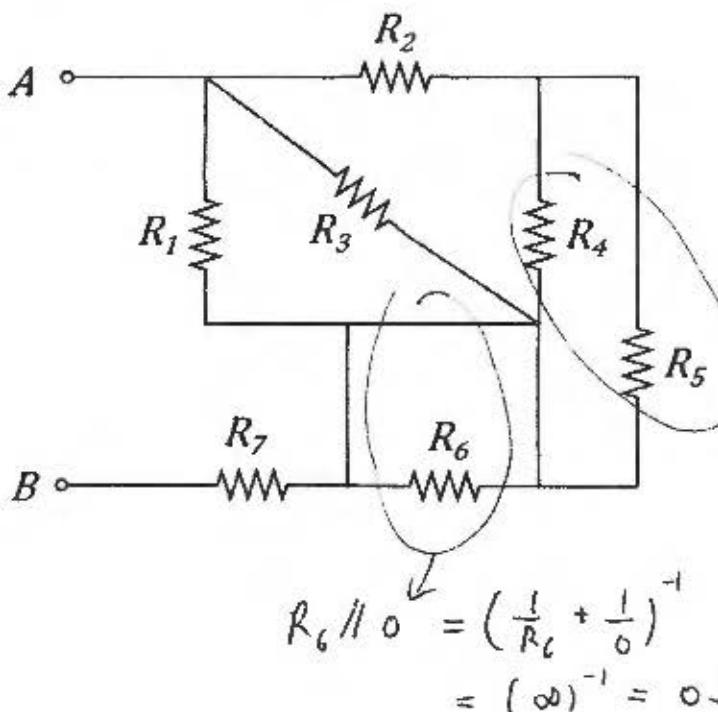

$$\frac{1}{R_a} = \frac{1}{R_1} + \frac{1}{12} + \frac{1}{R_3}$$


$$\frac{1}{R_3} = \frac{1}{R_a} - \frac{1}{R_1} - \frac{1}{12} = \frac{1}{3} - \frac{1}{6} - \frac{1}{12} = \frac{4-2-1}{12}$$

$R_3 = 12 \Omega$

Basic Analysis 010b

No more attempts left.

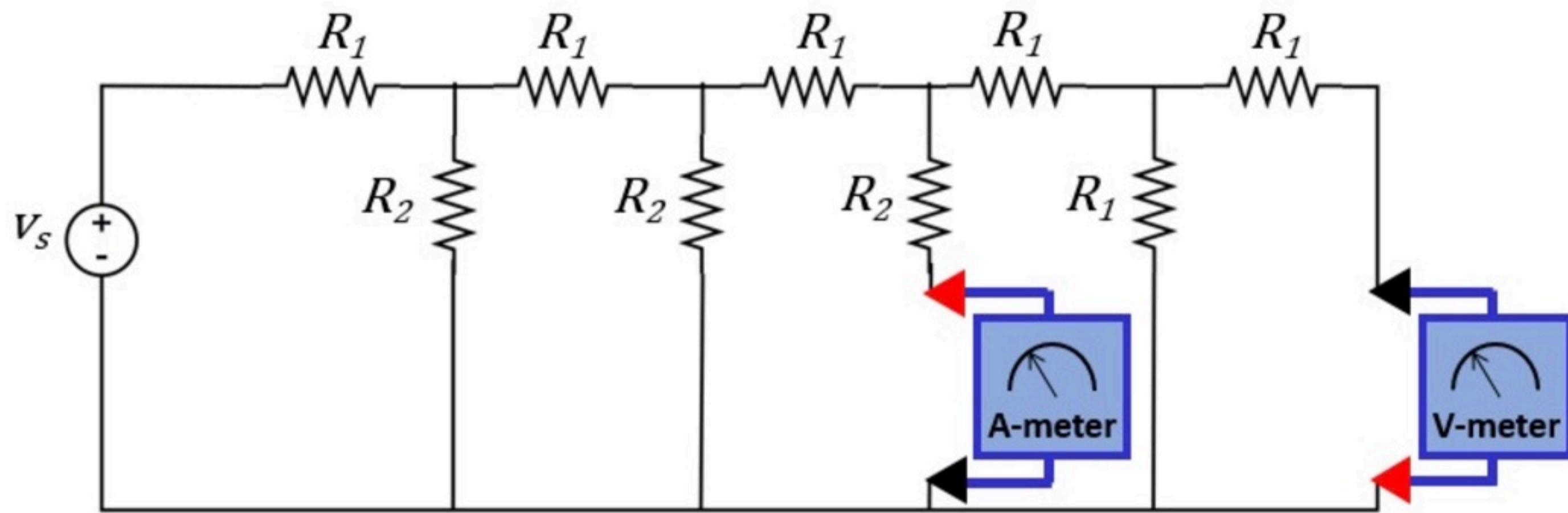Find the ammeter reading X and the volt-meter reading Y .



Given Variables:

vs : 32 V

R1 : 2 ohm

R2 : 4 ohm





Calculate the following:

X (A) :

$\mathbf{Y}(\mathbf{V}) :$

Hint: First find the current through V_s . Use series/parallel. Then find X with current divider.

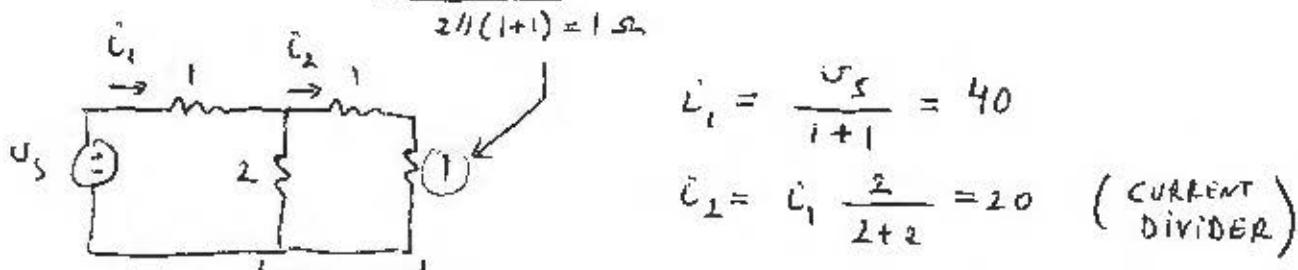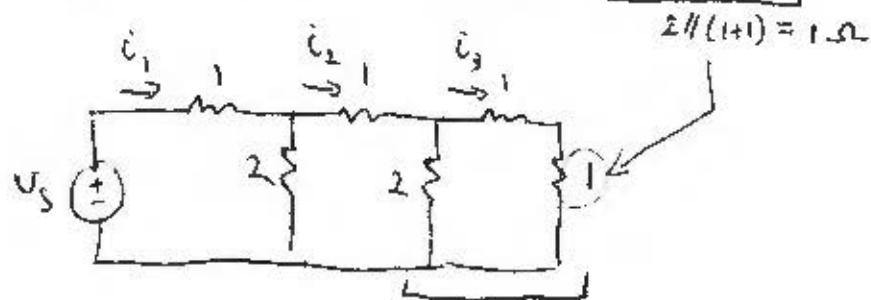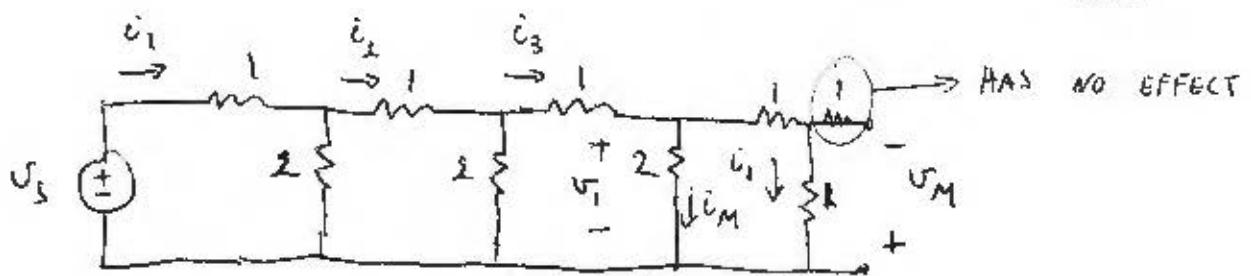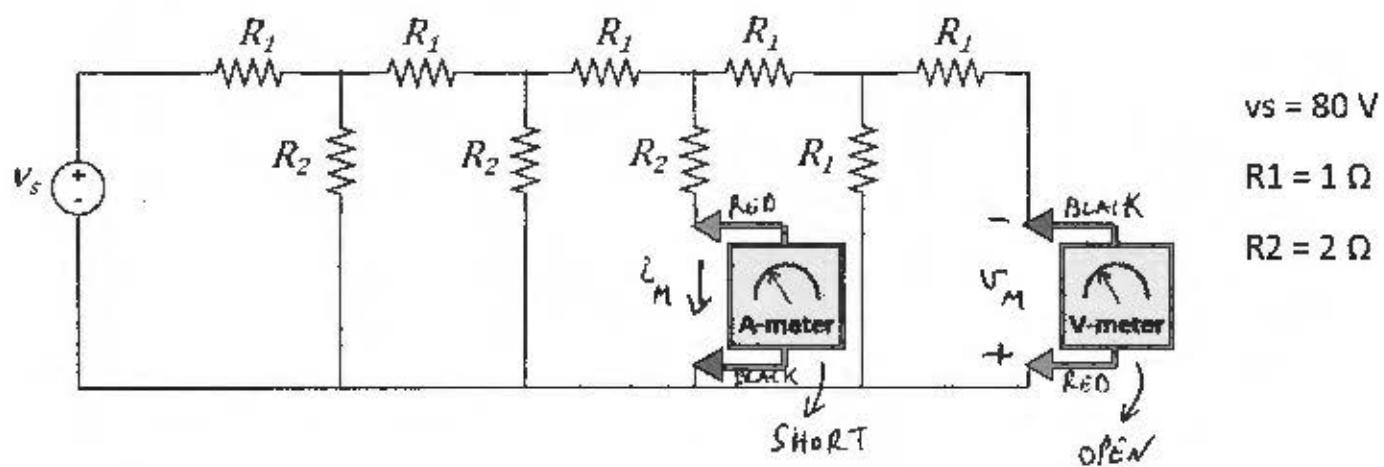Find the ammeter reading X and the voltmeter reading Y .



$$i_1 = \frac{V_s}{1+1} = 40$$

$$i_2 = i_1 \cdot \frac{2}{2+2} = 20 \quad (\text{CURRENT DIVIDER})$$

$$i_3 = i_2 \cdot \frac{2}{2+2} = 10 \quad (\text{CURRENT DIVIDER})$$

$$i_M = i_3 \cdot \frac{2}{2+2} = 5 \quad (\text{CURRENT DIVIDER})$$

$$\boxed{X = 5 \text{ A}}$$

$$V_1 = 2 \cdot i_M = 10$$

~~$$V_1 = 2 \cdot i_M = 10$$~~


$$V_1 = i_1 = 5 \Rightarrow -V_M = 1 \cdot i_1 = 5$$

$$\boxed{Y = -5 \text{ V}}$$

Basic analysis 012

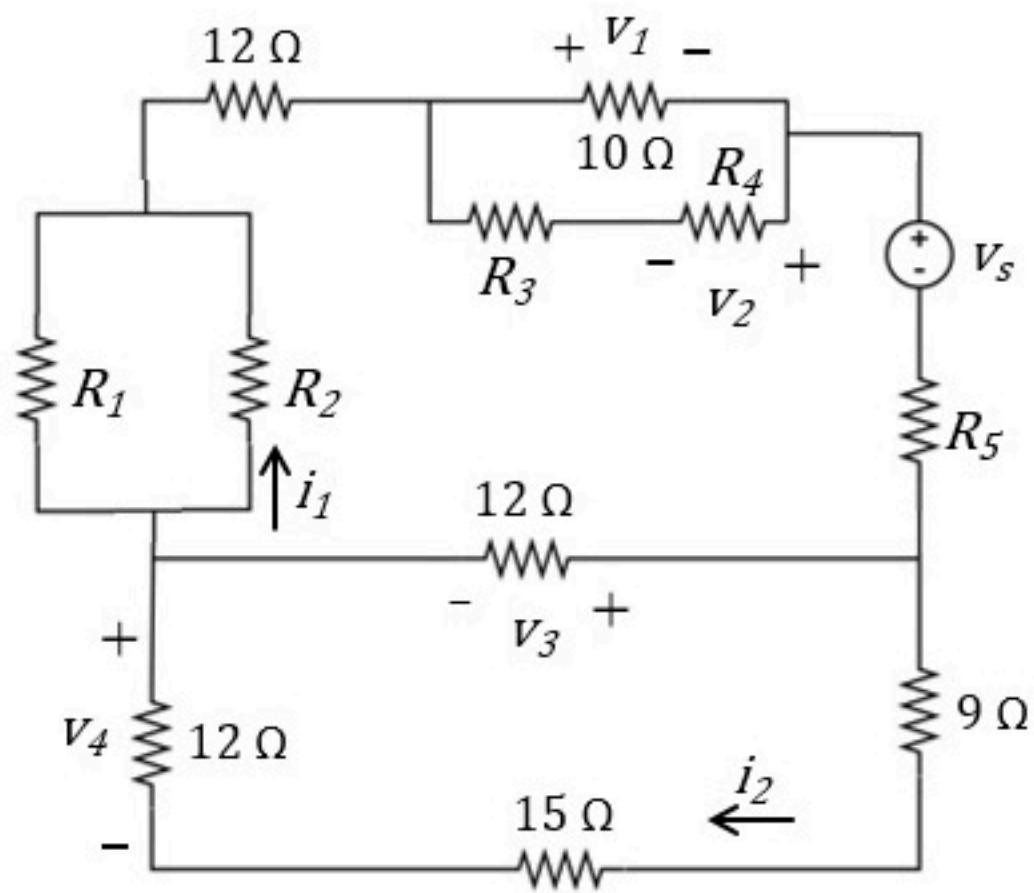Problem has been graded.

Determine the voltages v_1 , v_2 , v_3 and v_4 and the currents i_1 and i_2 .



Given Variables:

$v_s : 80\text{ V}$
 $R_1 : 24\ \text{ohm}$
 $R_2 : 8\ \text{ohm}$
 $R_3 : 6\ \text{ohm}$
 $R_4 : 9\ \text{ohm}$
 $R_5 : 7\ \text{ohm}$

Calculate the following:

$v_1\ (\text{V}) :$

$v_2\ (\text{V}) :$

$v_3\ (\text{V}) :$

$v_4\ (\text{V}) :$

$i_1\ (\text{A}) :$

$i_2\ (\text{A}) :$

Determine the voltages v_1 , v_2 , v_3 and v_4
and the currents i_1 and i_2 .

$$V_s = 80 \text{ V}$$



$$R_1 = 8 \Omega$$

$$R_2 = 24 \Omega$$

$$R_3 = 3 \Omega$$

$$R_4 = 12 \Omega$$

$$R_5 = 7 \Omega$$

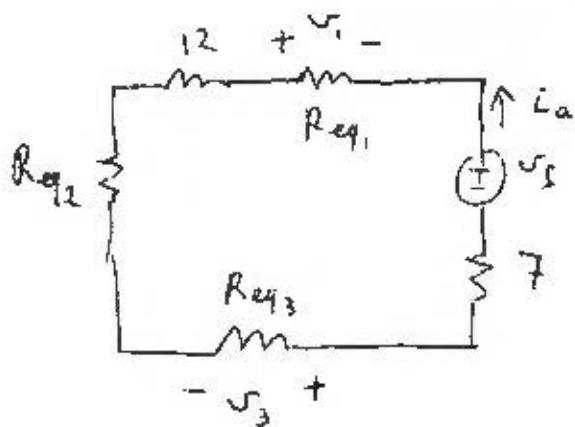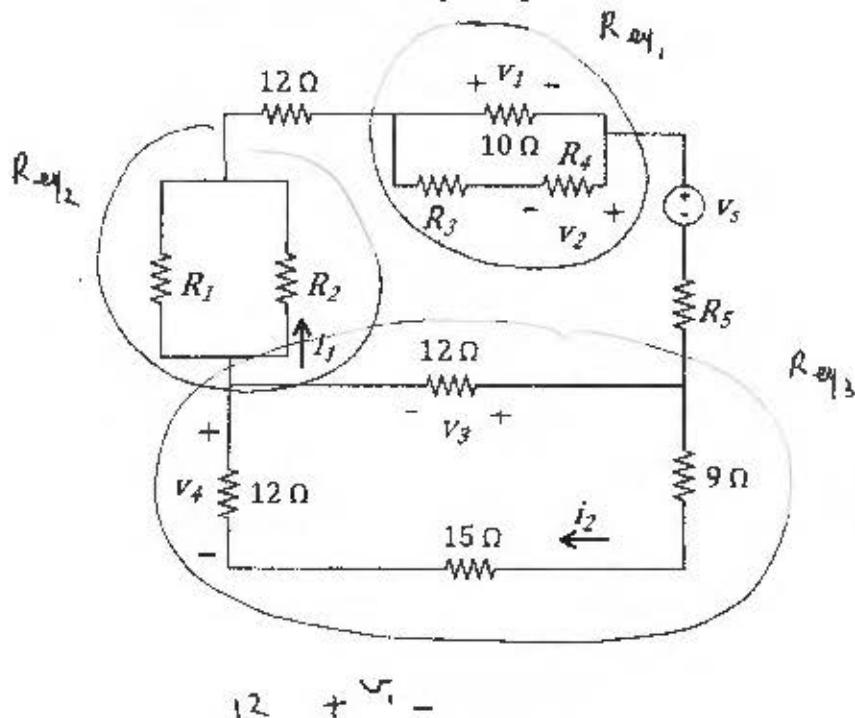

$$i_a = \frac{V_s}{R_{eq_1} + 12 + R_{eq_2} + R_{eq_3} + 7}$$

$$= \frac{V_s}{40} \Rightarrow i_a = 2 \text{ A}$$

$$v_1 = (-i_a) \cdot R_{eq_1} = (-2) \cdot 6 = -12 \text{ V}$$

$$v_2 = (-v_1) \cdot \frac{R_4}{R_3 + R_4} = 12 \cdot \frac{12}{12+5} = \frac{48}{5} \text{ V}$$

$$v_3 = (-i_a) R_{eq_3} = (-2) \cdot 9 = -18 \text{ V}$$

$$v_4 = (-v_3) \frac{12}{12+15+9} = 18 \cdot \frac{12}{36} = 6 \text{ V}$$

$$i_1 = (-i_a) \frac{R_1}{R_1 + R_2} = (-2) \cdot \frac{8}{32} = -0.5 \text{ A}$$

$$i_2 = (-i_a) \cdot \frac{12}{12+12+15+9} = (-2) \cdot \frac{12}{48} = -0.5 \text{ A}$$

$$v_1 = -12 \text{ V}$$

$$v_2 = 9.6 \text{ V}$$

$$v_3 = -18 \text{ V}$$

$$v_4 = 6 \text{ V}$$

$$i_1 = -0.5 \text{ A}$$


$$i_2 = -0.5 \text{ A}$$

Basic analysis 014

No more attempts left.

What is the reading X from the ammeter?

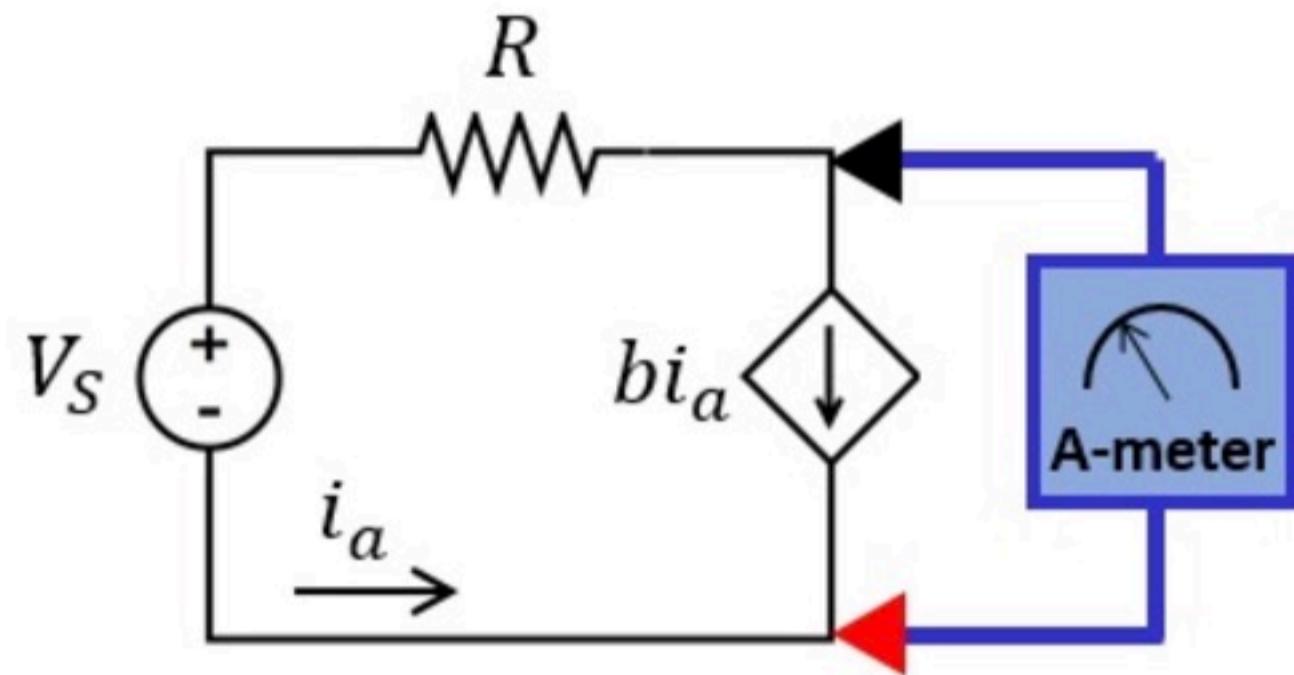What would be the reading Y if we replaced the ammeter by a volt-meter?



Given Variables:

$V_s : 8 \text{ V}$

$R : 4 \text{ ohm}$

$b : 2 \text{ A/A}$

Calculate the following:

$X (\text{A}) :$

$Y (\text{V}) :$



(a) What is the reading X from the ammeter?

$$V_s = 6 \text{ V}$$

(b) What would be the reading Y if we replaced the ammeter by a volt-meter?

$$R = 2 \Omega$$

$$b = 2 \text{ A/A}$$

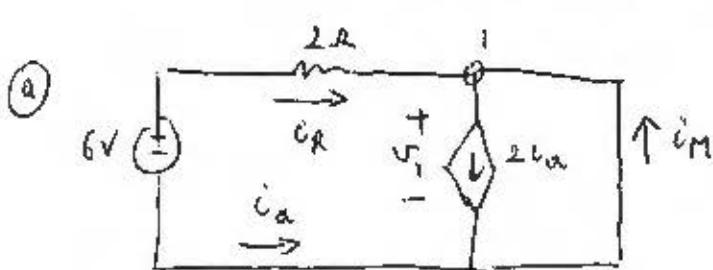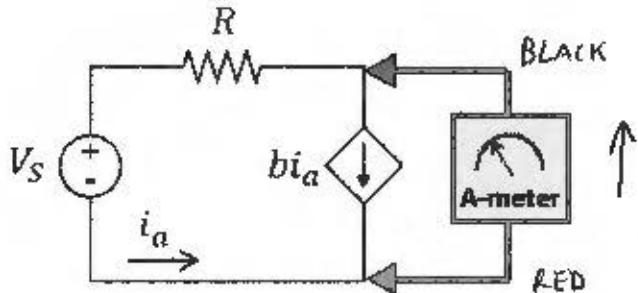

AMMETER EQUIVALENT
TO A SHORT

$$\Rightarrow v_i = 0 \text{ V}$$

$$\Rightarrow i_R = \frac{6 - v_i}{R} = \frac{6}{2} = 3 \text{ A}$$


$$\Rightarrow i_a = -i_R = -3 \text{ A}$$

$$\text{KCL at 1: } i_R + i_M = 2i_a$$

$$i_M = 2i_a - i_R = 3i_a = -9 \text{ A}$$

$$X = -9 \text{ A}$$

(b)

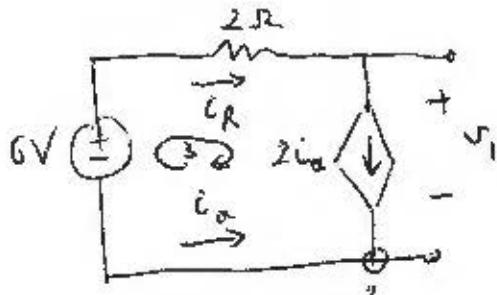

V-METER EQUIVALENT
TO AN OPEN

$$\text{KCL at 2: } i_a + 2i_a = 0 \Rightarrow 3i_a = 0 \Rightarrow i_a = 0$$

$$\Rightarrow i_R = 0$$




$$\text{KVL 3: } 6V = i_R \cdot 2 + v_i \Rightarrow v_i = 6 \text{ V}$$

$$Y = 6 \text{ V}$$

Basic Analysis 015

Problem has been graded.

Find v_a , v_b and i_c .

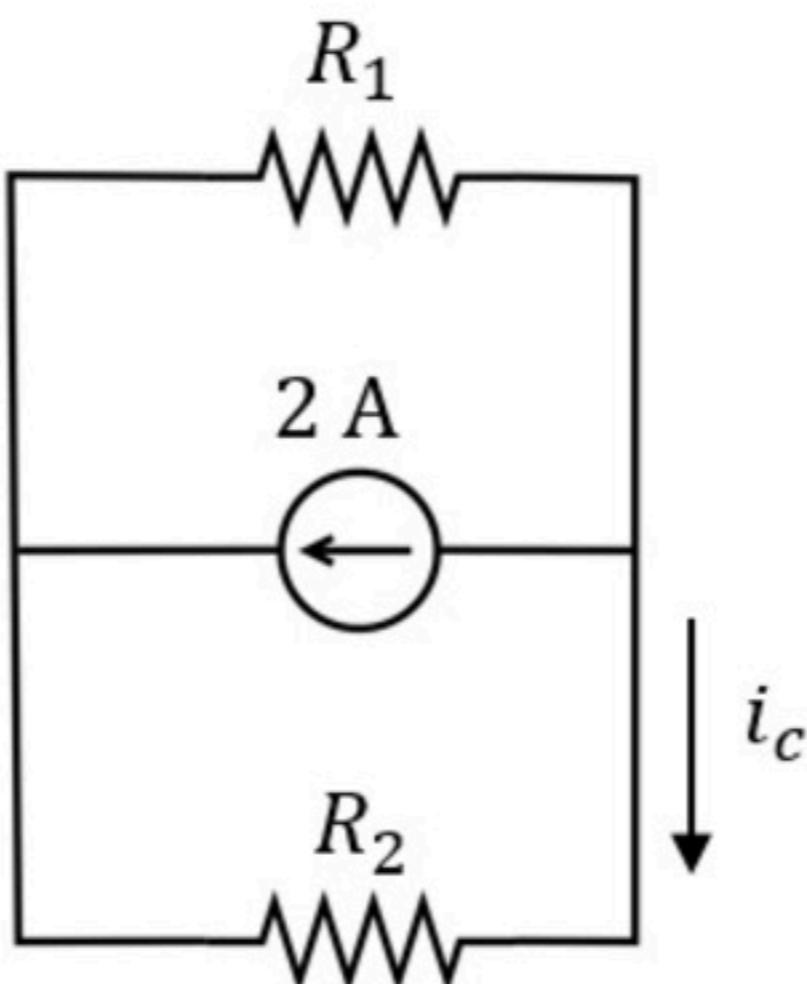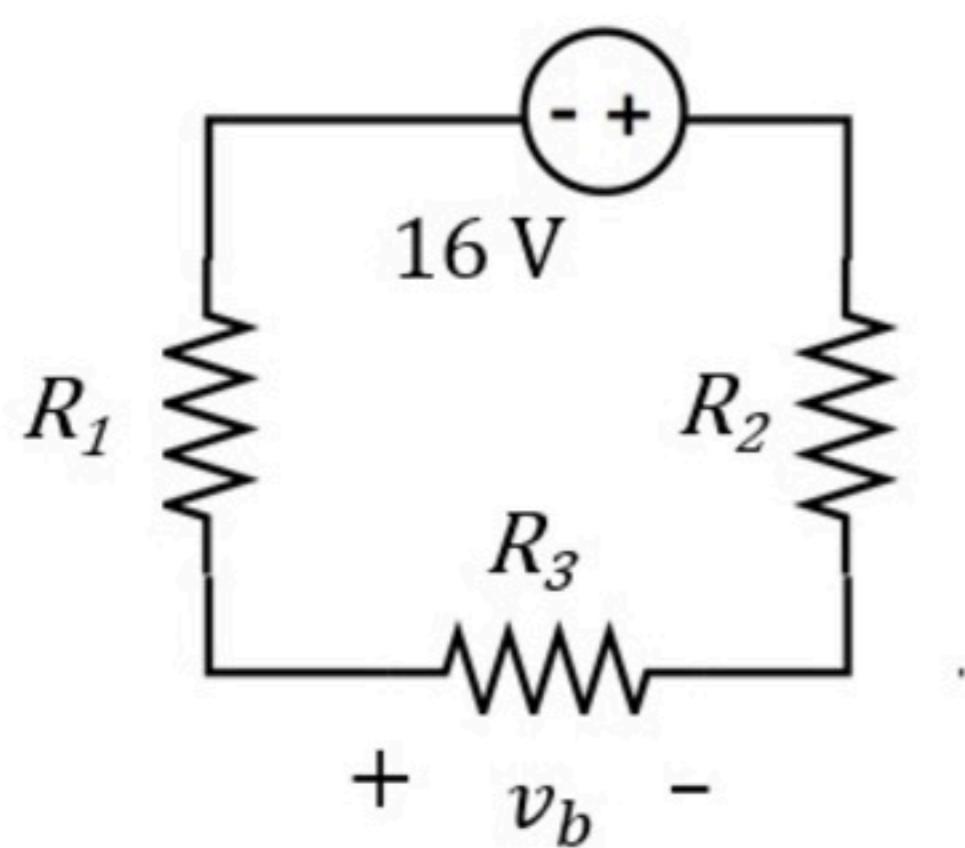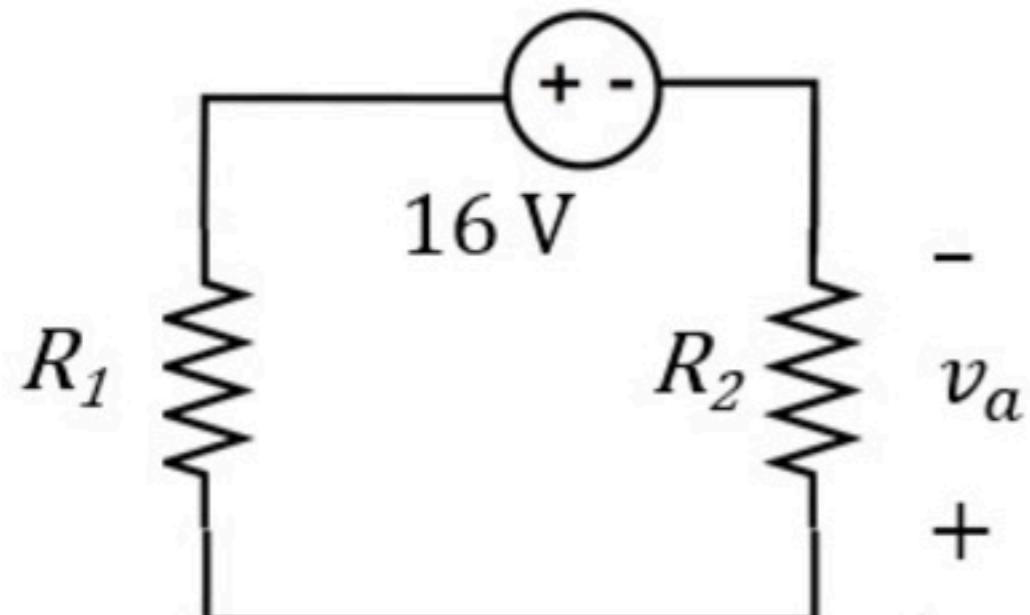

Given Variables:

$R_1 : 2 \text{ ohm}$

$R_2 : 6 \text{ ohm}$

$R_3 : 2 \text{ ohm}$



Calculate the following:

$v_a (\text{V}) :$

$v_b (\text{V}) :$

$i_c (\text{A}) :$


Find v_a , v_b and i_c .

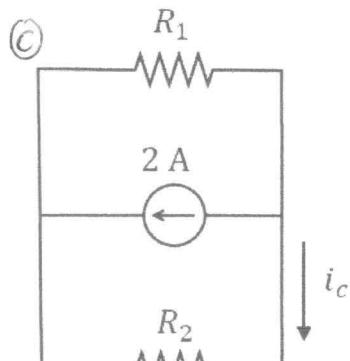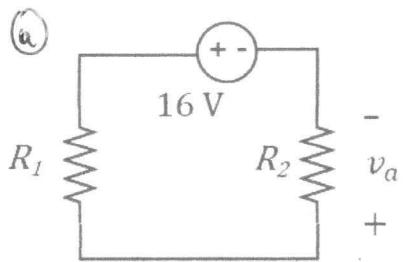

$$R1 = 2 \Omega$$

$$R2 = 6 \Omega$$

$$R3 = 2 \Omega$$

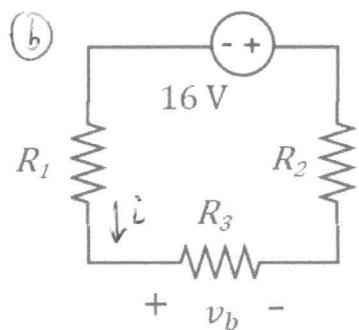

(a) VOLTAGE DIVIDER : $v_a = 16 \cdot \frac{R_2}{R_1 + R_2} = 16 \cdot \frac{6}{2+6} = 12$

$$v_a = 12 V$$

(b) VOLTAGE DIVIDER : $v_b = (-16) \cdot \frac{R_3}{R_1 + R_2 + R_3} = (-16) \cdot \frac{2}{2+6+2} = -3.2$

$$v_b = -3.2 V$$

BTW: WHERE THIS COMES FROM

$$i = \frac{(-16)}{R_1 + R_2 + R_3} \quad \text{AND} \quad v_b = R_3 \cdot i$$

$$\Rightarrow v_b = (-16) \frac{R_3}{R_1 + R_2 + R_3}$$


(c) CURRENT DIVIDER : $i_c = (-2) \frac{R_1}{R_1 + R_2} = (-2) \cdot \frac{2}{2+6} = -0.5$

$$i_c = -0.5 A$$

Basic concepts 007

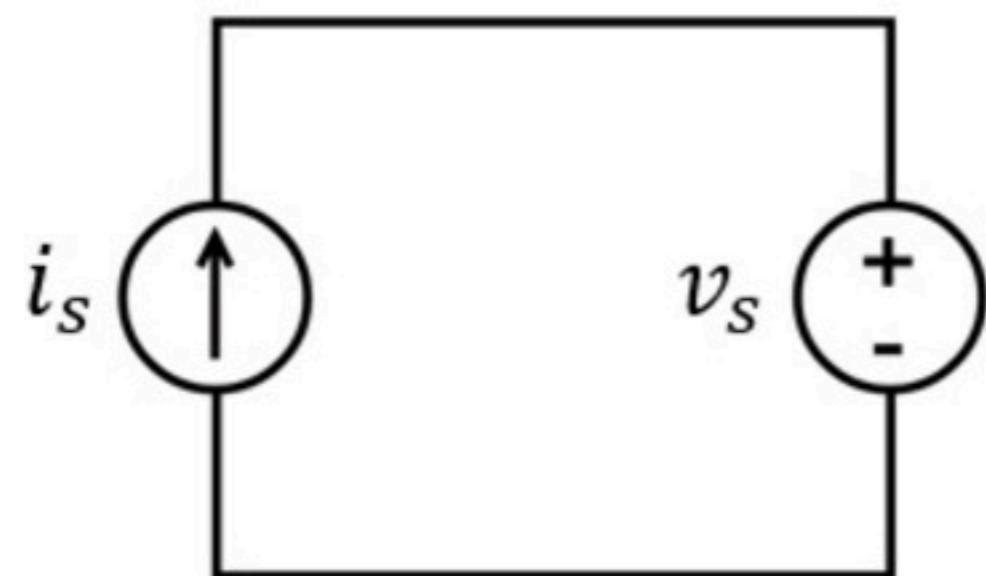Problem has been graded.

Find the power P_1 supplied by the current source and the power P_2 supplied by the voltage source.



Given Variables:

$$v_s : 10 \text{ V}$$

$$i_s : 6 \text{ A}$$

Calculate the following:

$$P_1 (\text{W}) :$$


$$P_2 (\text{W}) :$$

Hint: The voltage across a current source can be non-zero

Find the power P_1 supplied by the current source
and the power P_2 supplied by the voltage source.


$$V_s = 10 \text{ V}$$

$$I_s = 4 \text{ A}$$

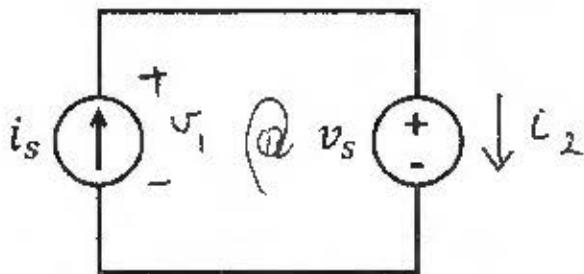

$$\text{KVL} \textcircled{1} : v_1 = v_s = 10 \text{ V}$$


$$\text{KCL} : i_2 = i_s = 4 \text{ A}$$

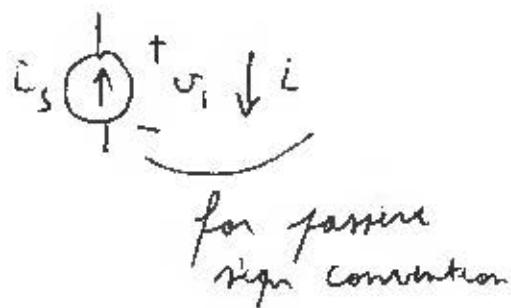

$$P_1 = v_1 \cdot i = 10 \cdot 4 = 40 \text{ W received}$$

$$i = -i_s = -4 \text{ A}$$

$$P_1 = 40 \text{ W supplied}$$

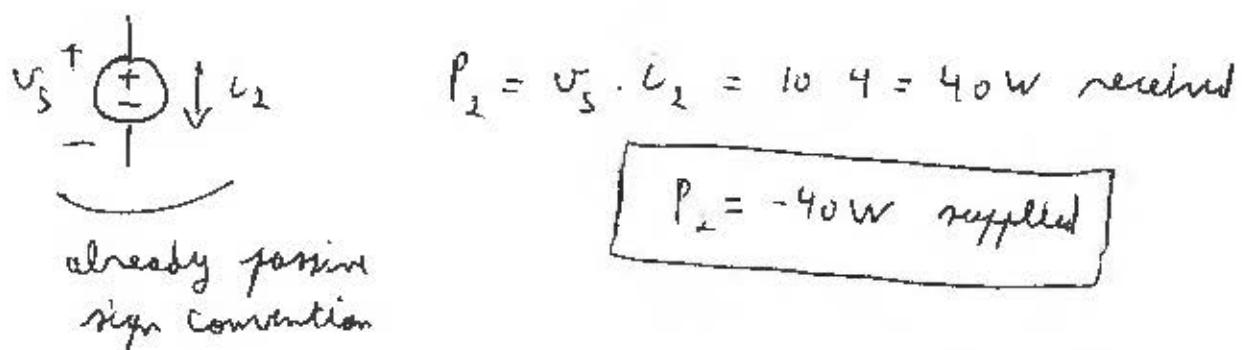

$$P_2 = v_s \cdot i_2 = 10 \cdot 4 = 40 \text{ W received}$$

$$P_2 = -40 \text{ W supplied}$$

$$\underline{\text{Check}} : \sum P_{\text{received}} = \sum P_{\text{supplied}} \Rightarrow 0 = 40 - 40 \quad \underline{\text{OK}}$$

Basic Concepts 008b


Problem has been graded.

The current source supplies 100 W of power.

What is the current i_1 ?

What is the voltage v_1 ?

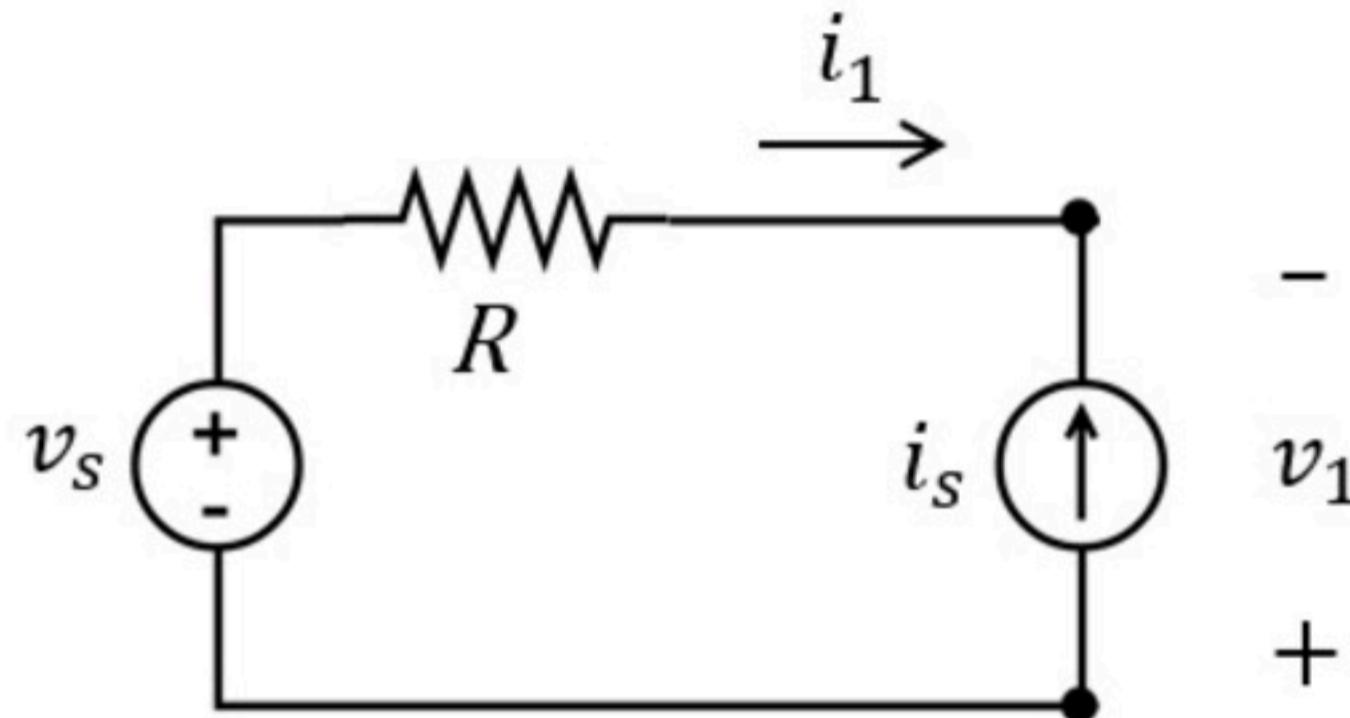What is the value of the voltage source v_s ?



Given Variables:

$R : 5 \text{ ohm}$

$i_s : 10 \text{ A}$

Calculate the following:

$i_1 (\text{A}) :$

$v_1 (\text{V}) :$

$v_s (\text{V}) :$

The current source supplies 100 W of power.


$$R = 2 \Omega$$

What is the current i_1 ?

$$i_s = 25 \text{ A}$$


What is the voltage v_1 ?

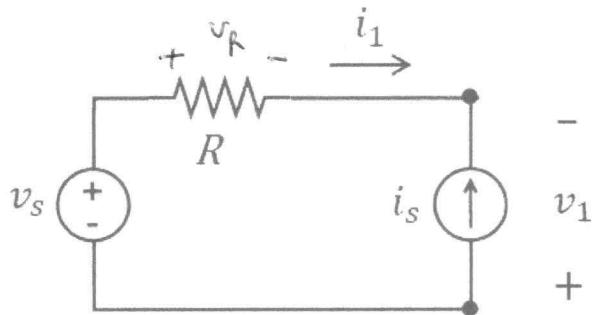What is the value of the voltage source v_s ?



$$i_1 = -i_s$$

$$i_1 = -25 \text{ A}$$

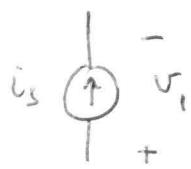

PASSIVE SIGN CONVENTION

$$P = 100 \text{ W} \text{ SUPPLIED} \Rightarrow P = -100 \text{ W RECEIVED}$$
$$= i_s \cdot v_1$$



$$v_1 = -4 \text{ V}$$

$$v_1 = -\frac{100}{25} = -4 \text{ V}$$

$$\text{KVL: } v_s + v_1 = v_R$$


$$v_s = v_R - v_1 = R \cdot i_1 - v_1 = 2(-25) - (-4)$$
$$= -50 + 4 = -46$$

$$v_s = -46 \text{ V}$$

PP - Basic concepts 009

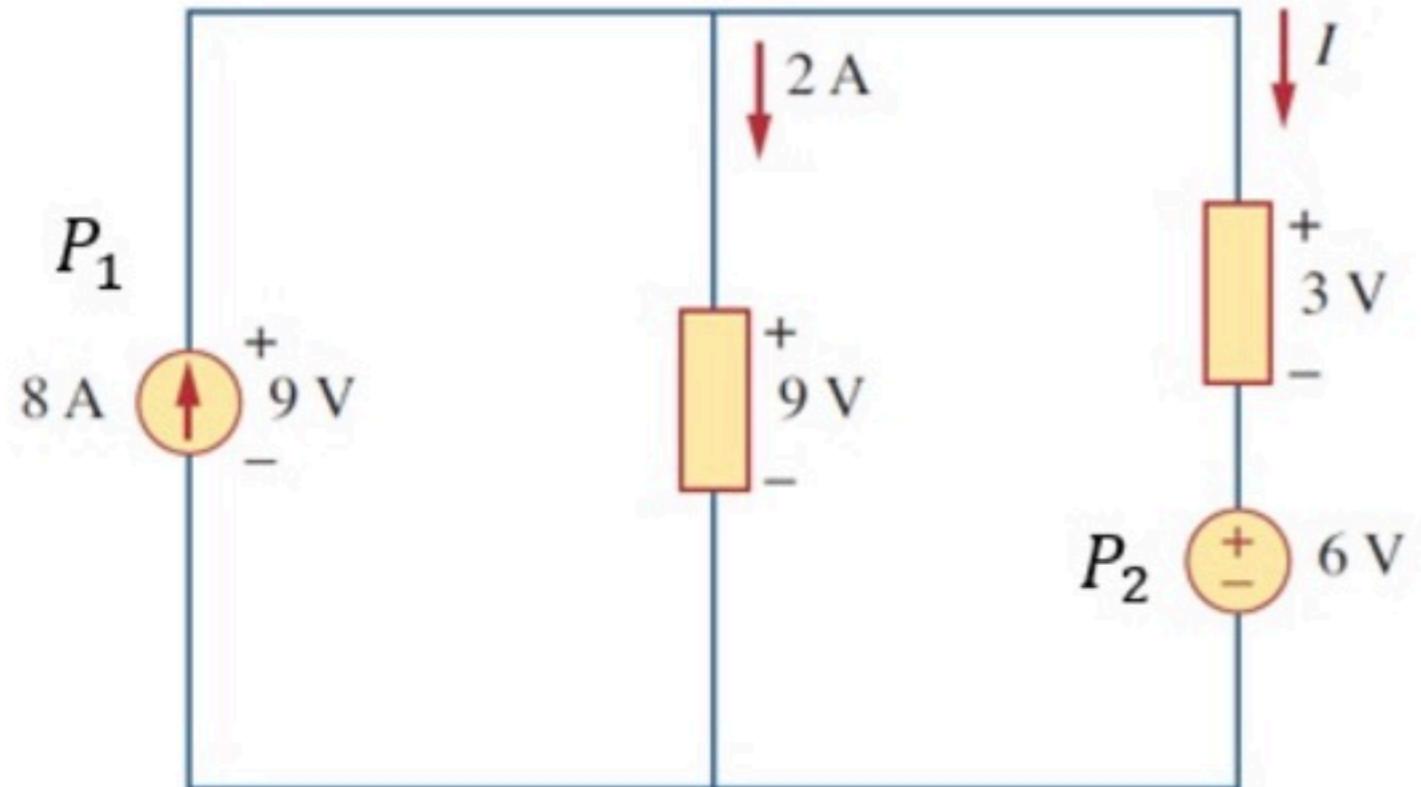Problem has been graded.

Find the power supplied by the current source and the voltage source.



Given Variables:

. . .

Calculate the following:

P_1 (W) :

72



P_2 (W) :

-36







Hint: Use KCL to find the missing current

Basic concepts 010

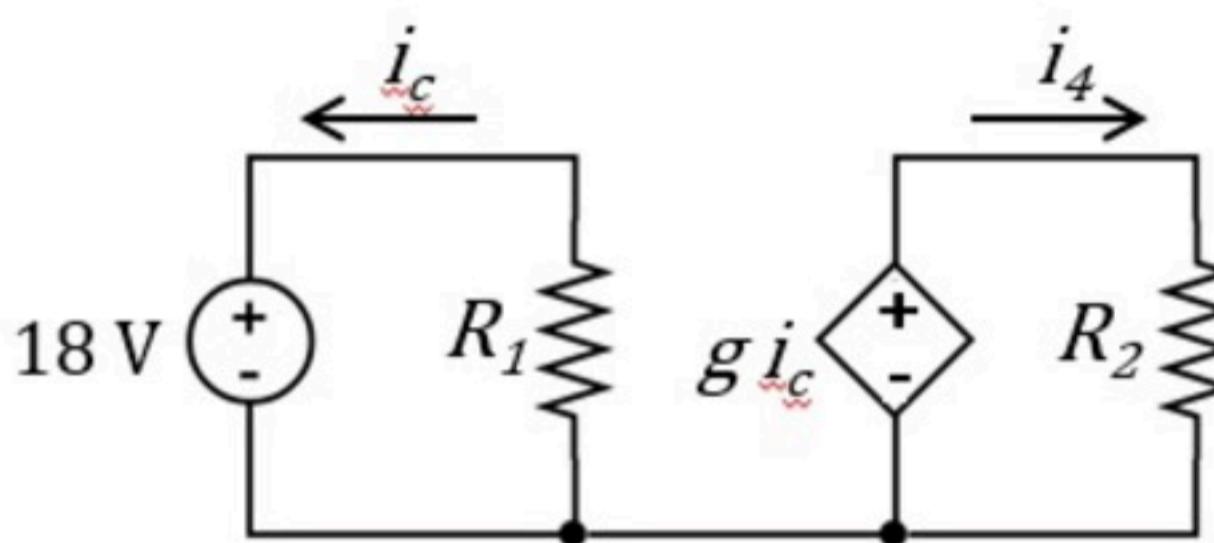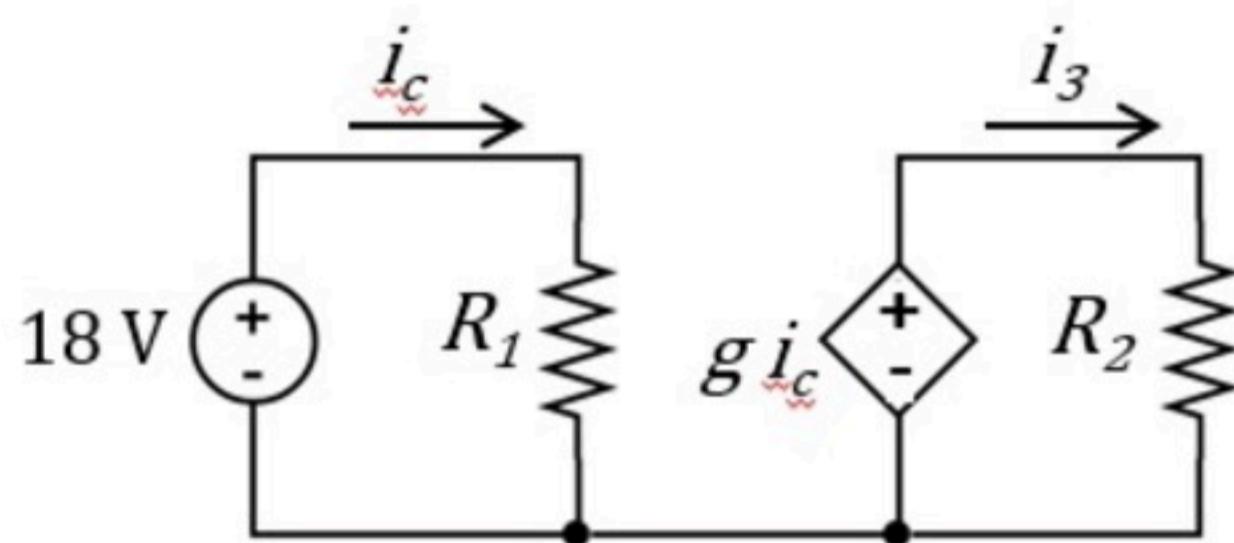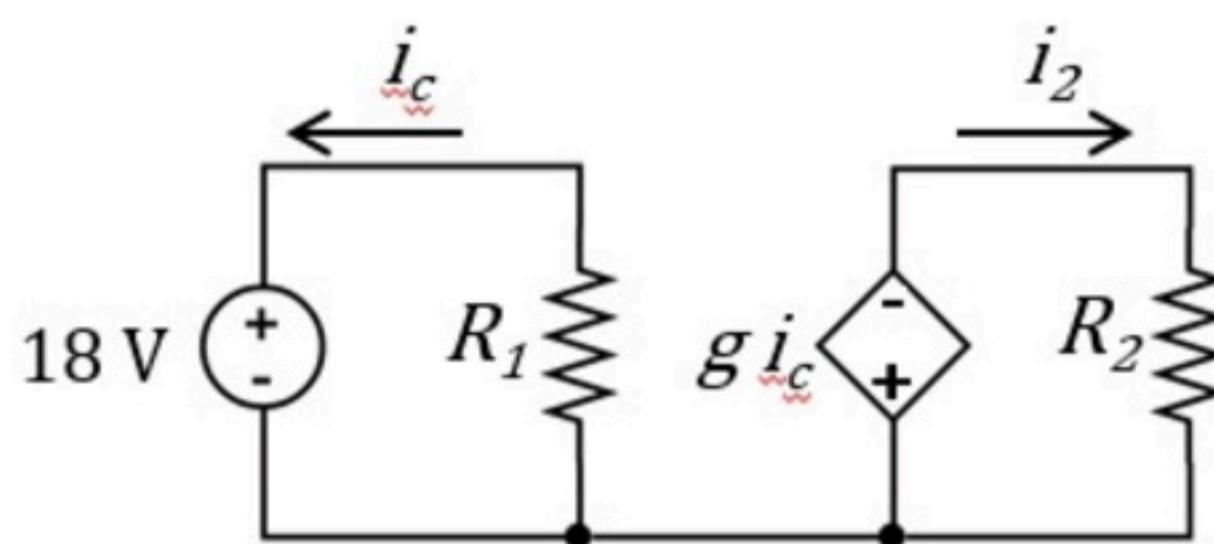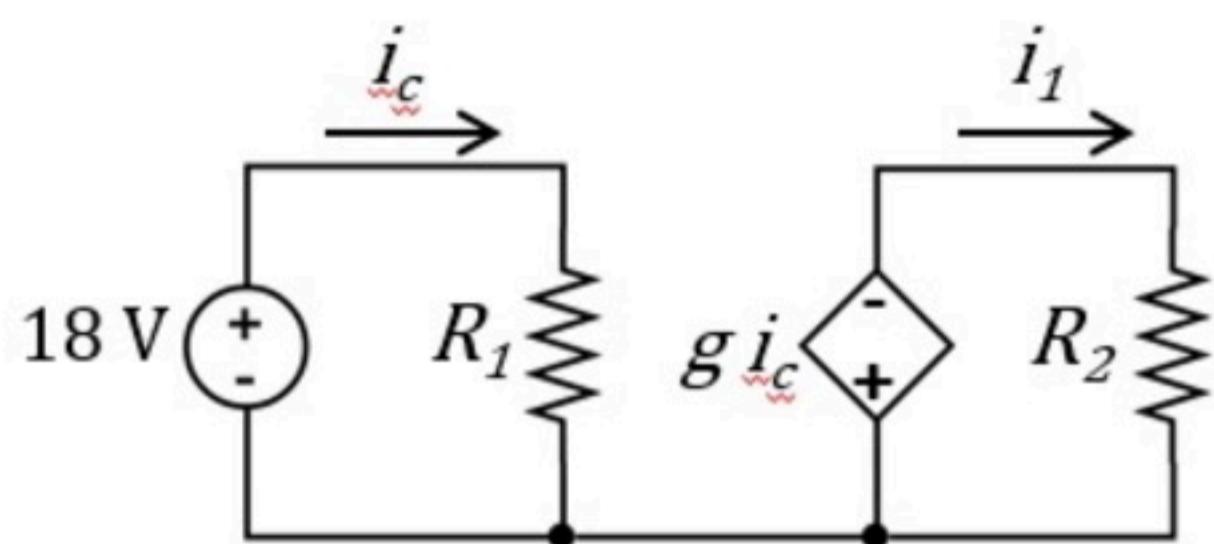Problem has been graded.

Find the currents i_1, i_2, i_3 and i_4 .



Given Variables:

$$R_1 : 4 \text{ ohm}$$

$$R_2 : 9 \text{ ohm}$$

$$g : 6 \text{ V/A}$$

Calculate the following:



$$i_1 (\text{A}) :$$

$$i_2 (\text{A}) :$$

$$i_3 (\text{A}) :$$

$$i_4 (\text{A}) :$$

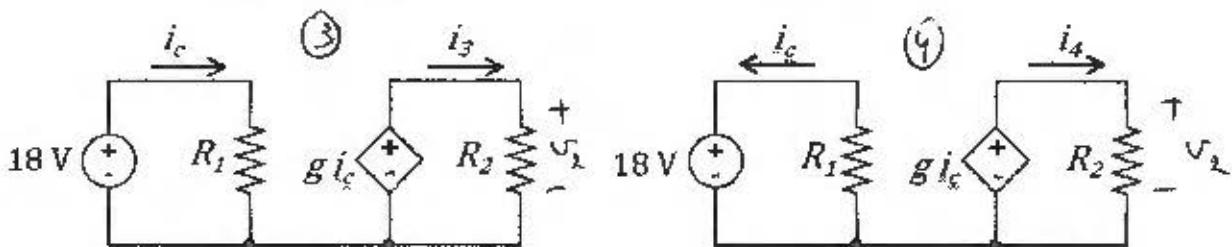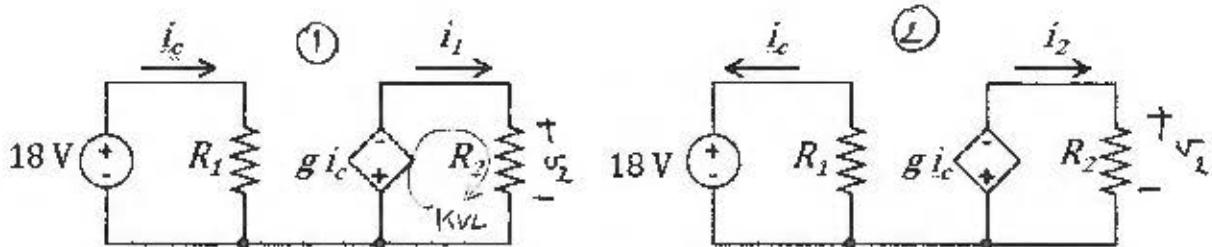Find the currents i_1, i_2, i_3 and i_4 .



$$R1 = 4 \Omega \quad \text{in } ① : \quad i_c = \frac{18}{R_1} = 4.5 \text{ A}$$

$$R2 = 3 \Omega$$

$$g = 2 \text{ V/A}$$

KVL in right part: $g i_c + V_2 = 0$

$$\Rightarrow V_2 = -g i_c = -9 \text{ V}$$

$$i_1 = \frac{V_2}{R_2} = \frac{-9}{3} \Rightarrow i_1 = -3 \text{ A}$$

$$\text{in } ② : \quad i_c = -4.5 \text{ A}$$

$$V_2 = -g i_c = 9 \text{ V}$$

$$i_2 = \frac{V_2}{R_2} = \frac{9}{3}$$

$$i_2 = 3 \text{ A}$$

$$\text{in } ③ : \quad i_c = 4.5 \text{ A}$$

$$V_2 = g i_c = 9 \text{ V}$$

$$i_3 = \frac{V_2}{R_2} = \frac{9}{3}$$

$$i_3 = 3 \text{ A}$$

$$\text{in } ④ : \quad i_c = -4.5 \text{ A}$$

$$V_2 = g i_c = -9 \text{ V}$$


$$i_4 = \frac{V_2}{R_2} = -\frac{9}{3}$$

$$i_4 = -3 \text{ A}$$

PP - Basic concepts 010

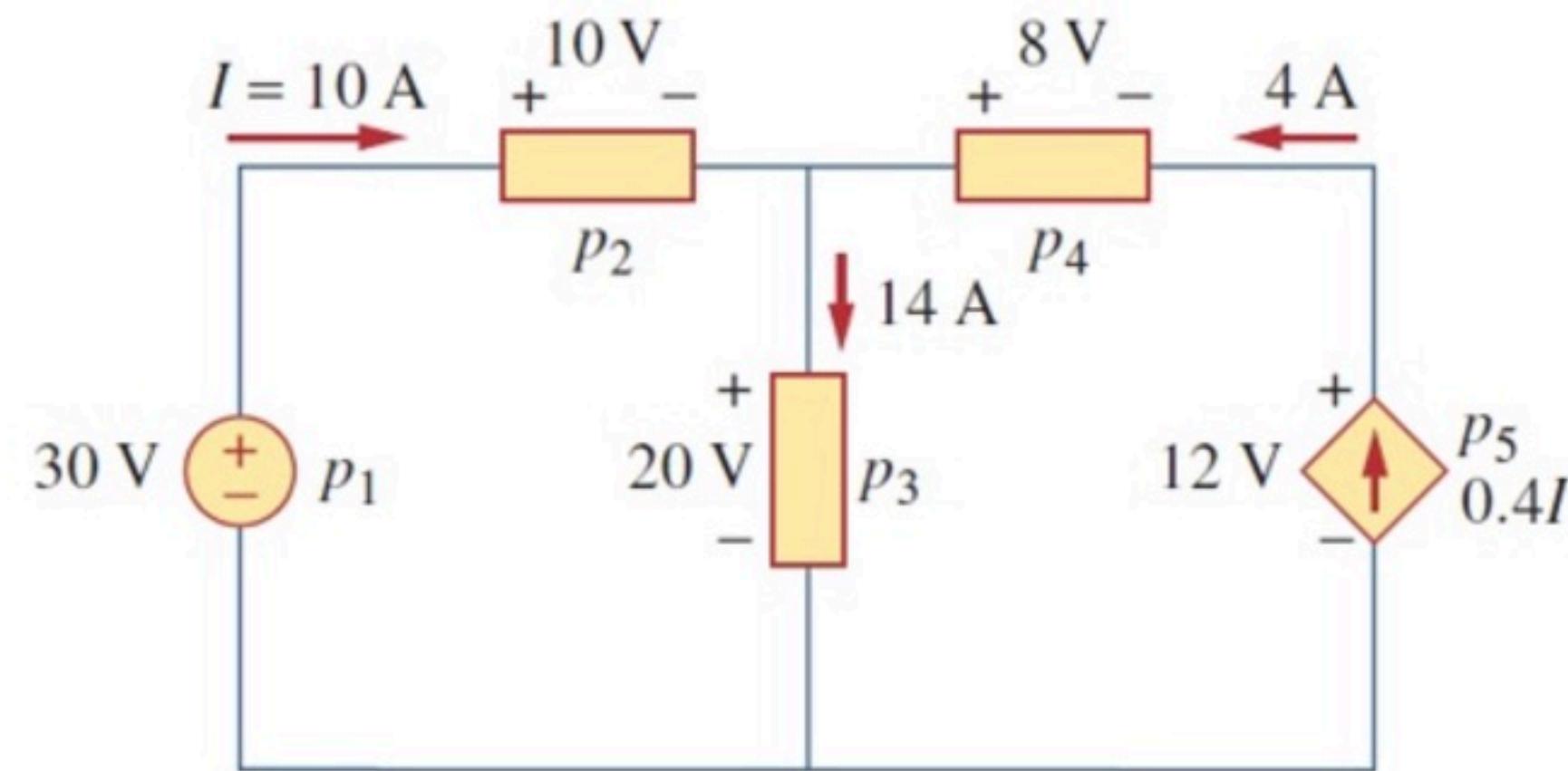Problem has been graded.

Find the power supplied by each of the elements.



Given Variables:

. . .

Calculate the following:

p_1 (W) :

300



p_2 (W) :

-100



p_3 (W) :

-280



p_4 (W) :

32



p_5 (W) :


48



PP - Basic concepts 011

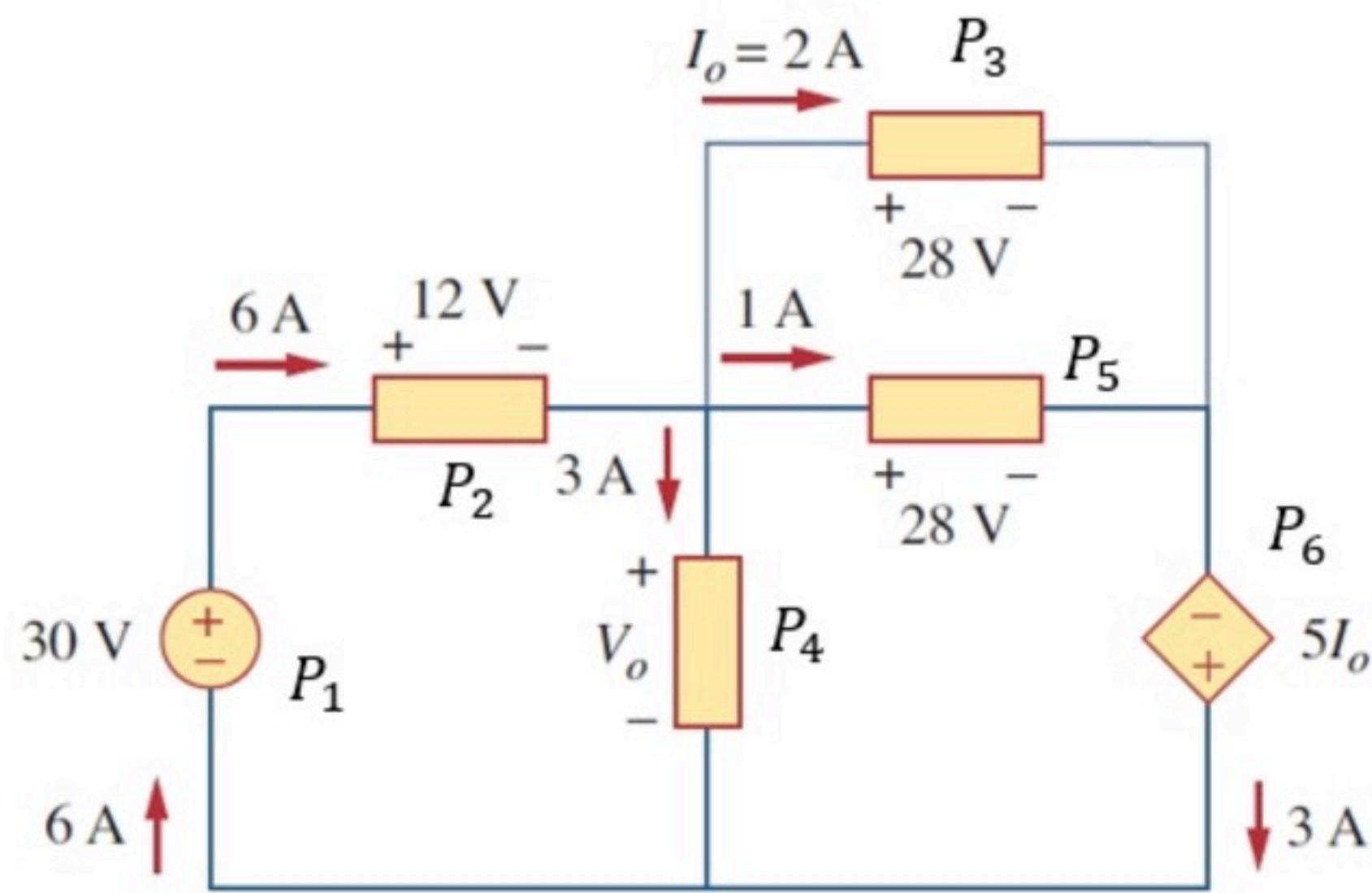Problem has been graded.

Find the power received by each of the elements.



Given Variables:

. . .

Calculate the following:

$P_1 (\text{W}) :$

-180



$P_2 (\text{W}) :$

72



$P_3 (\text{W}) :$

56



$P_4 (\text{W}) :$

54



$P_5 (\text{W}) :$

28



$P_6 (\text{W}) :$

-30




Basic Analysis 001b

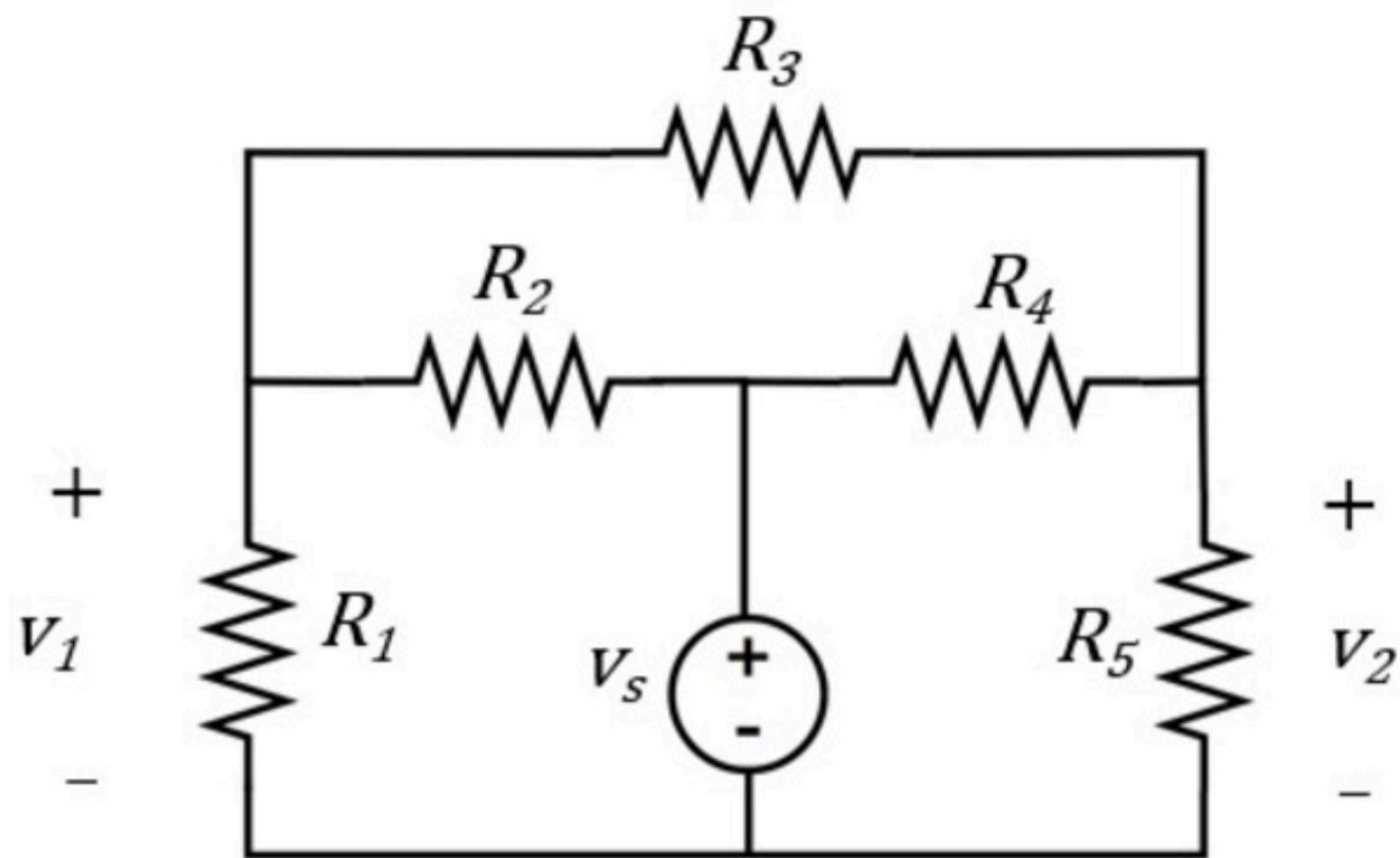Problem has been graded.

We measure v_1 and v_2 .

Determine the values of resistances R_2 and R_3 .



Given Variables:

$R_1 : 12 \text{ ohm}$

$R_4 : 12 \text{ ohm}$

$R_5 : 2 \text{ ohm}$

$v_s : 30 \text{ V}$

$v_1 : 12 \text{ V}$

$v_2 : 6 \text{ V}$

Calculate the following:

$R_2 (\text{ohm}) :$

$R_3 (\text{ohm}) :$

Hint: Find the currents and use Ohm's Law.

We measure v_1 and v_2 .

Determine the values of resistances R_2 and R_3 .

$$R_1 = 12 \Omega$$


$$R_4 = 9 \Omega$$

$$R_5 = 2 \Omega$$

$$v_S = 24 \text{ V}$$

$$v_1 = 12 \text{ V}$$

$$v_2 = 6 \text{ V}$$

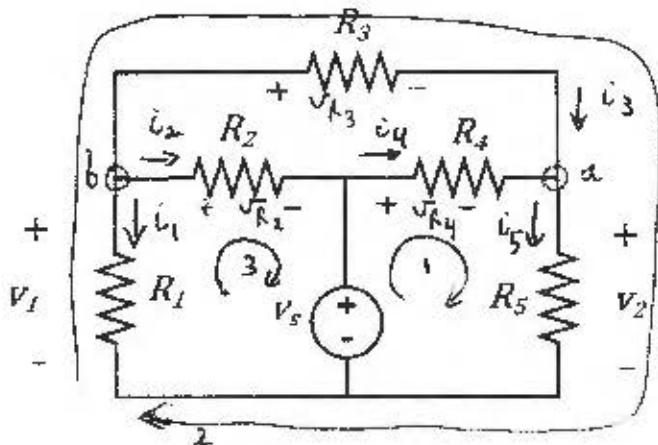

$$i_1 = \frac{v_1}{R_1} = \frac{12}{12} = 1 \quad i_5 = \frac{v_2}{R_5} = \frac{6}{2} = 3$$

$$\text{KVL 1: } v_3 = v_{R_4} + v_2 \Rightarrow v_{R_4} = v_3 - v_2 = 24 - 6 = 18$$

$$i_4 = \frac{v_{R_4}}{R_4} = \frac{18}{9} = 2$$

$$\text{KCL a: } i_3 + i_4 = i_5 \Rightarrow i_3 = i_5 - i_4 = 3 - 2 = 1$$

$$\text{KVL 2: } v_1 = v_{R_3} + v_2 \Rightarrow v_{R_3} = v_1 - v_2 = 6$$

$$R_3 = \frac{v_{R_3}}{i_3} = \frac{6}{1} \Rightarrow R_3 = 6 \Omega$$

$$\text{KCL b: } i_1 + i_2 + i_3 = 0 \Rightarrow i_2 = -i_1 - i_3 = -1 - 1 = -2$$

$$\text{KVL 3: } v_1 = v_{R_2} + v_S \Rightarrow v_{R_2} = v_1 - v_S = 12 - 24 = -12$$


$$R_2 = \frac{v_{R_2}}{i_2} = \frac{-12}{-2} \Rightarrow R_2 = 6 \Omega$$

PP - Basic analysis 001

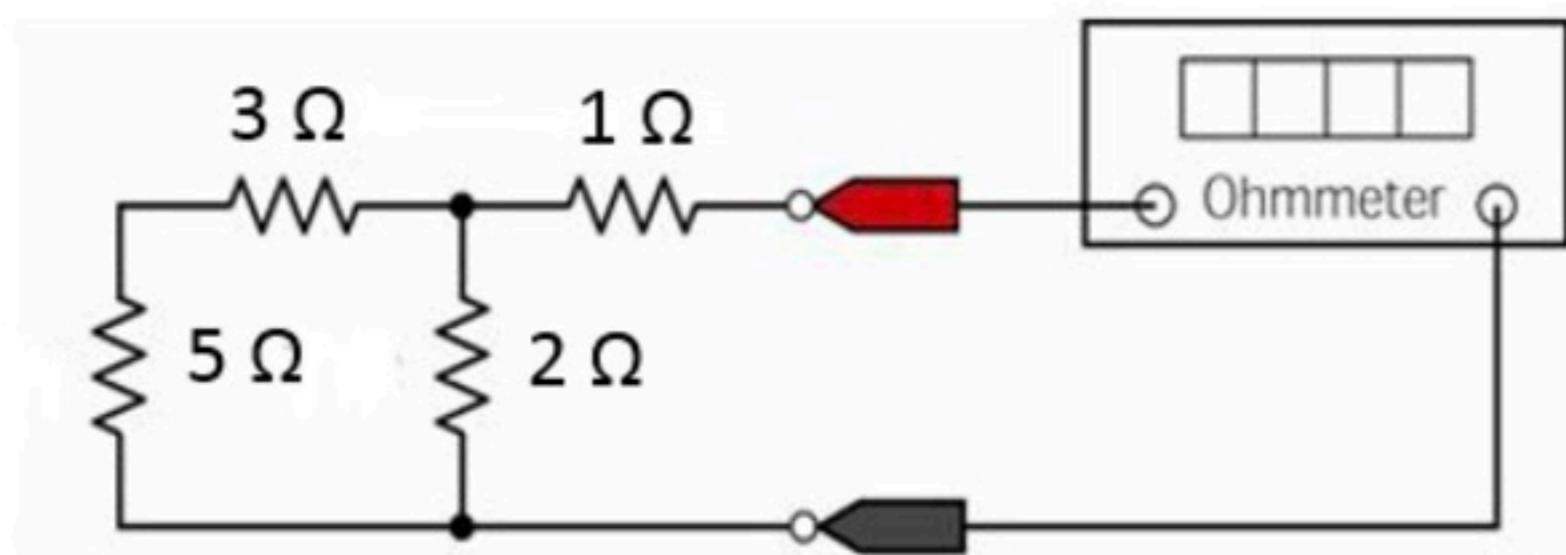Problem has been graded.

This circuit contains an ohmmeter. An ohmmeter is an instrument that measures the equivalent resistance of the circuit connected to its terminals. Note that you can set a multimeter to the ohm-setting to act as an ohmmeter, as you can test in the lab.

Determine the resistance, R , measured by the ohmmeter.



Given Variables:

. . .

Calculate the following:

R (ohm) :

2.6




Hint: Use series and parallel connection of resistors

PP - Basic analysis 002

Problem has been graded.

Find values of v_1 , i_1 , v_2 and i_2 .

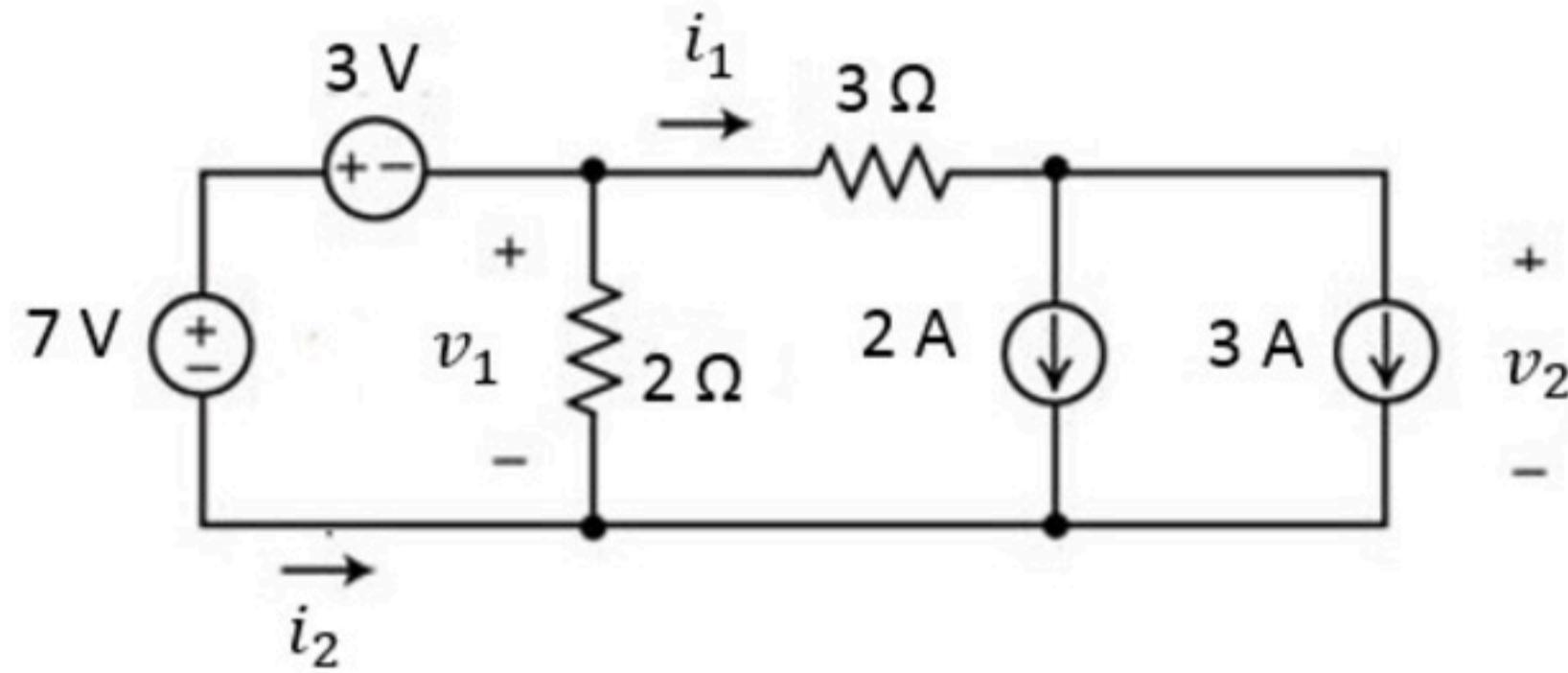

Given Variables:

. . .

Calculate the following:

v_1 (V) :

4



i_1 (A) :

5



v_2 (V) :

-11



i_2 (A) :

-7




Hint: Use KVL and KCL

PP - Basic analysis 003

Unlimited Attempts.

What is the reading X from the ammeter?

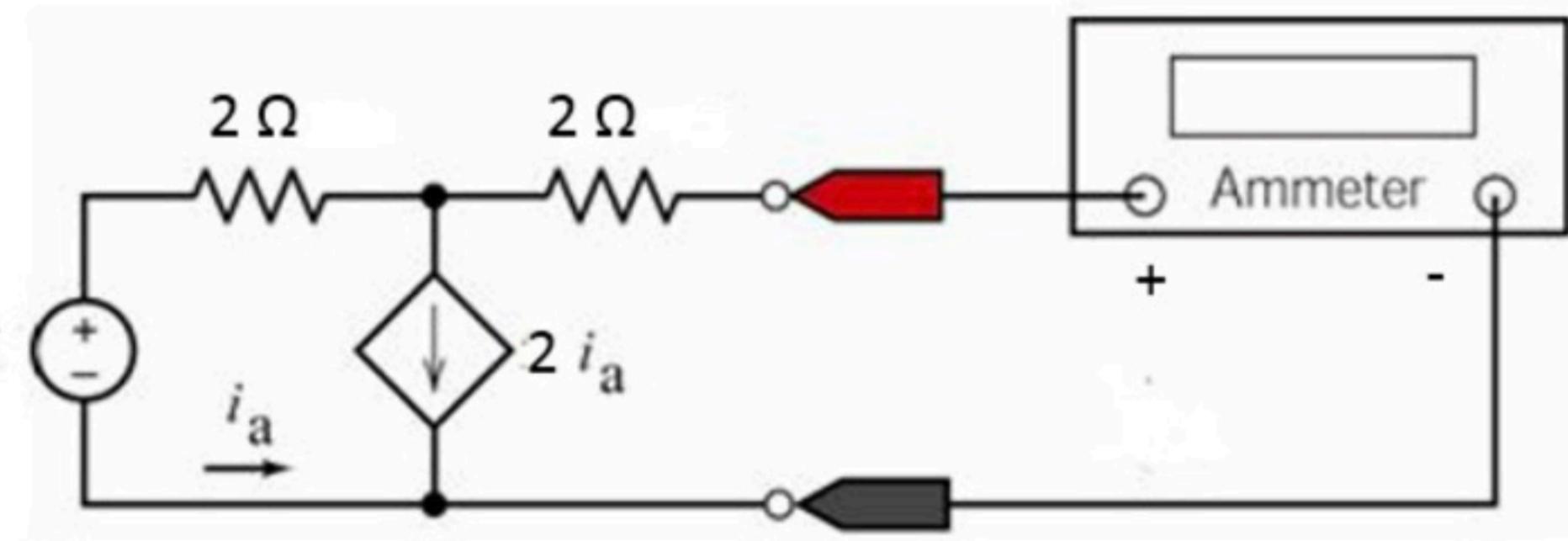What would be the reading Y if I replaced the ammeter by a volt-meter?



Given Variables:

...

Calculate the following:

X (A) :

3



Y (V) :

8







Hint: Ammeters and volt meters behave as short and open circuits respectively

Basic analysis 004

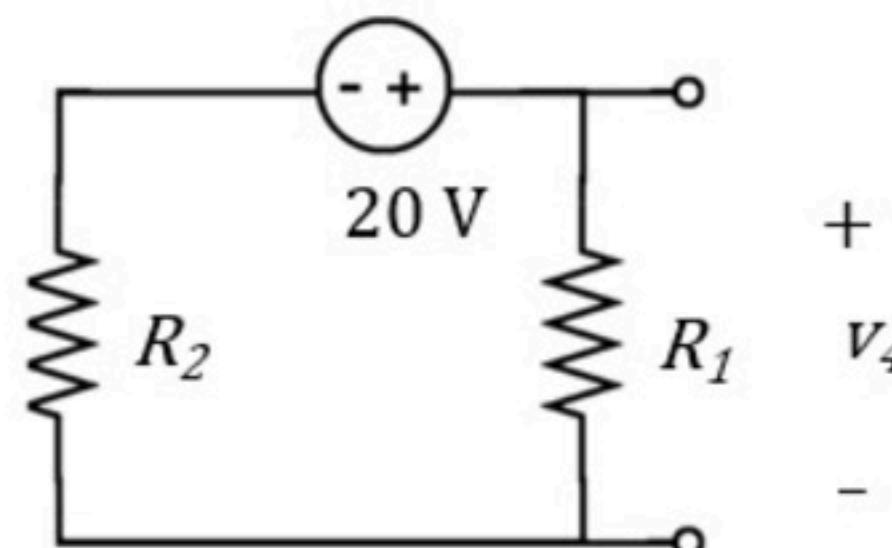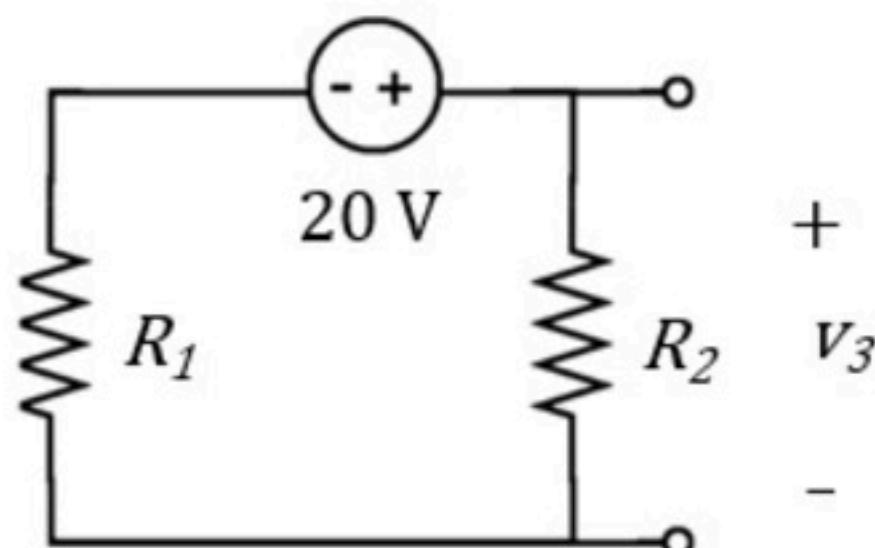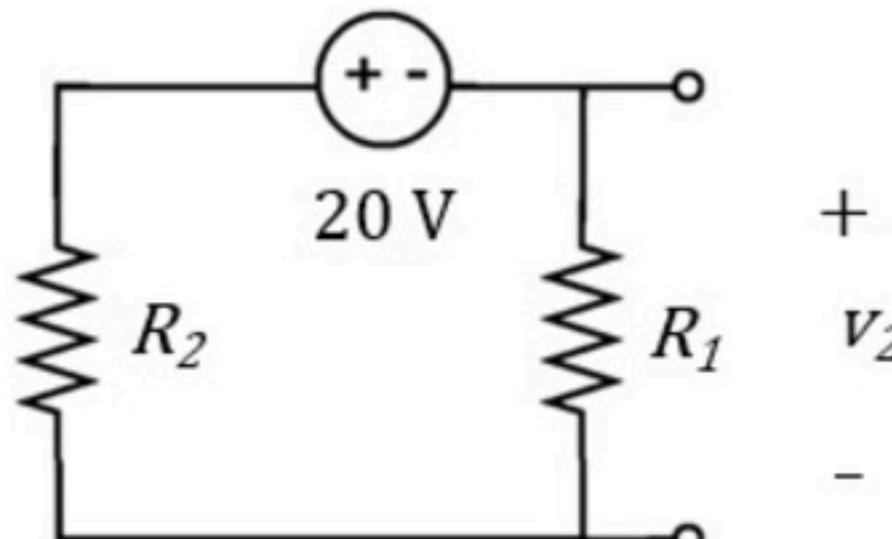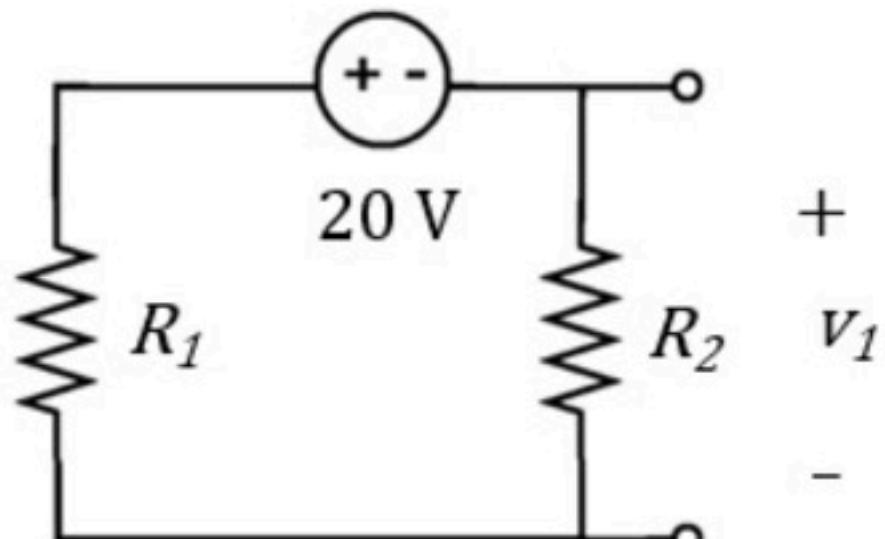Problem has been graded.

Determine the voltages v_1 , v_2 , v_3 and v_4



Given Variables:

$R_1 : 4 \text{ ohm}$

$R_2 : 6 \text{ ohm}$

Calculate the following:

$v_1 (\text{V}) :$



$v_2 (\text{V}) :$

$v_3 (\text{V}) :$

$v_4 (\text{V}) :$



Hint: Voltage divider and mind the signs.

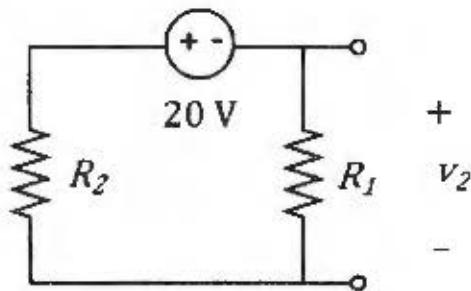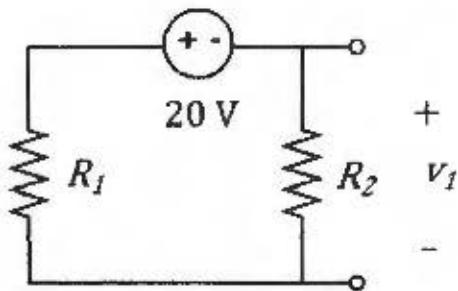Determine the voltages v_1, v_2, v_3 and v_4




$$R1 = 4 \Omega$$

$$R2 = 6 \Omega$$

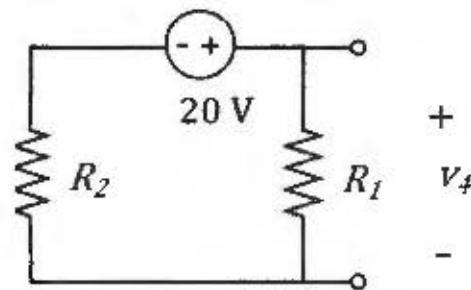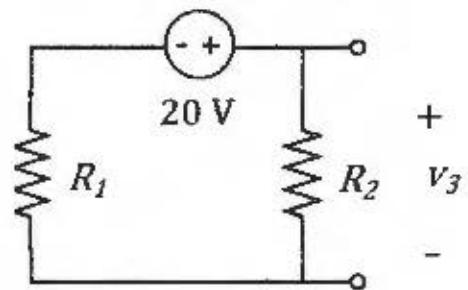

(a) VOLTAGE DIVIDER

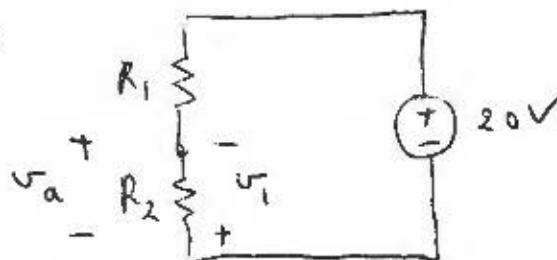


$$v_a = 20 \cdot \frac{R_2}{R_1 + R_2} = 20 \cdot \frac{6}{10} = 12 \text{ V}$$

$$v_1 = -v_a$$

$$v_1 = -12 \text{ V}$$

(b) SAME IDEA: $v_2 = -20 \cdot \frac{R_1}{R_1 + R_2} = -20 \cdot \frac{4}{10} = -8$

$$v_2 = -8 \text{ V}$$

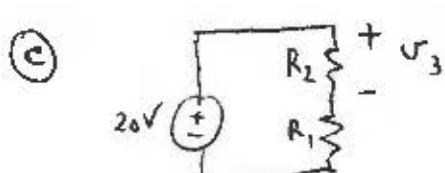

$$v_3 = 20 \cdot \frac{R_2}{R_1 + R_2} = 20 \cdot \frac{6}{10} = 12 \text{ V}$$

$$v_3 = 12 \text{ V}$$

(d) $v_4 = 20 \cdot \frac{R_1}{R_1 + R_2} = 20 \cdot \frac{4}{10} = 8$


$$v_4 = 8 \text{ V}$$

PP - Basic analysis 004

Unlimited Attempts.

What is the reading X from the ammeter?

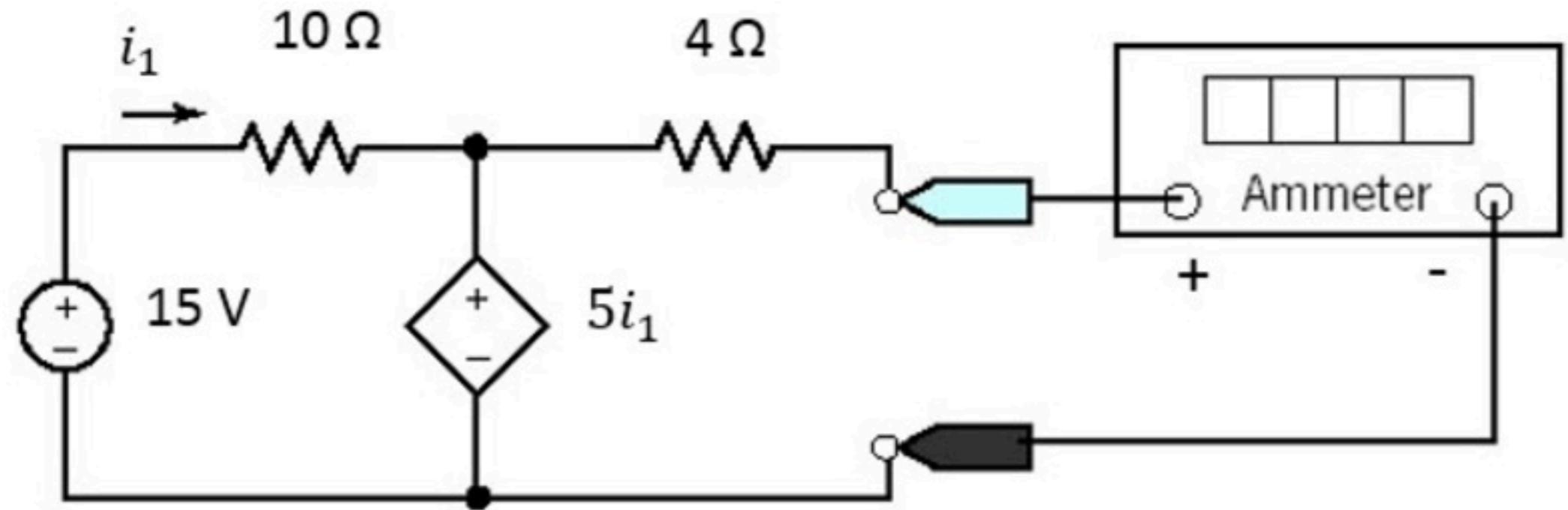What would be the reading Y if I replaced the ammeter by a volt-meter?



Given Variables:

. . .

Calculate the following:

X (A) :

1.25



Y (V) :

5




Hint: Ammeters and volt meters behave as short and open circuits respectively

Basic analysis 005

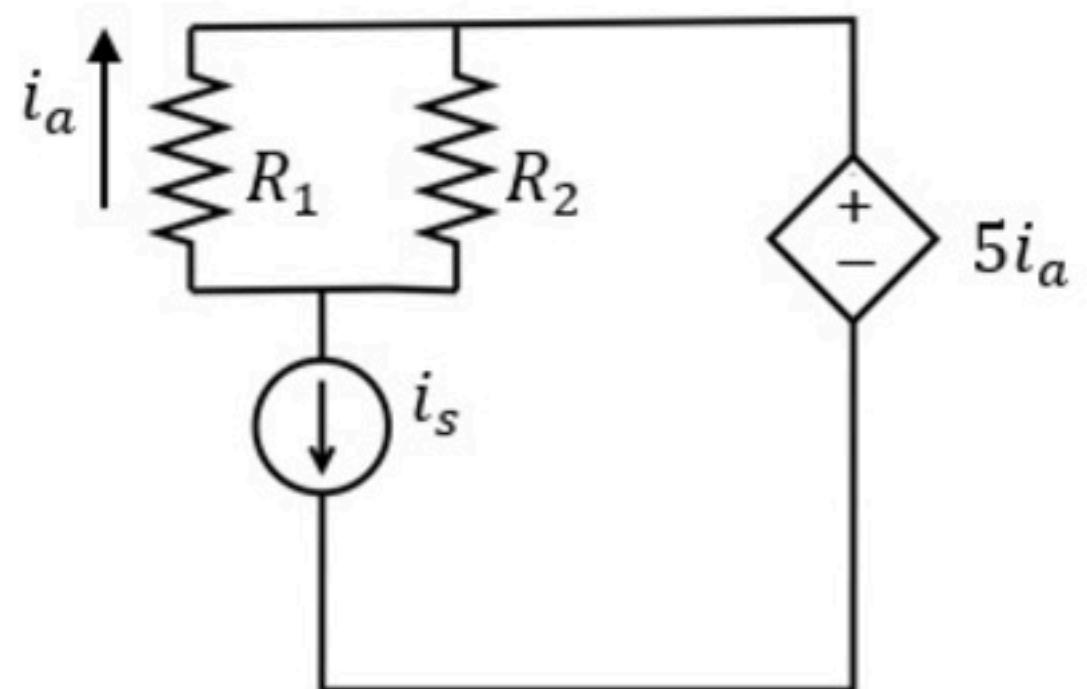Problem has been graded.

Find the power supplied by the dependent source.



Given Variables:

$R_1 : 5 \text{ ohm}$

$R_2 : 20 \text{ ohm}$

$i_s : 5 \text{ A}$

Calculate the following:

$P (\text{W}) :$



Hint: Use current divider

Find the power supplied by the dependent source.

$$R_1 = 14 \Omega$$


$$R_2 = 7 \Omega$$

$$i_s = 3 \text{ A}$$

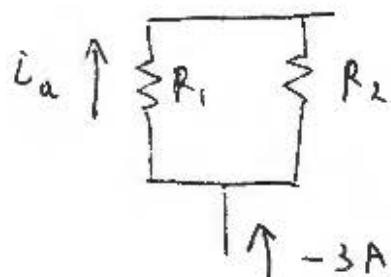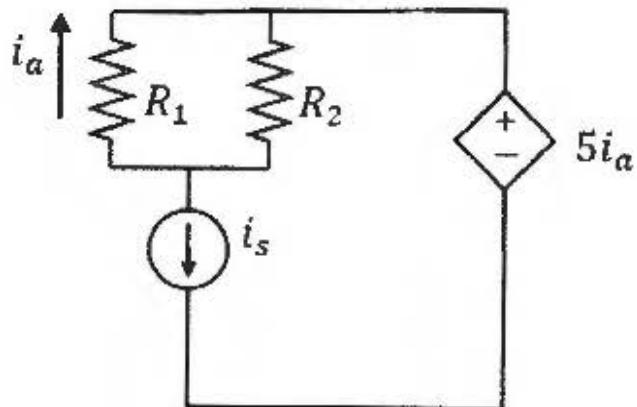

CURRENT DIVIDER
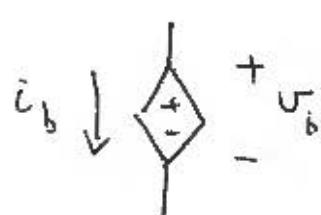
$$i_a = (-3) \cdot \frac{R_2}{R_1 + R_2} = -3 \cdot \frac{7}{21} = -1 \text{ A}$$



$$v_b = 5i_a = -5 \text{ V}$$

$$i_b = -i_s = -3 \text{ A}$$

$$P = v_b i_b = 15 \text{ W}$$

RECEIVED

(PASSIVE SIGN CONVENTION)

P = -15W SUPPLIED


PP - Basic analysis 005

Problem has been graded.

Someone did measurements on this circuit and found that

$$i_1 = 1 \text{ A}, v_2 = -20 \text{ V}, i_3 = -2 \text{ A} \text{ and } v_4 = -30 \text{ V}.$$

Find the values of R₁, R₂, R₃ and R₄.

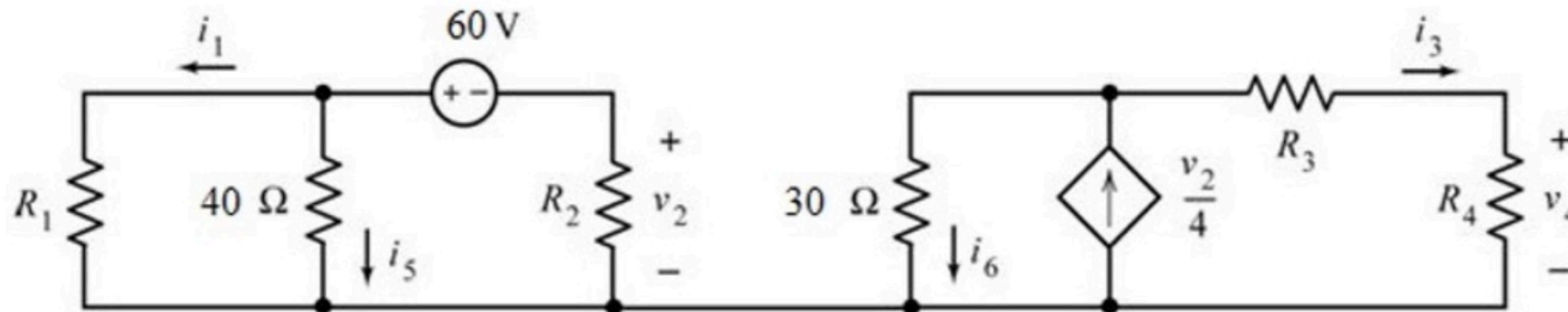

Given Variables:

...

Calculate the following:

R₁ (ohm) :

40



R₂ (ohm) :

10



R₃ (ohm) :

30



R₄ (ohm) :

15




Hint: Use KVL and KCL

Basic analysis 006

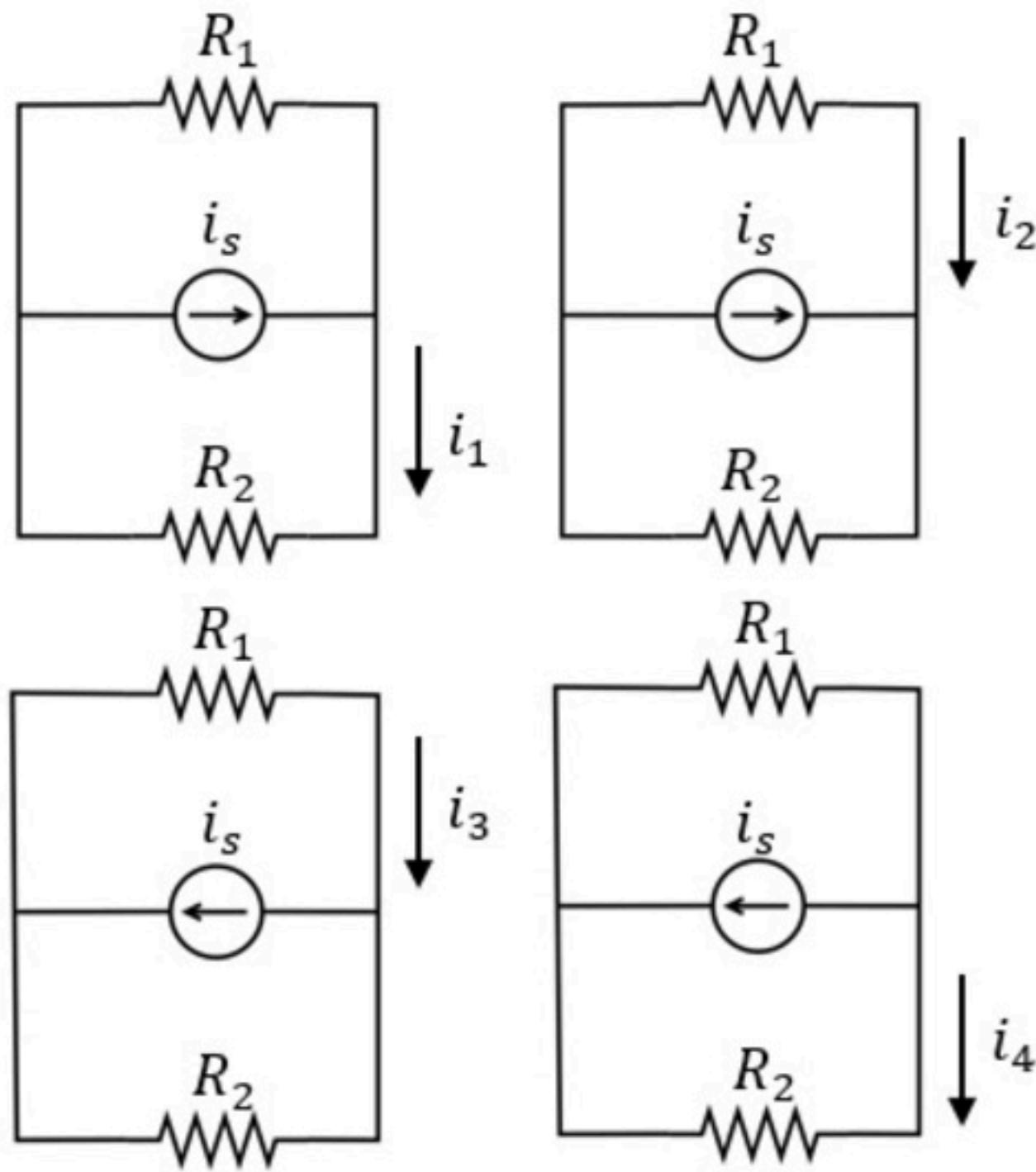Problem has been graded.

Determine the currents i_1, i_2, i_3 and i_4



Given Variables:

$R_1 : 25 \text{ ohm}$

$R_2 : 50 \text{ ohm}$

$i_s : 21 \text{ A}$

Calculate the following:

$i_1 (\text{A}) :$

$i_2 (\text{A}) :$

$i_3 (\text{A}) :$

$i_4 (\text{A}) :$





Hint: Use current divider

Determine the currents i_1, i_2, i_3 and i_4

$$R_1 = 30 \Omega$$

$$R_2 = 10 \Omega$$

$$i_s = 18 \text{ A}$$

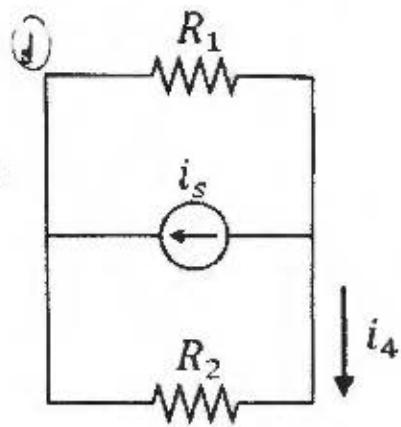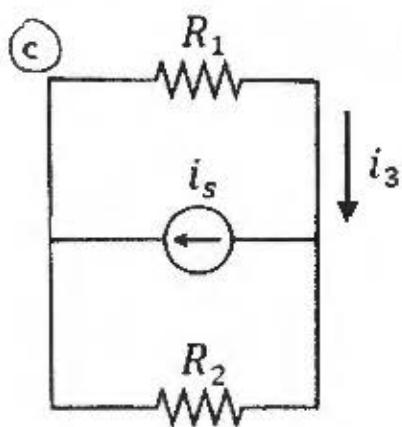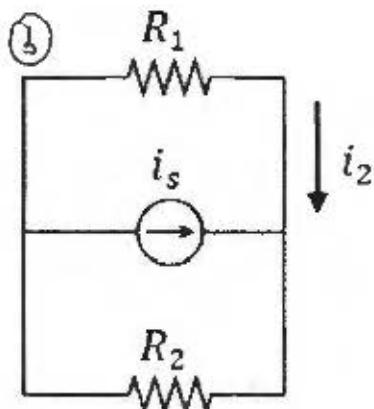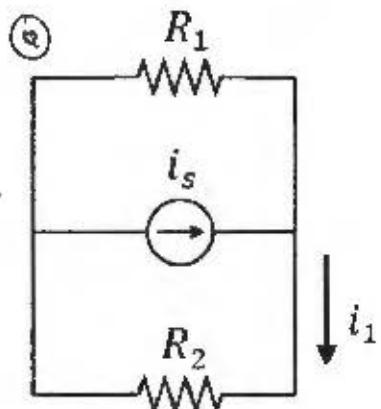

(a) CURRENT DIVIDER: $i_1 = i_s \cdot \frac{R_1}{R_1 + R_2} = 18 \cdot \frac{30}{40} = 13.5 \text{ A}$

$$i_1 = 13.5 \text{ A}$$

(b) $-i_2 = i_s \cdot \frac{R_2}{R_1 + R_2} = 18 \cdot \frac{10}{40} = 4.5 \text{ A} \Rightarrow i_2 = -4.5 \text{ A}$

$$i_2 = -4.5 \text{ A}$$

(c) $i_3 = i_s \cdot \frac{R_2}{R_1 + R_2} = 18 \cdot \frac{10}{40} = 4.5 \text{ A}$

$$i_3 = 4.5 \text{ A}$$


(d) $-i_4 = i_s \cdot \frac{R_1}{R_1 + R_2} = 18 \cdot \frac{30}{40} = 13.5 \text{ A}$

$$i_4 = -13.5 \text{ A}$$

PP - Basic analysis 006

Problem has been graded.

Find the values of the missing voltages.

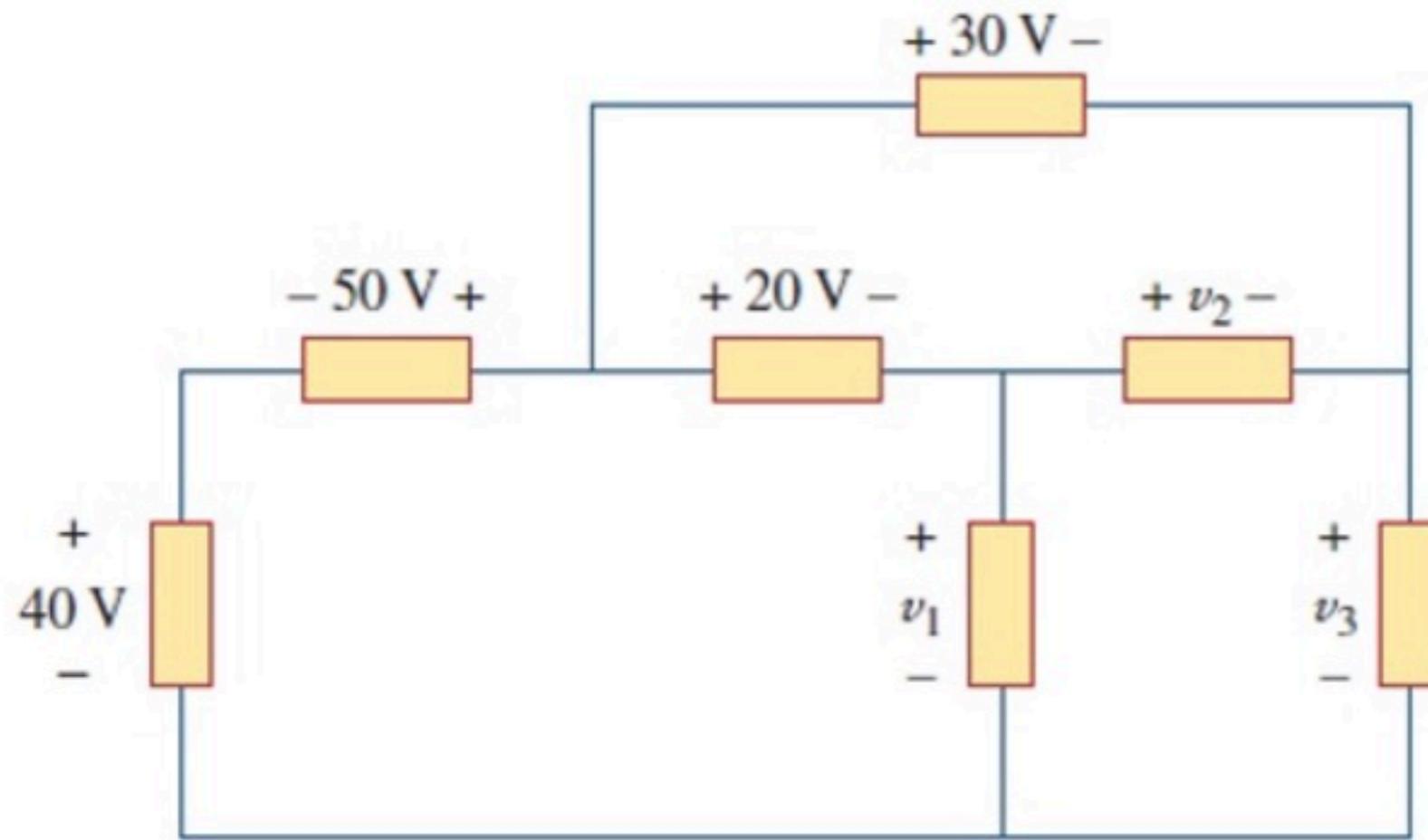

Given Variables:

. . .

Calculate the following:

v1 (V) :

70



v2 (V) :

10



v3 (V) :

60




Hint: Use KVL

PP - Basic analysis 007

Problem has been graded.

Calculate the voltage V_o .

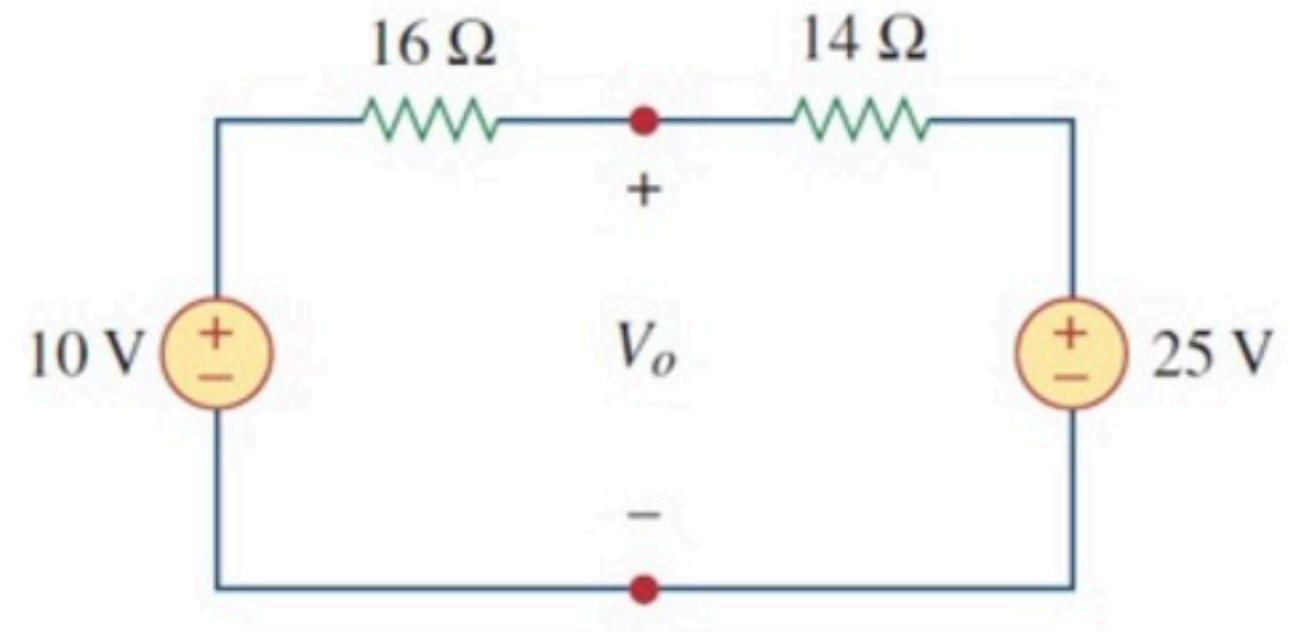

Given Variables:

. . .

Calculate the following:

V_o (V) :

18




Hint: Use KVL or combine the sources

Basic analysis 008

Problem has been graded.

Find the volt meter reading X.

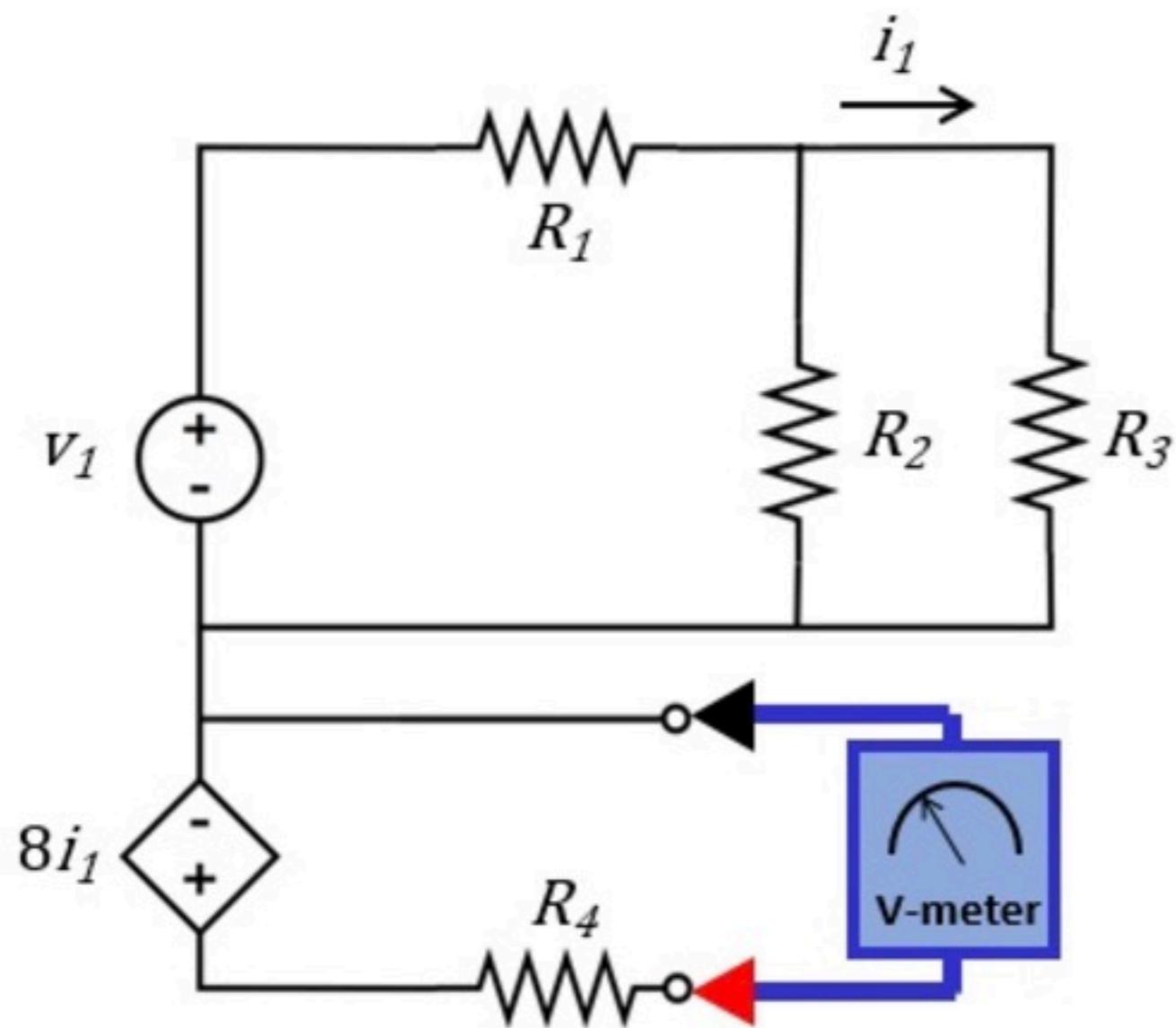

Given Variables:

$v1 : 20 \text{ V}$

$R1 : 10 \text{ ohm}$

$R2 : 15 \text{ ohm}$

$R3 : 10 \text{ ohm}$

$R4 : 20 \text{ ohm}$

Calculate the following:

$X (\text{V}) :$

Hint: Mind the direction of the V meter

Find the volt meter reading X.


$$v_1 = 10 \text{ V}$$

$$R_1 = 10 \Omega$$


$$R_2 = 15 \Omega$$

$$R_3 = 10 \Omega$$

$$R_4 = 10 \Omega$$

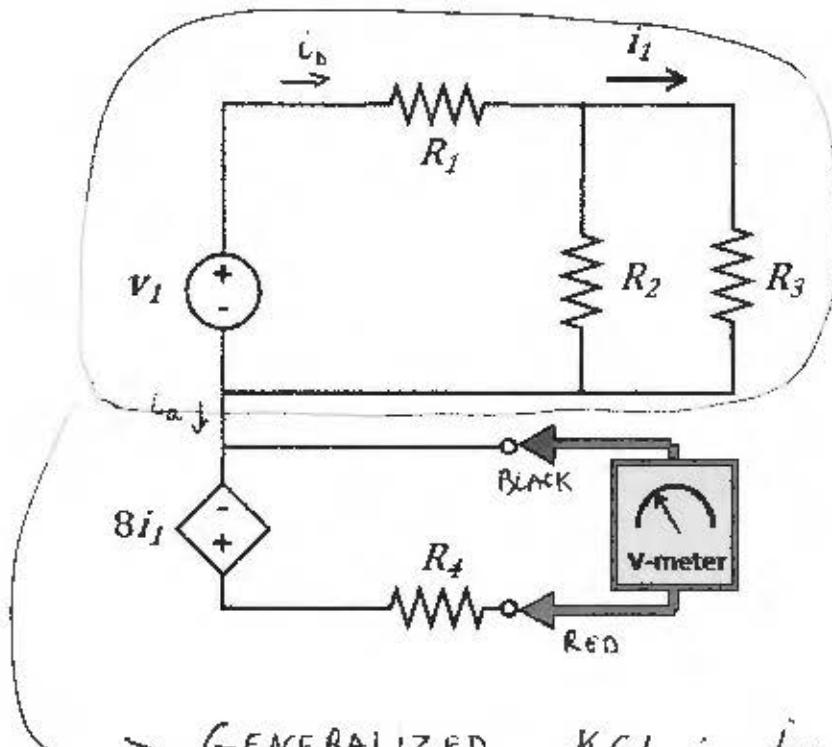


GENERALIZED KCL : $i_a = 0$

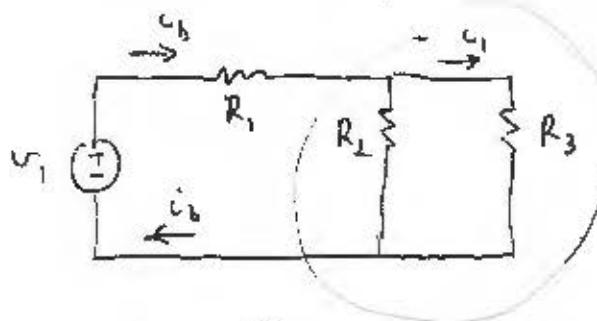

$$\begin{aligned} R_2 \parallel R_3 &= \left(\frac{1}{15} + \frac{1}{10} \right)^{-1} \\ &= \left(\frac{1}{5} \cdot \left(\frac{1}{3} + \frac{1}{2} \right) \right)^{-1} \\ &= \left(\frac{1}{5} \cdot \frac{5}{6} \right)^{-1} = 6 \Omega \end{aligned}$$

$$i_b = \frac{v_1}{R_1 + R_2 \parallel R_3} = \frac{10}{10 + 6} = \frac{10}{16}$$
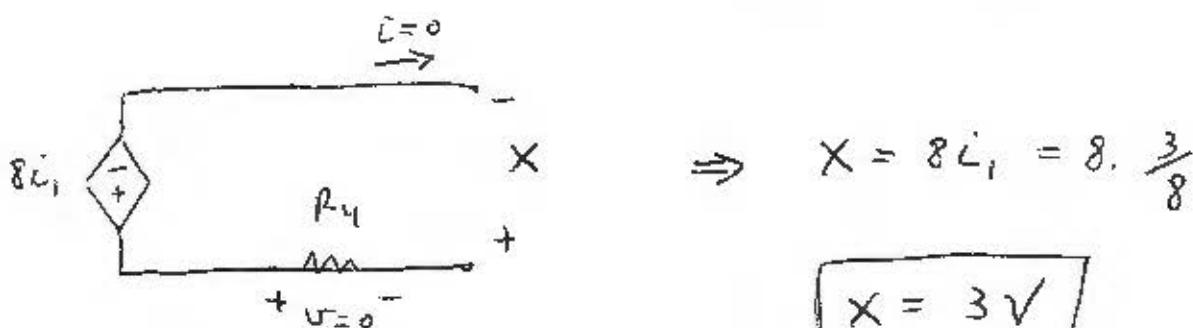
$$\text{CURRENT DIVIDER. } i_t = i_b \cdot \frac{R_2}{R_2 + R_3} = \frac{10}{16} \cdot \frac{15}{25} = \frac{3}{8}$$




$$X = 3V$$

PP - Basic analysis 008

Problem has been graded.

Calculate the voltage V_x .

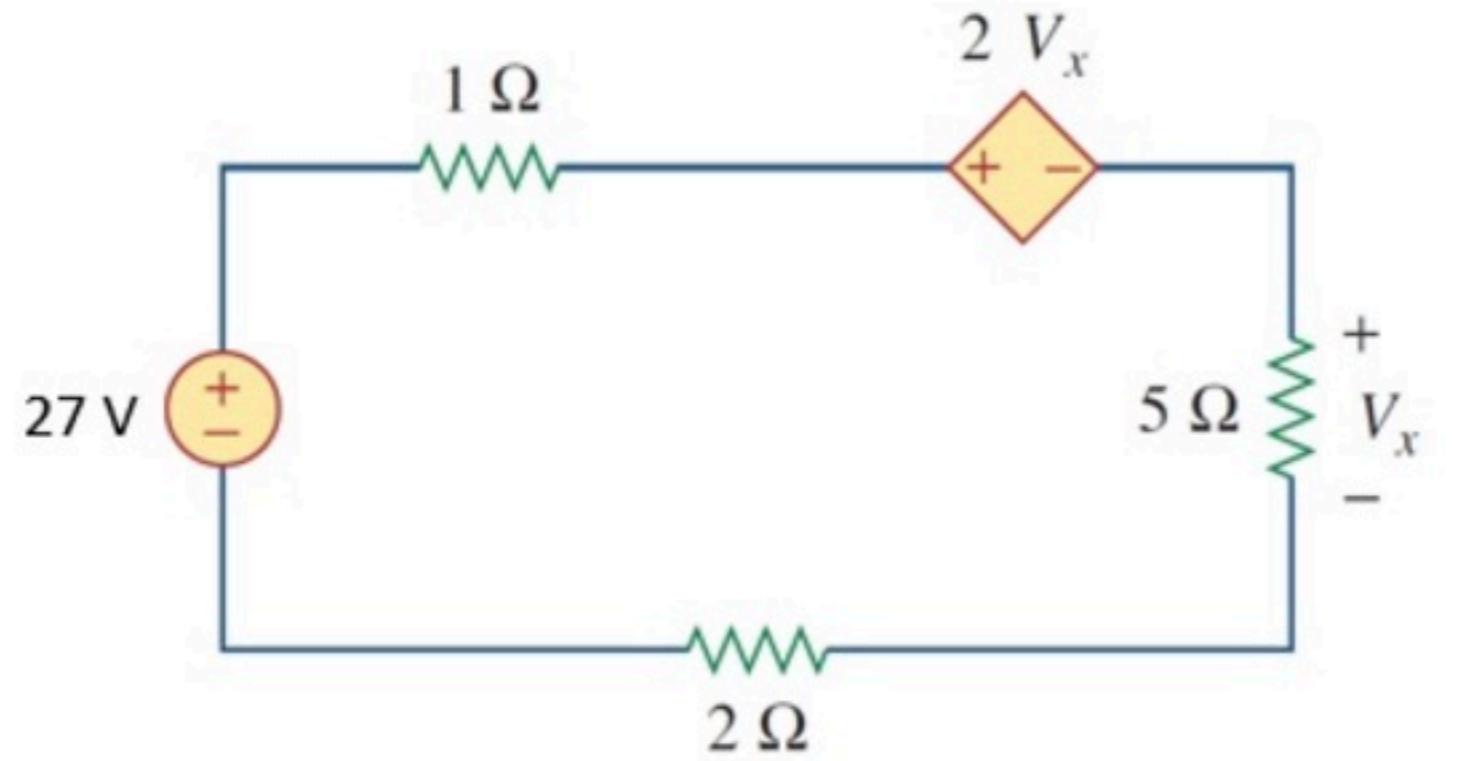

Given Variables:

. . .

Calculate the following:

V_x (V) :

7.5




Hint: Use KVL

PP - Basic analysis 009

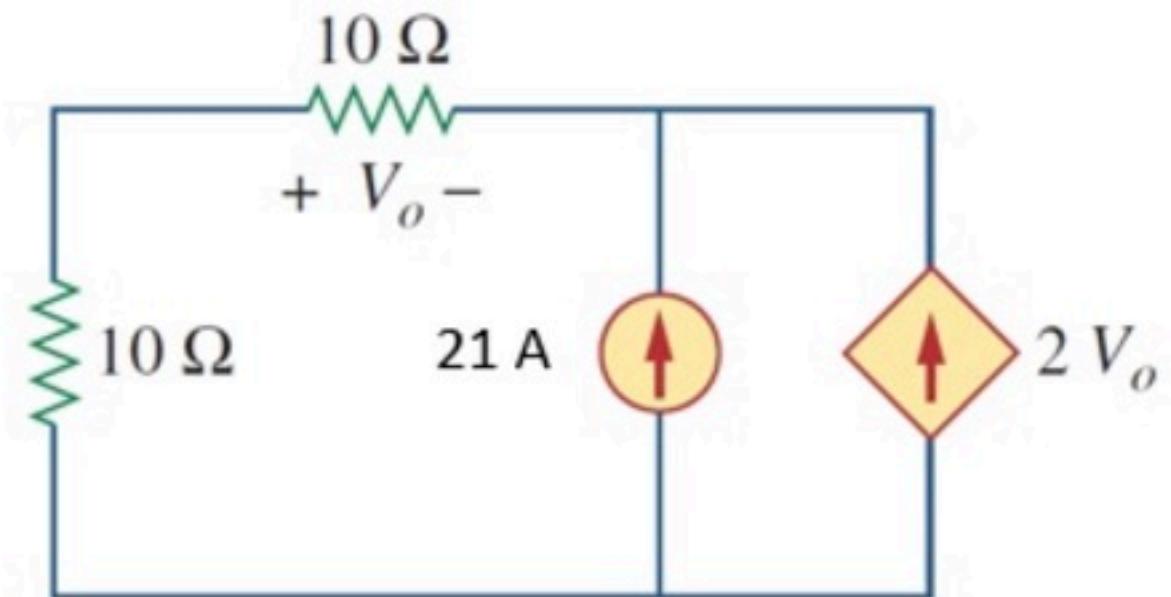Problem has been graded.

Find the power P supplied by the dependent source.



Given Variables:

. . .

Calculate the following:

P (W) :

-400




Hint: Use KCL to find the current through the resistors

PP - Basic analysis 010

Problem has been graded.

Find R_{eq} looking into the terminals.

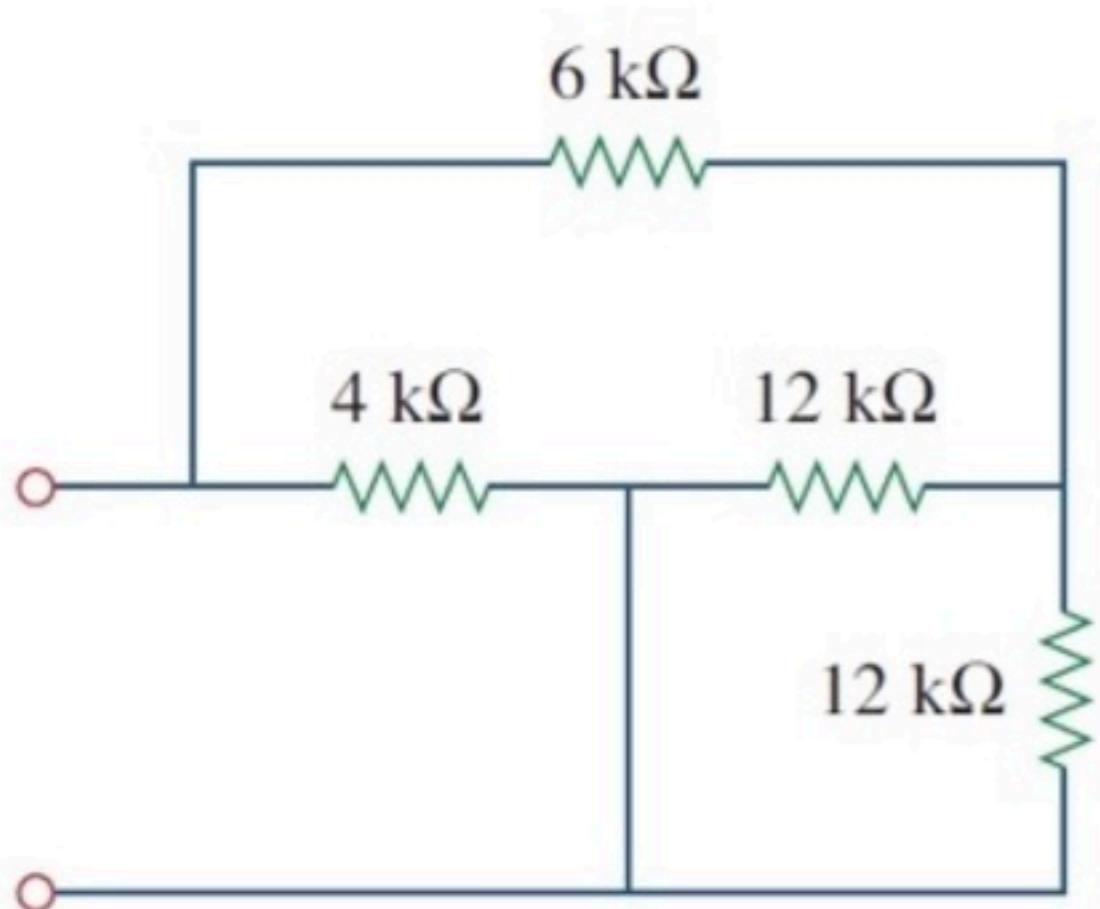

Given Variables:

...

Calculate the following:

Req (ohm) :

3000




Hint: Check units

PP - Basic analysis 011

Unlimited Attempts.

Find R_{eq} looking into the terminals.

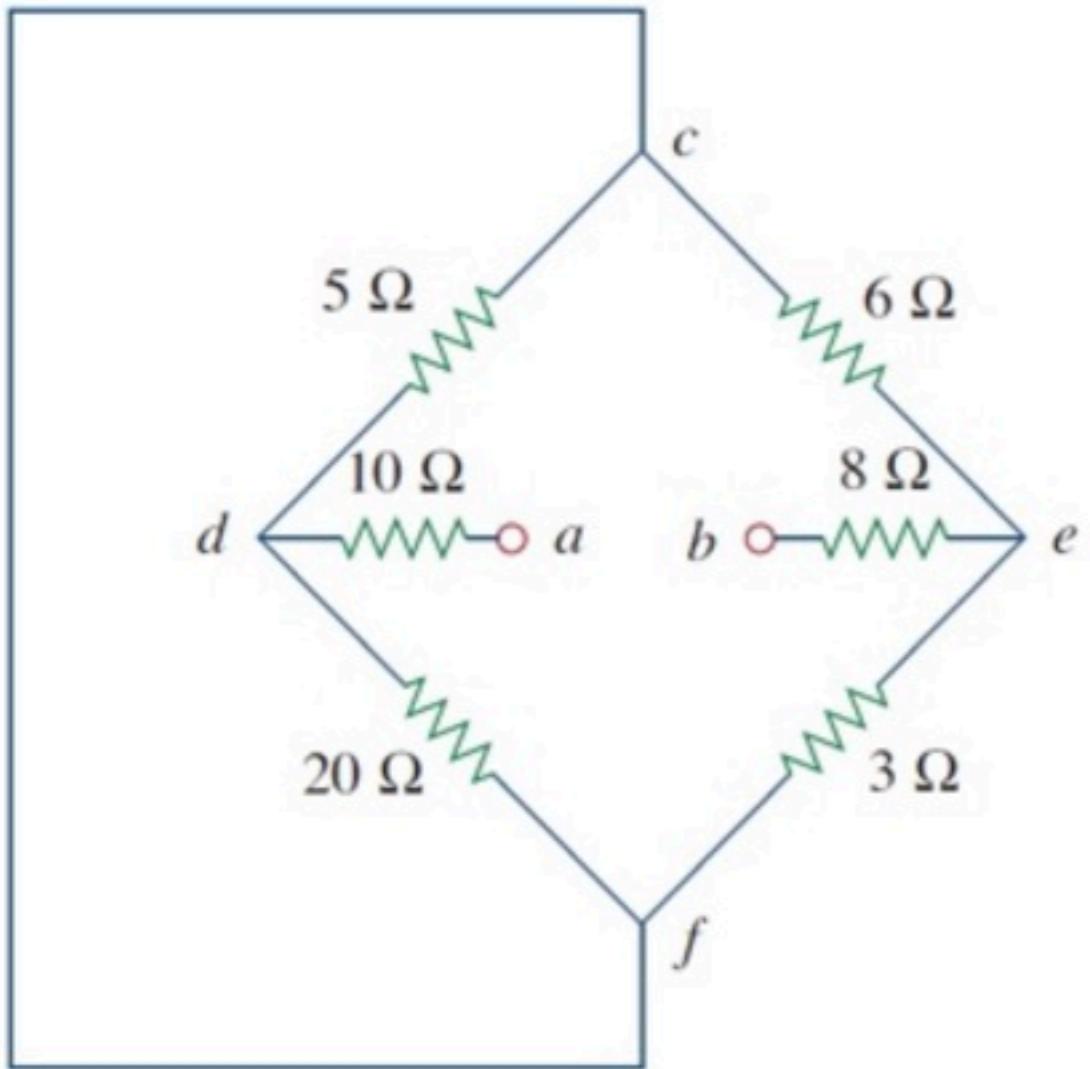

Given Variables:

...

Calculate the following:

Req (ohm) :

24




Hint: Use series and parallel connections of resistors

PP - Basic analysis 012

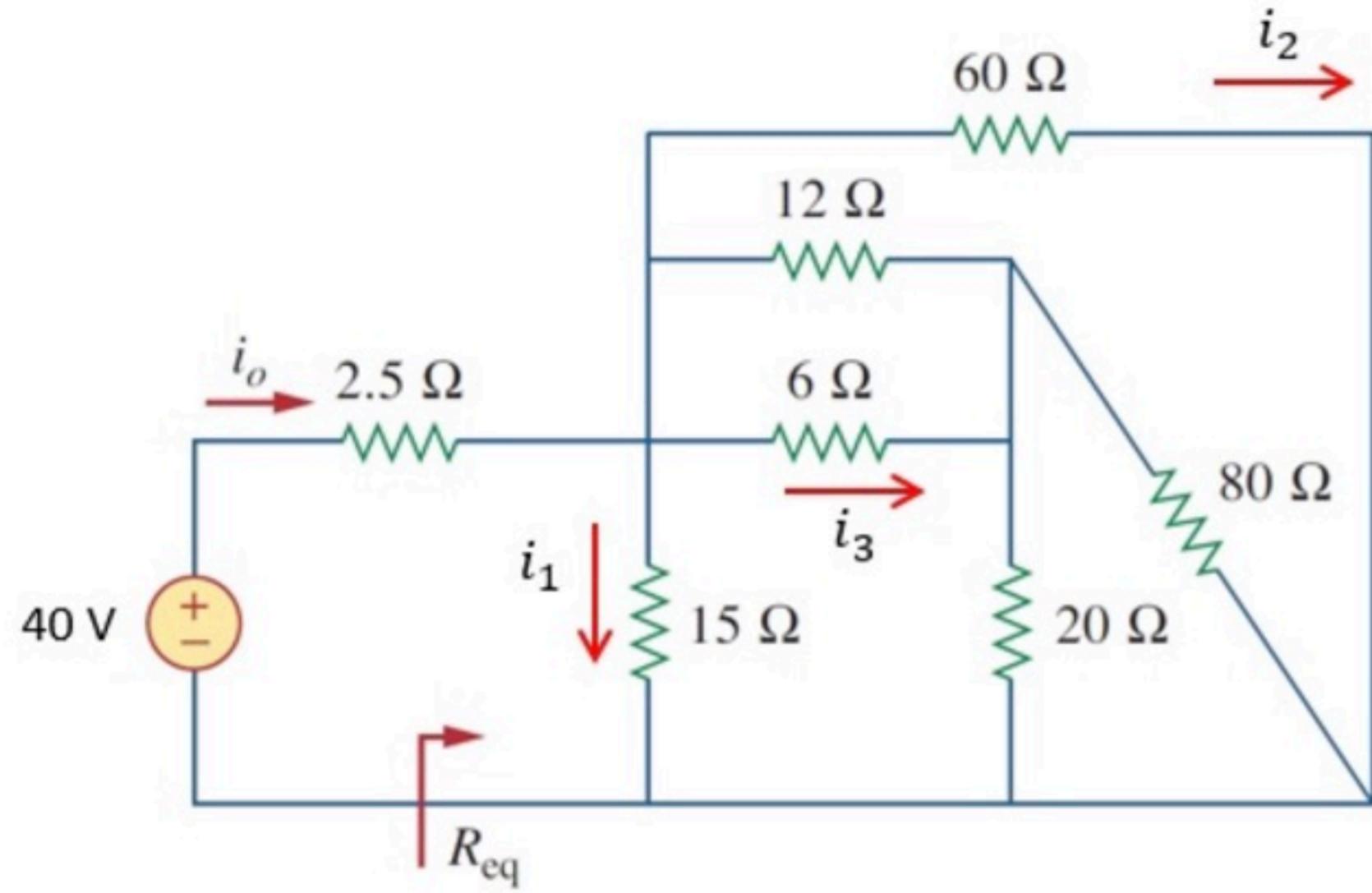Problem has been graded.

Calculate R_{eq} (does not include the $2.5\ \Omega$ resistor) and the currents i_o, i_1, i_2 and i_3 .



Given Variables:

...

Calculate the following:

Req (ohm) :

7.5



i_0 (A) :

4



i_1 (A) :

2



i_2 (A) :

0.5



i_3 (A) :

1



Hint: Use series and parallel connections of resistors