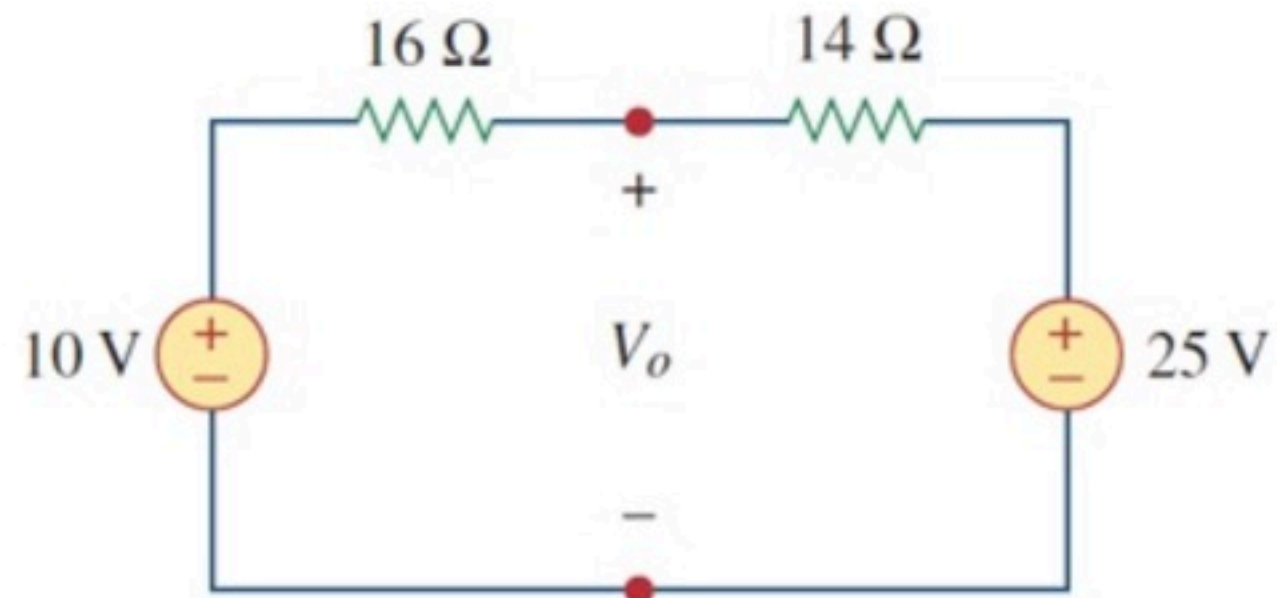


# PP - Basic analysis 007

Problem has been graded.

Calculate the voltage  $V_o$ .



Given Variables:

...

Calculate the following:

$V_o$  (V) :

18



Hint: Use KVL or combine the sources