

ECE 35, Spring 2020

Quiz 3

/ 10

Last name

First + middle  
name(s)


PID

(1) (5 points)

For  $t < 5$  s, the switch is open, and you may assume the system has reached steady state. The switch closes at time  $t = 5$  s.

(a) Find  $i_a(5^-)$ .

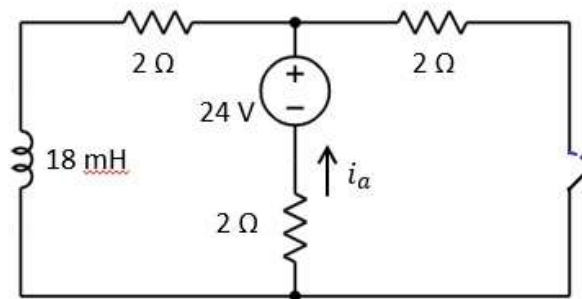(b) Find  $i_a(t)$  for  $t > 5$  s. Write the equation.



(2) (5 points)

- For time  $t < 0$  s, switch  $S_1$  is open and current source  $I_s$  is zero. The voltmeter reading is 1V.
- At time  $t = 0$  s, switch  $S_1$  remains open and the current source  $I_s$  jumps to  $Y$  (an unknown DC value).
- The moment the voltmeter reading becomes 9V, which happens at time  $t = 8$  s, switch  $S_1$  closes and the current source  $I_s$  becomes zero again.

(a) Find the voltmeter reading  $X$  at time  $t = 5$  s.

(b) Find the voltmeter reading  $X$  at time  $t = 11$  s.

