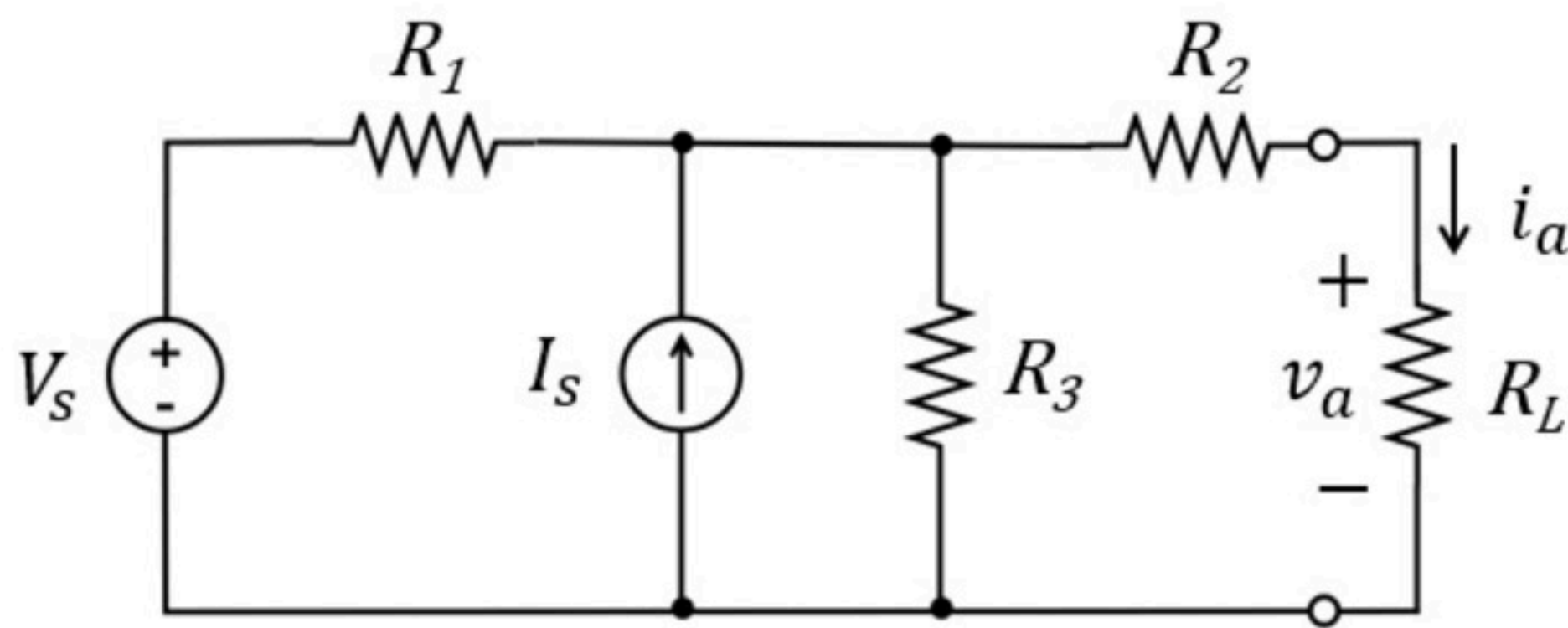


# Circuit theorems 010

Unlimited Attempts.

Find (and think about how to minimize your calculations)

1. The value of  $v_a = v_{a1}$  when  $R_L = 12\ \Omega$
2. The value of  $R_L = R_{L2}$  that results in  $v_a = 4\text{ V}$
3. The value of  $R_L = R_{L3}$  that results in  $i_a = 1\text{ A}$



Given Variables:

$V_s$  : 12 V

$I_s$  : 1 A

$R_1$  : 6 ohm

$R_2$  : 8 ohm

$R_3$  : 12 ohm

Calculate the following:

$v_{a1}$  (V) :

$R_{L2}$  (ohm) :

$R_{L3}$  (ohm) :

Hint: Find the Thevenin model of the circuit (without  $R_L$ ) first