
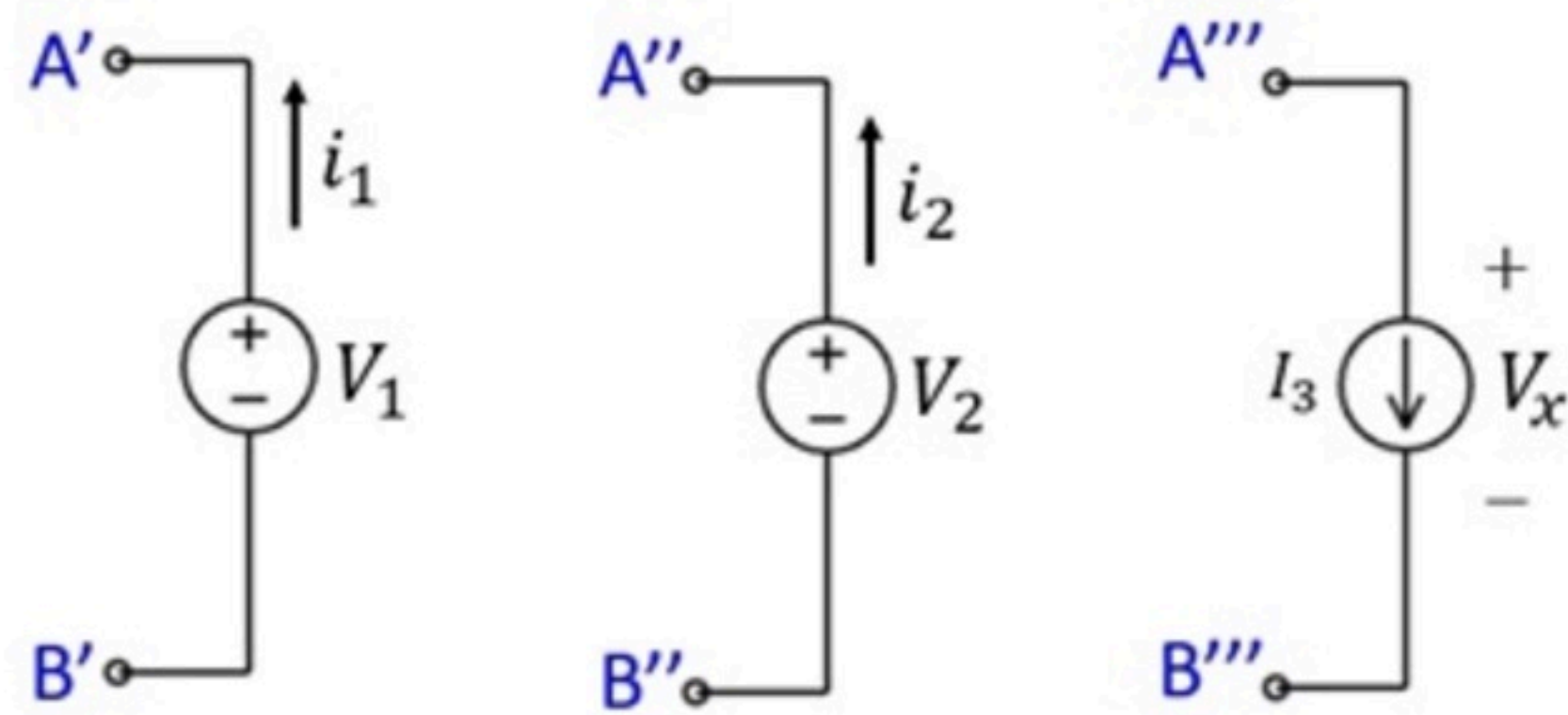


Circuit theorems 013

No more attempts left.

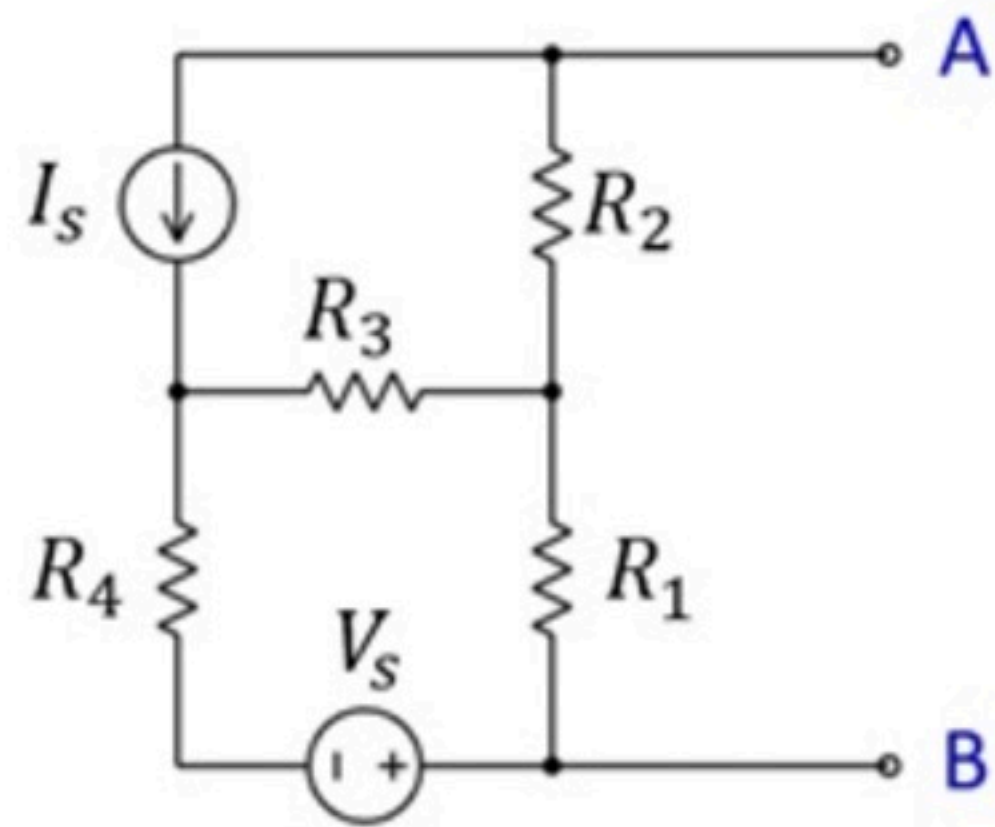Consider the circuit on the left. You are not given the values of V_S , I_S , R_1 , R_2 or R_3 .



You are told the value of current i_1 if V_1 is attached to this circuit, with A connected to A' and B connected to B' .

You are also told the value of current i_2 if V_2 is attached, with A connected to A'' and B connected to B'' . However, in this case, the independent sources were first turned off (i.e., $V_S = 0$ and $I_S = 0$).

Your task is to find V_x if current source I_3 is connected to the original circuit (i.e., with the independent sources V_S and I_S not turned off), with A connected to A''' and B connected to B''' .

Given Variables:

V_1 : 6 V

i_1 : 12 A

V_2 : 12 V

i_2 : 12 A

I_3 : -7 A

R_4 : 2 ohm

Calculate the following:

V_x (V) :

Hint: Redraw the circuit on the left as its Thevenin equivalent model