

Problem 1. (10 points)

Consider an op-amp connected in the inverting configuration to achieve a closed-loop gain of 40 dB (this is the absolute value of the voltage gain) using $1\text{ k}\Omega$ and $100\text{ k}\Omega$ resistors. A load resistance R_L is connected from the output to ground. A sine-wave signal of peak amplitude V_p is used as the input signal.

Assume an ideal op-amp with $V_{sat} = \pm 10\text{V}$ and $I_{out,max} = 20\text{ mA}$, and answer the following questions. Show your work.

- For $R_L = 400\ \Omega$, what is the maximum possible V_p while an undistorted output sinusoidal signal is obtained?
- If it is desired to obtain an output sinusoidal signal with a peak amplitude of 10V , What values of R_L are allowed?

Closed loop gain, of the op-amp = $10^{\frac{40}{20}} = 100$

For inverting amplifier,

$$\frac{V_{out}}{100\text{K}} + \frac{V_{out}}{R_L} = I_{out}$$

(a) For maximum possible V_p , with $R_L = 400\Omega$, we can write,

$$\begin{aligned} \frac{100V_{p,max}}{100k} + \frac{100V_{p,max}}{0.4k} &= I_{out,max} = 20\text{m} \\ \Rightarrow V_{p,max} &= \frac{20}{251}\text{V} = 79.68\text{ mV} \end{aligned}$$


(b) Similarly, for $V_{out} = 10\text{V}$, we can write,

$$\begin{aligned} \frac{10}{100k} + \frac{10}{R_{L,min}} &= I_{out,max} = 20\text{m} \\ \Rightarrow R_{L,min} &= 502.5\ \Omega \end{aligned}$$

So $R_L > 502.5\Omega$ to obtain output sinusoidal signal with a peak amplitude of 10 V .

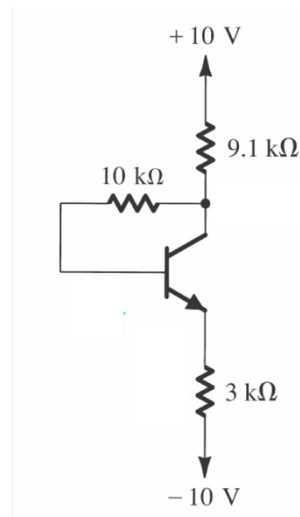Problem 2. (10 points)

In the following circuit, find the values of the collector, base and emitter currents and the collector, base and emitter node voltages. Assume $\beta = 100$, $V_{D0} = 0.7\text{ V}$, $V_{sat} = 0.2\text{ V}$.



Assuming, BJT is in active mode

$$\Rightarrow I_E = (\beta + 1)I_B \text{ and } I_C = \beta I_B$$

Now, from CE KVL,

$$10 = 9.1k \times I_E + 10k \times \frac{I_E}{\beta + 1} + V_{D0} + 3k \times I_E - 10$$

$$\Rightarrow I_E = 1.582\text{ mA}$$

$$\Rightarrow I_B = 15.663\text{ }\mu\text{A}$$

$$\Rightarrow I_C = 1.5663\text{ mA}$$

$$\Rightarrow V_C = 10 - 9.1 \times 1.582 = -4.3962\text{ V}$$

$$\Rightarrow V_E = -10 + 3 \times 1.582 = -5.254\text{ V}$$


$$\Rightarrow V_B = V_E + 0.7 = -4.554\text{ V}$$

$$\Rightarrow V_{CE} = 0.8578\text{ V} > V_{D0} \Rightarrow \text{Assumption correct}$$

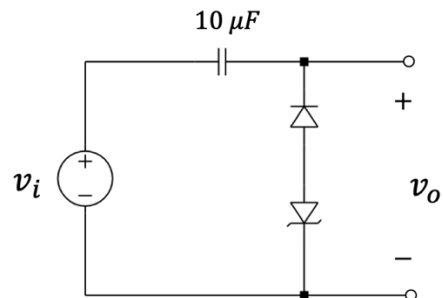Problem 3. (10 points)

In the circuit below, $v_i(t) = 4 \sin(\omega t)$ where $\omega = 1000 \text{ rad/s}$, $v_c(0) = 0$, $v_o(0) = 0$.

Use $V_{D0} = 0.7 \text{ V}$, $V_Z = 2.3 \text{ V}$.



- What is the value of $v_o(t)$ at $t = 2 \text{ ms}$?
- What is the value of $v_o(t)$ at $t = 6 \text{ ms}$?

$v_i(t) = 4 \sin(\omega t)$ where $\omega = 1000 \text{ rad/s}$, $v_c(0) = 0$, $v_o(0) = 0$, $V_{D0} = 0.7 \text{ V}$, $V_Z = 2.3 \text{ V}$.

Period of the input, $T = \left(\frac{\omega}{2\pi}\right)^{-1} = 6.2832 \text{ ms}$.

- (a) @ 2 ms , $v_i(t)$ is in first half cycle and diode is OFF. Since diode will not conduct in the first half cycle

$$\Rightarrow v_o(2 \text{ ms}) = v_i(2 \text{ ms}) = 3.6372 \text{ V}$$

- (b) Diode starts to conduct once $v_i(t)$ goes below -3 V or $t \geq 3.98965 \text{ ms}$ and input voltage reaches negative peak at $t = 4.7124 \text{ ms}$. After that, circuit will behave as a positive clamp circuit. So,

$$v_o(6 \text{ ms}) = v_i(6 \text{ ms}) + (V_{neg_peak} - V_Z - V_{D0}) = -0.11766 \text{ V}$$