

AC power 005

0 of 5 attempts made


$$v_s(t) = A_1 \cos(500t + B_1)$$

Find the complex power $\mathbf{S}_1 = a_1 + b_1j$ received by the source v_s .

Find the complex power $\mathbf{S}_2 = a_2 + b_2j$ received by the resistor R_1 .

Find the complex power $\mathbf{S}_3 = a_3 + b_3j$ received by the resistor R_2 .

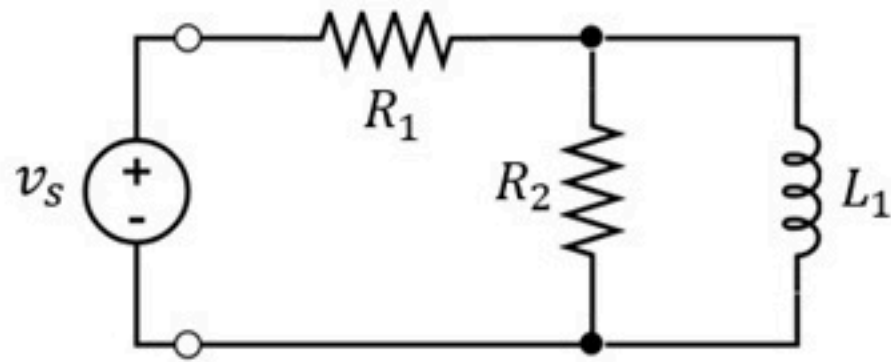Find the complex power $\mathbf{S}_4 = a_4 + b_4j$ received by the inductor L_1 .



Given Variables:

A1 : 6 V

B1 : 45 degrees

R1 : 4 ohm

R2 : 4 ohm

L1 : 8 mH

Calculate the following:

a1 (W) :

-2.7

✓

b1 (VAR) :

-0.9

✓

a2 (W) :

1.8

✓

b2 (VAR) :

0

✓

a3 (W) :

0.9

✓

b3 (VAR) :

0

✓

a4 (W) :

0

✓

b4 (VAR) :

0.9

✓