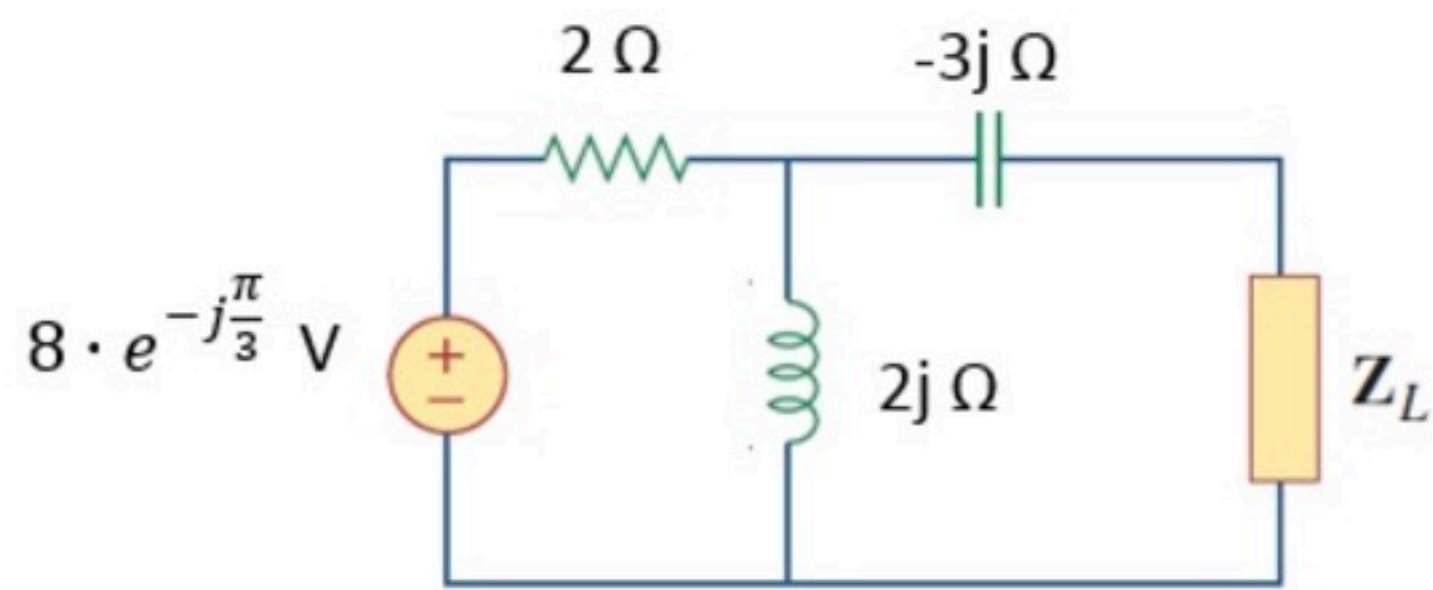


PP AC power 008

Unlimited Attempts.

Find the value of $\mathbf{Z_L} = a + jb$ that will receive the maximum amount of power

Find the resulting complex power $\mathbf{S} = c + jd$ received by the load.



Given Variables:

...

Calculate the following:

a (ohm) :

1



b (ohm) :

2



c (W) :

4




d (VAR) :

8



Hint: Set the independent source to zero. Find $\mathbf{Z_{th}}$.

①

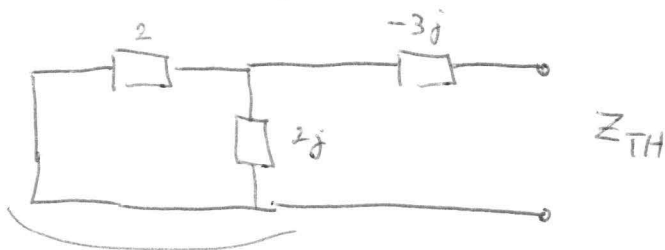


$$\hookrightarrow Z_1 = \frac{1}{\frac{1}{2} + \frac{1}{2j}} = \frac{4j}{2+2j} = \frac{2j}{1+j} = \frac{2j(1-j)}{2} = 1+j$$

$$\Rightarrow Z_{TH} = Z_1 - 3j = 1 - 2j$$

MAX POWER: $Z_L = Z_{TH}^* = 1 + 2j$

② OPTION 1:

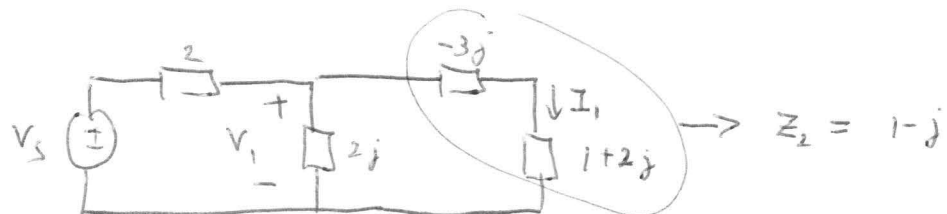

$$\hookrightarrow Z_3 = \frac{1}{\frac{1}{2j} + \frac{1}{1-j}} = \frac{2j(1-j)}{1-j+2j} = \frac{2j+2}{1+j} = 2$$


$$V_1 = V_S \frac{Z_3}{Z_3 + 2} = \frac{V_S}{2}$$

$$I_1 = \frac{V_1}{Z_2} \Rightarrow S_L = \frac{1}{2} Z_L |I_1|^2 = \frac{1}{2} (1+2j) \frac{|V_S|^2}{4} \cdot \frac{1}{|Z_2|^2}$$

$$= \frac{1}{2} \cdot \frac{64}{4} \cdot \frac{1}{2} (1+2j)$$

$$S_L = 4 + 8j$$

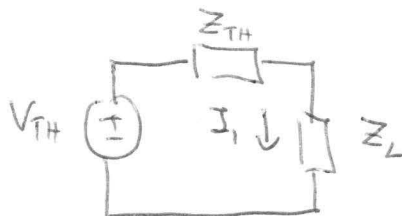OPTION 2: FIND $V_{TH} \Rightarrow V_{OC} = V_S \cdot \frac{2j}{2+j} = V_S \cdot \frac{j}{1+j} = V_{TH}$



$$I_1 = \frac{V_{TH}}{Z_{TH} + Z_L} = \frac{V_{TH}}{(1-2j) + (1+2j)} = \frac{V_{TH}}{2}$$

AS EXPECTED

$$S_L = \frac{1}{2} Z_L |I_1|^2 = \frac{1}{2} (1+2j) \frac{|V_{TH}|^2}{4} = \frac{(1+2j)}{8} |V_S|^2 \frac{|j|^2}{|1+j|^2}$$

$$S_L = (1+2j) \cdot \frac{64}{8} \cdot \frac{1}{2} \Rightarrow S_L = 4 + 8j$$