

# **ECE 65: Components & Circuits Lab**

## **Lecture 19**

### **BJT Amplifier small signal model**


Reference notes: sections 5.1, 5.2

Sedra & Smith (7<sup>th</sup> Ed): sections 7.1

Saharnaz Baghdadchi


# Course map
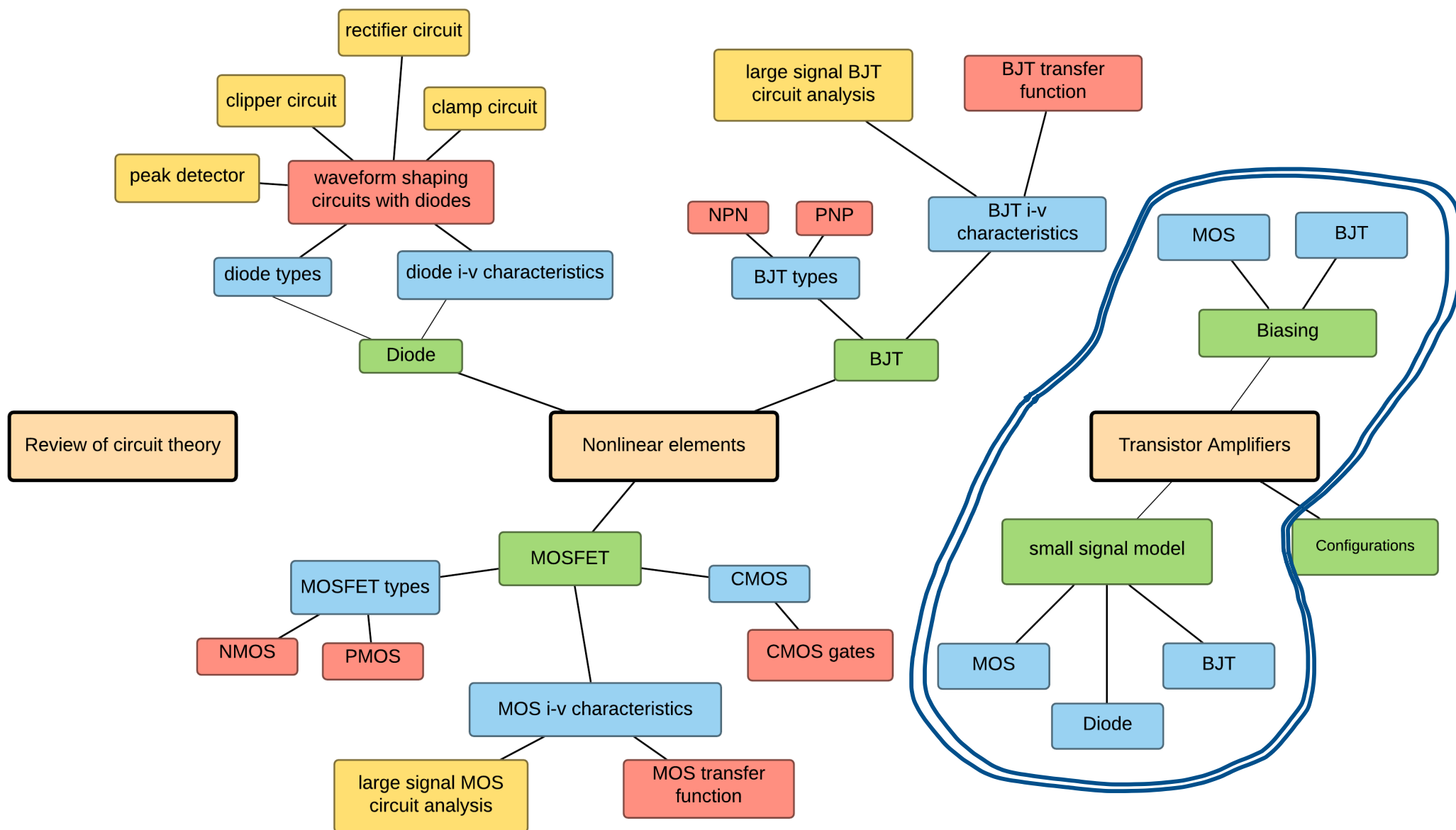
## 5. Transistor Amplifiers – Bias and small signal



# Derivation of BJT small signal model

The DC Bias point:  $v_{be} = 0$

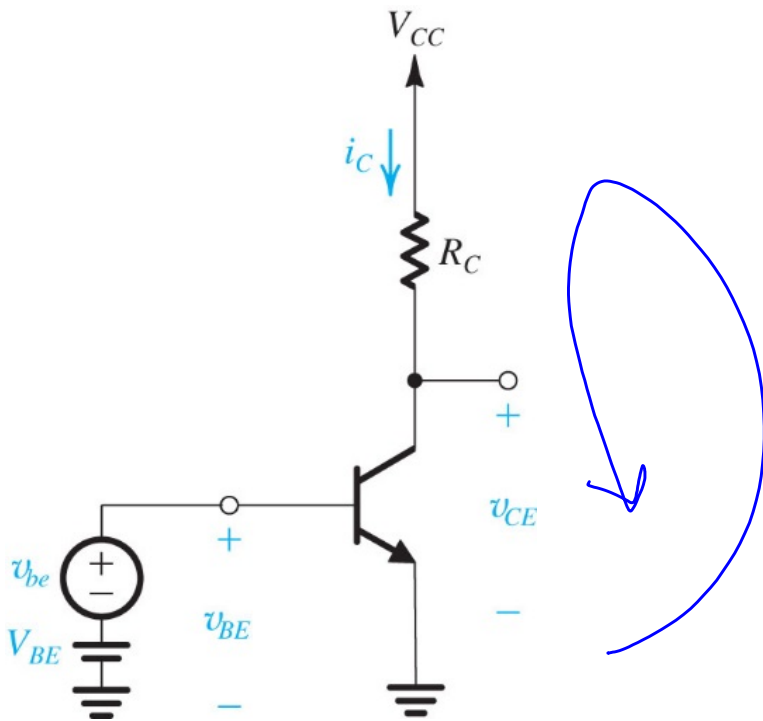

$$I_C = I_S e^{V_{BE}/V_T}$$

[The early effect is neglected here ( $\lambda = 0$ ) ]

$$I_B = I_C / \beta$$


$$I_E = \frac{\beta + 1}{\beta} I_C$$

$$V_{CE} = V_{CC} - R_C I_C$$
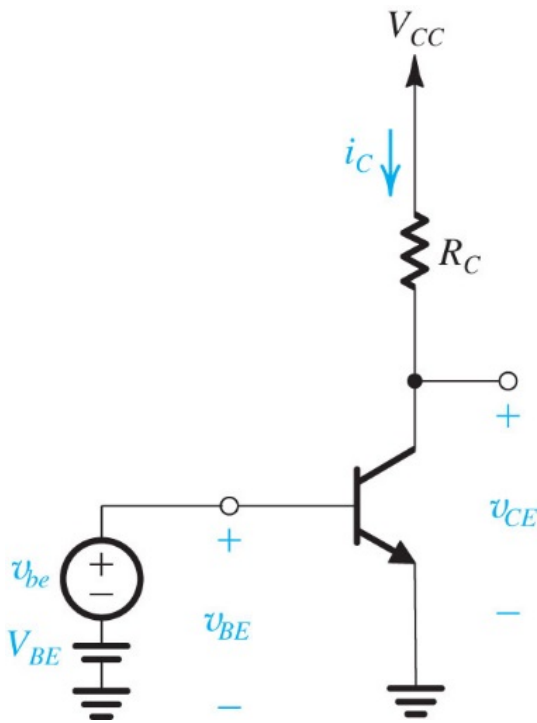
# Derivation of BJT small signal model

When  $v_{be}$  is applied:

The total instantaneous base-emitter voltage is:  $v_{BE} = V_{BE} + v_{be}$



$$i_C = I_S e^{v_{BE}/V_T} = I_S e^{(V_{BE}+v_{be})/V_T}$$


$$i_C = I_S e^{V_{BE}/V_T} e^{v_{be}/V_T}$$

Since  $I_C = I_S e^{V_{BE}/V_T}$ ,

$$i_C = I_C e^{v_{be}/V_T}$$

# Derivation of BJT small signal model


$$i_C = I_C e^{v_{be}/V_T}$$

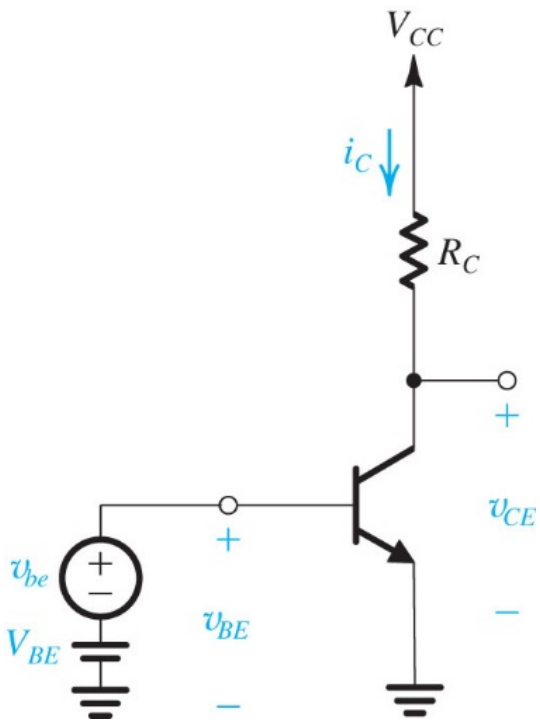

If  $v_{be} \ll V_T$ , using Taylor series expansion and neglecting the higher order terms in the exponential series expansion,

$$i_C \simeq I_C \left( 1 + \frac{v_{be}}{V_T} \right)$$

# Derivation of BJT small signal model

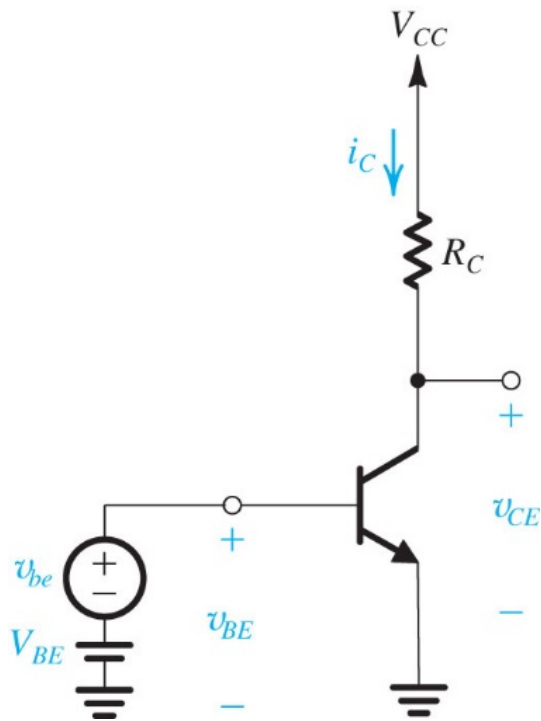

$$i_c \simeq I_C \left( 1 + \frac{v_{be}}{V_T} \right)$$

Under small signal approximation for BJT (  $\underline{v_{be}} \ll V_T$  ),

$$i_c = I_C + \frac{I_C}{V_T} v_{be}$$


$$i_c = \frac{I_C}{V_T} v_{be}$$

The BJT transconductance  $\textcolor{red}{g_m}$  is defined as  $g_m \equiv \frac{i_c}{v_{be}}$

$$g_m = \frac{I_C}{V_T}$$

$$i_c = g_m v_{be}$$

# Derivation of BJT small signal model

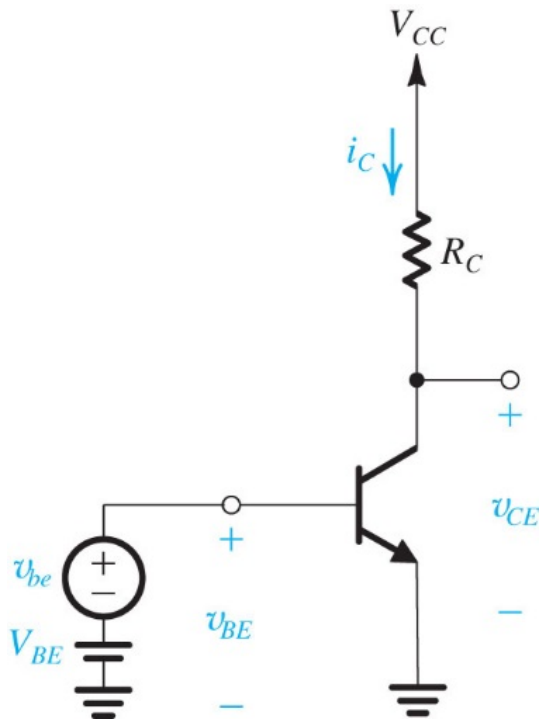

$$i_C = I_C + \frac{I_C}{V_T} v_{be}$$

$$i_B = \frac{i_C}{\beta} = \frac{I_C}{\beta} + \frac{1}{\beta} \frac{I_C}{V_T} v_{be}$$

$$i_B = I_B + i_b$$


$$i_b = \frac{1}{\beta} \frac{I_C}{V_T} v_{be} = \frac{g_m}{\beta} v_{be}$$

The small signal input resistance between base and emitter is denoted by  $r_{\pi}$

$$r_{\pi} \equiv \frac{v_{be}}{i_b} \rightarrow r_{\pi} = \frac{\beta}{g_m} = \frac{V_T}{I_B}$$
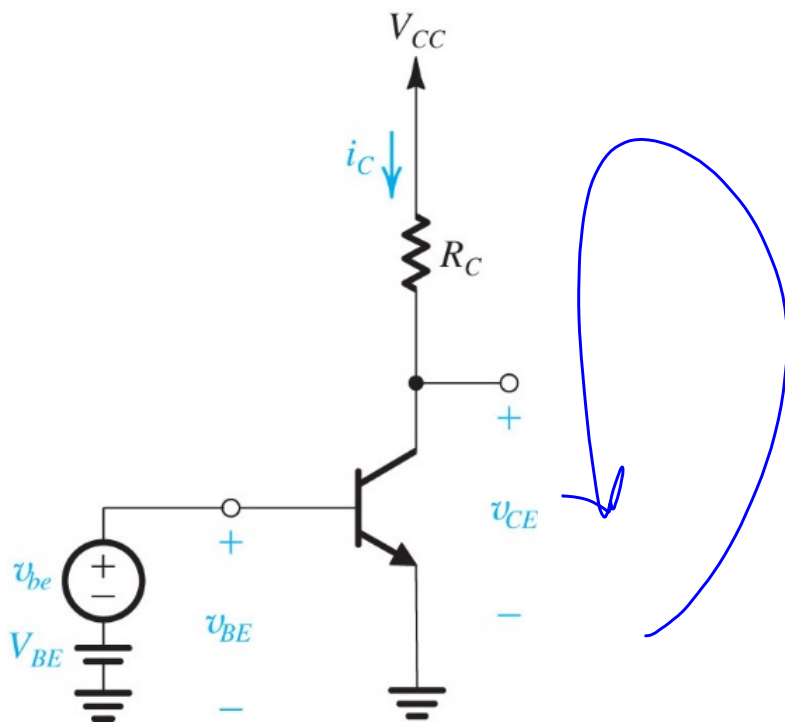
# Derivation of BJT small signal model

The voltage gain in this amplifier configuration:



$$v_{CE} = V_{CC} - i_c R_C$$

$$= V_{CC} - (i_c + I_C) R_C$$

$$= (V_{CC} - I_C R_C) - i_c R_C$$

$$= V_{CE} - i_c R_C$$

$$v_{ce} = -i_c R_C = -g_m v_{be} R_C$$


$$A_v \equiv \frac{v_{ce}}{v_{be}} = -g_m R_C$$



# BJT small signal model

$$i_b = \frac{v_{be}}{r_\pi}$$

$$i_c = g_m v_{be}$$


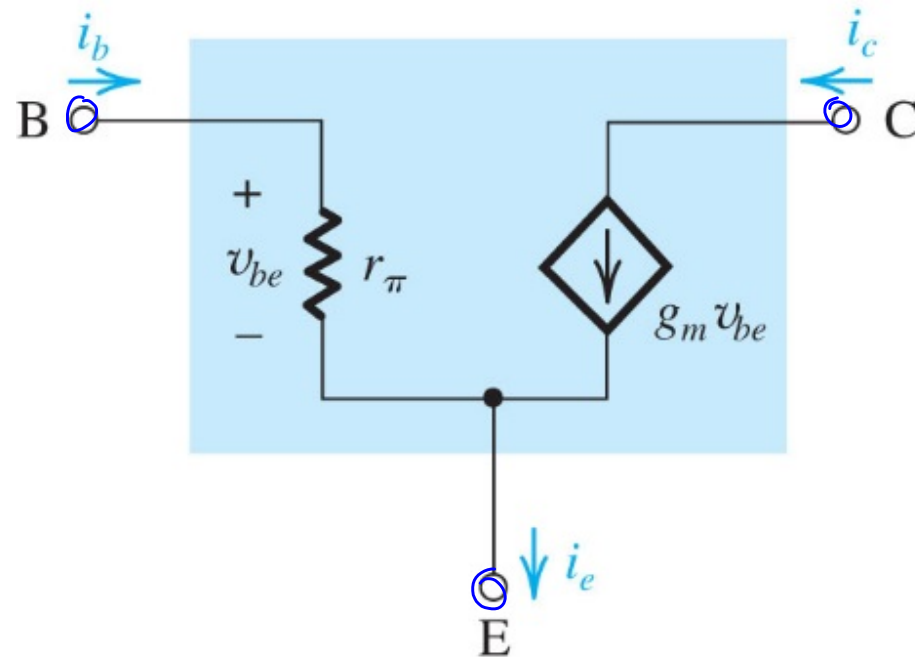


# BJT small signal model

$$v_{\pi} = v_{be}$$

$$i_b = \frac{v_{be}}{r_{\pi}}$$
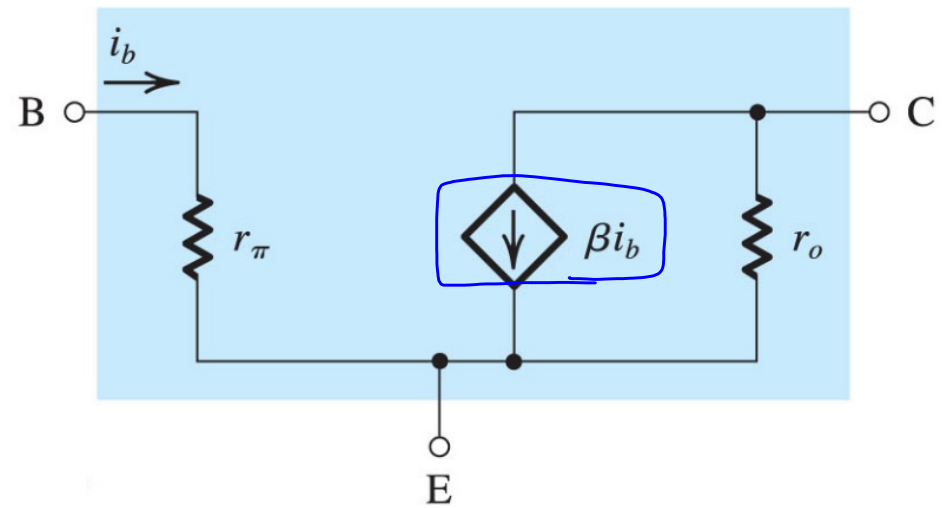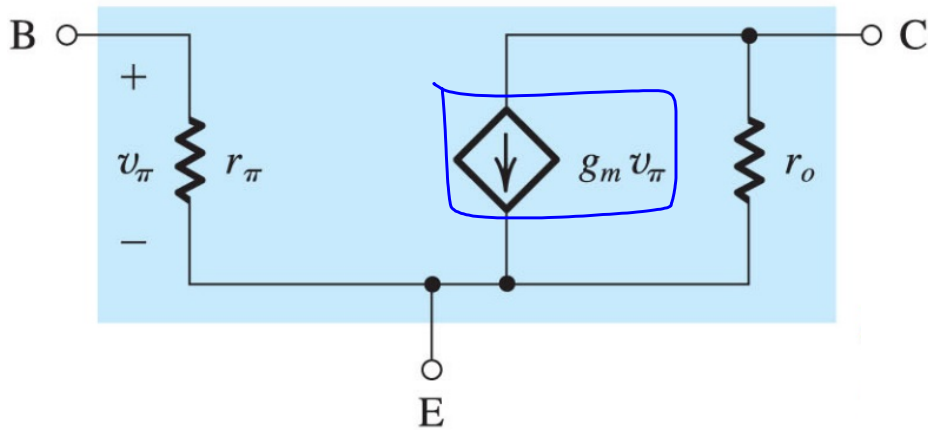
$$i_c = g_m v_{be} + \frac{v_{ce}}{r_o}$$



$$V_A = \frac{1}{\lambda}$$

$$g_m = \frac{I_C}{V_T}$$


$$r_o \approx \frac{V_A}{I_C}$$

$$r_{\pi} = \frac{\beta}{g_m} = \frac{V_T}{I_B}$$


$$g_m v_{be} = g_m (i_b r_{\pi}) = (g_m r_{\pi}) i_b = \beta i_b$$

# PNP small signal model is identical to NPN

PNP

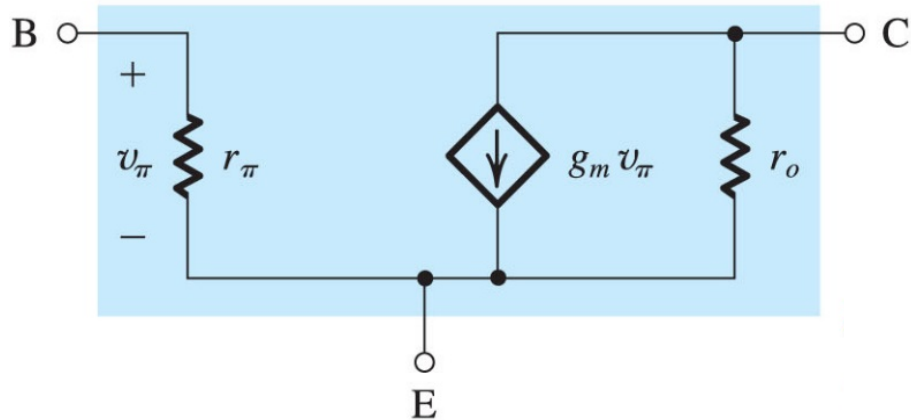

NPN

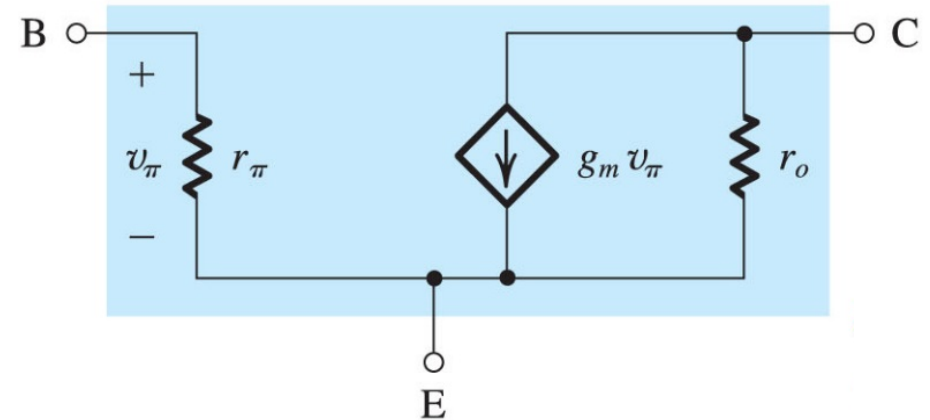


=


**PNP small-signal circuit model is identical to NPN**

# Summary of transistor small signal models

NMOS/PMOS

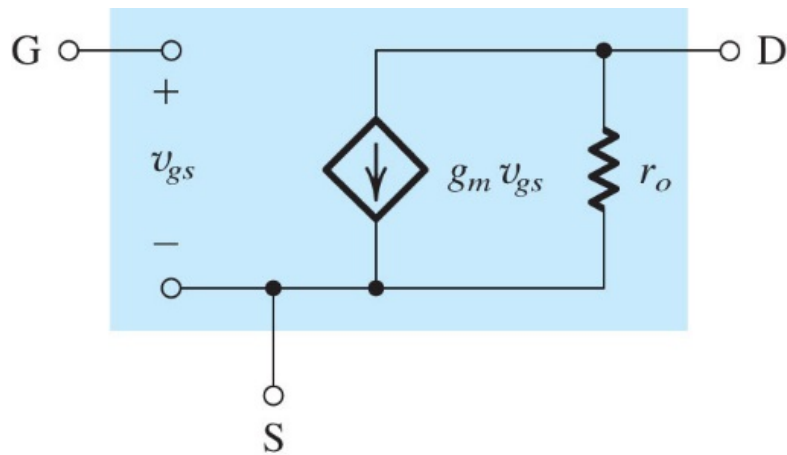


NPN/PNP BJT

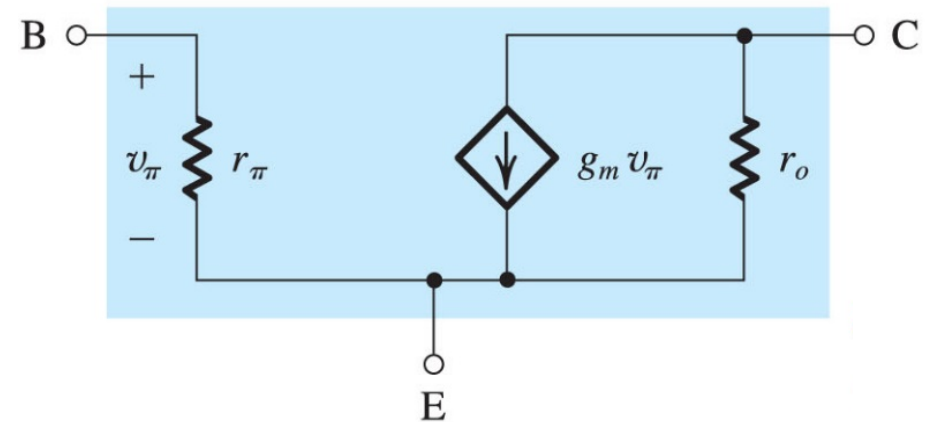

## Comparison of MOS and BJT small-signal circuit models:

1. MOS has an infinite resistor in the input ( $v_{gs}$ ) while BJT has a finite resistor,  $r_\pi$  (typically several  $k\Omega$ ).
2. BJT  $g_m$  is substantially larger than that of a MOS (BJT has a much higher gain).
3.  $r_o$  values are typically similar (10s of  $k\Omega$ ).

# BJT Small Signal Model

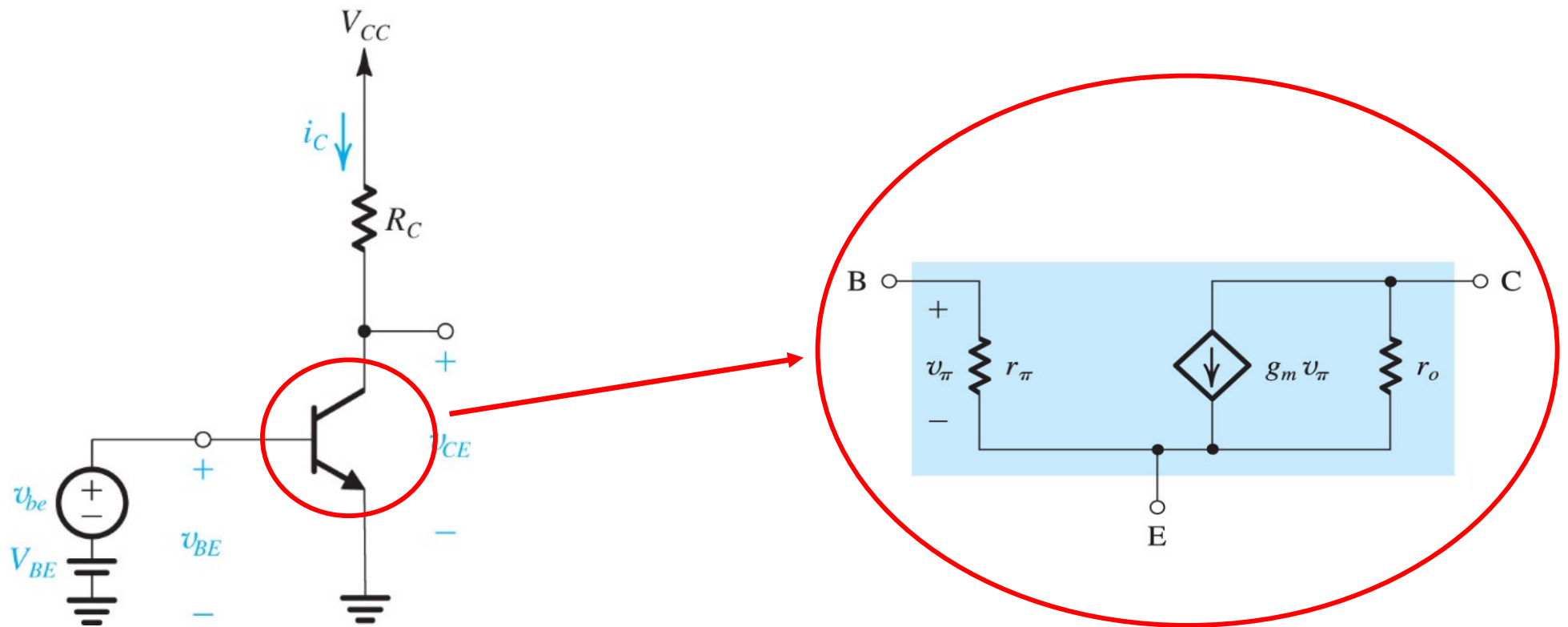

# Review of amplifier circuit analysis



- Under small signal approximation, we can analyze the **Signal** and **Bias** circuits separately for a given amplifier circuit.
- The **Signal** and **Bias** circuits are different.
- **Bias** is the state of the system when there is no signal. In drawing and analyzing the **Bias** circuit, the capacitors are open and signal sources are set to zero.
- **Signal** circuit  $\equiv$  signal equivalent circuit  
 $\equiv$  small signal equivalent circuit

# Review of amplifier analysis

- In drawing the **Signal** circuit you should
  - replace the transistors with their small signal models without changing anything in the model
  - keep the resistors – find the node they are connected to in the original circuit and connect them to the right node in the signal circuit.
  - short the capacitors
  - set the independent DC current and voltage sources to zero.
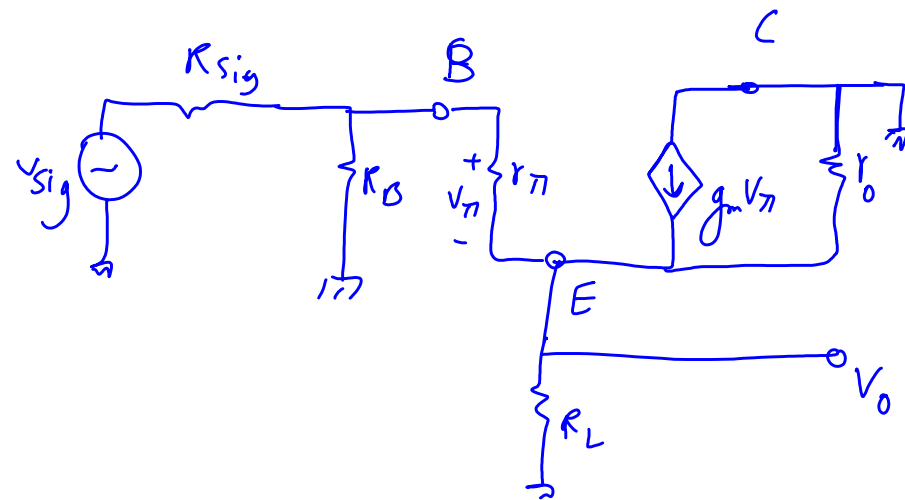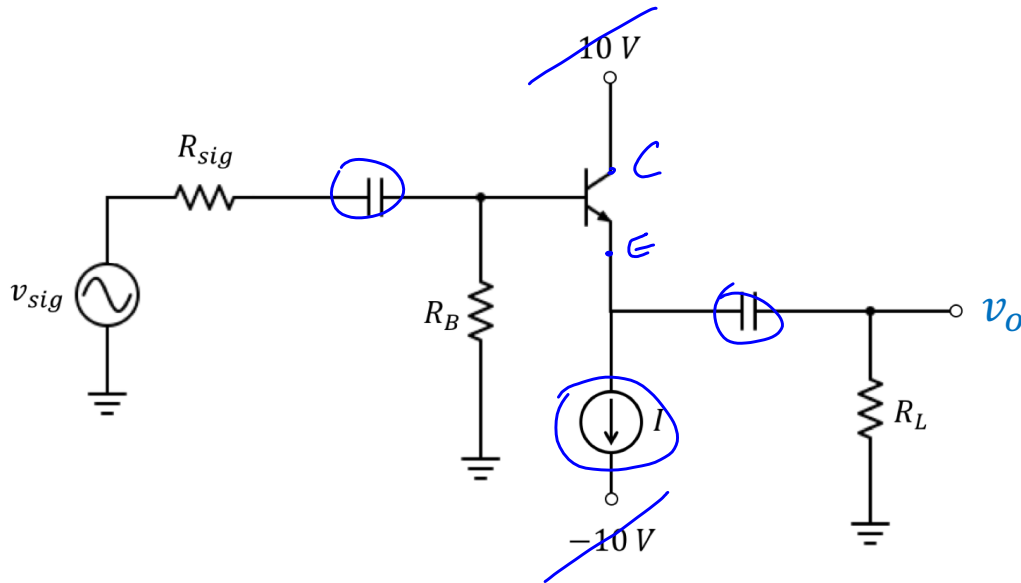
## Example:


Draw the signal circuit (assume capacitors are short for signal).





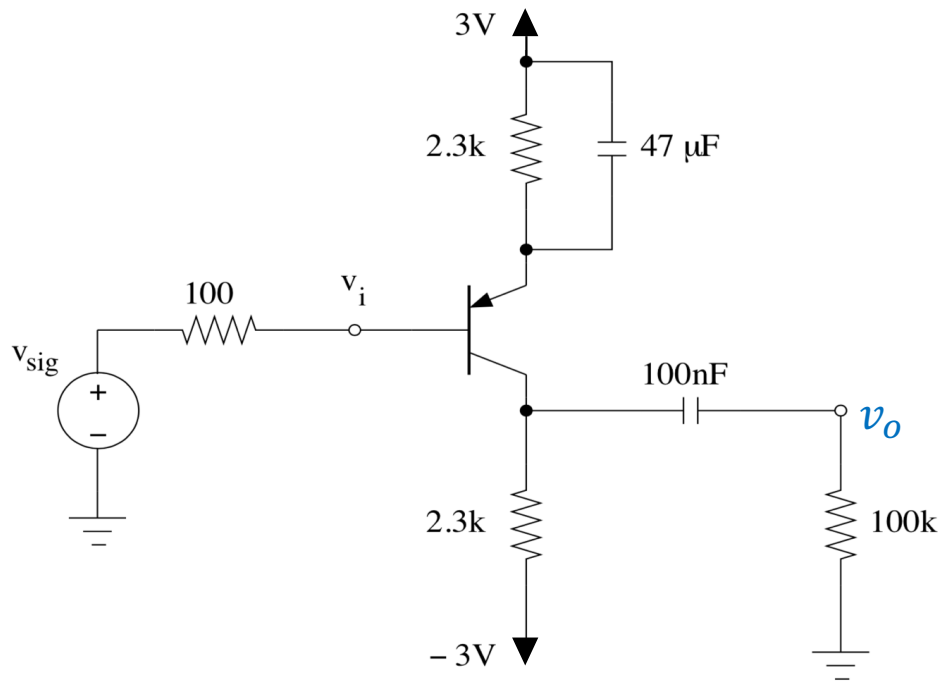
## Lecture 19 reading quiz:

Find the transconductance,  $g_m$ , in this circuit ( $V_{D0} = 0.7\text{ V}$ ,  $V_T = 26\text{ mV}$ ,  $V_A = 150\text{ V}$ ).



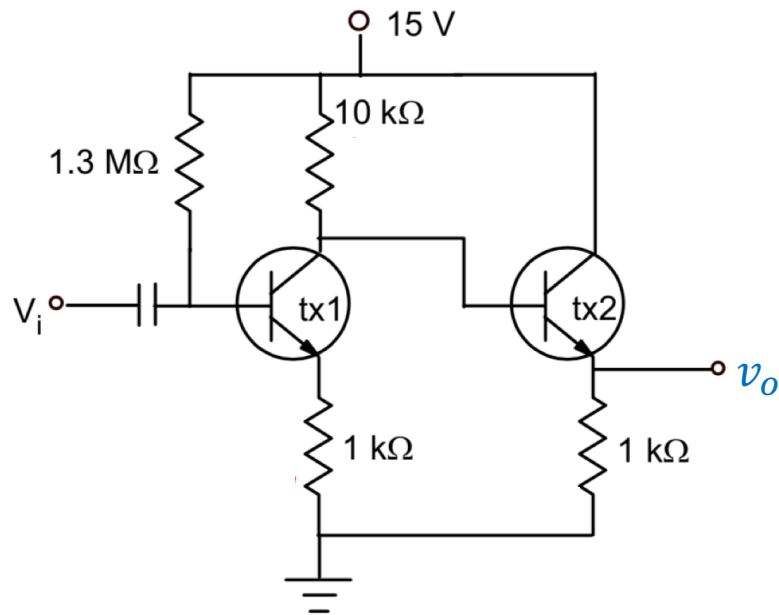
## Discussion question 1.

Draw the signal circuit (assume capacitors are short for signal).


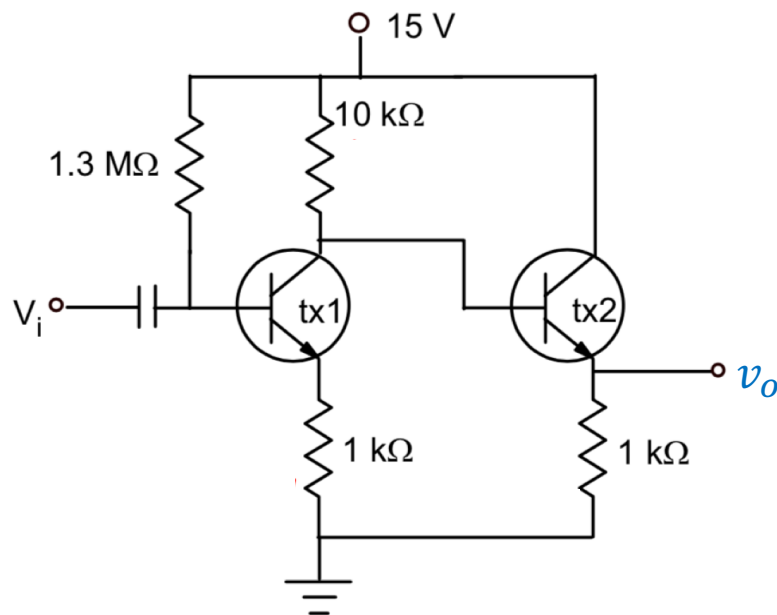
## Discussion question 1.


Draw the signal circuit (assume capacitors are short for signal).



- Label all the node voltages and currents on the given circuit.
- Draw the small signal model for two BJTs, and label all the node voltages.
- Add the other circuit elements to the small signal circuits according to how they are connected to the base, collector, and emitter terminals of the BJTs in the given circuit.
- The capacitors will be short and the DC voltage sources will be set to zero in the signal circuit.
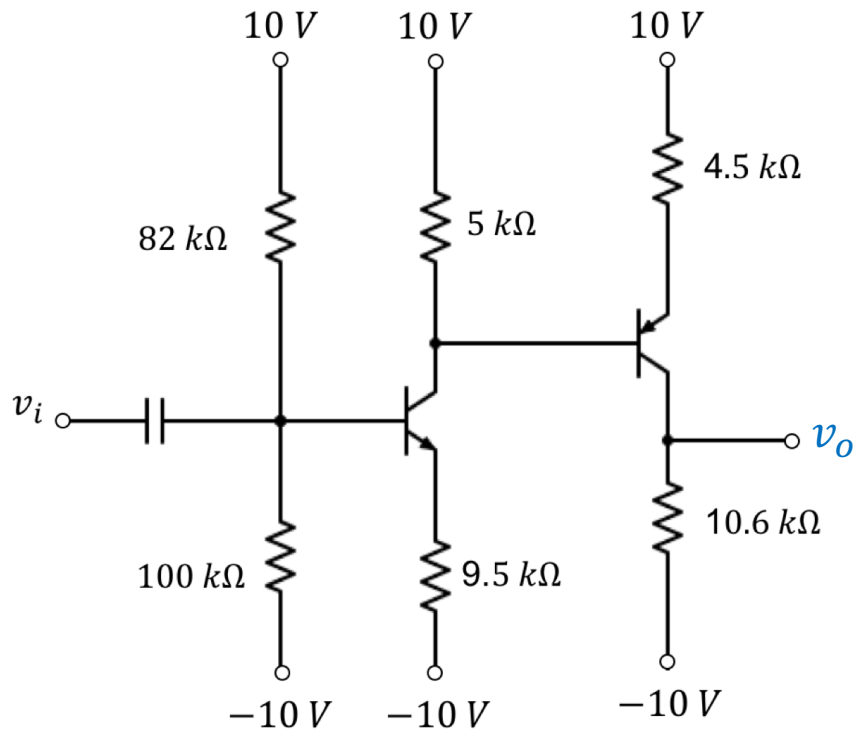
## Discussion question 2.


Draw the signal circuit (assume capacitors are short for signal).


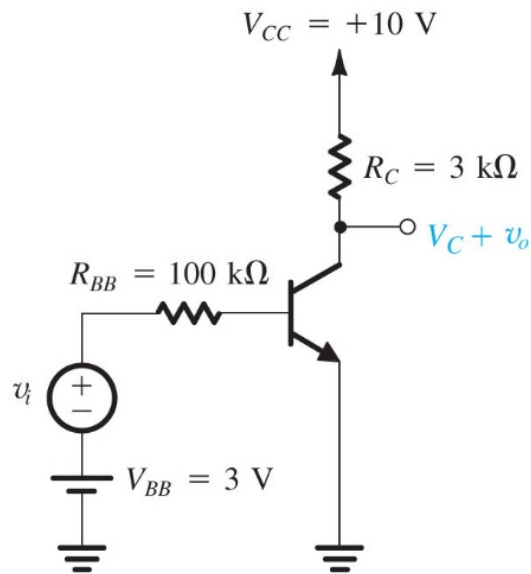
### Discussion question 3.

For this amplifier circuit, find the small signal parameters, draw the signal circuit (assume capacitors are short for signal) and find  $v_o/v_i$  .


Assume  $\beta = 100$ ,  $V_T = 25 \text{ mV}$  and neglect the early effect.


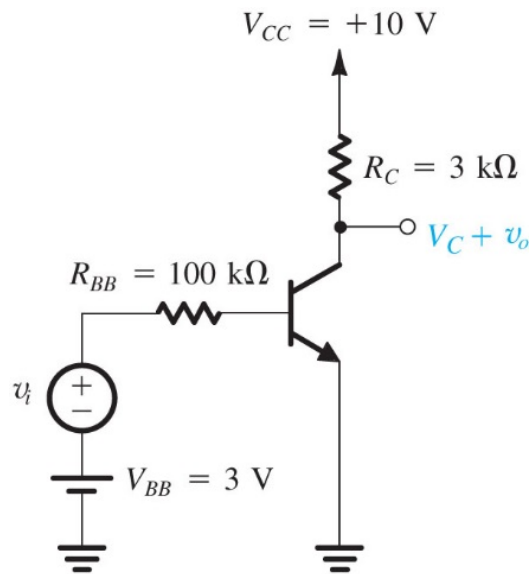
## Discussion question 3.

For this amplifier circuit, find the small signal parameters, draw the signal circuit (assume capacitors are short for signal) and find  $v_o/v_i$ .

Assume  $\beta = 100$ ,  $V_T = 25 \text{ mV}$  and neglect the early effect.



- Draw and solve the DC circuit to get all the DC node voltages and currents.
- Calculate the small signal parameters ( $r_{\pi}$ ,  $r_o$ ,  $g_m$ )
- Draw the small signal model for and label all the node voltages.
- Add the other circuit elements to the small signal circuit according to how they are connected to the base, collector, and emitter terminals of the BJT in the given circuit.
- To find  $v_o/v_i$ , write a KVL(or KCL) to relate  $v_o$  to  $v_{\pi}$  and another one to relate  $v_{\pi}$  to  $v_i$ . Use those two equations to relate  $v_o$  to  $v_i$ .