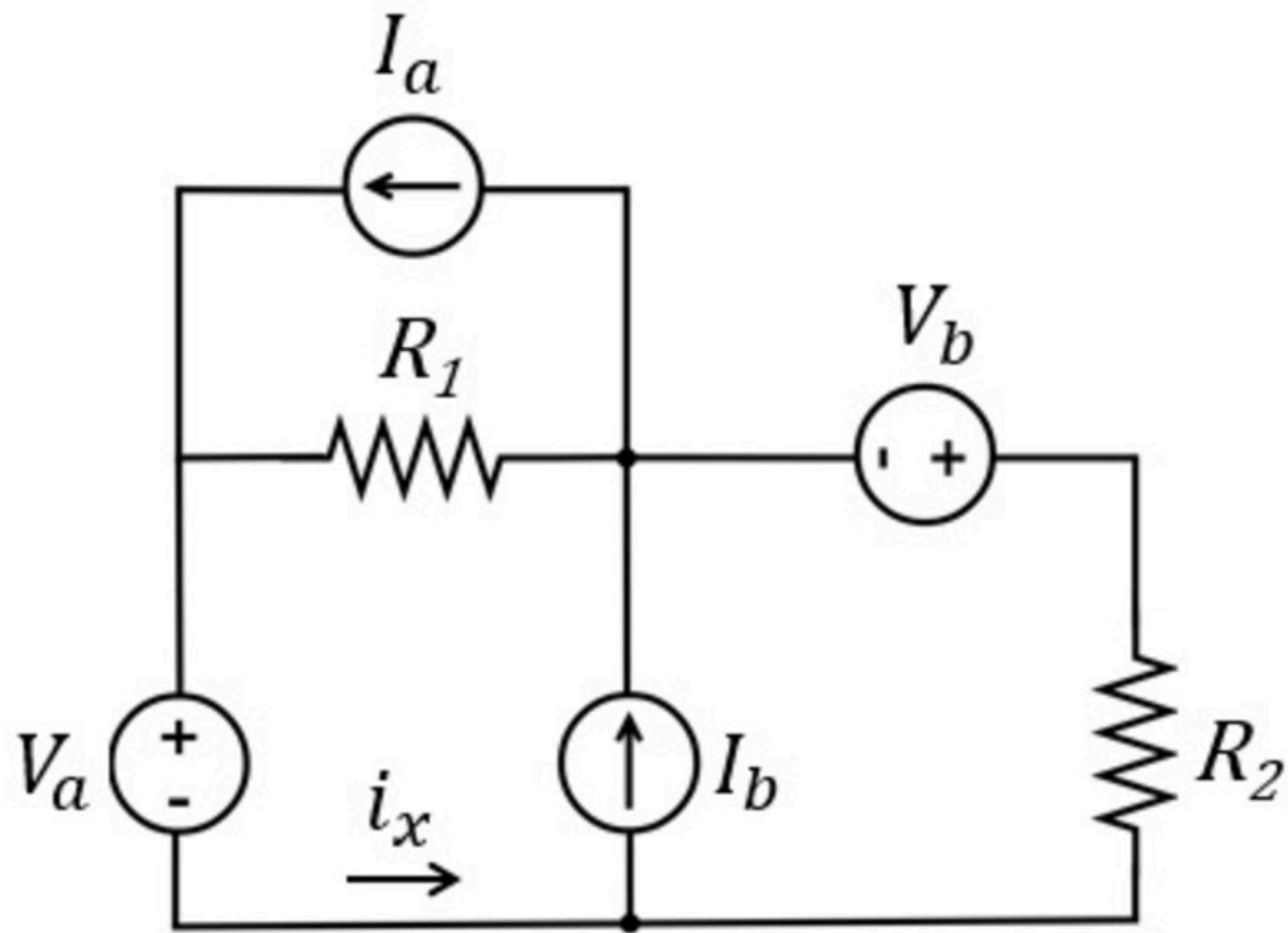


Circuit theorems 006

Problem has been graded.

Use source transformations to find the current i_x .



Given Variables:

V_a : 12 V

V_b : 6 V

I_a : 5 A

I_b : 2 A


R_1 : 15 ohm

R_2 : 12 ohm

Calculate the following:

i_x (A) :

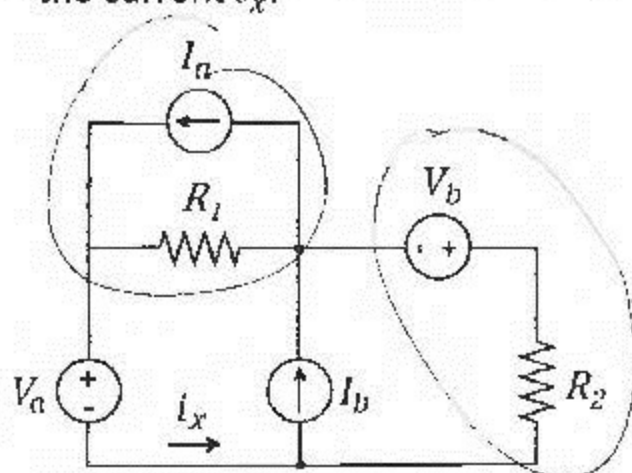Use source transformations to find the current i_x .



$$V_a = 12 \text{ V}$$


$$V_b = 6 \text{ V}$$

$$I_a = 4 \text{ A}$$

$$I_b = 6 \text{ A}$$


$$R_1 = 3 \text{ ohm}$$

$$R_2 = 3 \text{ ohm}$$

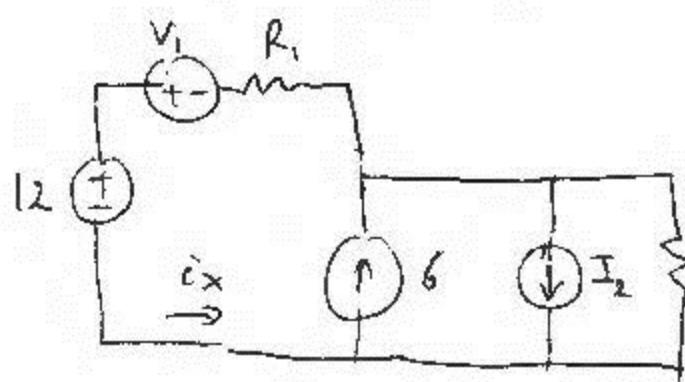

$$V_1 = I_a \cdot R_1 = 4 \cdot 3 = 12 \text{ V}$$
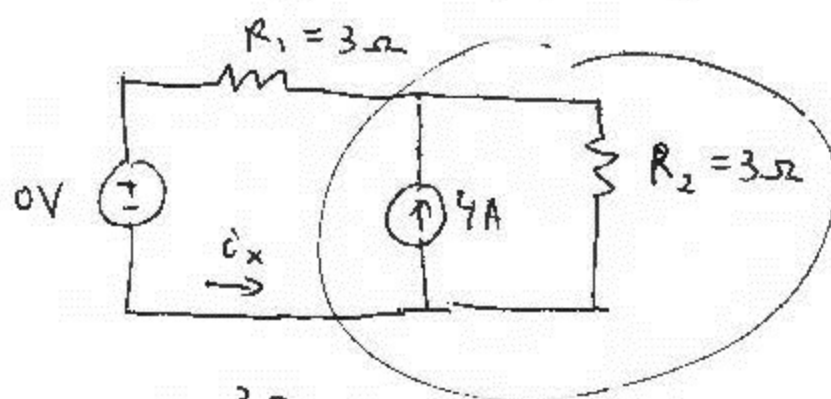
$$I_2 = \frac{V_b}{R_2} = \frac{6}{3} = 2 \text{ A}$$




$$i_x = \frac{12 \text{ V}}{6 \text{ ohm}} = 2 \text{ A}$$

$$\boxed{i_x = 2 \text{ A}}$$

Circuit theorems 008

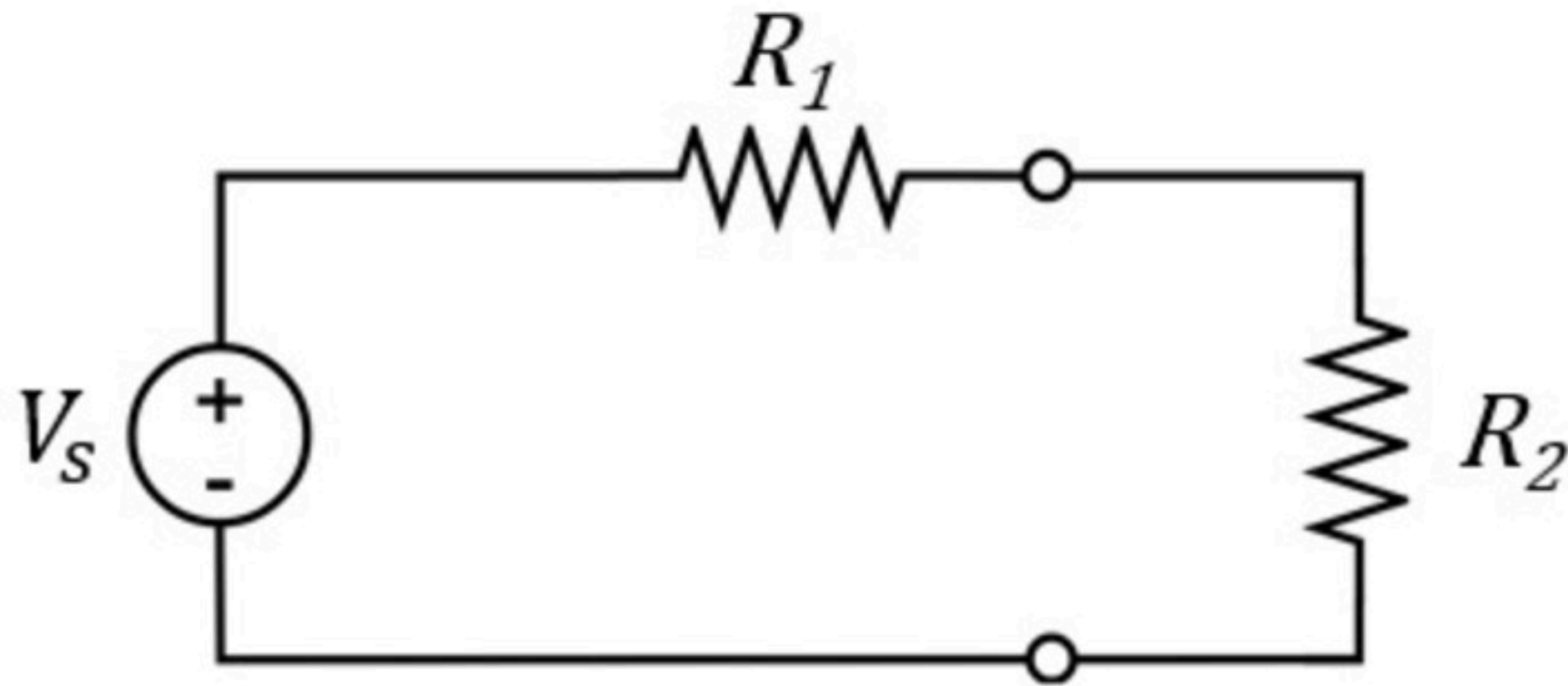Problem has been graded.

Determine the resistance R_1 such that the power dissipated in R_2 is maximum.



Given Variables:

V_s : 12 V

R_2 : 7 ohm


Calculate the following:

R_1 (ohm) :

Determine the resistance R_1 such that the power dissipated in R_2 is maximum.

$$V_s = 12 \text{ V}$$

$$R_2 = 3 \text{ ohm}$$

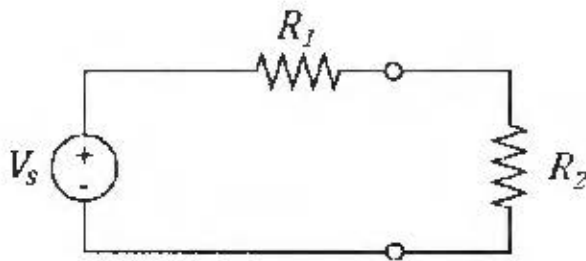

$$I = \frac{V_s}{R_1 + R_2}$$

$$\begin{aligned} P &= R_2 I^2 \\ &= \frac{R_2 V_s^2}{(R_1 + R_2)^2} \end{aligned}$$

$$P = \frac{3 \cdot 144}{(R_1 + 3)^2}$$

$$\frac{dP}{dR_1} = -2 \cdot \frac{3 \cdot 144}{(R_1 + 3)^3} = 0 \Leftrightarrow R_1 = \infty$$

\hookrightarrow ALWAYS DECREASING

P_{MAX}





WHEN

$$R_1 = 0 \Omega$$

Circuit theorems 013

No more attempts left.

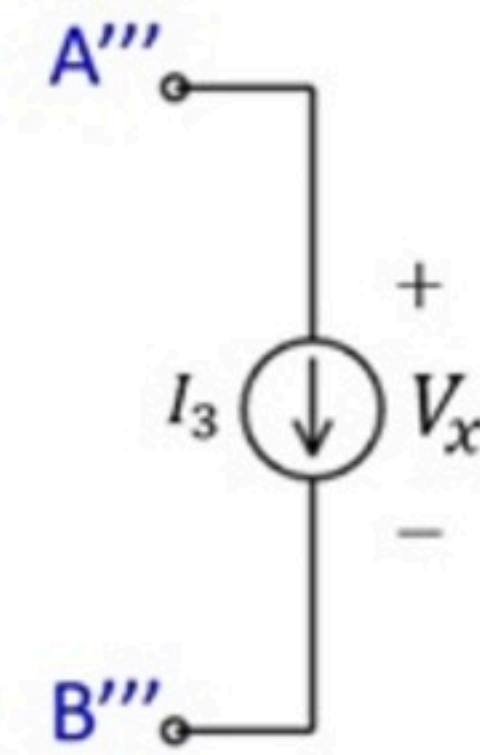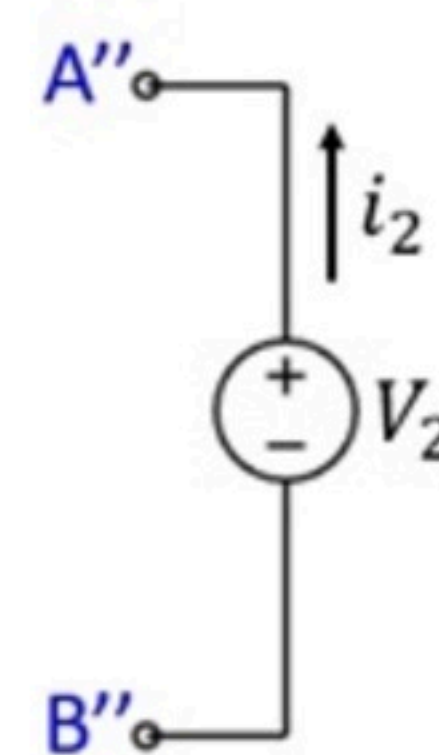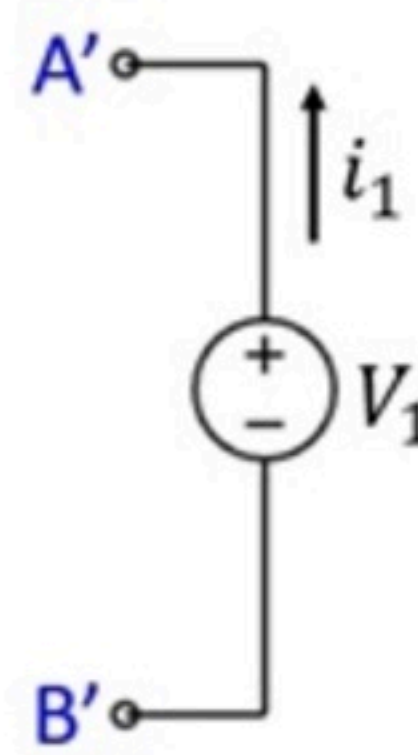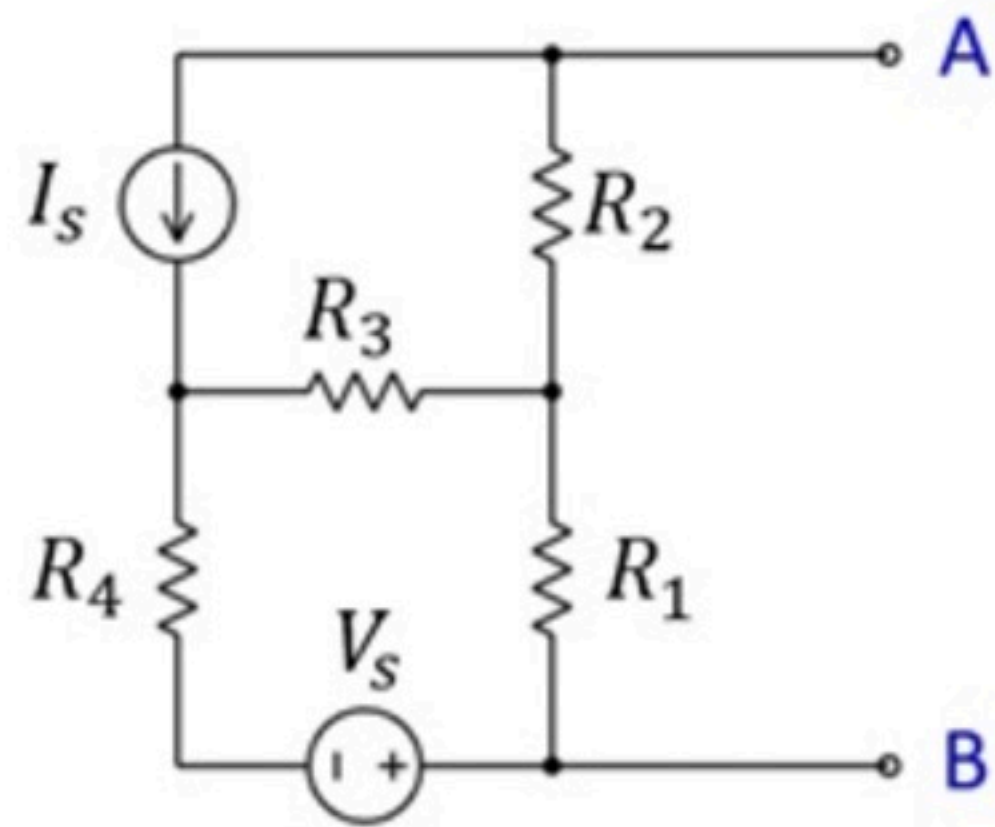Consider the circuit on the left. You are not given the values of V_S , I_S , R_1 , R_2 or R_3 .



You are told the value of current i_1 if V_1 is attached to this circuit, with A connected to A' and B connected to B' .

You are also told the value of current i_2 if V_2 is attached, with A connected to A'' and B connected to B'' . However, in this case, the independent sources were first turned off (i.e., $V_S = 0$ and $I_S = 0$).

Your task is to find V_x if current source I_3 is connected to the original circuit (i.e., with the independent sources V_S and I_S not turned off), with A connected to A''' and B connected to B''' .

Given Variables:

V_1 : 6 V

i_1 : 12 A

V_2 : 12 V

i_2 : 12 A

I_3 : -7 A



R_4 : 2 ohm

Calculate the following:

V_x (V) :

Hint: Redraw the circuit on the left as its Thevenin equivalent model

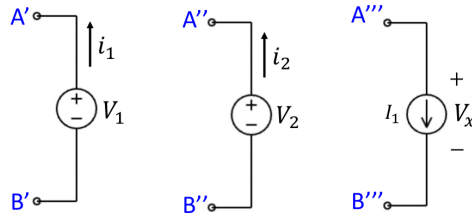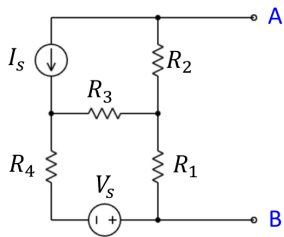Consider the circuit on the left. You are not given the values of V_S , I_S , R_1 , R_2 or R_3 .




$$\begin{aligned} V_1 &= 15 \text{ V} \\ i_1 &= 6 \text{ A} \\ V_2 &= 10 \text{ V} \\ i_2 &= 5 \text{ A} \\ I_1 &= 5 \text{ A} \\ R_4 &= 2 \Omega \end{aligned}$$

You are told the value of current i_1 if V_1 is attached to this circuit, with A connected to A' and B connected to B' .


You are also told the value of current i_2 if V_2 is attached, with A connected to A'' and B connected to B'' . However, in this case, the independent sources were first turned off (i.e., $V_S = 0$ and $I_S = 0$).

Your task is to find V_x if current source I_1 is connected to the original circuit (i.e., with the independent sources V_S and I_S not turned off), with A connected to A''' and B connected to B''' .

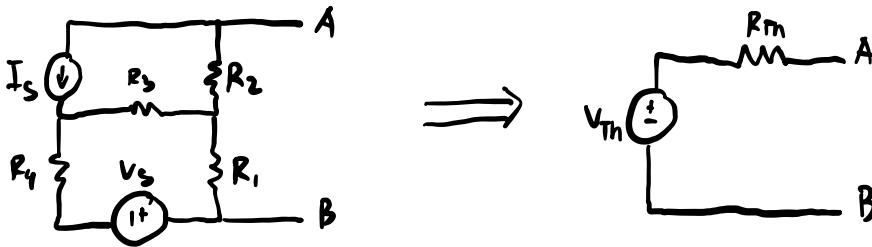Represent the left circuit as its Thevenin equivalent circuit



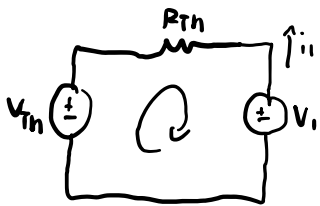
When $A \rightarrow A'$, $B \rightarrow B'$



$$\text{KVL: } -V_{Th} - i_1 R_{Th} + V_1 = 0$$

$$V_{Th} = V_1 - i_1 R_{Th}$$

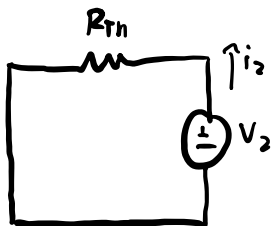when $A \rightarrow A''$, $B \rightarrow B''$ and $V_S = 0$, $I_S = 0$




$$R_{Th} = \frac{V_2}{i_2} = \frac{10}{5} = 2 \Omega$$

$$V_{Th} = 15 - 6(2)$$

$$V_{Th} = 3 \text{ V}$$

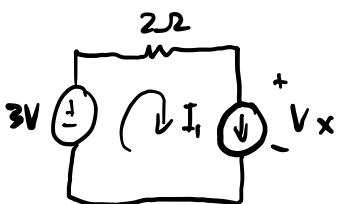when $A \rightarrow A'''$, $B \rightarrow B'''$



$$\text{KVL: } -3 + 2I_1 + V_x = 0$$


$$V_x = 3 - 2(5)$$

$$\boxed{V_x = -7 \text{ V}}$$

Circuit theorems 014

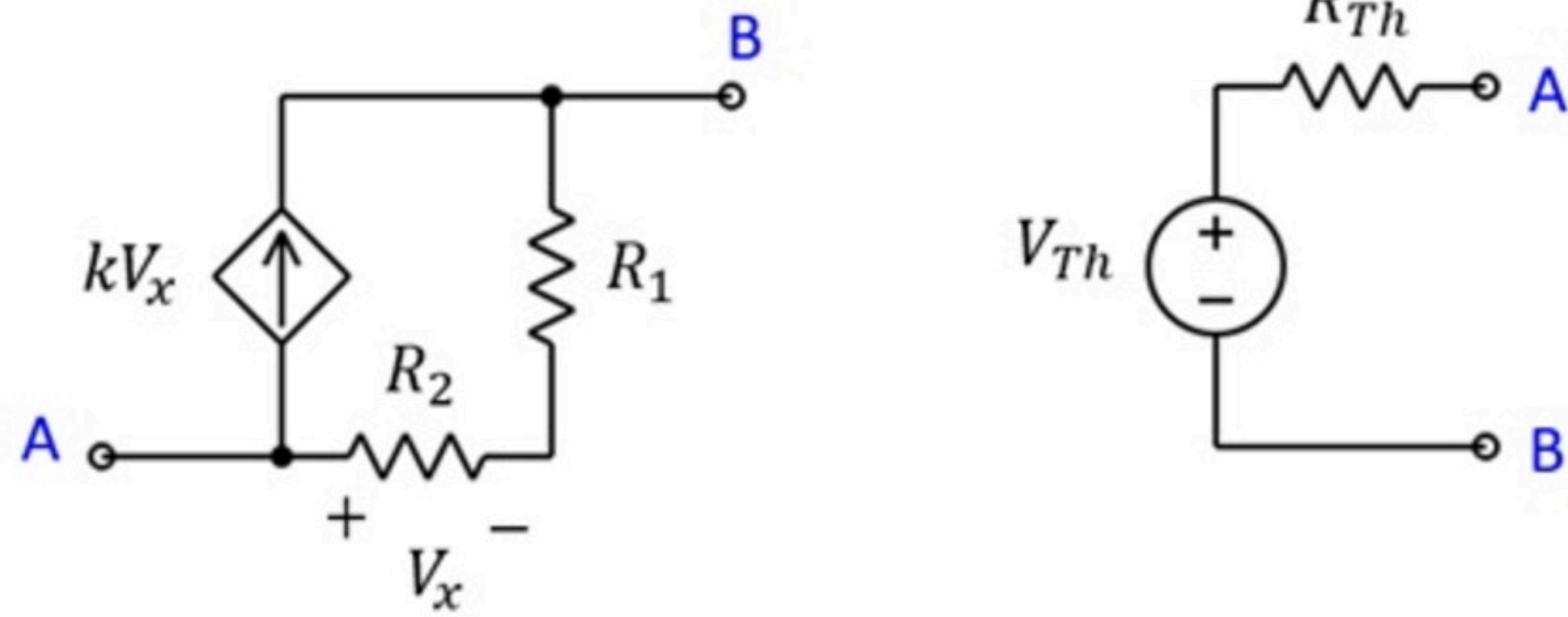Problem has been graded.

The circuit on the right represent the Thevenin model of the circuit on the left. Find the value of V_{Th} and R_{Th} .



Given Variables:

R_1 : 4 ohm

R_2 : 2 ohm



k : -2 A/V

Calculate the following:

V_{th} (V) :

R_{th} (ohm) :

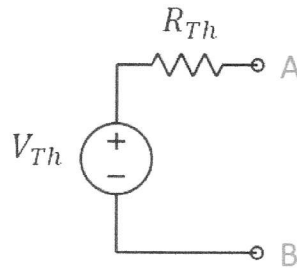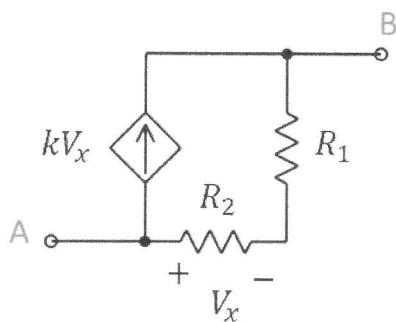The circuit on the right represent the Thevenin model of the circuit on the left. Find the value of V_{Th} and R_{Th} .




$$R_1 = 4 \Omega$$

$$R_2 = 2 \Omega$$

$$k = -2 \text{ A/V}$$


REDRAW:

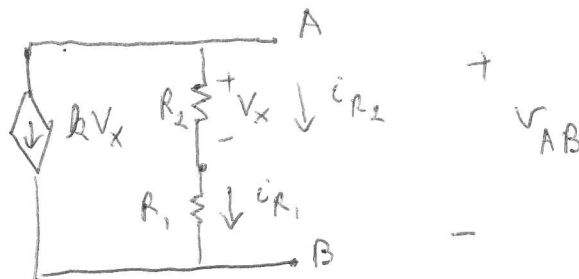

① LEAVE A-B OPEN: KCL: $kV_x + \frac{V_x}{R_2} = 0 \Rightarrow (k + \frac{1}{R_2})V_x = 0 \Rightarrow V_x = 0$

$\Rightarrow i_{R_2} = i_{R_1} = 0 \text{ A} \Rightarrow V_{AB} = 0 \Rightarrow \boxed{V_{Th} = 0 \text{ V}}$

② FOR R_{Th} , APPLY TEST VOLTAGE

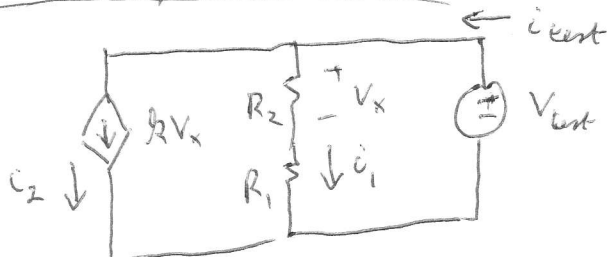

$$i_1 = \frac{V_{test}}{R_1 + R_2}$$

$$i_2 = kV_x = k V_{test} \frac{R_2}{R_1 + R_2}$$

voltage divider

$$i_{test} = i_1 + i_2 = V_{test} \frac{(1 + kR_2)}{R_1 + R_2}$$

$$\Rightarrow R_{Th} = \frac{V_{test}}{i_{test}} = \frac{R_1 + R_2}{1 + kR_2} = \frac{4 + 2}{1 + (-2)2} = \frac{6}{-3}$$


$$\boxed{R_{Th} = -2 \Omega}$$

Circuit theorems 016

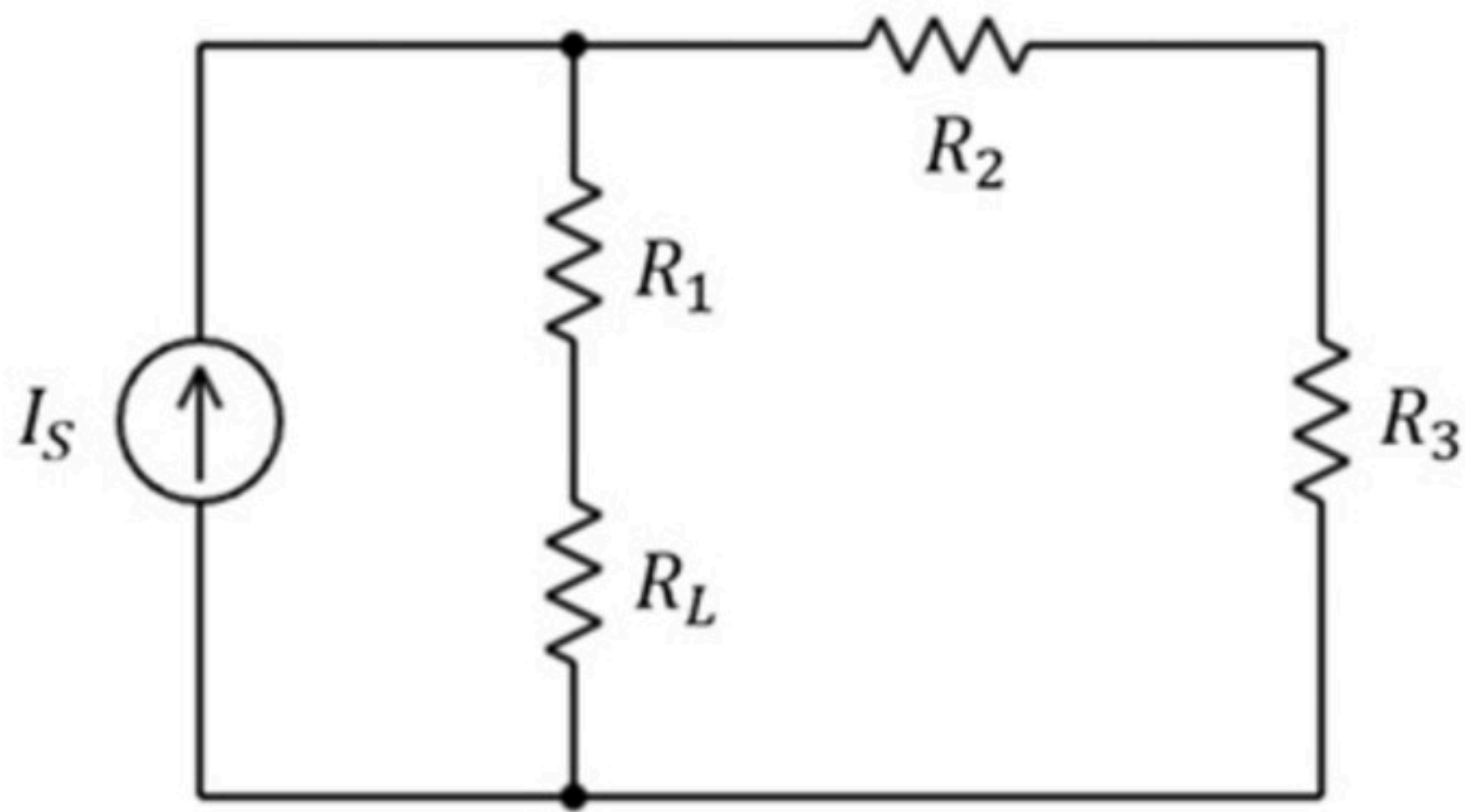Problem has been graded.

Find the value of R_L such that the power received by R_L is maximized.

Find the corresponding max power received by R_L .



Given Variables:

I_S : 2 A

R_1 : 2 ohm

R_2 : 1 ohm

R_3 : 1 ohm

Calculate the following:

R_L (ohm) :

P_{\max} (W) :

Hint: Find the Thevenin equivalent model of the circuit after taking out R_L .

Find the value of R_L such that the power received by R_L is maximized.


Find the corresponding max power received by R_L .

$$I_S = 2A$$


$$R_1 = 12\Omega$$

$$R_2 = 2\Omega$$

$$R_3 = 2\Omega$$

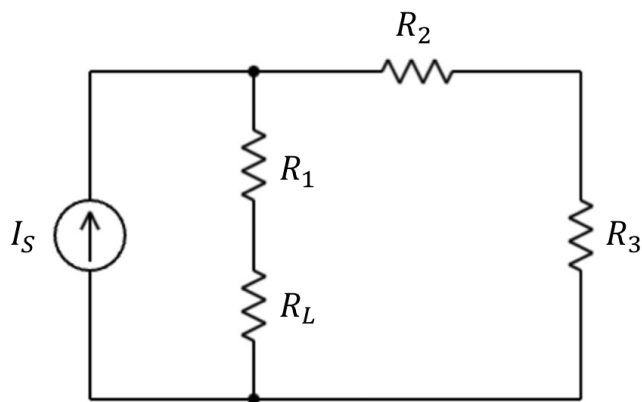

find R_{Th}

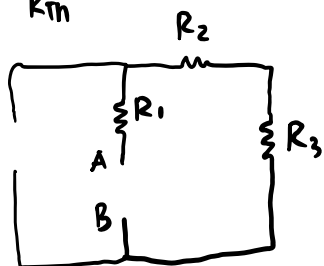


R_1, R_2, R_3 are in series

$$R_{Th} = R_1 + R_2 + R_3$$

$$= 12 + 2 + 2$$

$$R_{Th} = 16\Omega$$

find V_{Th}

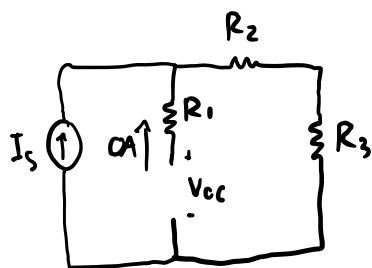

$$V_{OC} = I_S \cdot (R_2 + R_3)$$

$$= 2 \cdot (2 + 2)$$

$$V_{OC} = 8V$$

$$P_{max} = \frac{V_{Th}^2}{4R_{Th}}$$

$$= \frac{8^2}{4(16)}$$

$$P_{max} = 1W$$