

ECE 65: Components & Circuits Lab

Lecture 4

Diode introduction and review of circuit theory


Reference notes: sections 2.1-2.8

Sedra & Smith (7th Ed): sections 4.3-4.4

Saharnaz Baghdadchi


Course map

1. Review of Circuit theory

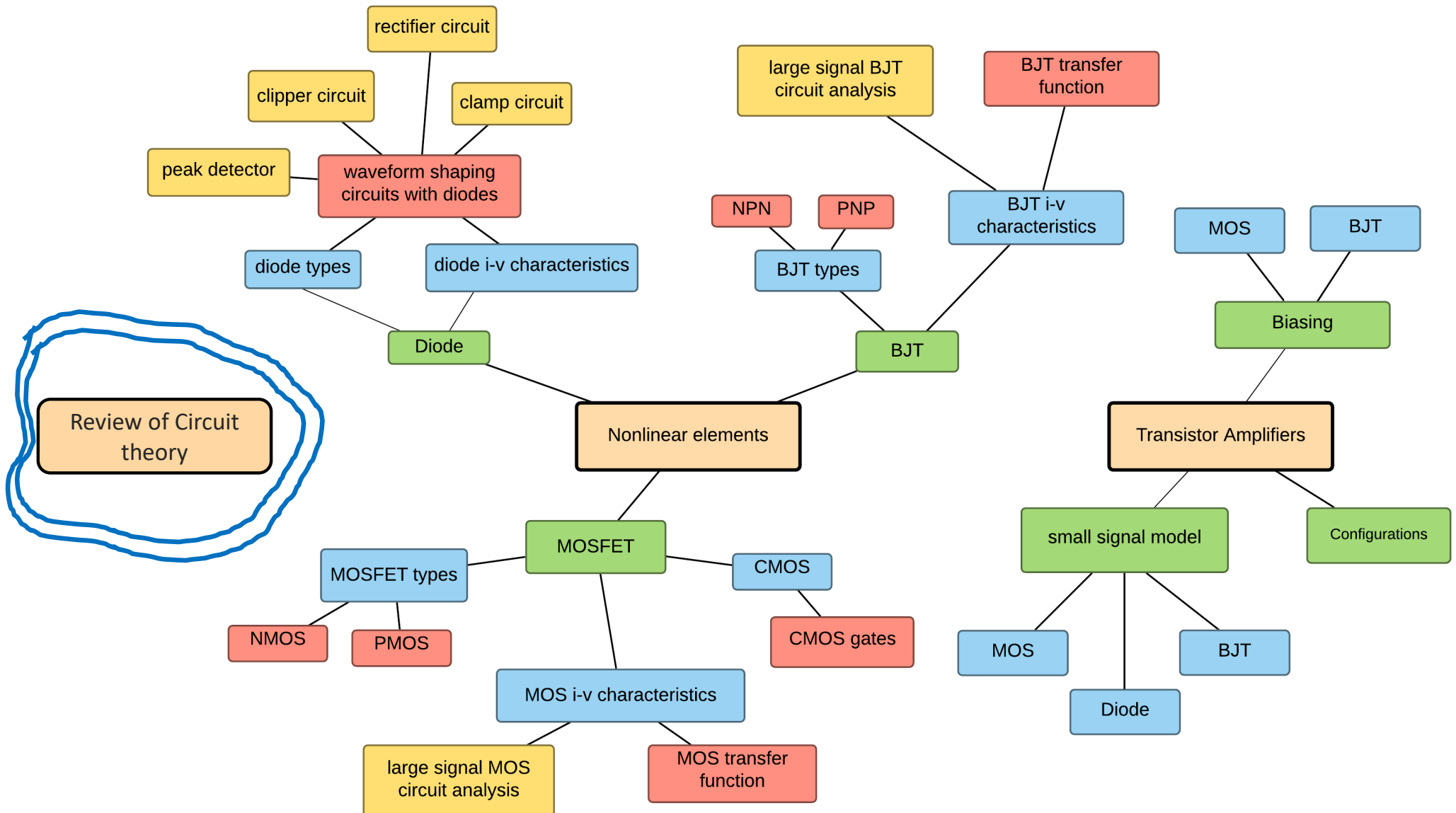


We will analyze many functional circuits

Two-terminal Networks

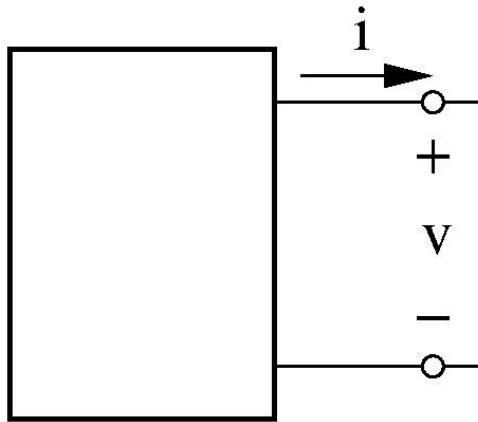

Function is defined by the iv equation


Two-port Networks

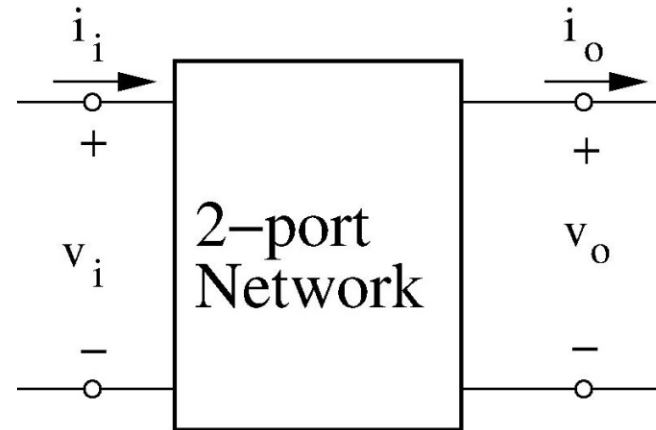

Function is defined by the transfer function (e.g., v_o in terms of v_i)

A typical analog circuit contains a load and a source (two-terminal networks) and several two-port networks

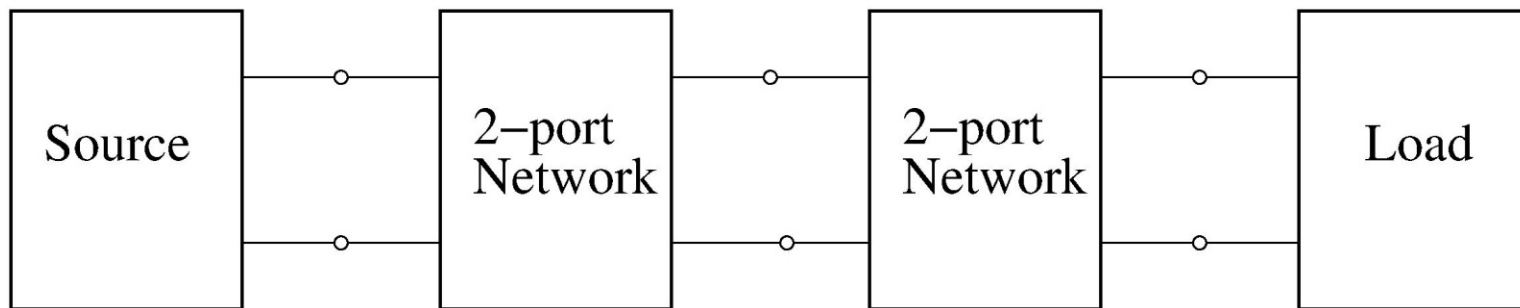We divide the circuit into building blocks to
simplify analysis and design



Two-terminal network
containing an
independent source


Two-terminal network
containing NO
independent source

In linear circuits:


Any two-terminal network can be replaced by its Thevenin equivalent circuit.

If a two-terminal network does not include an “independent source” it will be reduced to a single “impedance” (even if it includes dependent sources).

Source only sees a load resistor

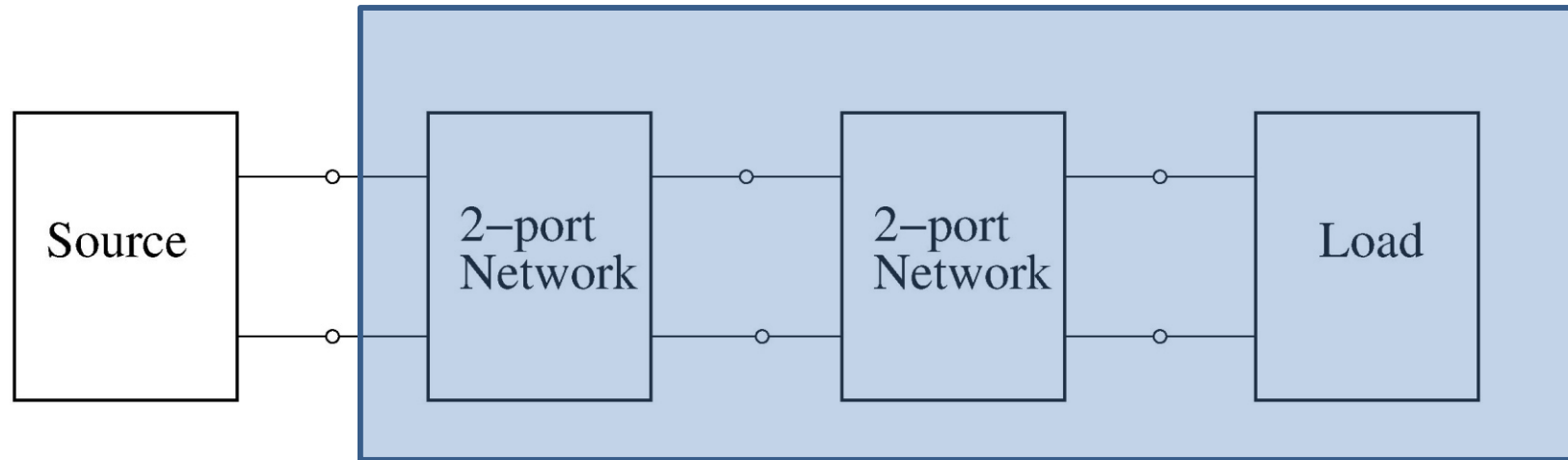


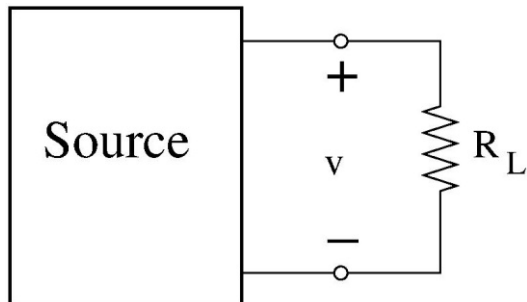A two-terminal network containing NO independent source




For a linear source, we only find the Thevenin parameters of the source.

Two-port network

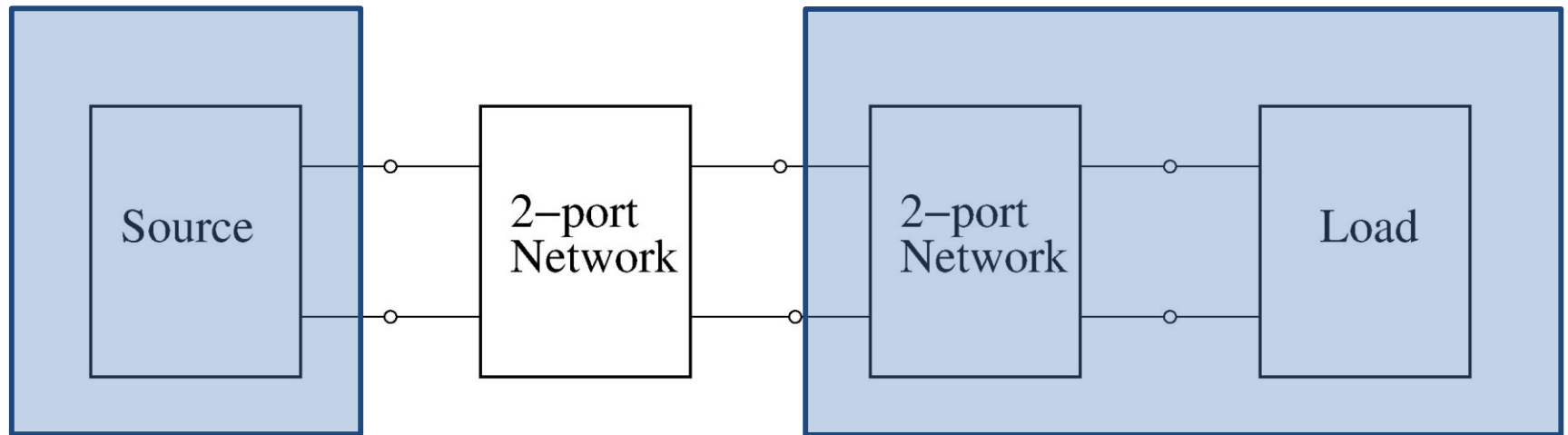

A two-terminal network containing an independent source

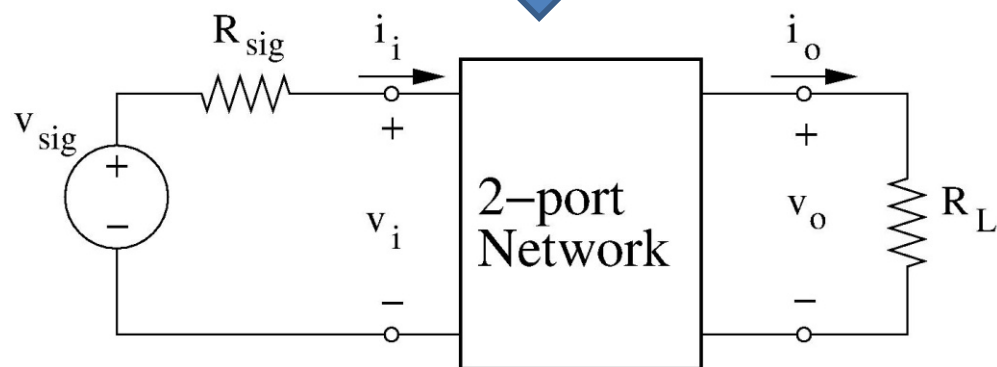
A two-terminal network containing no independent source




Transfer function of a two-port network can be found by solving the above circuit once.

Course map

2. Diodes

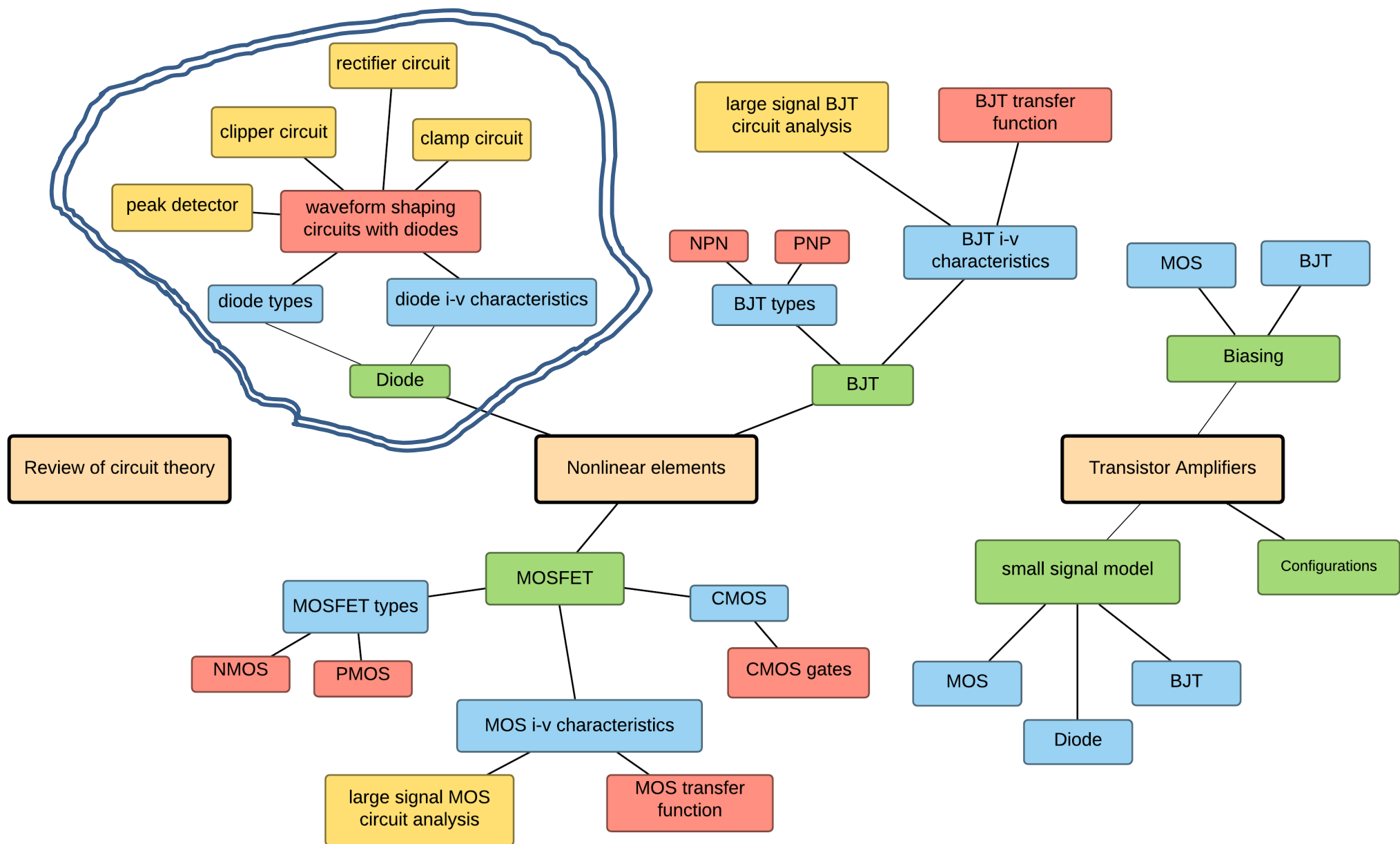

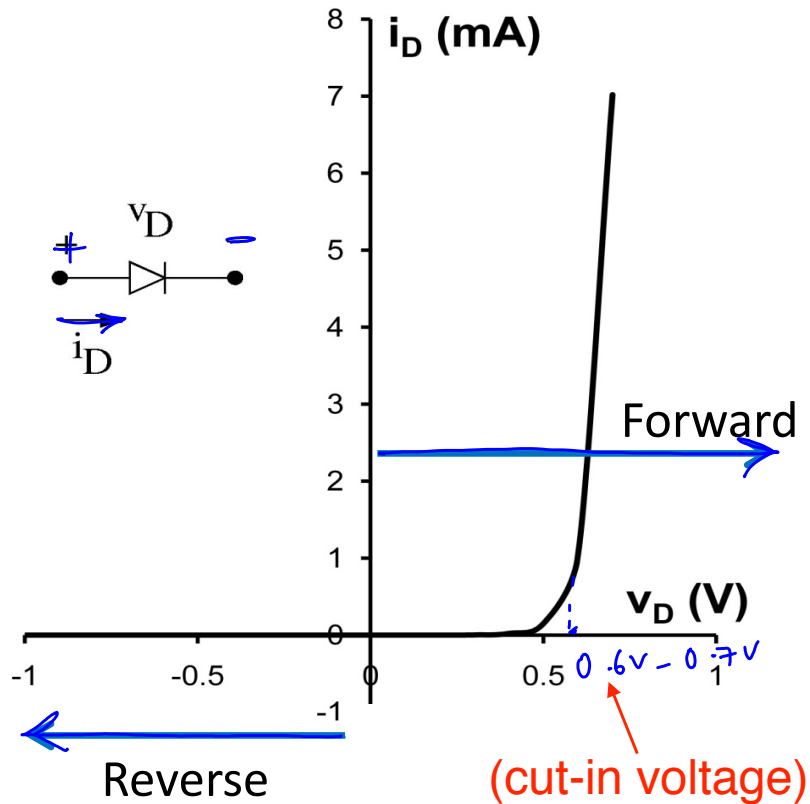The i v characteristics of a silicon junction diode




When the diode conducts,
 $i_D \gg I_S$ and:

$$i_D = I_S e^{v_D/V_T}$$

I_S : Saturation Current
(10^{-9} to 10^{-18} A)

V_T : Thermal voltage = 26mV at room temp.


Diode piecewise-linear model:

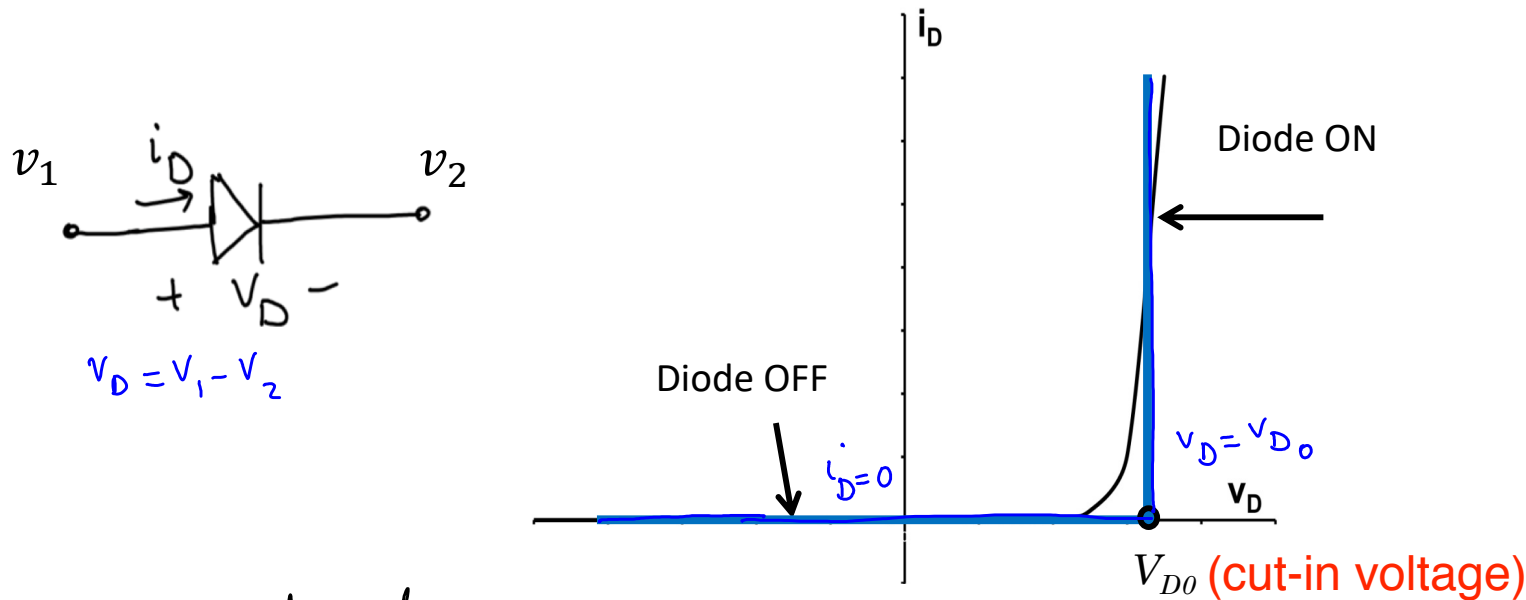

Assume Si Diode with $V_{D0} = 0.7V$



- (A) When $V_1 - V_2 < 0 \rightarrow$ diode is reverse-biased $\Rightarrow i_D = 0$
- (B) When $0 < V_1 - V_2 < 0.7 \rightarrow$ diode is forward-biased, but it's not ON, yet $\Rightarrow i_D = 0$
- (C) When $V_1 - V_2 = 0.7 \rightarrow$ diode is forward biased and it's ON $\Rightarrow i_D \geq 0$ & $V_D = V_{D0} = 0.7$

Diode piecewise-linear model:

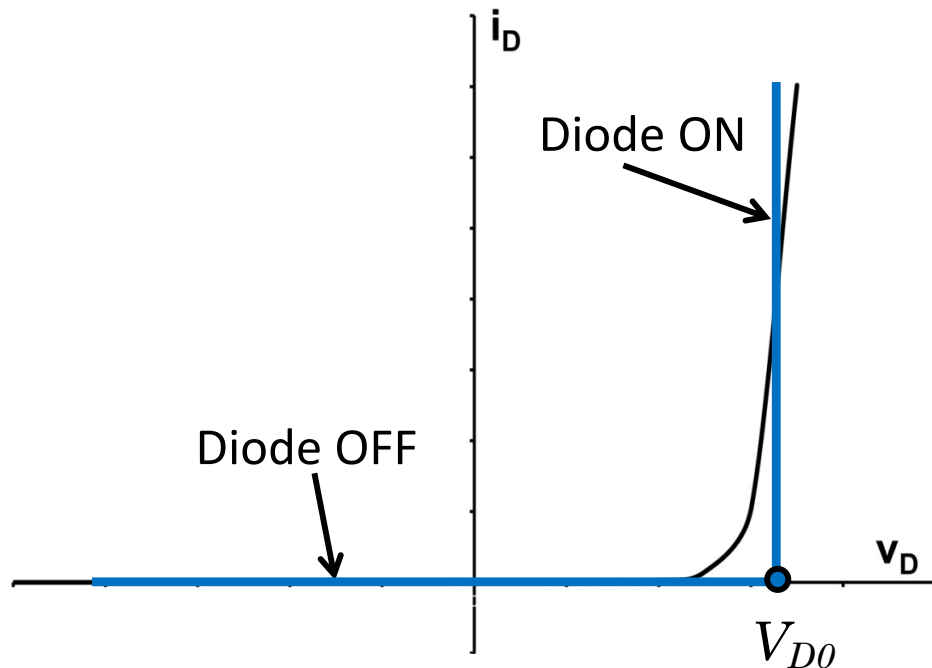

Constant Voltage drop Model:

Circuit Models:

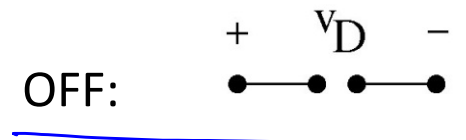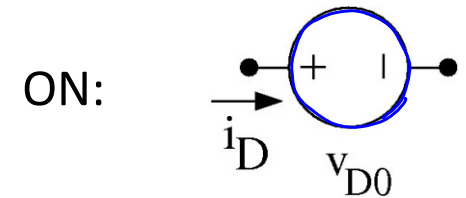


Diode ON: $v_D = V_{D0}$ and $i_D \geq 0$

Diode OFF: $i_D = 0$ and $v_D < V_{D0}$


(cut-in voltage) $V_{D0} = 0.6 - 0.7 \text{ V}$ for Si

Diode circuit models:

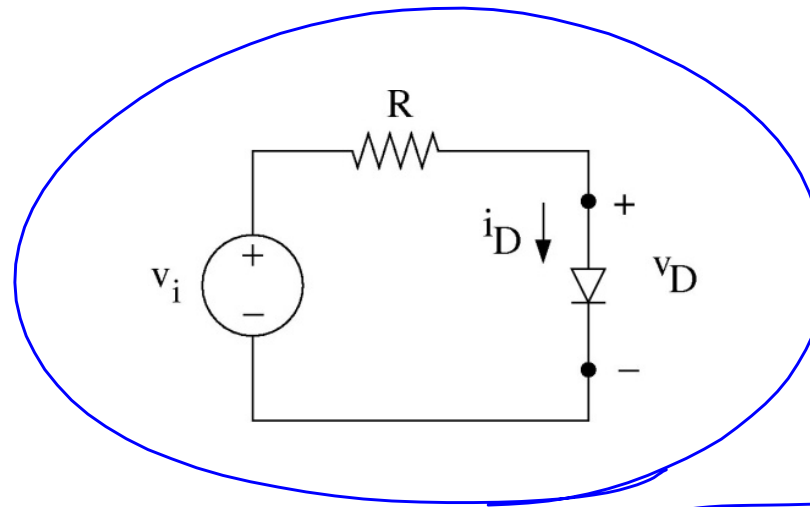


When Diode is OFF:

$i_D = 0$ and $v_D < V_{D0}$

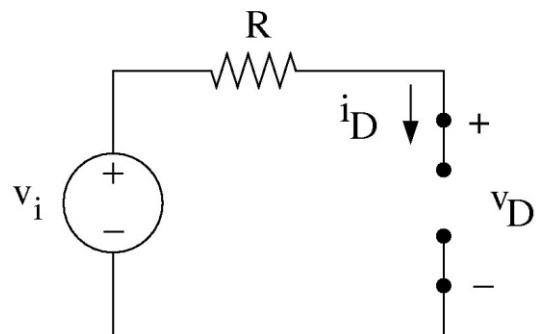

When Diode is ON:

$i_D \geq 0$ and $v_D = V_{D0}$

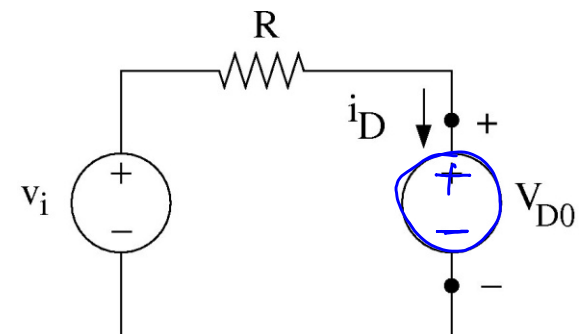


Example 1:

Find i_D and v_D for $R = 1k$, $V_i = 5V$, and Si Diode ($V_{D0} = 0.7V$).

Solution with diode circuit models:

Assume Diode is off

$$i_D = 0, \quad v_D < V_{D0}$$

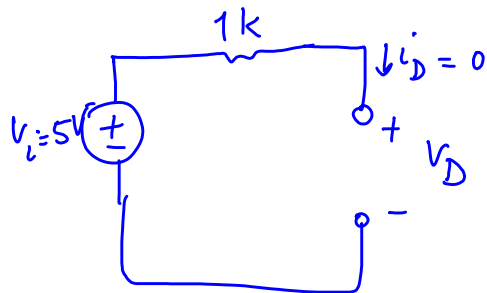


$$V_i = 1k \times i_D + v_D$$

$$V_i = v_D = 5V > 0.7 \rightarrow \text{Assumption was wrong.}$$

Assume Diode is ON


$$i_D \geq 0, \quad v_D = V_{D0}$$

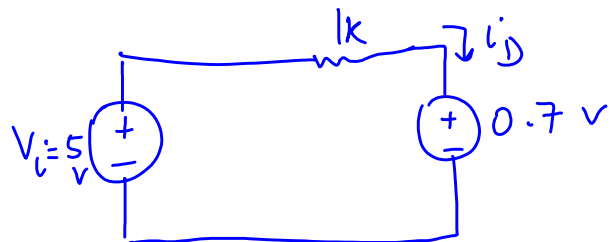

$$V_i = 1k \times i_D + 0.7V$$

$$\rightarrow i_D = \frac{5 - 0.7}{1k} = \underline{4.3mA} > 0$$

The diode is ON.

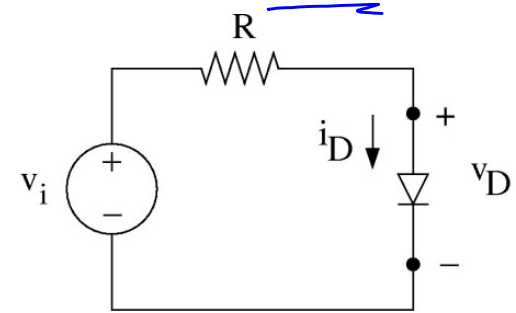

Example 2 :


For what range of V_i the diode will be ON and for what range it will be OFF?

Find i_D and v_D for each range.

When diode is ON : $i_D \geq 0$, $V_D = V_{D_0}$

$$V_i = R i_D + V_D = R i_D + 0.7$$
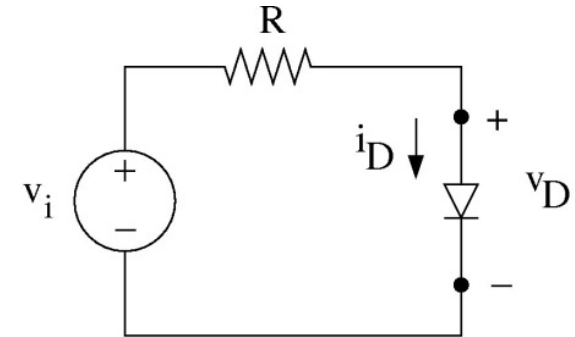
$$i_D = \frac{V_i - 0.7}{R} \geq 0 \rightarrow V_i \geq 0.7 \text{ V}$$



For $V_i \geq 0.7 \text{ V}$, diode is ON, $V_D = V_{D_0}$, $i_D \geq 0$

When the diode is off : $i_D = 0$, $V_D < V_{D_0}$


$$V_i = R i_D + V_D \rightarrow V_i = V_D, \quad V_D < V_{D_0} \rightarrow V_i < V_{D_0}$$

For $V_i < V_{D_0}$, diode is off, $i_D = 0$, $V_D < V_{D_0}$

Lecture 4 reading quiz

In this diode circuit, what is the value of V_R for $V_i = 5\text{ V}$ and $V_i = -5\text{ V}$?

Assume $V_{D0} = 0.7\text{ V}$

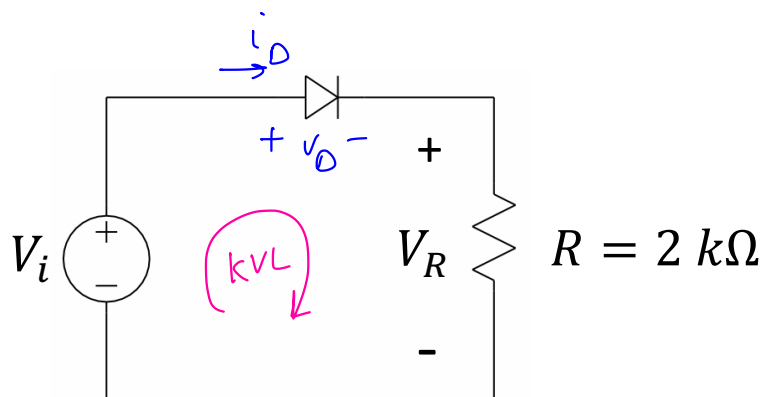

when $V_i = 5\text{ V}$:

Assume the diode is off :

$$v_D < V_{D0} \text{ and } i_D = 0$$


$$\text{KVL: } -V_i + v_D + R i_D = 0 \quad \rightarrow \quad -V_i + v_D = 0 \quad \rightarrow \quad v_i = v_D = 5 > V_{D0}$$

\Rightarrow The assumption was wrong.

Lecture 4 reading quiz

In this diode circuit, what is the value of V_R for $V_i = 5\text{ V}$ and $V_i = -5\text{ V}$?

Assume $V_{D0} = 0.7\text{ V}$

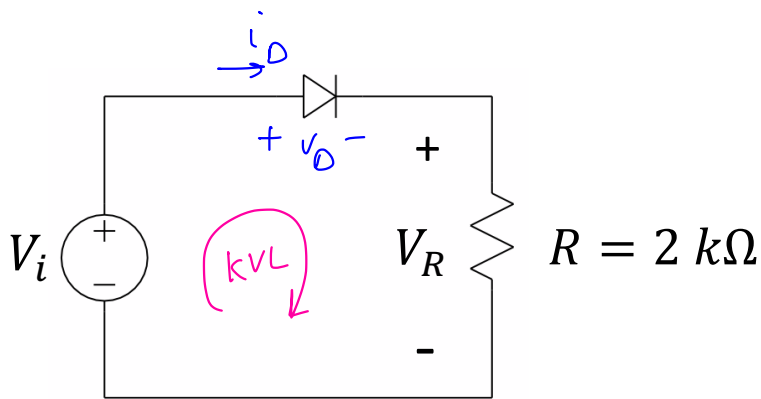

when $V_i = 5\text{ V}$:

Assume the diode is ON :

$$v_D = V_{D0} \text{ and } i_D \geq 0$$

$$\text{KVL: } -V_i + V_D + R i_D = 0 \quad \rightarrow \quad -V_i + V_{D0} + 2\text{ k}\Omega \times i_D = 0$$

$$\rightarrow -5\text{ V} + 0.7\text{ V} + 2\text{ k}\Omega \times i_D = 0 \quad \Rightarrow \quad i_D = 2.15\text{ mA} > 0$$


\Rightarrow The assumption was correct. The diode is ON, $v_D = V_{D0}$ and $i_D = 2.15\text{ mA}$.

$$V_R = 2\text{ k}\Omega \times 2.15\text{ mA} = 4.3\text{ V}$$

Lecture 4 reading quiz

In this diode circuit, what is the value of V_R for $V_i = 5\text{ V}$ and $V_i = -5\text{ V}$?

Assume $V_{D0} = 0.7\text{ V}$

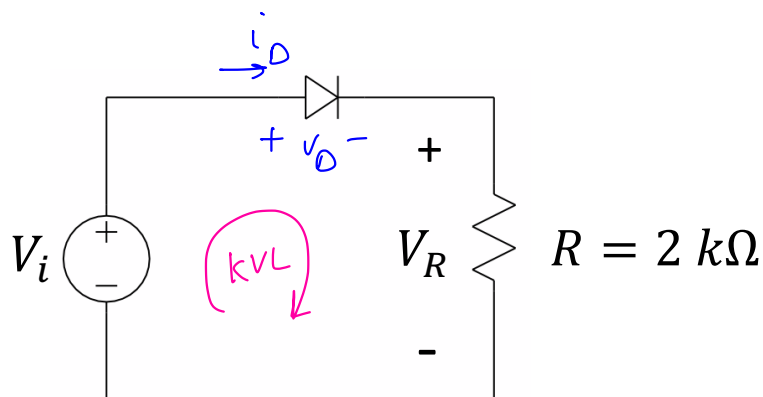

when $V_i = -5\text{ V}$:

Assume the diode is off :

$$v_D < V_{D0} \text{ and } i_D = 0$$

$$\text{KVL: } -V_i + v_D + R i_D = 0 \quad \rightarrow \quad -V_i + v_D = 0 \quad \rightarrow \quad v_i = v_D = -5\text{ V} < V_{D0}$$


\Rightarrow The assumption was correct. The diode is off, $i_D = 0$ and $v_D = -5\text{ V}$.

$$V_R = 2\text{ k}\Omega \times i_D = 0\text{ V}$$

Clicker question 1.

For what range of v_s , will the diode in the following circuit be ON??

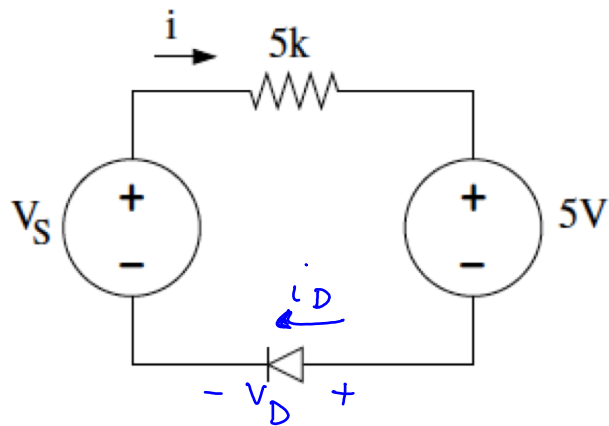(Si diodes with $V_{D0} = 0.7 \text{ V}$)




A. $v_s \geq 5 \text{ V}$

B. $v_s \geq 5.7 \text{ V}$

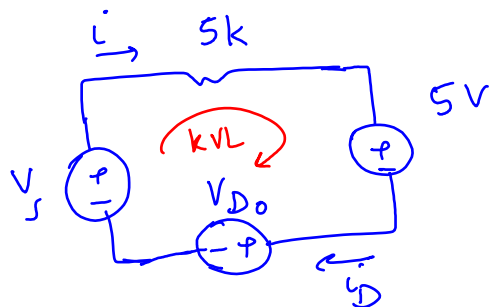C. $v_s \geq 4.3 \text{ V}$

Diode ON : $V_D = V_{D0}$, $i_D \geq 0$

replacing the diode with the constant voltage drop model:



$$\text{KVL: } -V_s + 5k\Omega \times i + 5\text{V} + V_{D0} = 0$$


$$\Rightarrow i = i_D = \frac{V_s - 5.7}{5k\Omega} \geq 0$$

$$\rightarrow V_s \geq 5.7 \text{ V}$$

Clicker question 3.

Find v_R and i in the below circuit for $v_s = 3V$.

(Assume Si diodes with $V_{D0} = 0.7 V$)

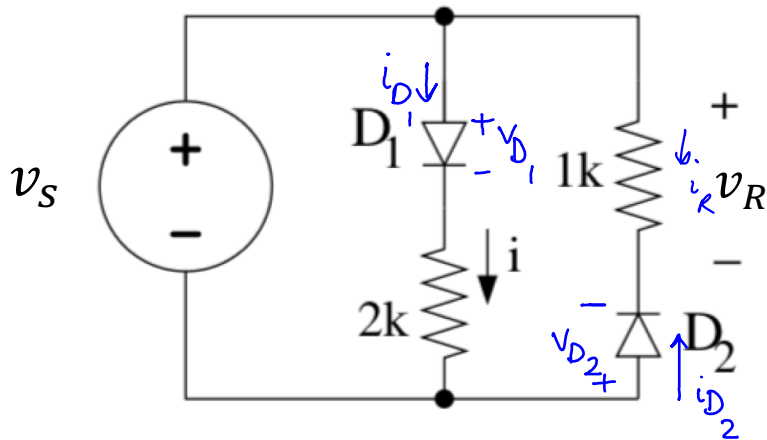


$$V_R = 1k\Omega \times i_R$$

$$\text{KCL: } i_R = -i_{D2}$$

$$\rightarrow V_R = -1k\Omega \times i_{D2}$$

- A. $v_R = 2.3 V, i = 1.15 mA$
- B. $v_R = 0 V, i = 1.15 mA$
- C. $v_R = 0.6 V, i = 0.3 mA$
- A. $v_R = -2.3 V, i = 1.15 mA$

All the states for D_1 and D_2 :

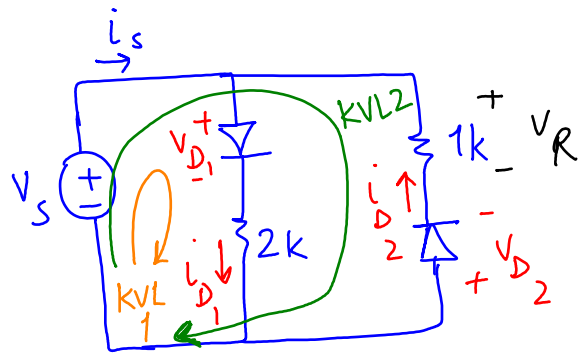

D_1	D_2	
ON	OFF	Case 1
OFF	OFF	Case 2
ON	ON	Case 3
OFF	ON	Case 4

Case 1: Assume D_1 is ON and D_2 is OFF

$$V_{D_1} = V_{D_0} \text{ \& } i_{D_1} \geq 0 \text{ \& } V_{D_2} < V_{D_0} \text{ \& } i_{D_2} = 0$$


$$\begin{aligned} \text{KVL 1: } -V_s + V_{D_1} + 2k \times i_{D_1} &= 0 \rightarrow -3V + 0.7V + 2k \times i_{D_1} = 0 \\ &\rightarrow i_{D_1} = 1.15 \text{ mA} \geq 0 \end{aligned}$$

$$\text{KVL 2: } -V_s + 1k \times (-i_{D_2}) - V_{D_2} = 0 \rightarrow -3V + 0 - V_{D_2} = 0 \rightarrow V_{D_2} = -3V < 0.7V$$

$i_{D_1} \geq 0$ and $V_{D_2} < V_{D_0} \rightarrow$ the assumption was correct.

$$V_R = -1k \times i_{D_2} = 0V \rightarrow \boxed{V_R = 0V}$$

Let's show that other cases are not valid.

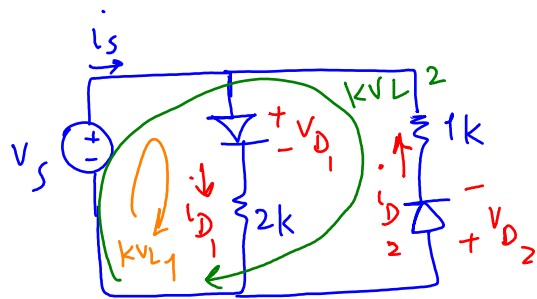

Case 2: Assume D_1 is OFF and D_2 is OFF

$$i_{D1} = 0 \text{ \& } V_{D1} < V_{D0} \text{ \& } i_{D2} = 0 \text{ \& } V_{D2} < V_{D0}$$

$$\text{KVL 1: } V_S = V_{D1} + 2k \times i_{D1} \rightarrow V_{D1} = V_S = 3V > V_{D0} \rightarrow \text{Assumption was wrong}$$

Case 3: Assume D_1 and D_2 are ON

$$V_{D1} = V_{D0} \text{ \& } i_{D1} \geq 0 \text{ \& } V_{D2} = V_{D0} \text{ \& } i_{D2} \geq 0$$

$$\text{KVL 2: } V_S = -1k \times i_{D2} - V_{D2} \rightarrow i_{D2} = \frac{-3 - 0.7}{1k} = -3.7 \text{ mA} < 0 \rightarrow \text{Assumption was wrong}$$

Case 4: Assume D_1 is OFF and D_2 is ON

$$V_{D1} < V_{D0} \text{ \& } i_{D1} = 0 \text{ \& } V_{D2} = V_{D0} \text{ \& } i_{D2} \geq 0$$

$$\text{KVL 1: } V_S = V_{D1} + 2k \times i_{D1} \rightarrow V_{D1} = V_S = 3V > V_{D0} \rightarrow \text{Assumption was wrong}$$