
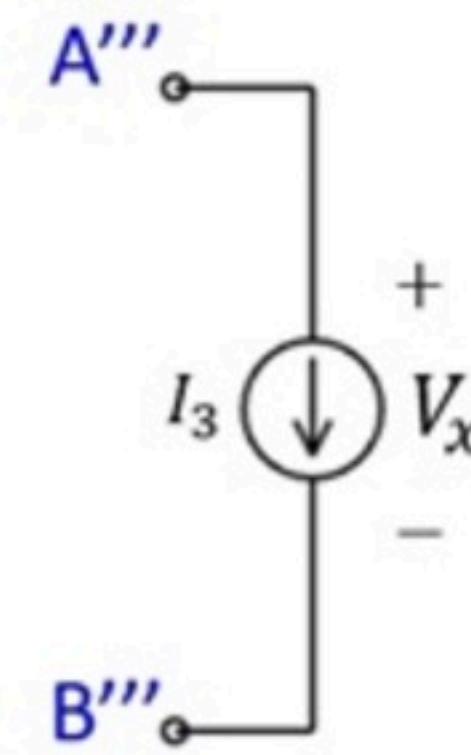
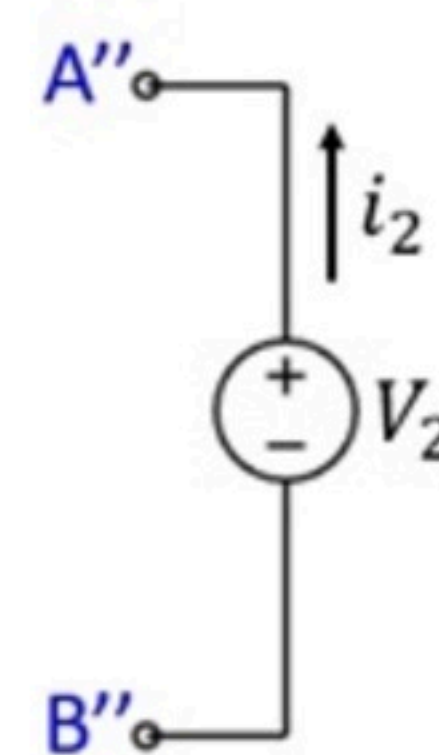
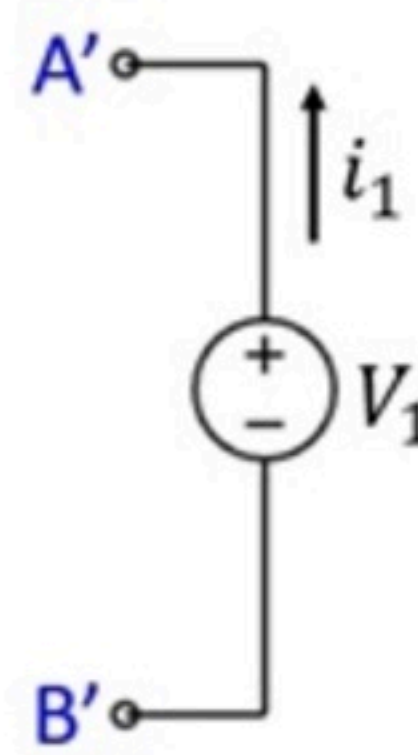


Circuit theorems 013

No more attempts left.

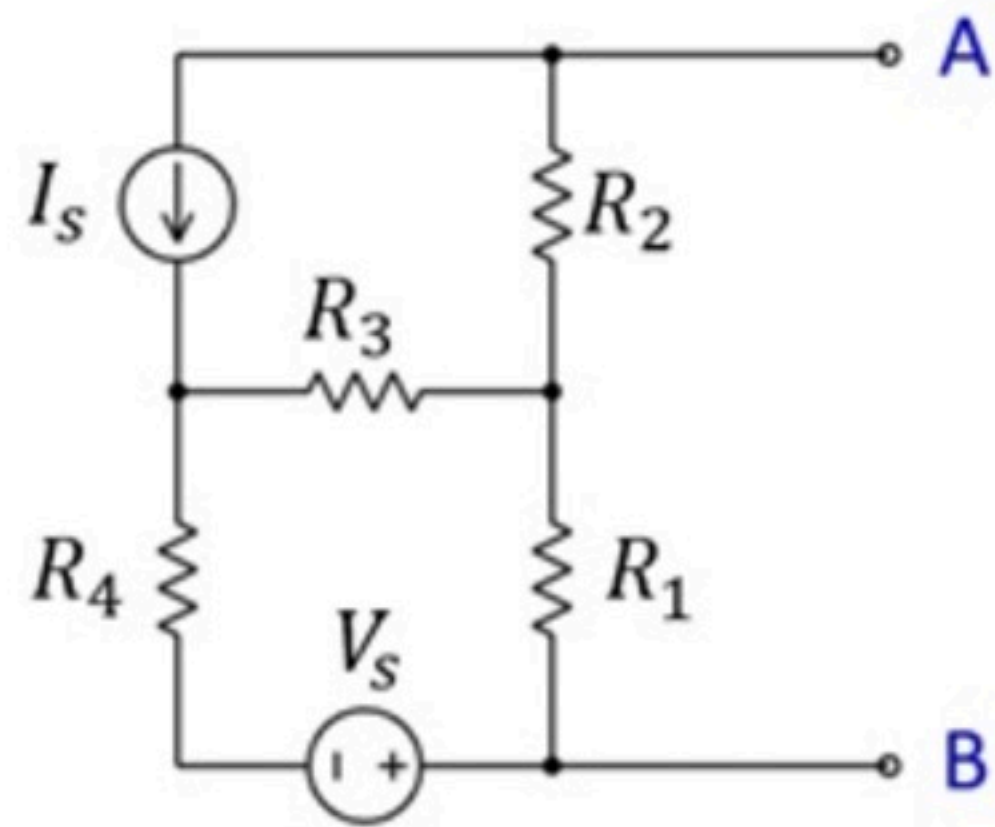Consider the circuit on the left. You are not given the values of V_S , I_S , R_1 , R_2 or R_3 .



You are told the value of current i_1 if V_1 is attached to this circuit, with A connected to A' and B connected to B' .

You are also told the value of current i_2 if V_2 is attached, with A connected to A'' and B connected to B'' . However, in this case, the independent sources were first turned off (i.e., $V_S = 0$ and $I_S = 0$).

Your task is to find V_x if current source I_3 is connected to the original circuit (i.e., with the independent sources V_S and I_S not turned off), with A connected to A''' and B connected to B''' .

Given Variables:

V_1 : 6 V

i_1 : 12 A

V_2 : 12 V

i_2 : 12 A

I_3 : -7 A



R_4 : 2 ohm

Calculate the following:

V_x (V) :

Hint: Redraw the circuit on the left as its Thevenin equivalent model

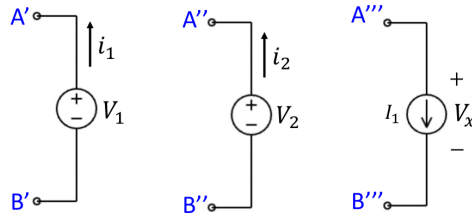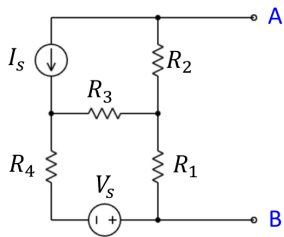Consider the circuit on the left. You are not given the values of V_S , I_S , R_1 , R_2 or R_3 .




$$\begin{aligned} V_1 &= 15 \text{ V} \\ i_1 &= 6 \text{ A} \\ V_2 &= 10 \text{ V} \\ i_2 &= 5 \text{ A} \\ I_1 &= 5 \text{ A} \\ R_4 &= 2 \Omega \end{aligned}$$

You are told the value of current i_1 if V_1 is attached to this circuit, with A connected to A' and B connected to B' .


You are also told the value of current i_2 if V_2 is attached, with A connected to A'' and B connected to B'' . However, in this case, the independent sources were first turned off (i.e., $V_S = 0$ and $I_S = 0$).

Your task is to find V_x if current source I_1 is connected to the original circuit (i.e., with the independent sources V_S and I_S not turned off), with A connected to A''' and B connected to B''' .

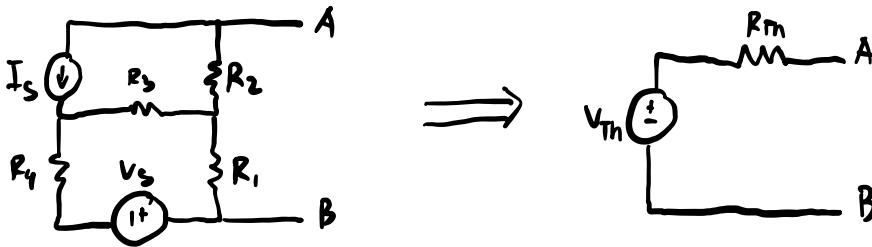Represent the left circuit as its Thevenin equivalent circuit



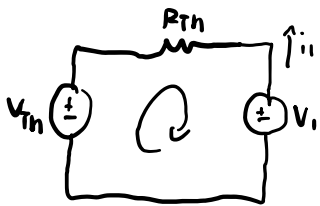
When $A \rightarrow A'$, $B \rightarrow B'$



$$\text{KVL: } -V_{Th} - i_1 R_{Th} + V_1 = 0$$

$$V_{Th} = V_1 - i_1 R_{Th}$$

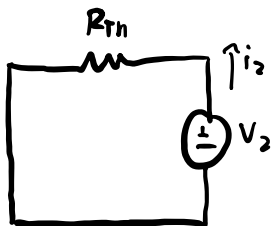when $A \rightarrow A''$, $B \rightarrow B''$ and $V_S = 0$, $I_S = 0$




$$R_{Th} = \frac{V_2}{i_2} = \frac{10}{5} = 2 \Omega$$

$$V_{Th} = 15 - 6(2)$$

$$V_{Th} = 3 \text{ V}$$

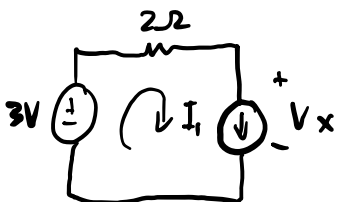when $A \rightarrow A'''$, $B \rightarrow B'''$



$$\text{KVL: } -3 + 2I_1 + V_x = 0$$

$$V_x = 3 - 2(5)$$

$$\boxed{V_x = -7 \text{ V}}$$