
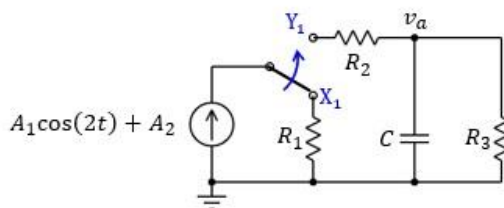


Q1

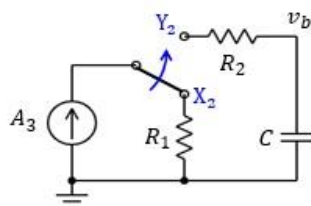
- (a) For $t < \frac{\pi}{6}$ s, the switch is in position X_1 , and at time $t = 0$ s the capacitor is fully discharged. At time $t = \frac{\pi}{6}$ s, the switch moves from position X_1 to position Y_1 . Find the steady state node voltage waveform $v_a(t)$.




- (b) For $t < \frac{\pi}{6}$ s, the switch is in position X_2 , and at time $t = 0$ s the capacitor is fully discharged. At time $t = \frac{\pi}{6}$ s, the switch moves from position X_2 to position Y_2 . Find the node voltage $v_b(\pi)$ s, i.e., at time $t = \pi$ s.



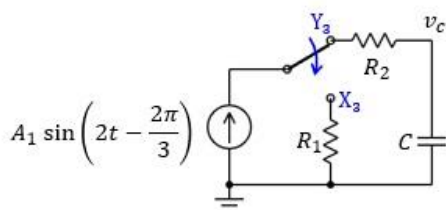- (c) For $t < \frac{\pi}{6}$ s, the switch is in position Y_3 , and you may assume the system has reached steady state. At time $t = \frac{\pi}{6}$ s, the switch moves from position Y_3 to position X_3 . Find the node voltage $v_c(\pi)$ s.



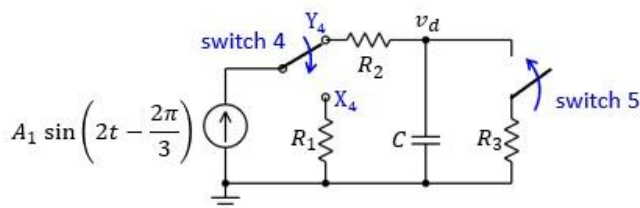- (d) For $t < \frac{\pi}{6}$ s, switch 4 is in position Y_4 and switch 5 is open, and you may assume the system has reached steady state. At time $t = \frac{\pi}{6}$ s, switch 4 moves from position Y_4 to position X_4 and switch 5 closes. Find the node voltage $v_d(\pi)$ s.



R1:	1 Ω
R2:	1 Ω
R3:	1 Ω
C:	500 mF
A1:	3 A
A2:	2 A
A3:	3 A



Q2

The AC circuit below has $\omega = 10 \text{ rad/s}$ and is in steady state. The phasor diagram shows the phasors of i_S and v_L . You are given the angles α (between \mathbf{I}_S and the x-axis), β (between \mathbf{V}_L and the x-axis), $|\mathbf{I}_S|$ and $|\mathbf{V}_L|$. The diagram is not necessarily drawn to scale.

The element represented by the rectangular box is either an inductor or a capacitor but you are not told which.

- Find the complex power \mathbf{S}_L received by the inductor.
- Find the complex power \mathbf{S}_S supplied by the current source.
- Find the complex power \mathbf{S}_M received by the mystery element.
- What is the mystery element (capacitor or inductor)? (You do not need to find its value, but your answer needs to be motivated)


$ \mathbf{I}_S $:	3 A
alpha:	20 degrees
$ \mathbf{V}_L $:	4 V
Beta:	80 degrees
R1:	2 Ω
L:	200 mH

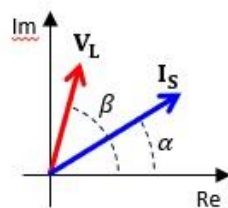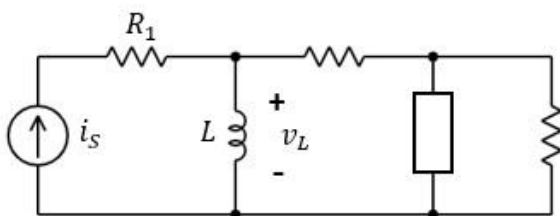

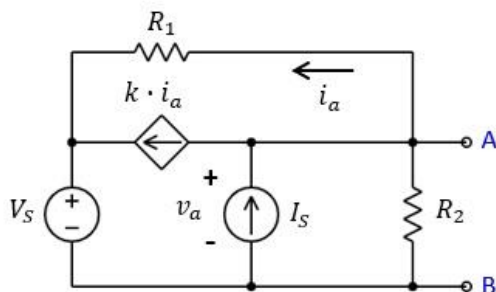Q3


Consider the circuit below.

- Find the voltage v_a .
- Draw the Thevenin model for the circuit between A and B (make sure you label A and B in your drawing).



R1:	18 Ω
R2:	3 Ω
k:	2 A/A
V_S :	3 V
I_S :	2 A
R3:	2 Ω
R4:	2 Ω

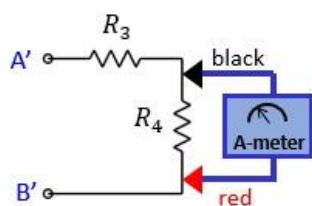
- Connect the circuit on the right to the one on top (A' connected to A and B' connected to B). What is the reading X of the ideal **ammeter**?



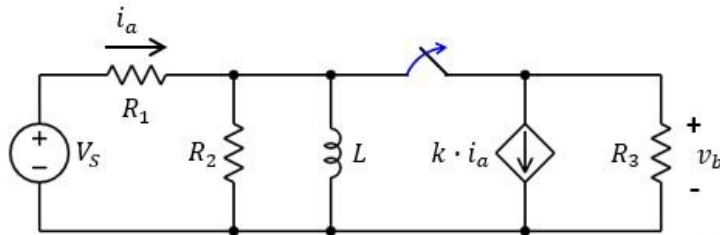Q4

For $t < 2$ s, the switch is closed, and you may assume the system has reached steady state. The switch opens at time $t = 2$ s.

- Find $v_b(t)$ for $t > 2$ s.
- What is the instantaneous power received by the inductor at time $t = 2^+$ s.




V_s : 4 V
 R_1 : 2 Ω
 R_2 : 2 Ω
 R_3 : 3 Ω
 L : 200 mH
 k : 3 A/A

Q5

The circuit below is an AC circuit and is in steady state. The three independent sources all have $\omega = 10$ rad/s.

You measure the waveform $i_a(t) = A_1 \cos(10t + B_1)$.

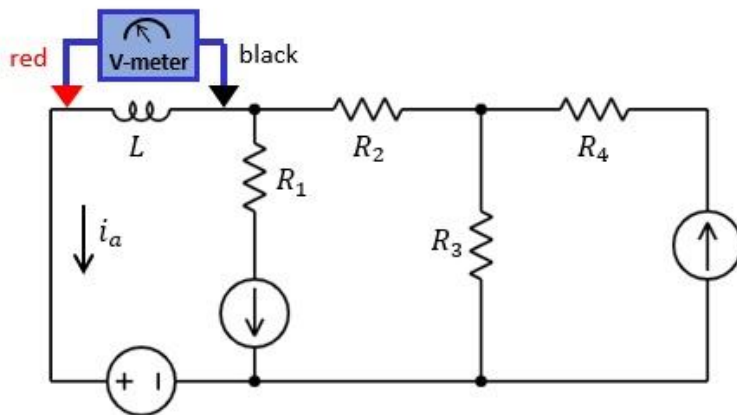Now the circuit is changed: the inductor **L** is replaced by capacitor **C**. In this changed circuit, what will be the reading of the ideal volt-meter?



R_1 : 2 Ω
 R_2 : 2 Ω
 R_3 : 3 Ω
 R_4 : 2 Ω
 A_1 : 10 A
 B_1 : 60 degrees
 L : 300 mH
 C : 40 mF