

Basic concepts 009


Problem has been graded.

The reading of the voltmeter is x and that of the ammeter is y .

What is the power P supplied by the VCVS?

What is the value of the current source i_s ?

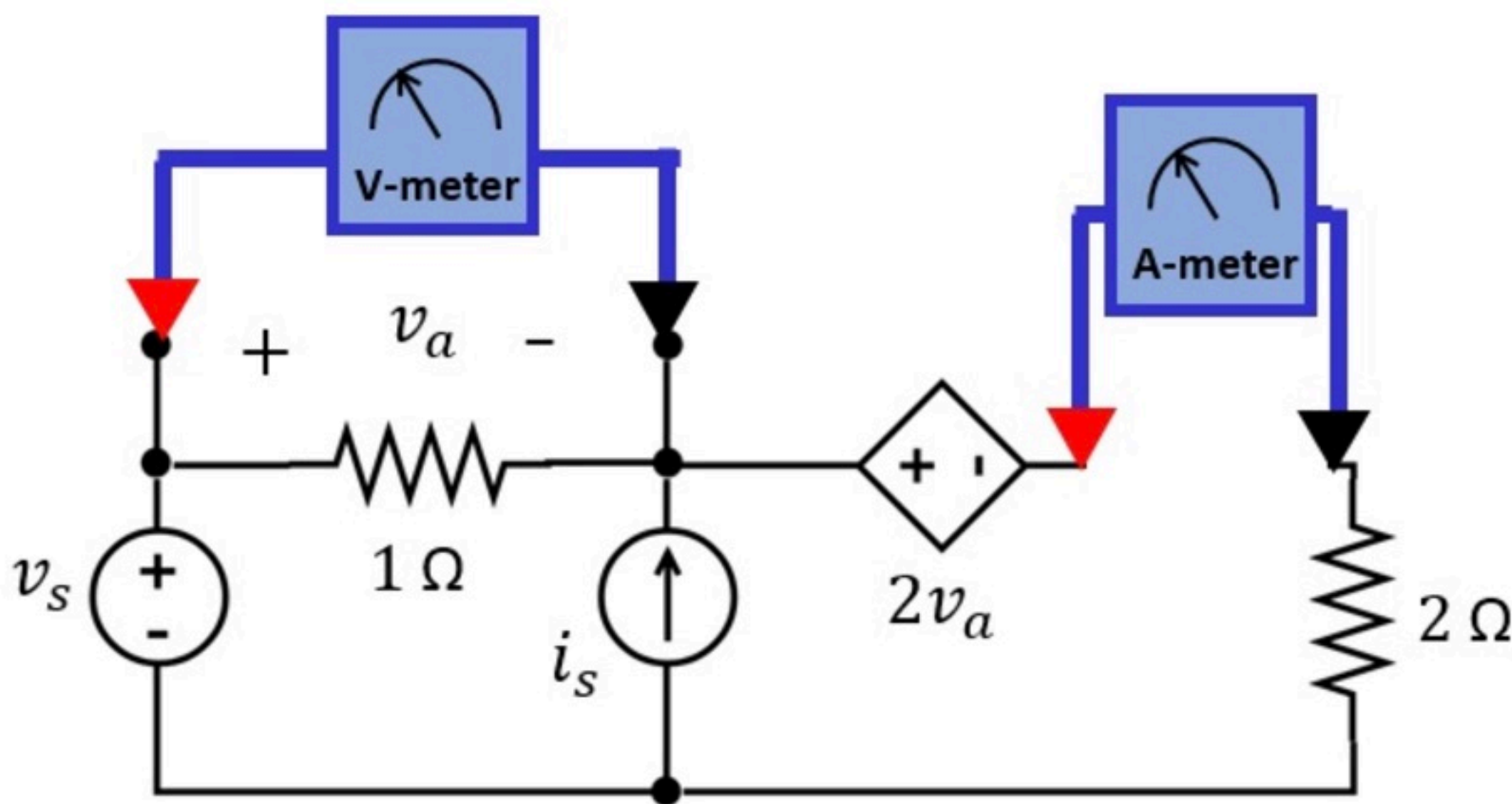What is the value of the voltage source v_s ?



Given Variables:

$x : 3 \text{ V}$

$y : 5 \text{ A}$

Calculate the following:

$P \text{ (W)} :$

$i_s \text{ (A)} :$

$v_s \text{ (V)} :$

The reading of the voltmeter is x and that of the ammeter is y .


What is the power P supplied by the VCVS?

$$X = 6 \text{ V}$$

What is the value of the current source i_s ?

$$Y = 3 \text{ A}$$

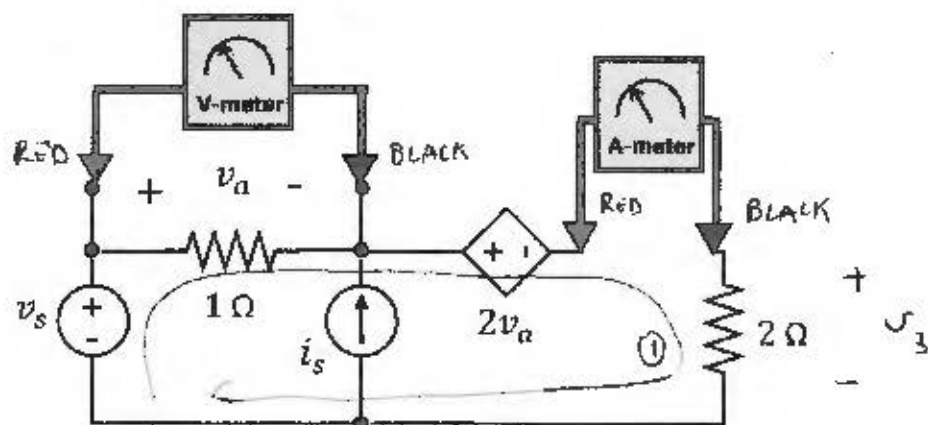What is the value of the voltage source v_s ?




①

$$v_a = X = 6$$

$$i_1 = Y = 3$$

$$v_1 = 2v_a = 12$$

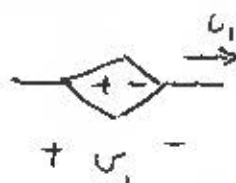


$$P = v_1 \cdot i_1 = 36 \text{ W}$$

RECEIVED

$$P = -36 \text{ W SUPPLIED}$$

②

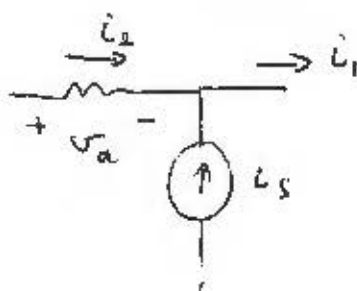

$$i_1 = \frac{v_a}{1} = 6 \text{ A}$$

$$\text{KCL: } i_2 + i_s = i_1 \Rightarrow i_s = 3 - 6 = -3$$

$$i_s = -3 \text{ A}$$

③ KVL in ①:

$$\begin{aligned} v_s &= v_a + 2v_a + v_3 \\ &= 3 \cdot 6 + 6 \\ &= 24 \end{aligned}$$

$$v_3 = i_1 \cdot 2 = 6 \text{ V}$$


$$v_s = 24 \text{ V}$$

Basic analysis 007

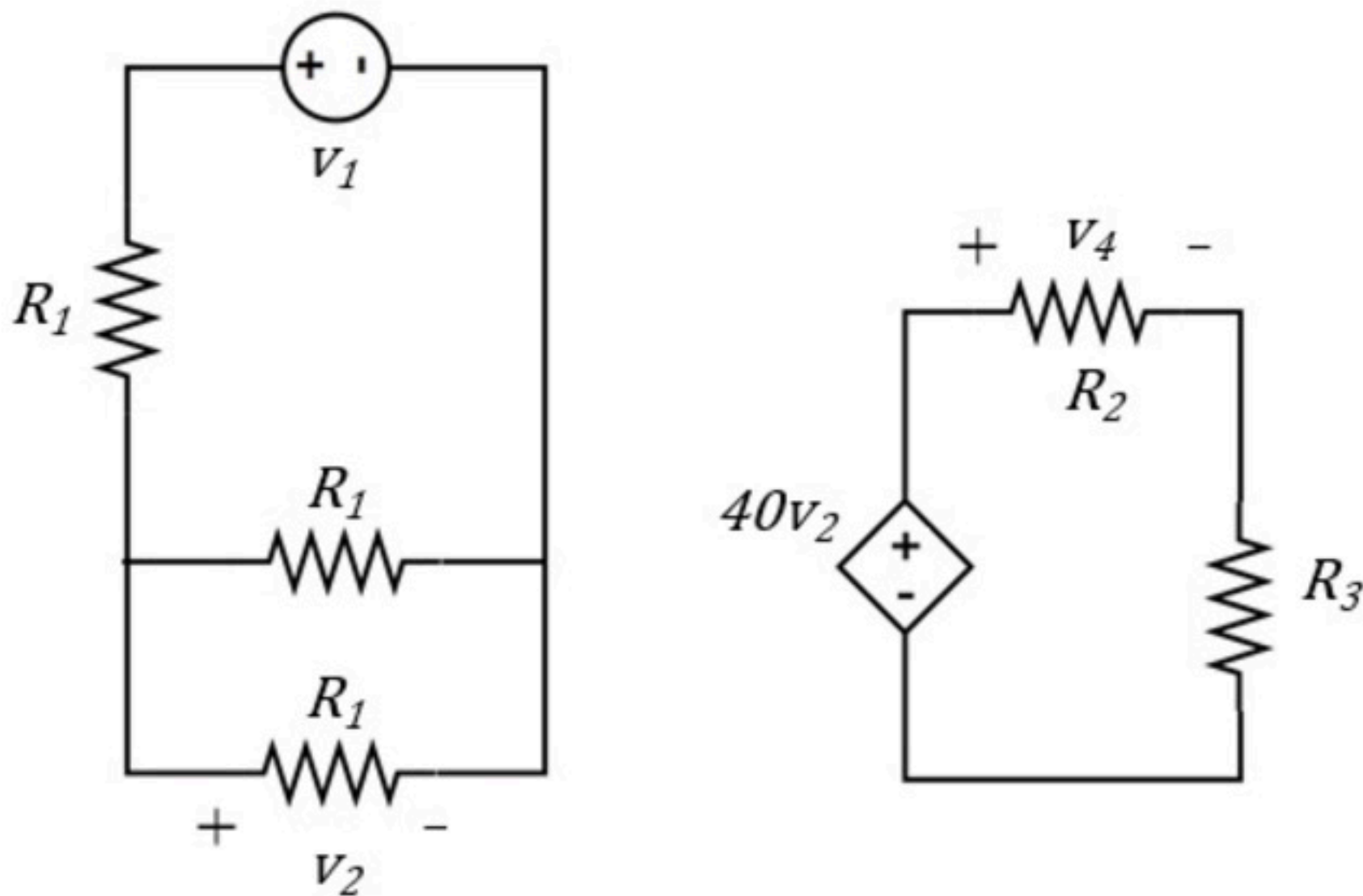Problem has been graded.

In this circuit, v_1 is an input, but you don't know what its value is. Find v_4 as a function of v_1 .

More specifically, find $X = \frac{v_4}{v_1}$.



Given Variables:

R_1 : 10 ohm

R_2 : 3 ohm

R_3 : 5 ohm

Calculate the following:

X (V/V) :



In this circuit, v_I is an input, but you don't know what its value is. Find v_4 as a function of v_I .

More specifically, find $X = \frac{v_4}{v_I}$.

$$R_1 = 20 \, \Omega$$


$$R_2 = 12 \, \Omega$$

$$R_3 = 20 \, \Omega$$

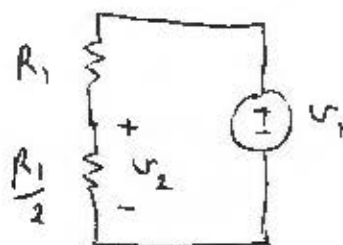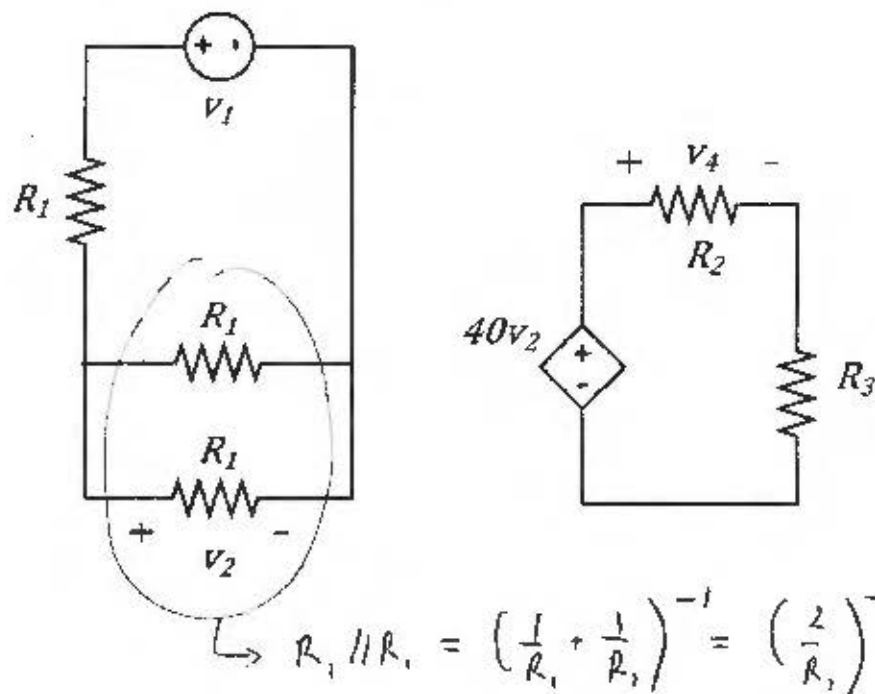

VOLTAGE DIVIDER
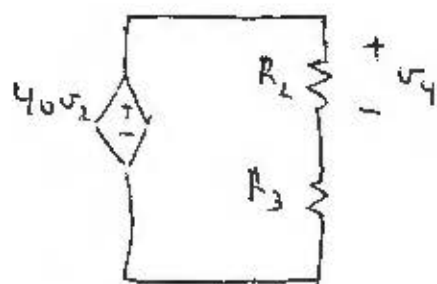
$$v_2 = v_I \cdot \frac{\frac{R_1}{2}}{R_1 + \frac{R_1}{2}} = v_I \cdot \frac{\frac{1}{2}}{1 + \frac{1}{2}} = \frac{v_I}{3}$$



VOLTAGE DIVIDER


$$v_4 = 40 v_2 \cdot \frac{R_2}{R_2 + R_3} = \frac{40 \cdot v_I}{3} \cdot \frac{12}{12 + 20} = 5 v_I$$

$$X = \frac{v_4}{v_I} = 5$$

Basic analysis 009

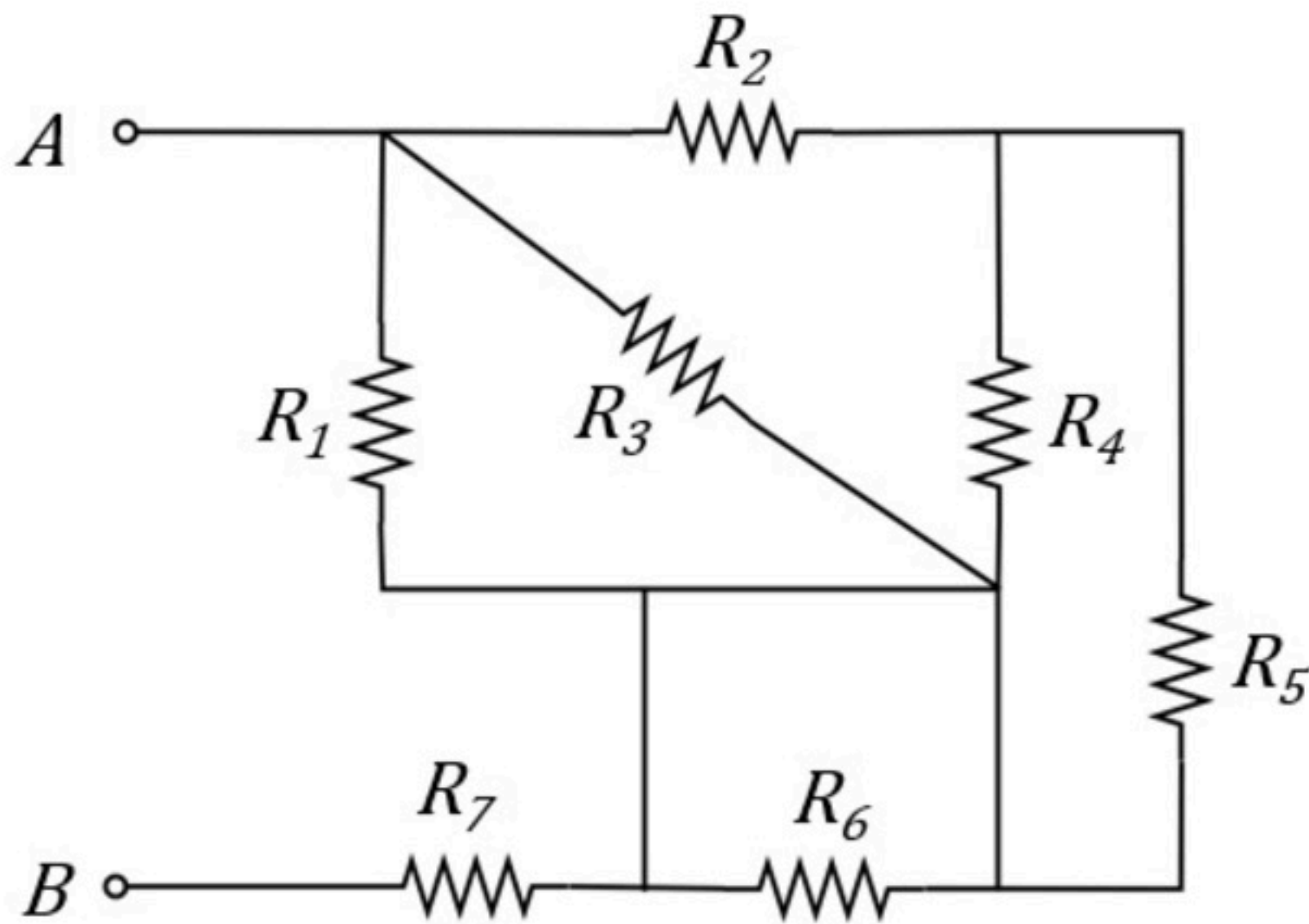Problem has been graded.

You are given that the equivalent resistance between A and B is R_{eq} . Find the value of R_3 .



Given Variables:

R_{eq} : 8 ohm

R_1 : 3 ohm

R_2 : 4 ohm

R_4 : 24 ohm

R_5 : 12 ohm

R_6 : 12 ohm

R_7 : 6 ohm

Calculate the following:

R_3 (ohm) :

You are given that the equivalent resistance between A and B is R_{eq} . Find the value of R_3 .

$$R_{eq} = 8 \Omega$$

$$R_1 = 6 \Omega$$


$$R_2 = 4 \Omega$$

$$R_4 = 40 \Omega$$

$$R_5 = 10 \Omega$$


$$R_6 = 12 \Omega$$

$$R_7 = 5 \Omega$$

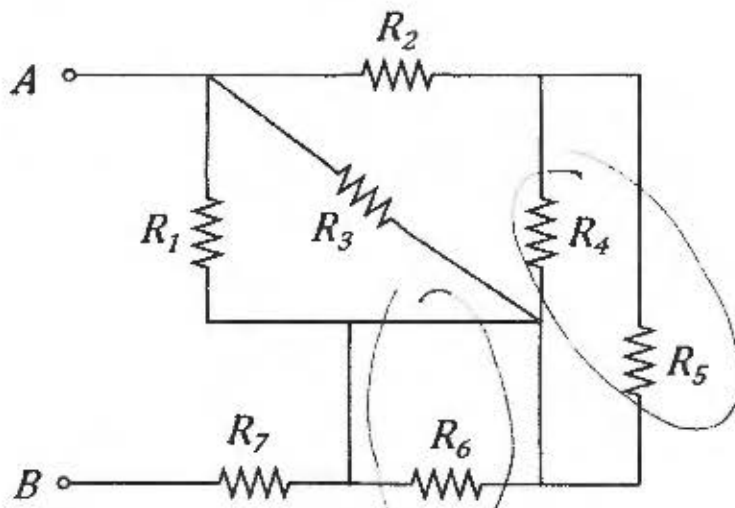

$$R_4 // R_5 = \left(\frac{1}{40} + \frac{1}{10} \right)^{-1} = \left(\frac{1+4}{40} \right)^{-1} = 8 \Omega$$
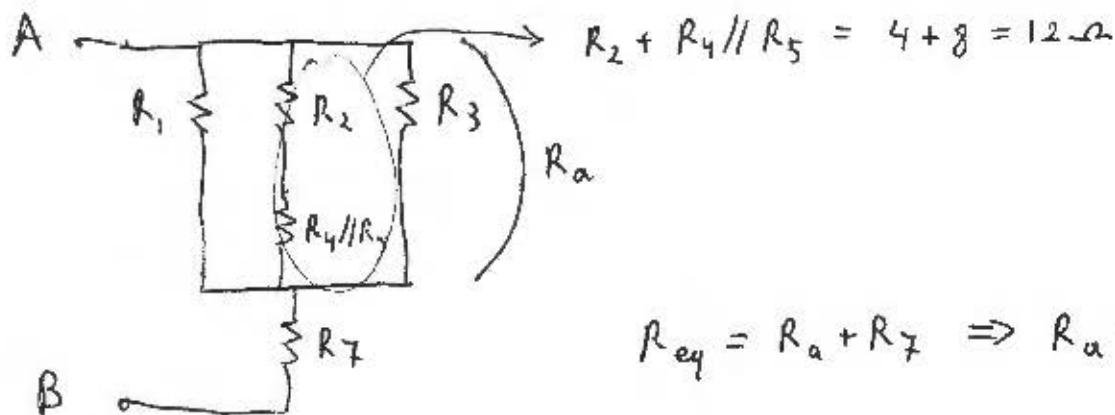
$$R_6 // \infty = \left(\frac{1}{R_6} + \frac{1}{\infty} \right)^{-1} = (\infty)^{-1} = 0 \Omega$$



$$R_{eq} = R_a + R_7 \Rightarrow R_a = R_{eq} - R_7 = 8 - 5 = 3 \Omega$$

$$\frac{1}{R_a} = \frac{1}{R_1} + \frac{1}{12} + \frac{1}{R_3}$$

$$\frac{1}{R_3} = \frac{1}{R_a} - \frac{1}{R_1} - \frac{1}{12} = \frac{1}{3} - \frac{1}{6} - \frac{1}{12} = \frac{4-2-1}{12}$$

$$R_3 = 12 \Omega$$

No more attempts left.





vs : 32 V
R1 : 2 ohm
R2 : 4 ohm

X (A) :

$$Y(V):$$

Hint: First find the current through V_s . Use series/parallel. Then find X with current divider.

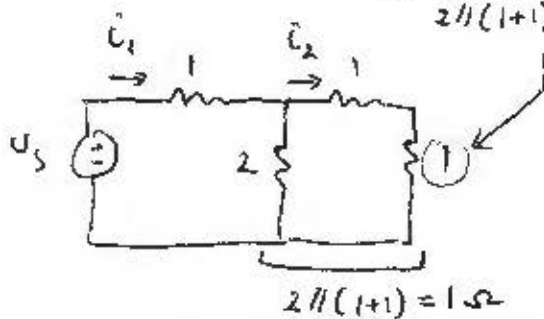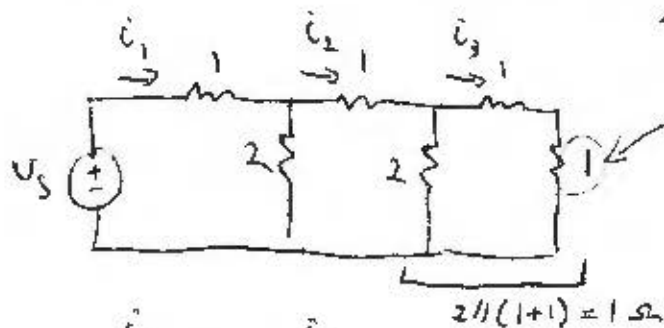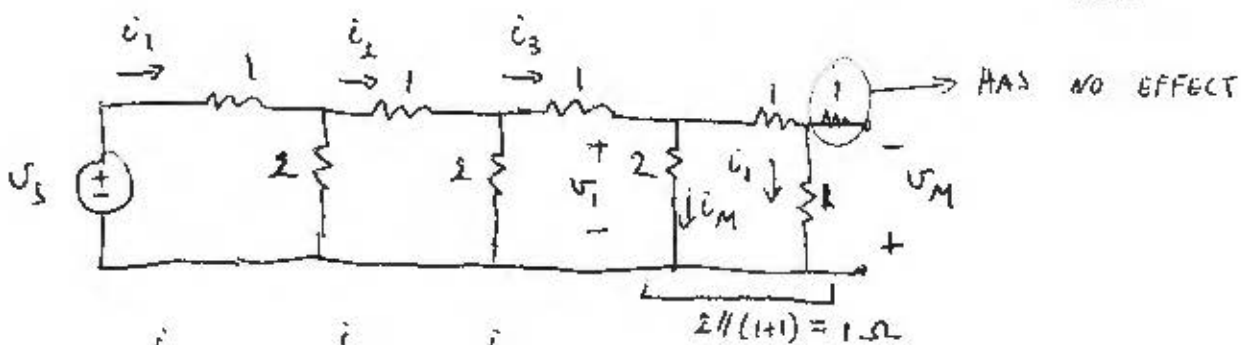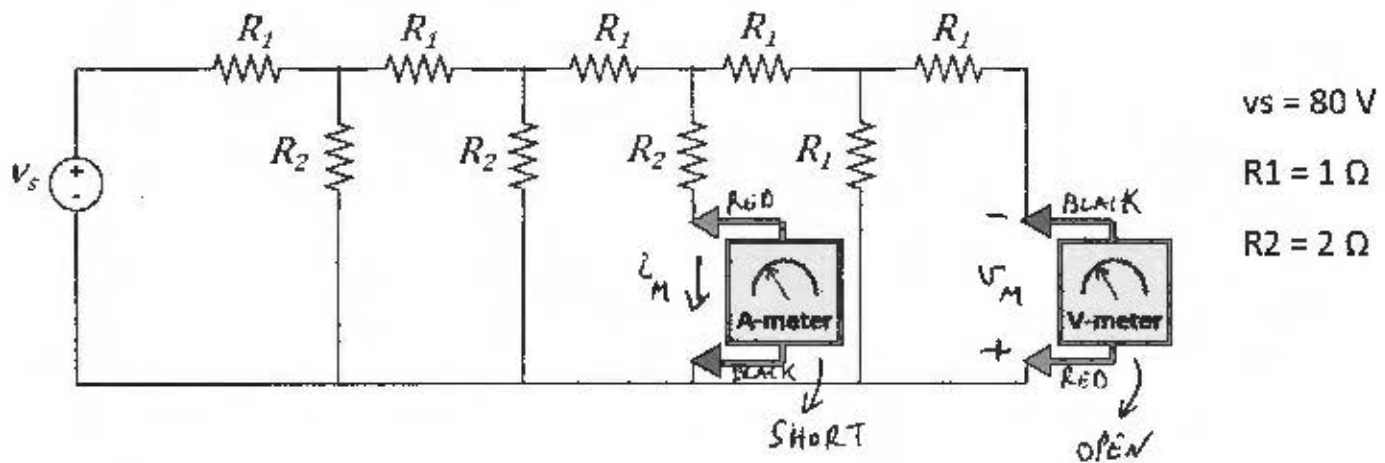Find the ammeter reading X and the volt-meter reading Y .



$$I_1 = \frac{v_s}{1+1} = 40$$

$$I_2 = I_1 \cdot \frac{2}{2+2} = 20 \quad (\text{CURRENT DIVIDER})$$

$$I_3 = I_2 \cdot \frac{2}{2+2} = 10 \quad (\text{CURRENT DIVIDER})$$

$$I_M = I_3 \cdot \frac{2}{2+2} = 5 \quad (\text{CURRENT DIVIDER})$$

$$X = 5 \text{ A}$$

$$V_1 = 2 \cdot I_M = 10$$


$$I_1 = I_M = 5 \Rightarrow -V_M = 1 \cdot I_1 = 5$$

$$Y = -5 \text{ V}$$

Basic analysis 012

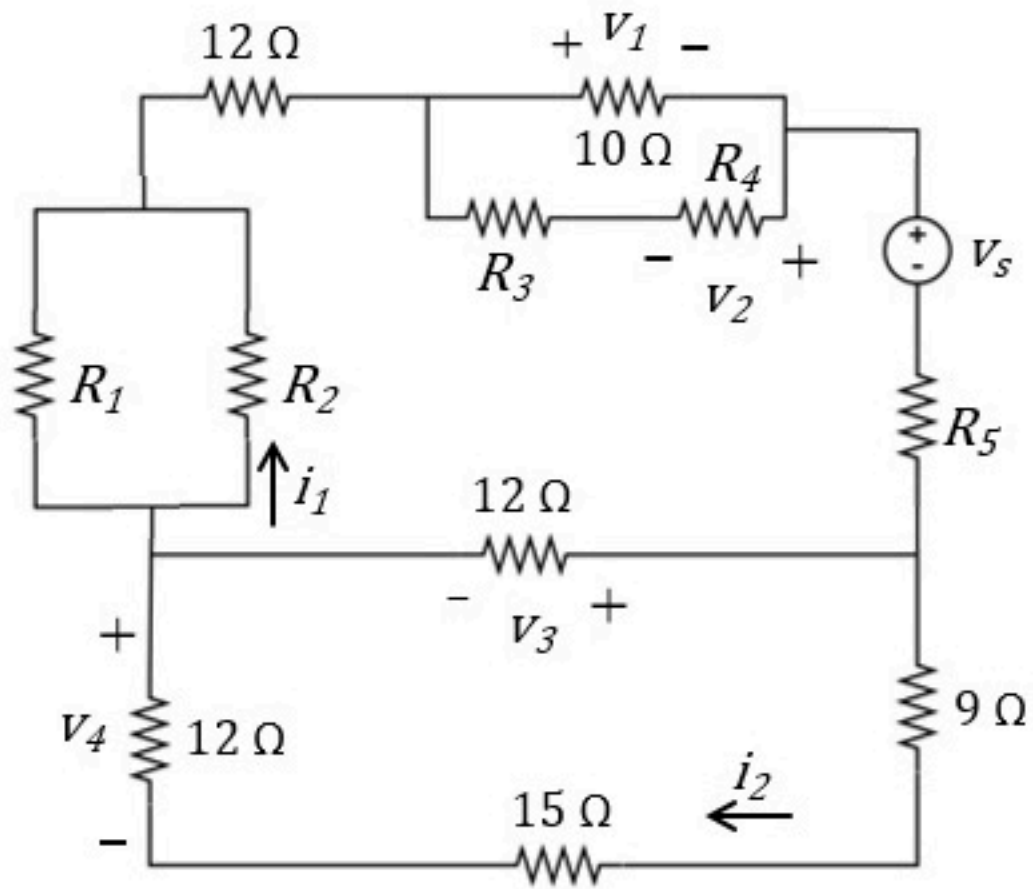Problem has been graded.

Determine the voltages v_1 , v_2 , v_3 and v_4 and the currents i_1 and i_2 .



Given Variables:

v_s : 80 V
 R_1 : 24 ohm
 R_2 : 8 ohm
 R_3 : 6 ohm
 R_4 : 9 ohm
 R_5 : 7 ohm

Calculate the following:

v_1 (V) :

v_2 (V) :

v_3 (V) :

v_4 (V) :

i_1 (A) :

i_2 (A) :

Determine the voltages v_1, v_2, v_3 and v_4 and the currents i_1 and i_2 .

$$V_s = 80 \text{ V}$$


$$R_1 = 8 \Omega$$

$$R_2 = 24 \Omega$$

$$R_3 = 3 \Omega$$

$$R_4 = 12 \Omega$$


$$R_5 = 7 \Omega$$

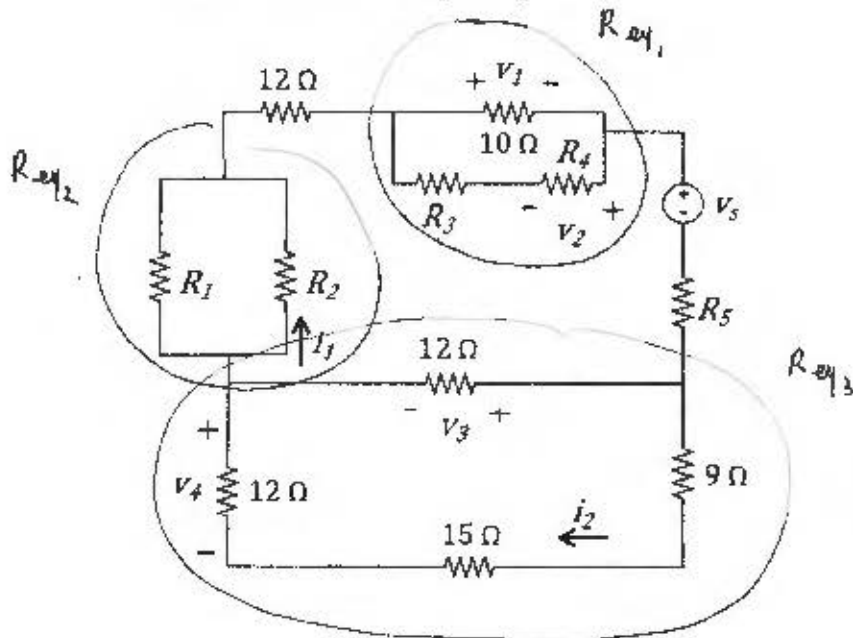

$$R_{eq1} = \left(\frac{1}{10} + \frac{1}{3+12} \right)^{-1} = 6 \Omega$$

$$R_{eq2} = \left(\frac{1}{8} + \frac{1}{24} \right)^{-1} = 6 \Omega$$
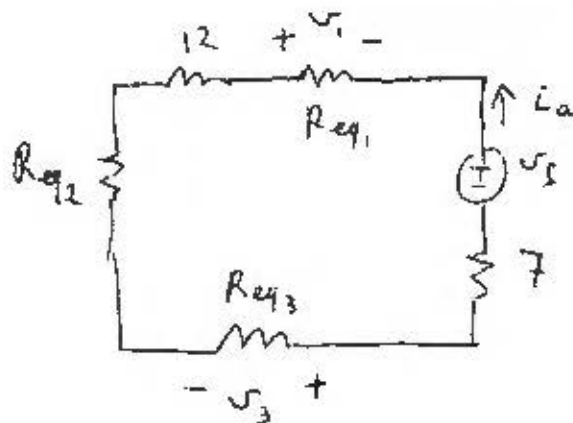
$$R_{eq3} = \left(\frac{1}{12} + \frac{1}{12+15+9} \right)^{-1} = 9 \Omega$$



$$i_a = \frac{V_s}{R_{eq1} + 12 + R_{eq2} + R_{eq3} + 7}$$

$$= \frac{V_s}{40} \Rightarrow i_a = 2 \text{ A}$$

$$v_1 = (-i_a) \cdot R_{eq1} = (-2) \cdot 6 = -12 \text{ V}$$

$$v_2 = (-v_1) \cdot \frac{R_4}{R_3 + R_4} = 12 \cdot \frac{12}{15} = \frac{48}{5} \text{ V}$$

$$v_3 = (-i_a) R_{eq3} = (-2) \cdot 9 = -18 \text{ V}$$

$$v_4 = (-v_3) \cdot \frac{12}{12+15+9} = 18 \cdot \frac{12}{36} = 6 \text{ V}$$

$$i_1 = (-i_a) \cdot \frac{R_1}{R_1 + R_2} = (-2) \cdot \frac{8}{32} = -0.5 \text{ A}$$

$$i_2 = (-i_a) \cdot \frac{12}{12+12+15+9} = (-2) \cdot \frac{12}{48} = -0.5 \text{ A}$$

$$v_1 = -12 \text{ V}$$

$$v_2 = 9.6 \text{ V}$$

$$v_3 = -18 \text{ V}$$

$$v_4 = 6 \text{ V}$$

$$i_1 = -0.5 \text{ A}$$


$$i_2 = -0.5 \text{ A}$$

Basic analysis 014

No more attempts left.

What is the reading X from the ammeter?

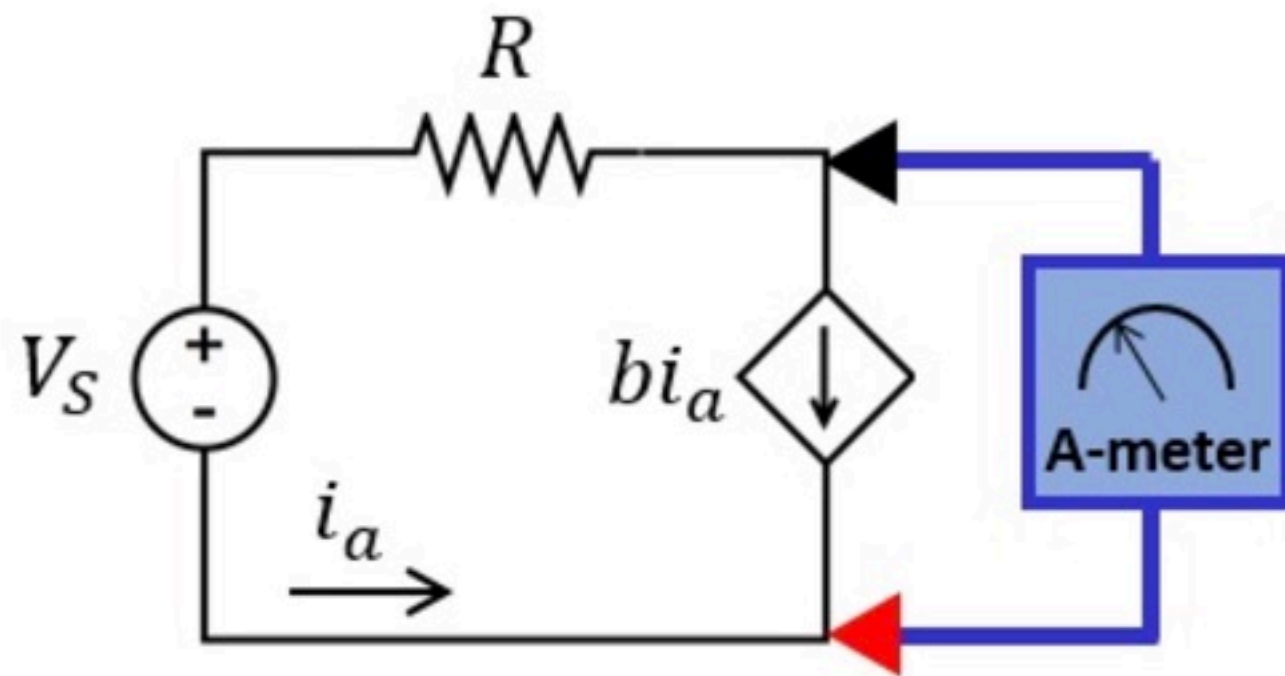What would be the reading Y if we replaced the ammeter by a volt-meter?



Given Variables:

V_S : 8 V

R : 4 ohm

b : 2 A/A

Calculate the following:

X (A) :

Y (V) :



Hint: Ammeters and volt meters behave as short and open circuits respectively. Trust the math.

- a) What is the reading X from the ammeter?
- b) What would be the reading Y if we replaced the ammeter by a volt-meter?

$$V_s = 6 \text{ V}$$

$$R = 2 \Omega$$

$$b = 2 \text{ A/A}$$

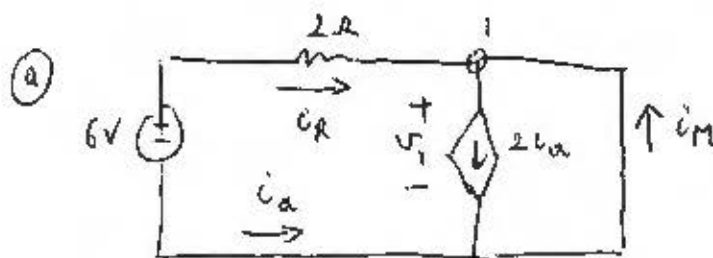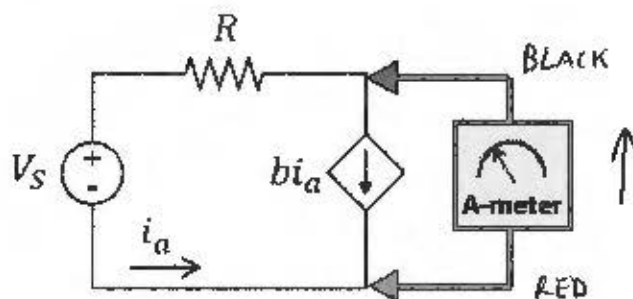

AMMETER EQUIVALENT
TO A SHORT

$$\Rightarrow v_1 = 0 \text{ V}$$


$$\Rightarrow i_R = \frac{6 - v_1}{R} = \frac{6}{2} = 3 \text{ A}$$

$$\Rightarrow i_a = -i_R = -3 \text{ A}$$

$$\text{KCL @ 1: } i_R + i_M = 2 i_a$$

$$i_M = 2 i_a - i_R = 3 i_a = -9$$

$$\boxed{X = -9 \text{ A}}$$

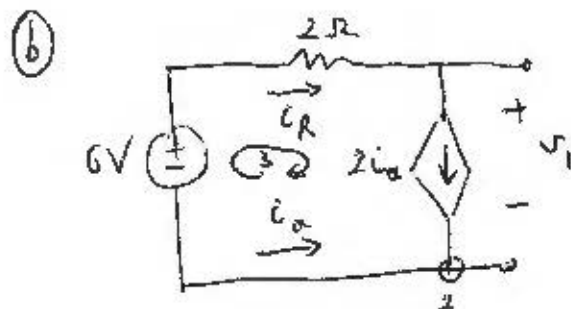

V-METER EQUIVALENT
TO AN OPEN

$$\text{KCL @ 2: } i_a + 2 i_a = 0 \Rightarrow 3 i_a = 0 \Rightarrow i_a = 0$$

$$\Rightarrow i_R = 0$$




$$\text{KVL 3: } 6 \text{ V} = i_R \cdot 2 + v_1 \Rightarrow v_1 = 6 \text{ V}$$

$$\boxed{Y = 6 \text{ V}}$$

Basic Analysis 015

Problem has been graded.

Find v_a , v_b and i_c .

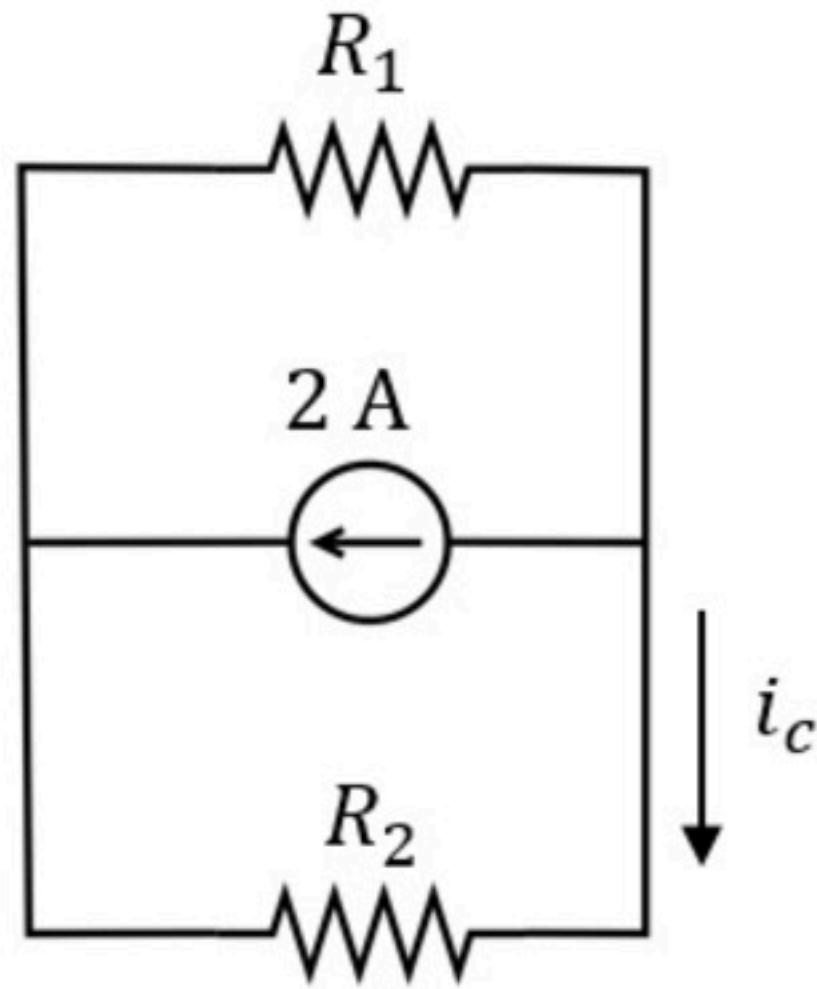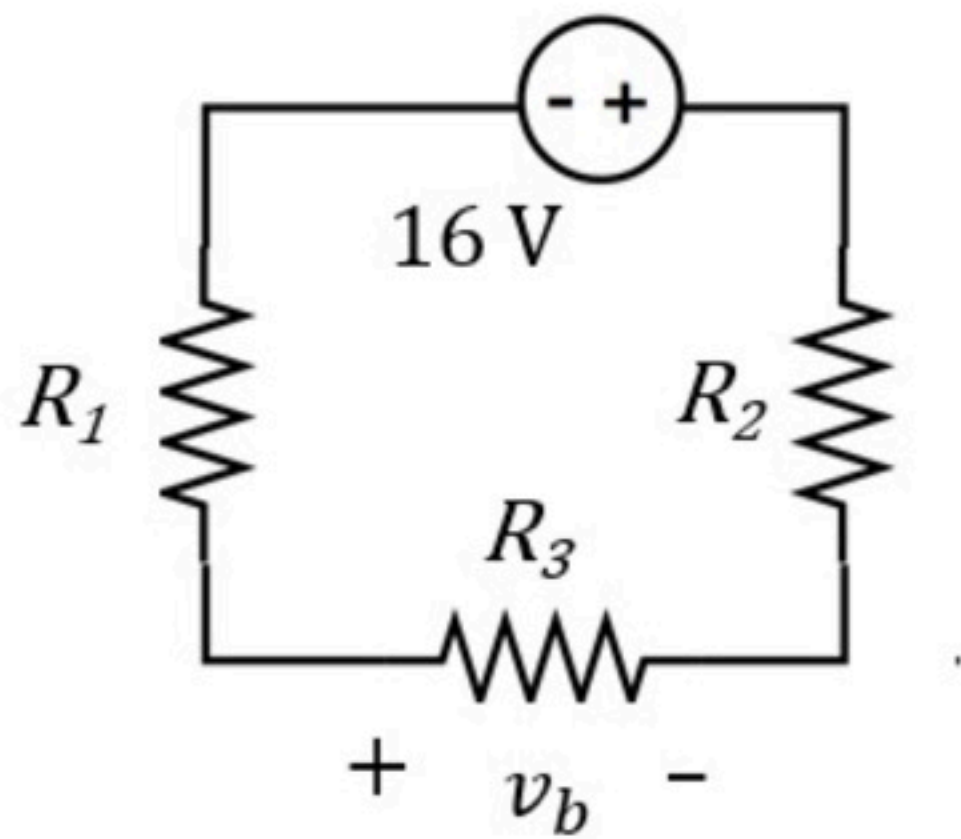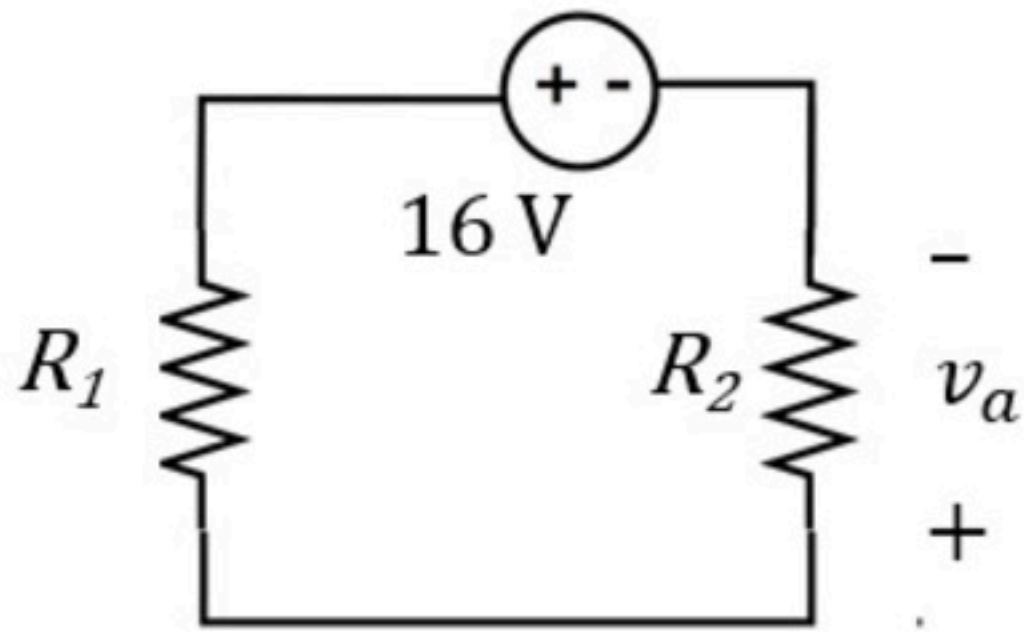

Given Variables:

R_1 : 2 ohm

R_2 : 6 ohm

R_3 : 2 ohm

Calculate the following:

v_a (V) :

v_b (V) :




i_c (A) :

Find v_a , v_b and i_c .

$$R_1 = 2 \Omega$$

$$R_2 = 6 \Omega$$

$$R_3 = 2 \Omega$$

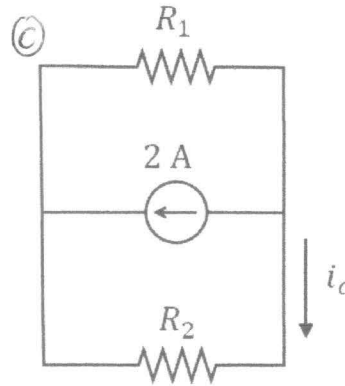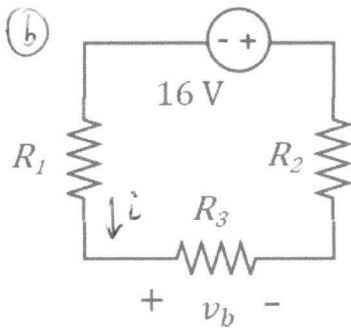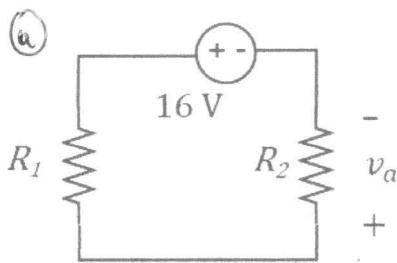

(a) VOLTAGE DIVIDER: $V_a = 16 \cdot \frac{R_2}{R_1 + R_2} = 16 \cdot \frac{6}{2 + 6} = 12$

$$\boxed{V_a = 12V}$$

(b) VOLTAGE DIVIDER: $V_b = (-16) \cdot \frac{R_3}{R_1 + R_2 + R_3} = (-16) \cdot \frac{2}{2 + 6 + 2} = -3.2$

$$\boxed{V_b = -3.2V}$$

BTW: WHERE THIS COMES FROM

$$I = \frac{(-16)}{R_1 + R_2 + R_3} \quad \text{AND} \quad V_b = R_3 \cdot I$$

$$\Rightarrow V_b = (-16) \cdot \frac{R_3}{R_1 + R_2 + R_3}$$

(c) CURRENT DIVIDER: $i_c = (-2) \cdot \frac{R_1}{R_1 + R_2} = (-2) \cdot \frac{2}{2 + 6} = -0.5$

$$\boxed{i_c = -0.5A}$$