

ECE 35, Fall 2021  
Final – Section A

Your sequence number

--

Grade

--

 / 45

Last name


First + middle  
name(s)**PID**


**Instructions:**

- Do not look at the questions or start writing until it is announced you can do so.
- Make sure you write your PID on EACH page.
- Read each problem completely and thoroughly before beginning.
- Answers without supporting calculations will receive zero credit. If you are using intuition, write a short explanation.
- All calculations must be done on these pages. It should be clear which question they belong to. Use the front for your actual work and the back as scratch paper.
- Write clearly and make sure your answer is structured properly. We will not hunt for your work or answers.
- Write your final answers in the answer boxes. Make sure you list units.
- You must follow the Final Exam Procedures that were posted on Canvas. If you are unsure of anything, ask. As a reminder:
  - Your phone should be turned off and put inside your bag
  - Calculators are not allowed.
  - This is a closed book exam.
  - Follow the Academic Integrity standards.



- (1) (4 points) Consider the circuit below.  
What is the reading  $X$  of the voltmeter?

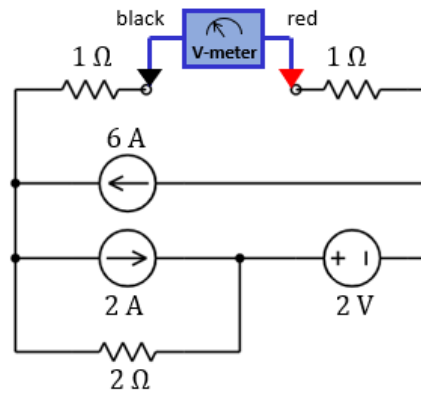 $X$ 

(2) (7 points) Consider the circuit below.


(a) Find the current  $i_b$ .

 $i_b$ 

(b) Find the power  $P_1$  received by the independent source.


 $P_1$ 

(c) Find the power  $P_2$  supplied by the dependent source.

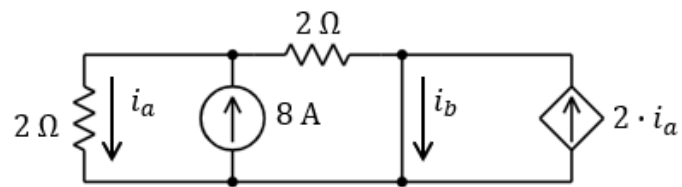
 $P_2$ 

(3) (7 points)

- (a) Consider the circuit below. What is the Thevenin equivalent resistance between A and B?

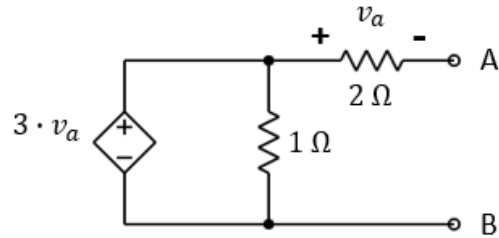 $R_{TH}$ 

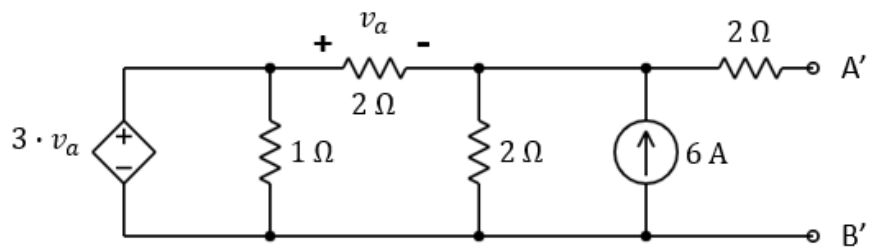- (b) Consider the circuit below (which contains the circuit above). Draw the Norton equivalent model between A' and B' (make sure you label A' and B').



- (4) (10 points) Consider the circuit below. For  $t < 2$  s, the switch is in position 1 and you may assume the system has reached steady state. The switch moves from position 1 to position 2 at  $t = 2$  s and remains in position 2.


*Note: make sure you don't mix up  $i_a$  and  $i_b$  in the questions below.*


(a) Find the current  $i_a(2^- \text{ s})$ . (i.e., just before the switch moves).  $i_a(2^- \text{ s})$


(b) Find the current  $i_b(2^+ \text{ s})$ . (i.e., just after the switch moves).  $i_b(2^+ \text{ s})$

(c) Find the current  $i_a(7 \text{ s})$ .  $i_a(7 \text{ s})$

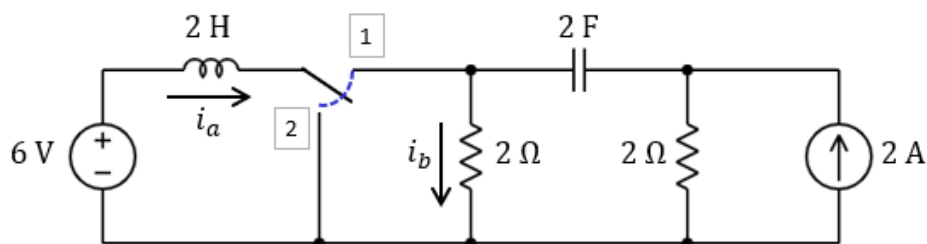(d) Find the current  $i_b(\infty)$ .  $i_b(\infty)$



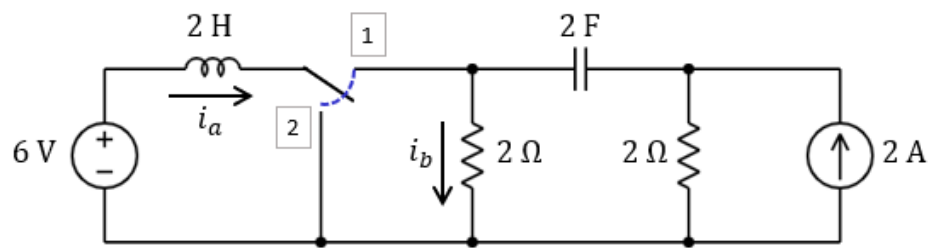

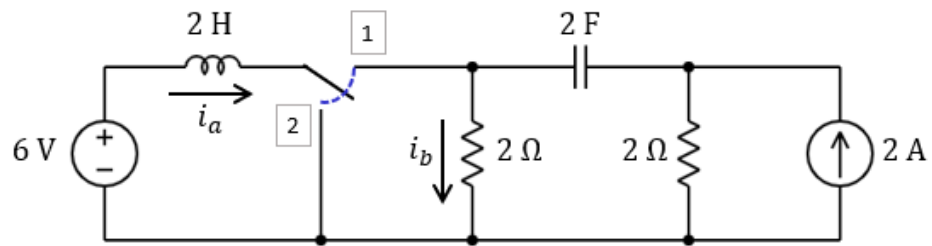



- (5) (9 points) Consider the circuit below. For  $t < \frac{\pi}{4}$  ms, the switch is closed and you may assume the system has reached steady state. The source  $i_s$  is an AC source with  $\omega = 4000$  rad/s. Its phasor diagram is shown on the left. The switch opens at  $t = \frac{\pi}{4}$  ms and remains open.

(a) Find the node voltage  $v_a\left(\frac{\pi^-}{4} \text{ ms}\right)$ . (i.e., just before the switch opens).



$v_a\left(\frac{\pi^-}{4} \text{ ms}\right)$

(b) Find the node voltage  $v_a(\pi \text{ ms})$ .

$v_a(\pi \text{ ms})$

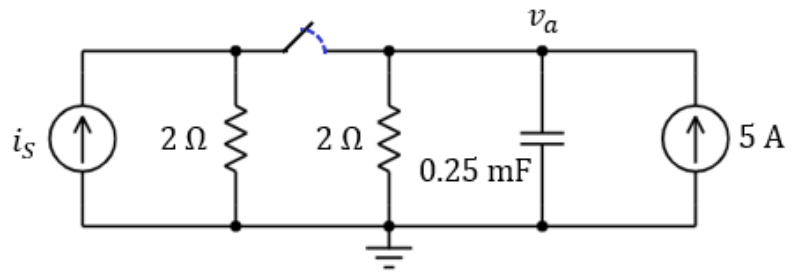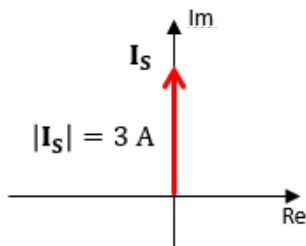



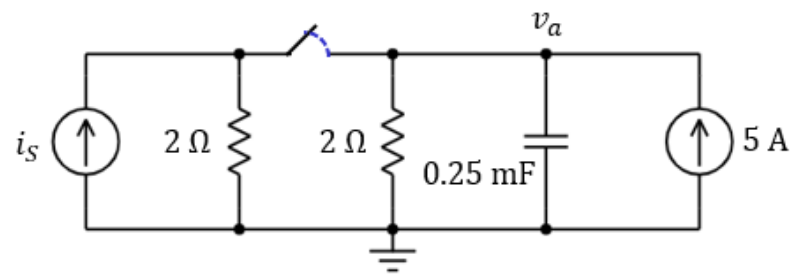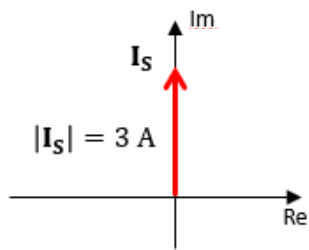

(6) (8 points) The circuit below is in steady state.


- (a) Sketch the phasor of  $v_a$  (make sure the magnitude and phase are labeled).




- (b) Find average power  $P_R$  received by the resistor.

 $P_R$ 

- (c) If the reactive power received by all capacitors and inductors combined is **21.6 VAR**, what is the complex power  $S$  supplied by the independent source?

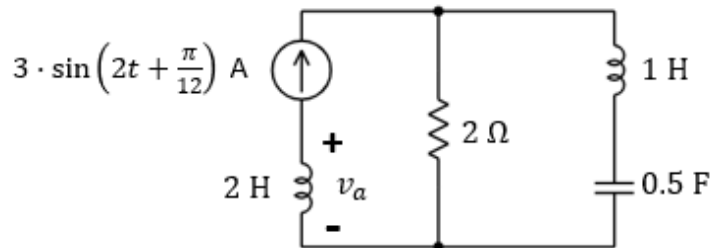 $S$ 

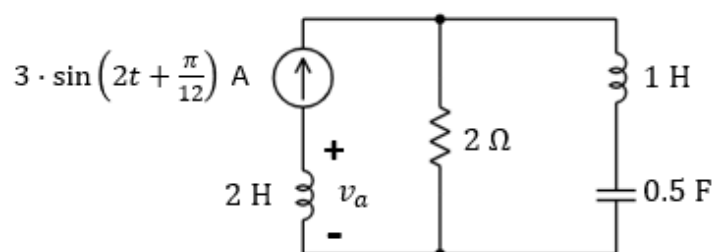

## ECE35 Equation Sheet

**Basics:**  $i \triangleq \frac{dq}{dt}$   $v_{ab} \triangleq \frac{dw}{dq}$   $R = \rho \frac{l}{A}$

**Capacitors:**  $C = \epsilon \cdot \frac{A}{d}$   $Q = C \cdot v$   $w_C = \frac{1}{2} C v^2$

**Inductors:**  $L = \mu \cdot \frac{N^2 A}{l}$   $B \sim i$   $w_L = \frac{1}{2} L i^2$

**AC power:**  $p(t) = \frac{1}{2} V_m I_m \cdot \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \cdot \cos(2\omega t + \theta_v + \theta_i)$

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) \quad Q = \frac{1}{2} V_m I_m \sin(\theta_v - \theta_i) \quad X_{rms} = \sqrt{\frac{1}{T} \int_0^T x(t)^2 dt}$$

**Trigonometry:**

$$\begin{aligned} \sin(-\alpha) &= -\sin(\alpha) & \cos(-\alpha) &= \cos(\alpha) \\ \sin(\pi - \alpha) &= \sin(\alpha) & \cos(\pi - \alpha) &= -\cos(\alpha) \\ \sin\left(\frac{\pi}{2} - \alpha\right) &= \cos(\alpha) & \cos\left(\frac{\pi}{2} - \alpha\right) &= \sin(\alpha) \\ \sin\left(\alpha - \frac{\pi}{2}\right) &= -\cos(\alpha) & \cos\left(\alpha - \frac{\pi}{2}\right) &= \sin(\alpha) \\ \sin(2\alpha) &= 2 \sin(\alpha) \cos(\alpha) & \cos(2\alpha) &= \cos^2(\alpha) - \sin^2(\alpha) \end{aligned}$$

$\sin(\alpha \pm \beta) = \sin(\alpha) \cos(\beta) \pm \cos(\alpha) \sin(\beta)$	$\alpha:$	0	$\frac{\pi}{6}$	$\frac{\pi}{4}$	$\frac{\pi}{3}$	$\frac{\pi}{2}$
$\cos(\alpha \pm \beta) = \cos(\alpha) \cos(\beta) \mp \sin(\alpha) \sin(\beta)$						
$\sin(\alpha) \sin(\beta) = 0.5 \cdot (\cos(\alpha - \beta) - \cos(\alpha + \beta))$	$\sin(\alpha):$	0	$\frac{1}{2}$	$\frac{\sqrt{2}}{2}$	$\frac{\sqrt{3}}{2}$	1
$\cos(\alpha) \cos(\beta) = 0.5 \cdot (\cos(\alpha - \beta) + \cos(\alpha + \beta))$	$\tan(\alpha):$	0	$\frac{\sqrt{3}}{3}$	1	$\sqrt{3}$	$\infty$
$\sin(\alpha) \cos(\beta) = 0.5 \cdot (\sin(\alpha - \beta) + \sin(\alpha + \beta))$						