

Lectures 4: Introduction to SystemVerilog

UCSD ECE 111

Prof. Farinaz Koushanfar

Fall 2024

Important announcements (Details in Canvas)

- **TA office hours:** are now MWF 9-11am for Fall'24
 - Zoom Meeting ID: 948 6397 0932; Passcode 004453
 - <https://ucsd.zoom.us/j/94863970932?pwd=iXcQXbLYjOaAQTdOJlrmglCYMSyeir.1>
- **TA Discussion session:** Wed 4-4:50PM (in person) Location: CNTRE 214
- **Oct 1:** Homework 1 was posted on Canvas
 - Due on Friday, **10/11/24**
- **Oct 8:** Homework 2 was posted on Canvas
 - Due on Wednesday, **10/16/24**
 - Cloudlabs is now up and running so you should all have cloud access to SW
 - **Late homework policy:** Max of 2 late days, with 20% grade reduction per day

Homework 2 overview

- You will learn how to:
 - Create parameterized modules, how to instantiate a module in another module, how to connect primary ports of 2 modules using explicit name based binding approach
 - Design functional behavior of SystemVerilog arithmetic and logical operators and understand hardware generated for each of the operator post synthesis.
- You will observe change in value of signals in sensitivity list of always block and how it impacts the behavior of the circuit
- There will be two parts for this homework:
 - **Homework-2a**: designing a synthesizable SystemVerilog Model of 4-bit ALU (Arithmetic Logic Unit)
 - **Homework-2b**: developing a synthesizable SystemVerilog code for 4-bit up down binary counter

SystemVerilog

Hello World!

Simple logic gate in SystemVerilog

- Module

```
module not_gate(in, out); // module name+ports
    // comments: declaring port type
    input in;
    output out;

    // Defining circuit functionality
    assign out = ~in;


endmodule
```

Synthesis

SystemVerilog:

```
module example(input  logic a, b, c,  
               output logic y);  
    assign y = ~a & ~b & ~c | a & ~b & ~c | a & ~b &  c;  
endmodule
```

Module Abstraction:

 


Synthesis

SystemVerilog:


```
module example(input  logic a, b, c,  
               output logic y);  
    assign y = ~a & ~b & ~c | a & ~b & ~c | a & ~b &  c;  
endmodule
```

 Synthesis: translates into a netlist (i.e., a list of gates and flip-flops, and their wiring connections)



* Schematic after some
logic optimization

Basics of digital design with HDL

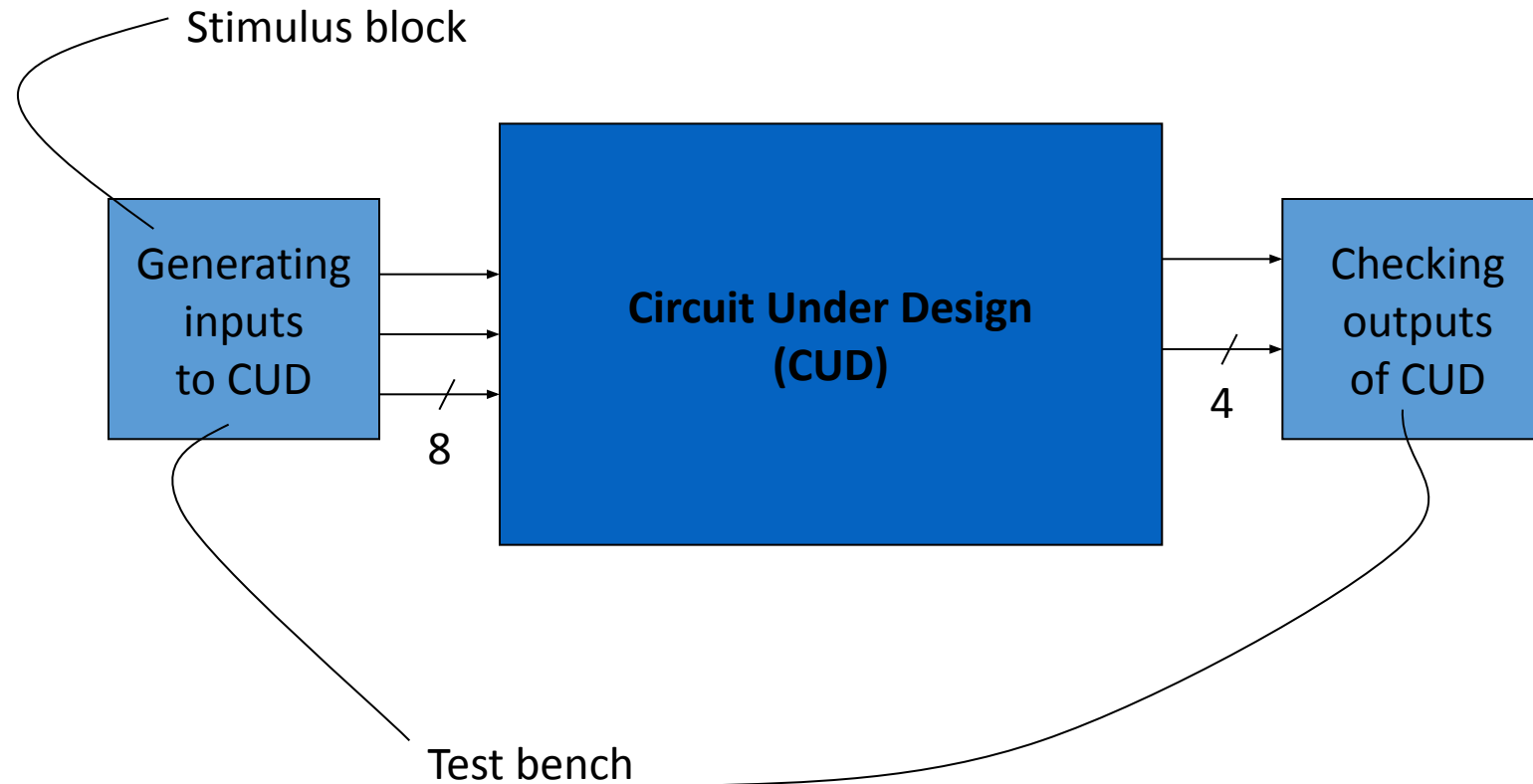

Useless SystemVerilog Example

```
module useless;
```

```
    initial
```

```
        $display("Hello World!");
```

```
endmodule
```

- Note the message-display statement
 - Compare to printf() in C

SystemVerilog Syntax

- Case sensitive
 - **Example:** `reset` and `Reset` are not the same signal.
- No names that start with numbers
 - **Example:** `2mux` is an invalid name
- Whitespace ignored
- Comments:
 - `//` single line comment
 - `/*` multiline
comment `*/`


SystemVerilog Modeling Abstractions

Combinational vs Sequential Circuit



Combinational Circuit

 - The output only depends on the inputs by itself at present time
- Does not store any intermediate values, therefore, no **memory elements** required
- No clock signal needed
- Behavior is described by set of output functions $\rightarrow y = f(x)$
- Some examples: Full Adder, half adder, comparator, multiplexer, decoder, encoder, etc




Sequential Circuit


- Present values of outputs are determined by two values, the present inputs and past state (i.e. sequence of past inputs or known as past outputs)
- Past outputs are stored in memory elements and it requires clock signal
- Behavior is described by set of output functions and set of next states functions stored in **memory**
- Examples: Flipflop, Latch, Shift Register, etc

Modeling Styles in SystemVerilog

 
- **SystemVerilog modeling language supports three kinds of modeling styles:**
 - Behavioral level (Algorithmic or RTL level)
 - Dataflow level
 - Gate level (Structural level)
 - Switch level (Transistor level)
- RTL (Register Transfer Level) model utilizes combination of behavioral and dataflow styles



Design View Point Through Y-Diagram

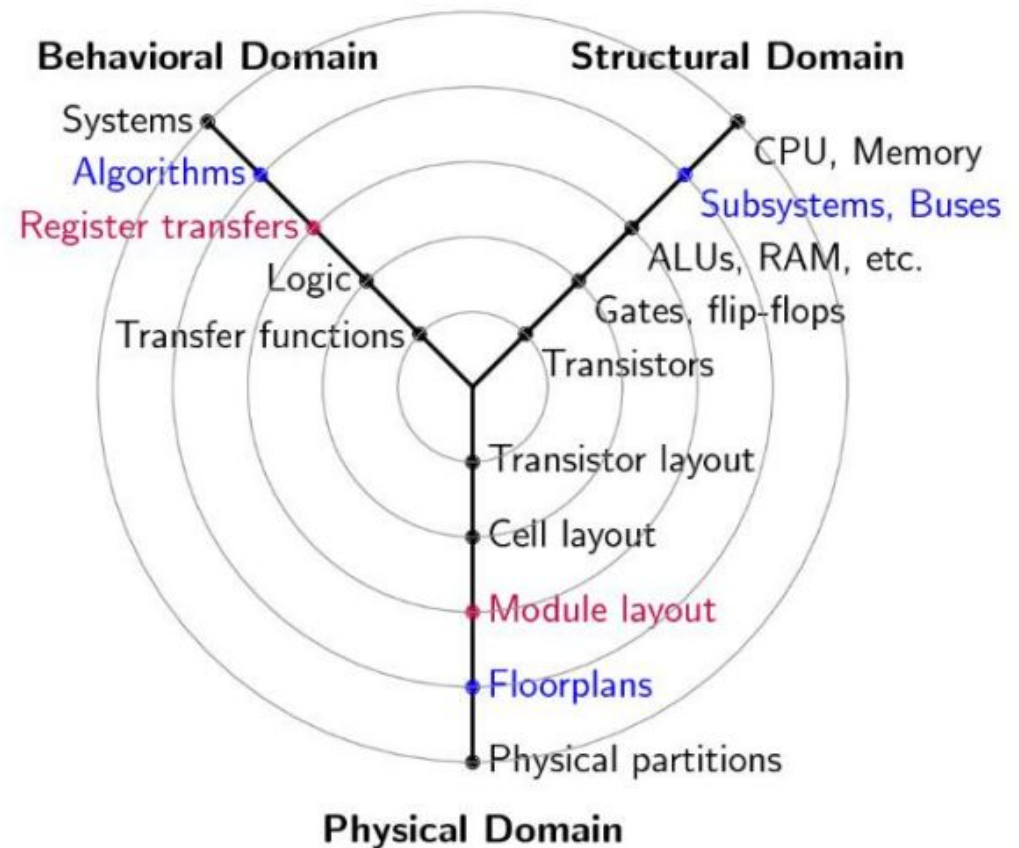

Behavioral Level Modeling

 


Hardware circuit is specified in terms of its expected behavior or an algorithm without concern of internal hardware implementation

- Full functionality of a complex circuit specified in **C** type natural language description
- It is **not** a cycle accurate representation of hardware circuit
- It may contain algorithms, boolean equations, truth tables (Tables of input and output values), which is also called LUT(lookup tables)
- Models at this abstraction level are also called as bus-functional or algorithmic models
- This is the **highest** level of abstraction provided by SystemVerilog HDL
- It is primarily used to model sequential circuits, but can also be used to model pure combinatorial circuits
- **Advantage :**
 - Behavioral models are faster to simulate compared to gate level models since it has less timing details


Behavioral level Modeling

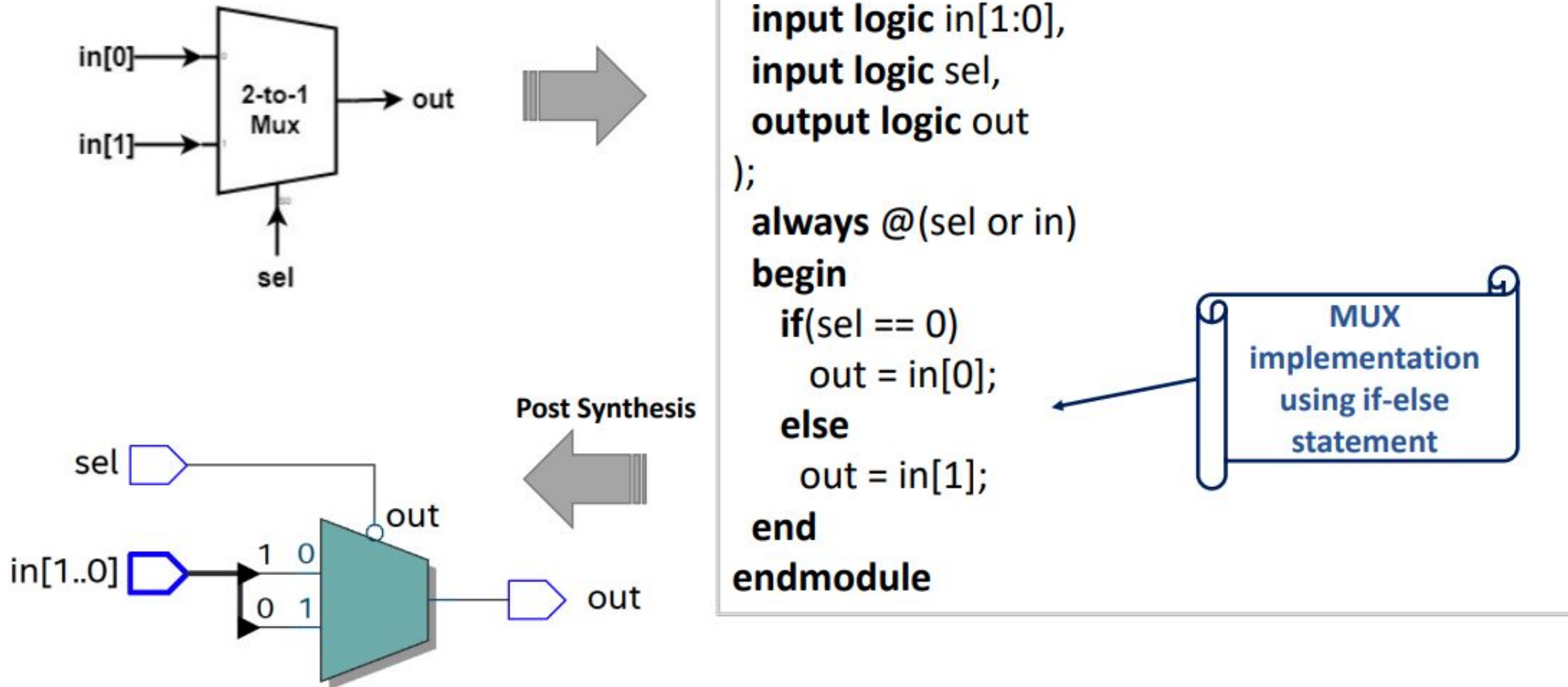Behavioral level description of a 2-to-1 Multiplexer using “if/else” statement



Behavioral level Modeling

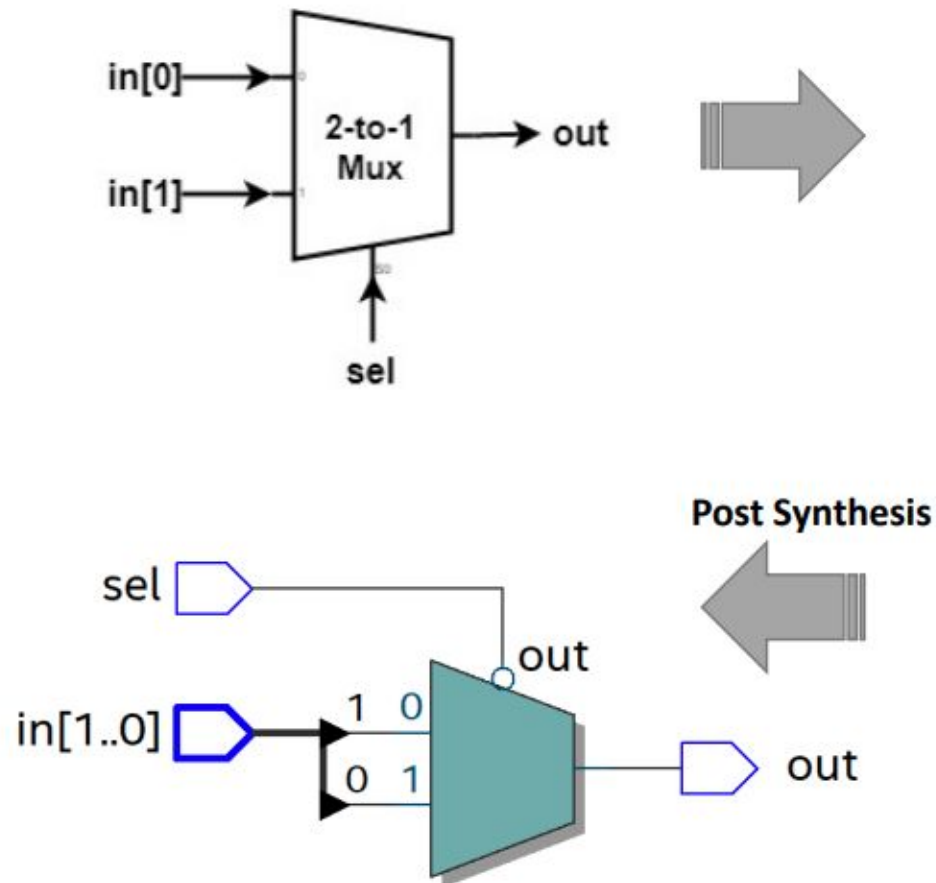Behavioral level description of a 2-to-1 Multiplexer using “case” statement




```
module mux_2x1_behavioral (  
    input logic in[1:0],  
    input logic sel,  
    output logic out  
);  
    always @(sel or in)  
    begin  
        case(sel)  
            1'b0 : out = in[0];  
            1'b1 : out = in[1];  
            default : out = 1'bx;  
        endcase  
    end  
endmodule
```

MUX
implementation
using case
statement

Behavioral Level Modeling

- How does behavioral modeling work?
 - “**initial**” and “**always**” are most common constructs.
 - All the other behavioral statements appear only inside initial and always blocks
 - What can be in a module?
 - a number of initial or always blocks,
 - one or more procedural statements.
 - Initial blocks execute only once and in the beginning ($t=0$)
 - Always blocks execute repeatedly ($t=0$ and $t>0$)
 - initial and always blocks execute concurrently (i.e. to model parallelism)
- Behavioral model even though mimics the intended hardware behavior but it may not be necessarily synthesizable ▪
 - It can utilize **full** set of constructs in SystemVerilog (both synthesizable and non synthesizable constructs)




Dataflow Modeling

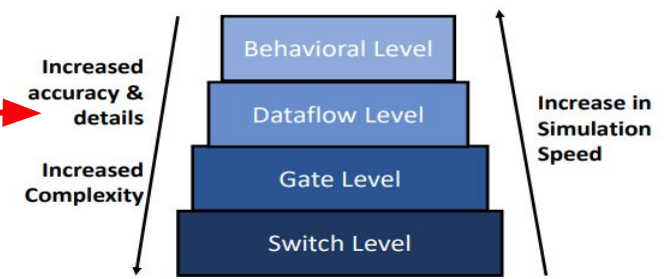

- In dataflow modeling, module is designed by describing how data flows through a circuit
 - This is a higher level of abstraction than the gate level, therefore, no hardware implementation details required
 - Using **logical equations** or **boolean expressions** for data processing.
 - Used for combinational circuits in most cases.
 - Can be translated into a gate level design through process of logic synthesis
- In dataflow modeling most of the design is implemented using continuous assignments, which are used to drive a value onto a net.
 - Continuous statements are always active statements.
 - Continuous assignments are made using the keyword assign. Syntax Format :
 - *assign [delay_specification] LHS = RHS*
 - Example : *assign #20 out = InA & InB;*
- Note : The RHS expression is evaluated whenever one of its operands changes. Then the result is assigned to the LHS, which is usually a wire/bus

Dataflow Modeling

 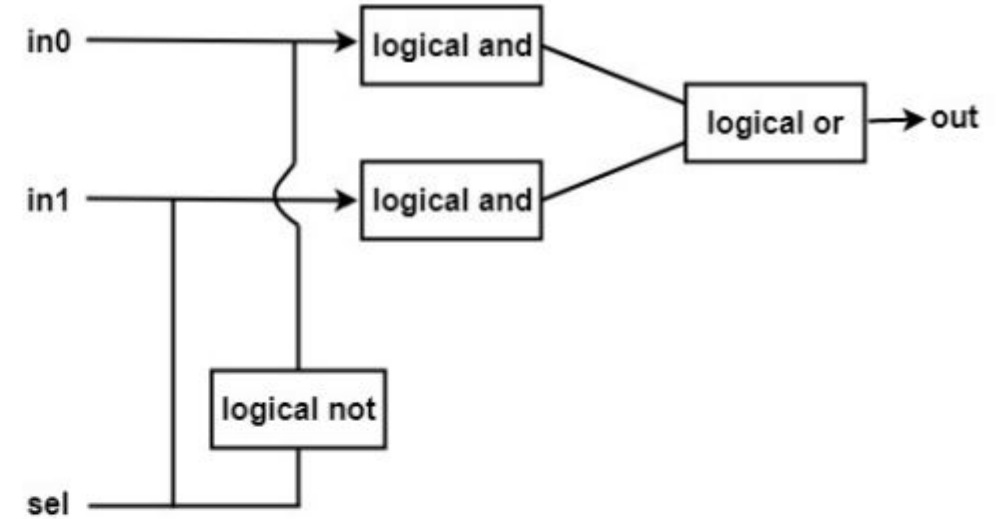 Dataflow description of a 2-to-1 Multiplexer




Post Synthesis

```
module mux_2x1_df (  
  input logic in0,in1,sel,  
  output logic out);  
  assign out = (!sel && in0) || (sel && in1);  
endmodule
```

Mux representation using logical expression.
No gates or hardware implementation details specified.

Gate Level Modeling

 


Gate level module is described with **logic gates** and **interconnections** between these gates.

- Resembles a schematic drawing with components connected with signals
- Low level of modeling abstraction
- Gate level module focus on hardware implementation details & accuracy:
 - **Actual logic gates**
 - **Timing** (gate propagation delays).

Gate level Modeling

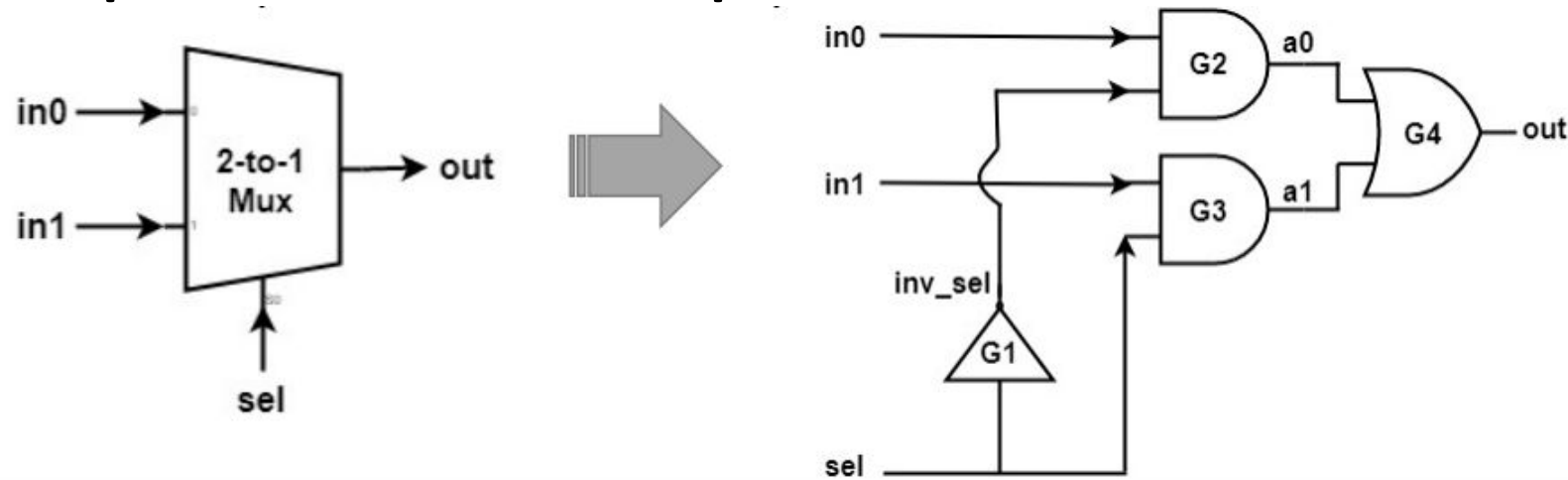Gate-level description of a 2-to-1 Multiplexer




```
module mux_2x1_gatelevel(  
    input logic in0, input logic in1, input logic sel, output logic out  
);  
    wire a0, a1, inv_sel;  
    not G1(inv_sel, sel);  
    and G2(a0, in0, inv_sel);  
    and G3(a1, in1, sel);  
    or #1.5 G4(out, a0, a1);  
endmodule
```

Mux representation using built-in gate level primitives

// or gate defined with 1.5 time units of propagation delay


Gate level Modeling

 Gate Level description of a 2-to-1 Multiplexer post synthesis schematic




Gate level Modeling

 - SystemVerilog supports modeling digital logic using built-in gate-level primitives
 - Gate level primitives can closely approximate silicon implementation
 - Gate-level models are provided by the silicon manufacturing vendor in case of ASIC or by



Gate level Modeling

- Gate level primitives can be modeled with or without propagation delays
 - If no delay is specified, output will be reflected immediately. Also called zero delay gate level model.
 - Gate-level modeling can represent the propagation delays of transistors that would be in an actual silicon with a high degree of **accuracy**.
- Types of delays which can be specified in each primitive
 - Rise delay: From (0 or X) to 1 (for a gate output)
 - Fall delay: From (0 or X) to 0 (for a gate output)
 - Turn-off delay: a gate output transition to the high impedance value (**Z**) from another value (0,1 or X).

 


Gate level Modeling

- **If one delay value is specified – its value is used for all gate's transitions**
// Delay is equal to trans_delay (or transport delay) for all transitions
nand #(3) g1 (out, in1, in2) ; → 3 time units delay
- **If two delay values are specified – they refer to gate's rise and fall delay values respectively**
// Rise and Fall delays are specified
and #(2, 3) g2 (out, in1, in2) ; → rise=2, fall=3 time units
- **If three delay values are specified – they refer to gate's rise, fall and turn-off delay values respectively**
// Rise, Fall and Turn-off delays (or trans_delay) are specified
bufif0 #(2, 3, 4) b1(out, in, control) ; → rise=2, fall=3, turn_off=4 time units
- **Default gate delay value is zero**
// Zero delay
buf b1(a, b) ; → rise=0, fall=0, turn_off=0 time units


Gate level Modeling

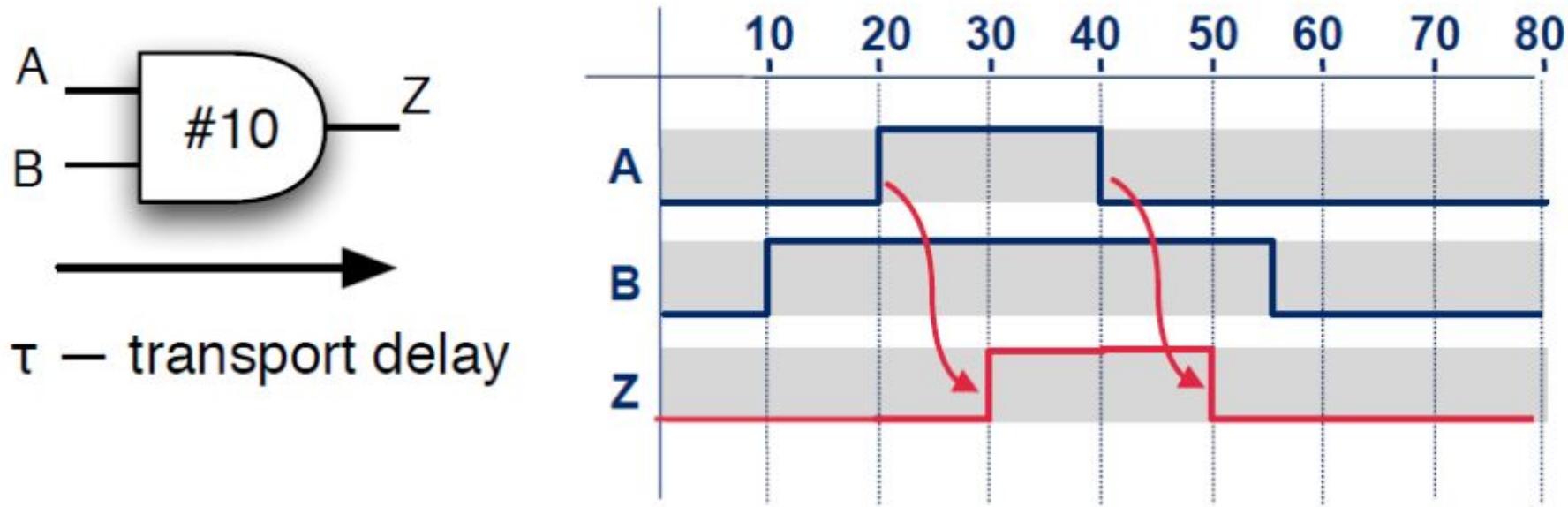- Example: AND gate
 - The output follows the inputs according to the AND function [after a certain delay](#).
 - Delay (#10 here) is the input to output (“transport”) delay



- The delay is defined in time units, could be any time length, e.g. 1ps, 100ns, 1ms, etc

Switch Level Modeling

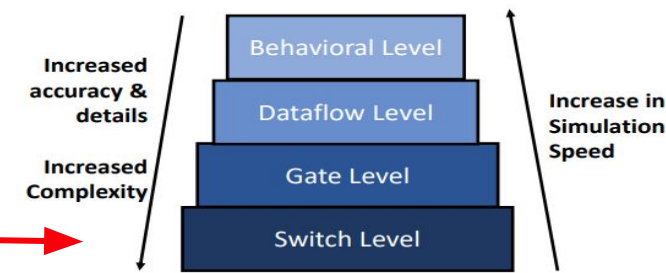

- **Switch level modeling consists transistors, switches, storage nodes, and the interconnections between them**
 - Lowest modeling level of abstraction provided by SystemVerilog
 - Describe the detail interconnection inside of gates
 - Can represent actual silicon implementation → the most accurate representation of design
 - At this level designer requires knowledge of transistor-level implementation details
- **For switch-level modeling, SystemVerilog language provides switch primitives, (such as pmos, cmos and nmos), resistive switch primitives (such as rpmos, rnmos, rcmos) and capacitive nets.**
 - Only **digital systems** can be modeled at switch level using Standard SystemVerilog
 - Digital simulators does not accurately reflect transistor behavior
 - Slowest to simulate compared to other model levels
 - Typically **not used** in ASIC and FPGA design flows with SystemVerilog
 - Used only in some cases such as leaf level modeling


Switch Level Modeling

- **SystemVerilog supports two types of switch primitives :**
 - **Ideal switch :**
 - When switch is closed(ON), there is zero resistance, hence no signal degradation
 - **Resistive switch :**
 - When switch is closed(ON), there is low resistance, hence signal degradation
 - When signal passes resistive switch signal strength decreases
 - Resistive switch primitives in SystemVerilog starts with “r” such as rnmos, rpmos
- **Some of the Switch primitives supported in SystemVerilog are mentioned in table below:**

Switch Type	SystemVerilog Switch Primitives
Ideal MOS switches	pmos, nmos, cmos
Resistive MOS switches	rpmos, rnmos, rcmos
Ideal Bidirectional switches	tran, tranifo0, tranif1
Resistive Bidirectional switches	rtran, rtanif0, rtranif1
Power and Ground nets	supply1 and supply0
Pullup and Pulldown	pullup and pulldown

Switch Level Modeling

- nmos, pmos and cmos switches

 


nmos		control			
		0	1	x	z
in	0	z	0	L	L
	1	z	1	H	H
	x	z	x	x	x
	z	z	z	z	z

(a) nMOS switch



pmos		control			
		0	1	x	z
in	0	0	z	L	L
	1	1	z	H	H
	x	x	z	x	x
	z	z	z	z	z

(b) pMOS switch

 

(a) Symbol

control		data			
n	p	0	1	x	z
0	0	0	1	x	z
	1	z	z	z	z
	x	L	H	x	z
	z	L	H	x	z
1	0	0	1	x	z
	1	0	1	x	z
	x	0	1	x	z
	z	0	1	x	z
x	0	0	1	x	z
	1	L	H	x	z
	x	L	H	x	z
	z	L	H	x	z
z	0	0	1	x	z
	1	L	H	x	z
	x	L	H	x	z
	z	L	H	x	z

Switch Instance Syntax :



nmos <instance name> (out, in, ncontrol);

pmos <instance name> (out, in, ncontrol);

cmos <instance name> (out, in, ncontrol);

Switch Level Modeling

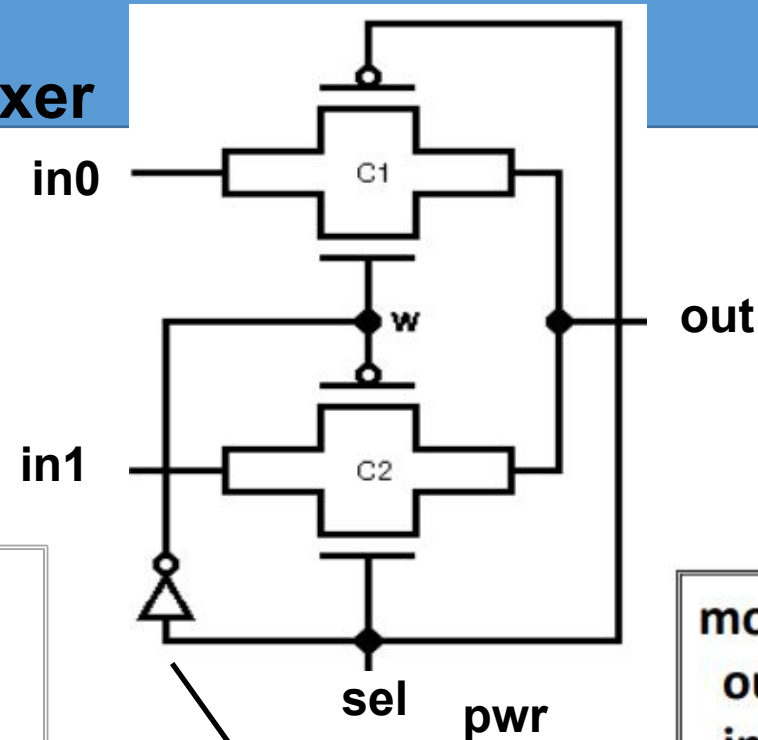 Switch level description of a 2-to-1 Multiplexer




```

module mux_2x1_switchlevel (
  input in0, input in1, input sel, output out
);
  wire w;
  inv G1(w, sel); // inverter switch model instantiated
  cmos C1(out, in0, w, sel);
  cmos C2(out, in1, sel, w);
endmodule
    
```

SV Built-in switch primitives instantiated

Inverter modeled using switch primitives

 

```

module inv(out, in);
  output out;
  input in;
  supply1 pwr;
  supply0 gnd;
  pmos (out, pwr, in);
  nmos (out, gnd, in);
endmodule
    
```

- When sel=0 then w = 1 and cmos C1 is ON and cmos C2 is OFF hence in0 will propagate to out
- When sel=1 then w = 0 and cmos C1 is OFF and cmos C2 is ON hence in1 will propagate to out

2to1 Mux Simulation Result


- Waveform (Same results for behavioral, dataflow and gatelevel model simulation)



- Simulation output log

```
Vsim > run 500ns
# time=0   , in=00 sel=0 out=0
# time=150, in=01 sel=0 out=1
# time=200, in=10 sel=0 out=0
# time=250, in=00 sel=1 out=0
# time=300, in=01 sel=1 out=0
# time=350, in=10 sel=1 out=1
```


RTL (Register Transfer Level) Modeling

 

- RTL modeling utilizes **combination of behavioral and dataflow modeling**
 - **Register:** Storage element like Flipflop, latches
 - **Transfer:** Transfer data between input, output and register using combinational logic.
 - **Level:** Level of Abstraction modeled using HDL
- RTL is a **Cycle accurate** model unlike behavioral model
- Does **not contain low level hardware** implementation details
- Complex and larger designs can be **quickly and concisely modeled** using RTL modeling technique compared to gate level modeling
- RTL models do simulate **faster** than gate-level and **switch-level** models, making it possible to verify larger and more complex designs
- Two primary constructs for RTL modeling :
 - continuous assignments (“*assign*”) and always procedural blocks (“*always*”)
 - RTL code is **easy to read** and interpret compared to gate-level code
- RTL model **supports vectors** (multi-bit signal) unlike gate-level and switch-level modeling which works on scalar signals in SystemVerilog

Behavioral vs RTL Level Modeling


- **Behavioral model describes what intended design does. An RTL model describes how it does it.**
 - For example, an RTL half adder must describe the registers for the operands, the carry method, and a clock. It may be done in various ways to balance speed and accuracy
 - For a behavioral adder, $A + B = C$ is sufficient. $A + B = C$ also simulates a lot faster than all those gates and registers in the RTL model
- **Behavioral model are similar to RTL model since both uses *always* procedural blocks, however they differ :**
 - RTL model executes its programming statements in **a single clock cycle**, or in zero cycles if combinational logic. While behavioral block can take **arbitrary number of clock cycles** to execute its statements.

Behavioral vs RTL Level Modeling

- **RTL (Register-Transfer-Level) model is synthesizable.**
 - Hardware functionality is described using ***always*** blocks and ***assign*** statements that are synthesizable (can be translated into gate level).
 - RTL model follows some constraints that are understandable by RTL synthesis compilers or tools.
 - It's also called synchronous finite state machine(FSM) description
- **Behavioral though mimics the desired functionality of the hardware but not necessarily synthesizable.**
 - Most of the behavioral modeling is done using two important constructs: ***initial*** and ***always***
 - There is no strict rules as long as the code generates the desired behavior
 - A behavioral model can utilize full SystemVerilog Language and may not be synthesizable.

Behavioral Model of a Decoder

 - Behavioral level description of a 2-to-4 decoder



```
module decoder_2x4_behav(  
  input logic[1:0] sel, output  
  logic[3:0] out); always @(sel or  
  out) begin  
    case (sel)  
      2'b00 : out = 4'b0001;  
      2'b01 : out = 4'b0010;  
      2'b10 : out = 4'b0100;  
      2'b11 : out = 4'b1000;  
      default : out = 4'b0000;  
    endcase end  
endmodule
```


Dataflow Model of a 2-to-4 decoder




Truth Table

sel[0]	sel[1]	out[3]	out[2]	out[1]	out[0]
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

 $out[0] = \overline{sel[0]} \cdot \overline{sel[1]}$
 $out[1] = \overline{sel[0]} \cdot sel[1]$
 $out[2] = sel[0] \cdot \overline{sel[1]}$
 $out[3] = sel[0] \cdot sel[1]$
Boolean Expression


 
```
module decoder_2x4_dataflow(  
    input logic[1:0] sel,  
    output logic[3:0] out);  
    assign out[0] = (!sel[0]) && (!sel[1]);  
    assign out[1] = (sel[0]) && (!sel[1]);  
    assign out[2] = (!sel[0]) && (sel[1]);  
    assign out[3] = (sel[0]) && (sel[1]);  
endmodule
```




Gate level Model of a 2-to-4 decoder

❑ Gate level description of a 2-to-4 decoder



Truth Table



sel[0]	sel[1]	out[3]	out[2]	out[1]	out[0]
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

 

```
module decoder_2x4_gate(  
  input logic[1:0] sel,  
  output logic[3:0] out);  
  wire w0, w1;  
  not i0(w0, sel[0]);  
  not i1(w1, sel[1]);  
  and g0(out[0], w1, w0);  
  and g1(out[1], w1, sel[0]);  
  and g2(out[2], sel[1], w0);  
  and g3(out[3], sel[1], sel[0]);  
endmodule
```




  $out[0] = \overline{sel[0]}. \overline{sel[1]}$
 $out[1] = \overline{sel[0]}. sel[1]$
 $out[2] = sel[0]. \overline{sel[1]}$
 $out[3] = sel[0]. sel[1]$
Boolean Expression



2-to-4 Decoder Simulation Result

 - Waveform (Same results for behavioral, dataflow and gatelevel model simulation)




- Simulation output log

```
Vsim > run 500ns
```

```
# time=0   , sel=00  out=0001
# time=150, sel=10  out=0100
# time=200, sel=01  out=0010
# time=250, sel=11  out=1000
```

Behavioral Model of Full Adder

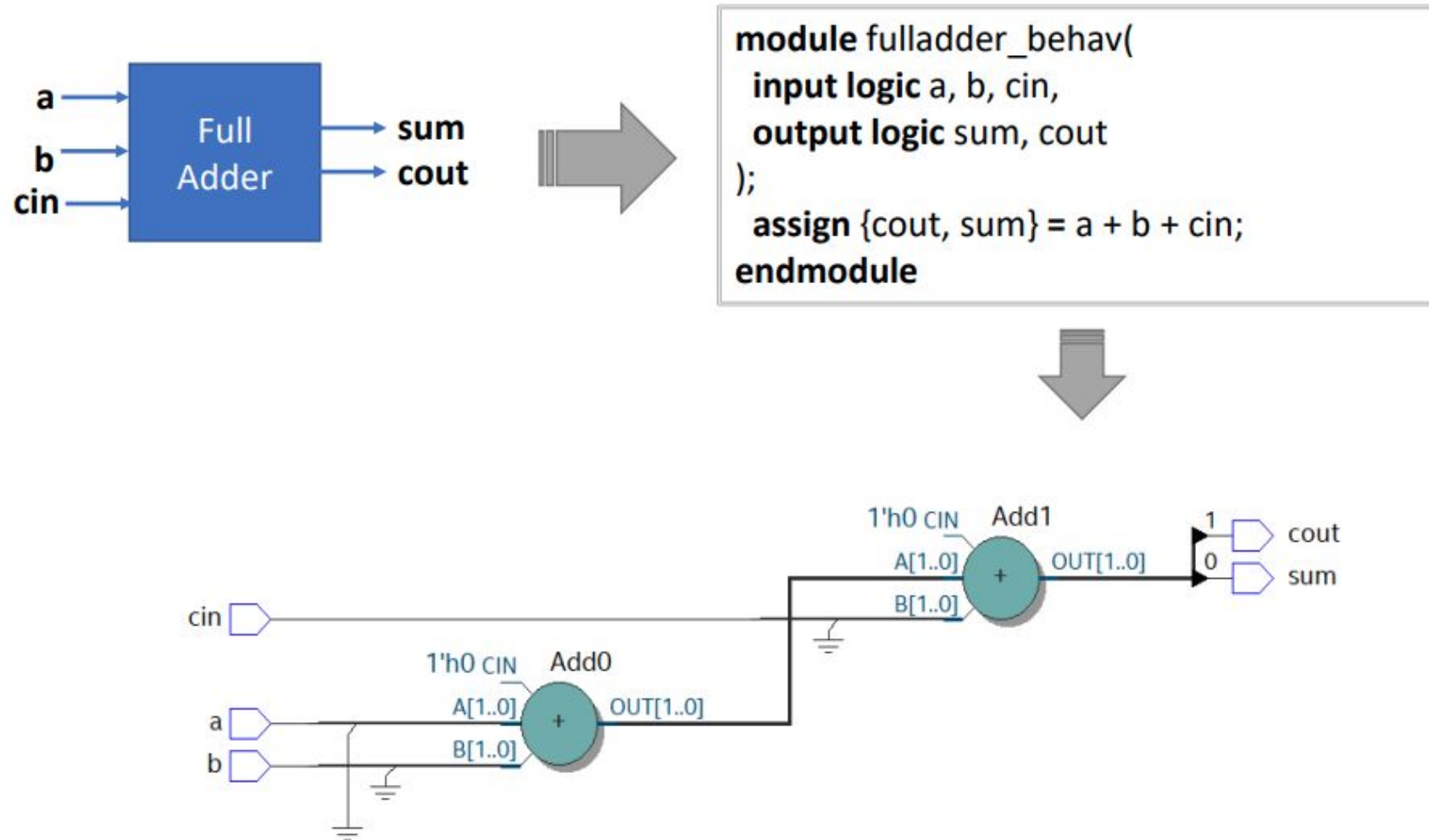- Behavioral level description of Full Adder



Dataflow level Model of Full Adder

□ Dataflow level description of Full Adder




Full Adder Truth Table

inputs			outputs	
a	b	cin	sum	cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Boolean Expression for Full Adder
based on Truth Table

$\text{sum} = ((a \text{ xor } b) \text{ xor } \text{cin});$
 $\text{cout} = (a \text{ and } b) \text{ or } ((a \text{ xor } b) \text{ and } \text{cin})$

```
module fulladder_dataflow(  
  input logic a, b, cin,  
  output logic sum, cout  
);  
  logic p, q;  
  assign p = a ^ b;  
  assign q = a & b;  
  assign sum = p ^ cin;  
  assign cout = q | (p & cin);  
endmodule
```

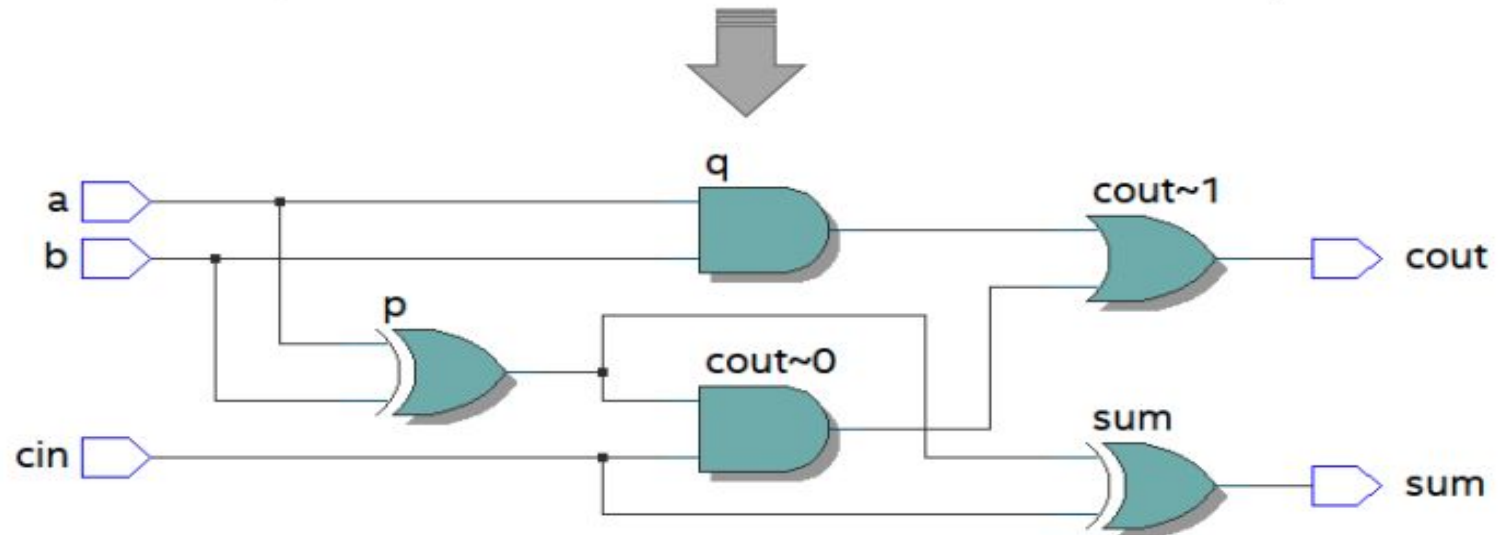

Gatelevel Model of Full Adder

Gate level description of Full Adder



Full Adder Truth Table


inputs			outputs	
a	b	cin	sum	cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Boolean Expression for Full Adder
based on Truth Table

$$\text{sum} = ((a \text{ xor } b) \text{ xor } \text{cin});$$


$$\text{cout} = (a \text{ and } b) \text{ or } ((a \text{ xor } b) \text{ and } \text{cin})$$
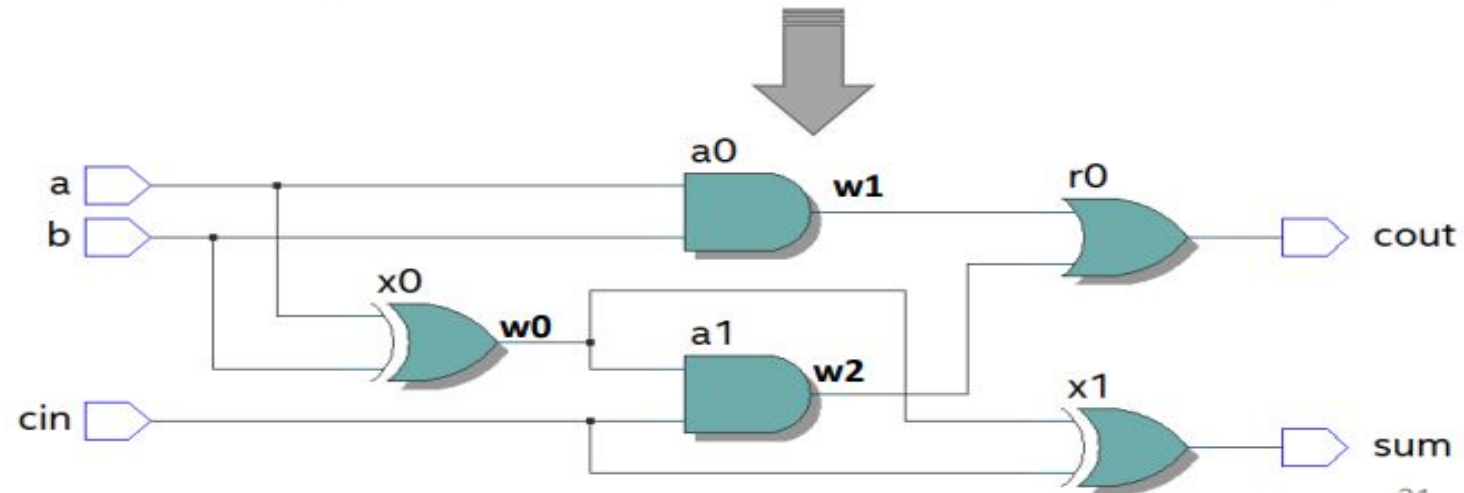
```
module fulladder_gatelevel(  
  input logic a, b, cin,  
  output logic sum, cout  
);  
  wire w0, w1, w2;  
  xor x0(w0, b, a);  
  and a0(w1, b, a);  
  and a1(w2, w0, cin);  
  or r0(cout, w2, w1);  
  xor x1(sum, w0, cin);  
endmodule
```



FullAdder Simulation Result

 - Waveform (Same results for behavioral, dataflow and gatelevel model simulation)



- Simulation output log

Vsim > run 500ns

```
# time=0    a=0  b=0  c=0  sum=0  cout=0
# time=150  a=1  b=0  c=0  sum=1  cout=0
# time=200  a=0  b=1  c=0  sum=1  cout=0
# time=250  a=1  b=1  c=0  sum=0  cout=1
# time=300  a=0  b=0  c=1  sum=1  cout=0
# time=350  a=1  b=0  c=1  sum=0  cout=1
# time=400  a=0  b=1  c=1  sum=0  cout=1
# time=450  a=1  b=1  c=1  sum=1  cout=1
```