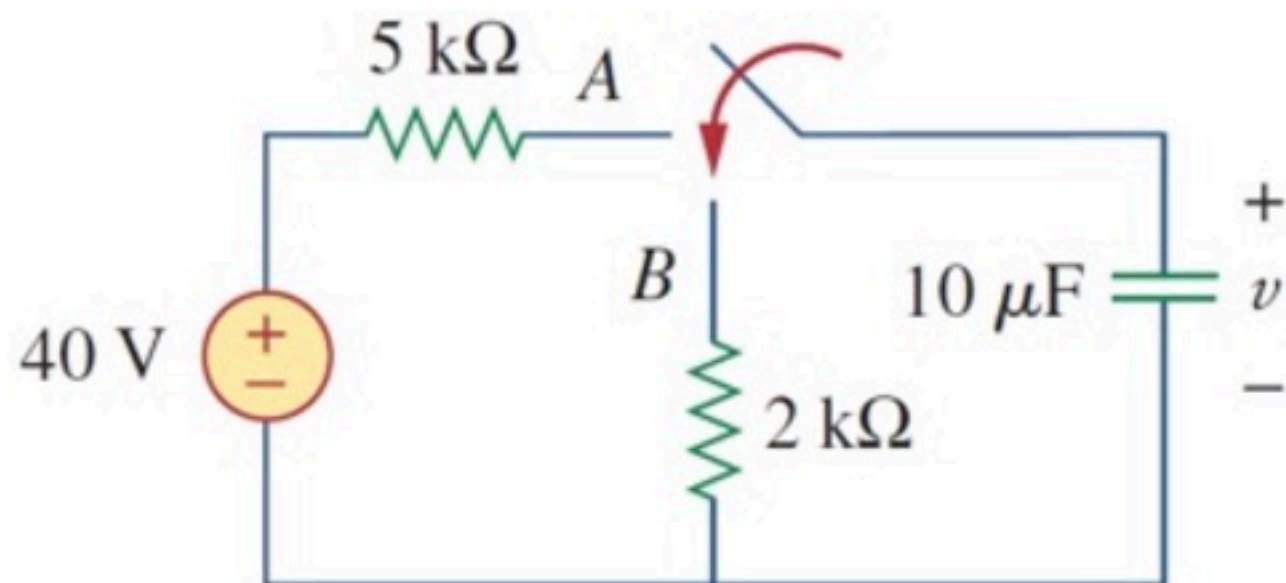


# PP First order circuits 001

Unlimited Attempts.

The switch has been in position A for a long time.  
At time  $t = 0$ , the switch moves to position B.

Find  $v(t) = D$  for  $t = 0^-$   
 $= A \cdot e^{-t/\tau} + B$  for  $t > 0$



Given Variables:

...

Calculate the following:

D (V) :

40

✓

A (V) :

40

✓

B (V) :

0

✓

$\tau$  (s) :

0.02

✓

Hint: At steady state, the capacitor is an open circuit


# PP First order circuits 002

Unlimited Attempts.

The switch has been closed for a long time.

At time  $t = 0$ , the switch is opened.

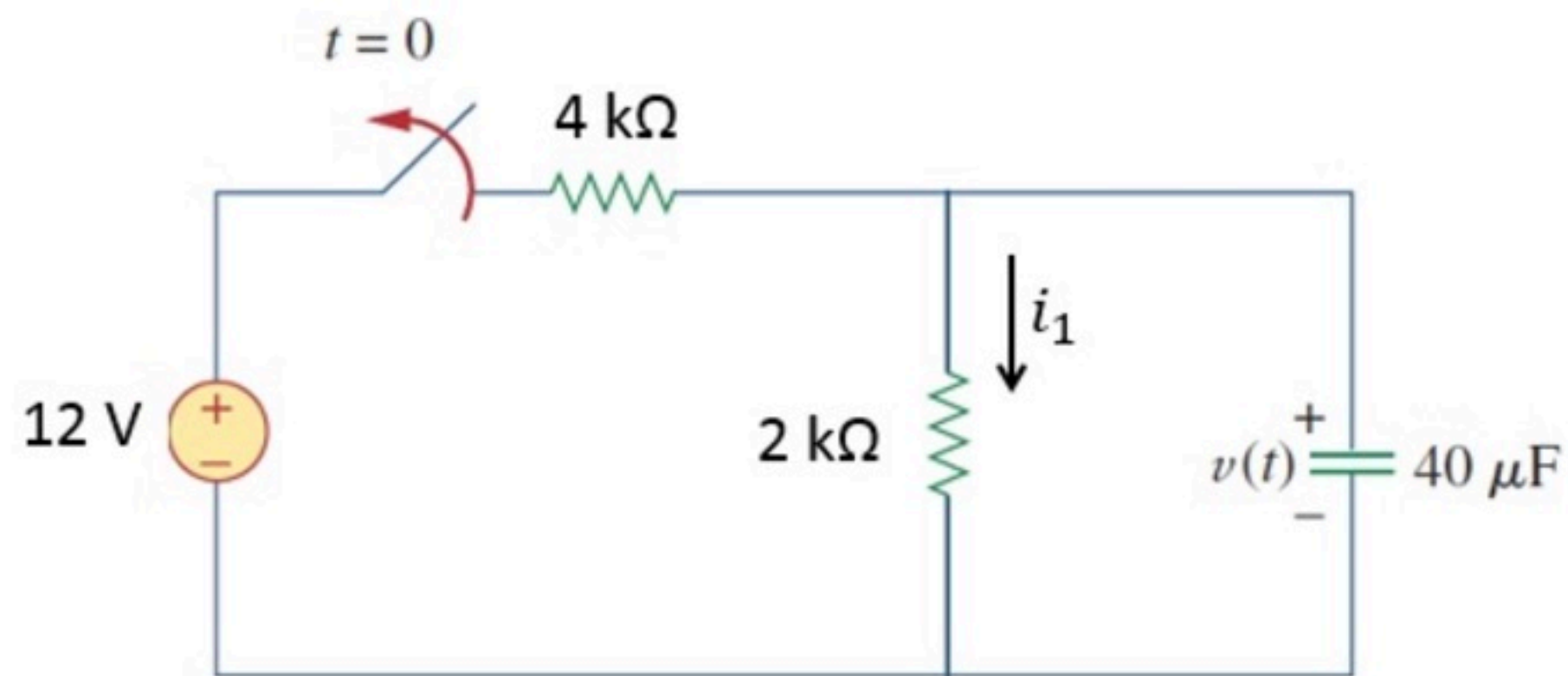Find  $i_1(t) = D$  for  $t = 0^-$   
 $= A \cdot e^{-t/\tau} + B$  for  $t > 0$



Given Variables:

...

Calculate the following:

D (mA) :

2



A (mA) :

2



B (mA) :

0



$\tau$  (ms) :

80




Hint: The capacitor voltage does not change instantaneously
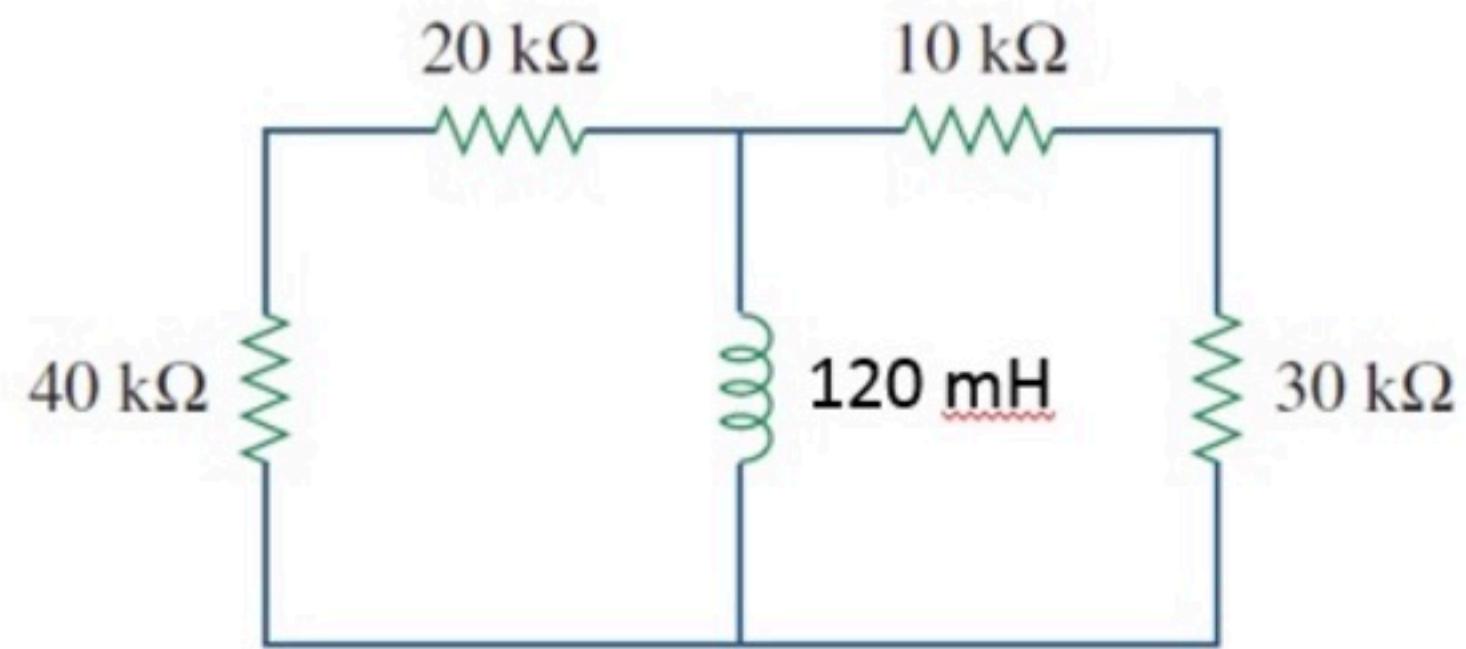
# PP First order circuits 003

Unlimited Attempts.

What is the time constant tau in this circuit?



Given Variables:

...

Calculate the following:

tau (us) :

5



Hint: Find Req


# PP First order circuits 004

Unlimited Attempts.

The switch has been in position A for a long time. At time  $t = 0$ , the switch moves to position B.

Find  $v_1(t) = D1$  for  $t = 0^-$   
 $= A1 \cdot e^{-t/\tau_{au1}} + B1$  for  $t > 0$

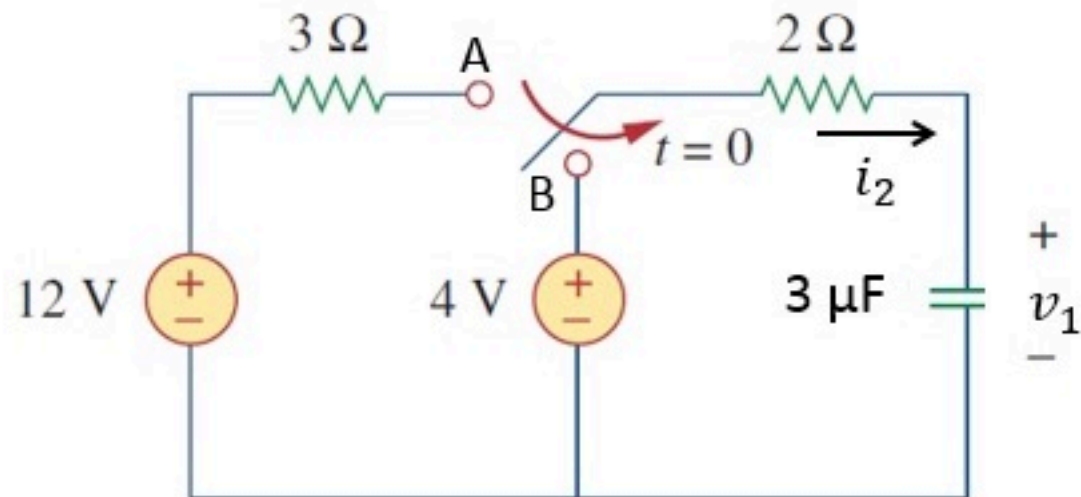Find  $i_2(t) = D2$  for  $t = 0^-$   
 $= A2 \cdot e^{-t/\tau_{au2}} + B2$  for  $t > 0$



Given Variables:

...

Calculate the following:

D1 (V) :

12

✓

A1 (V) :

8

✓

B1 (V) :

4

✓

$\tau_{au1}$  (us) :

6

✓

D2 (A) :

0

✓

A2 (A) :

-4

✓

B2 (A) :

0

✓

$\tau_{au2}$  (us) :

6

✓

Hint: Find the capacitor voltage before and after the switch




# PP First order circuits 005

Unlimited Attempts.

The switch has been closed for a long time.

At time  $t = 0$ , the switch is opened.

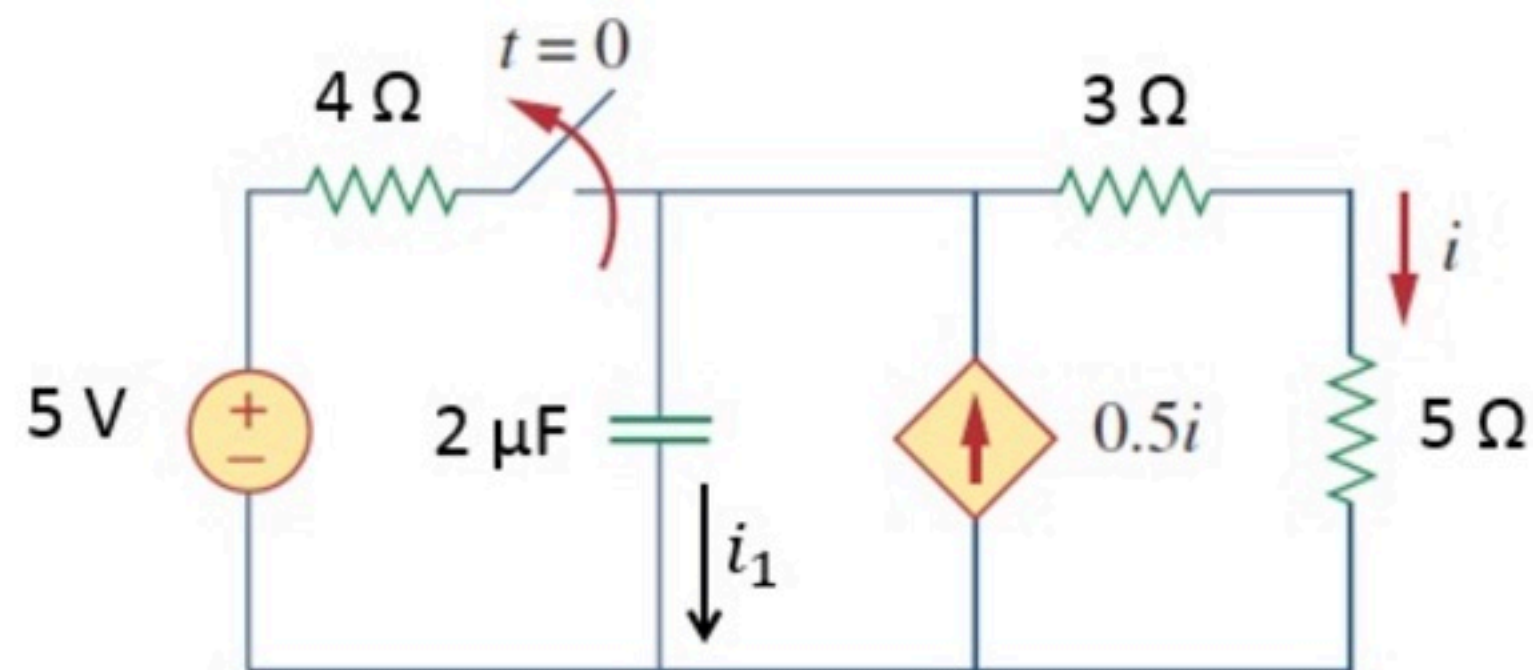Find  $i_1(t) = D$  for  $t = 0^-$   
 $= A \cdot e^{-t/\tau} + B$  for  $t > 0$



Given Variables:

...

Calculate the following:

D (A) :

0

✓

A (A) :

-0.25

✓

B (A) :

0

✓

$\tau$  (us) :

32

✓

Hint: Use a test source to find Req.


# PP First order circuits 006

Unlimited Attempts.

The switch has been open for a long time.

At time  $t = 0$ , the switch is closed.

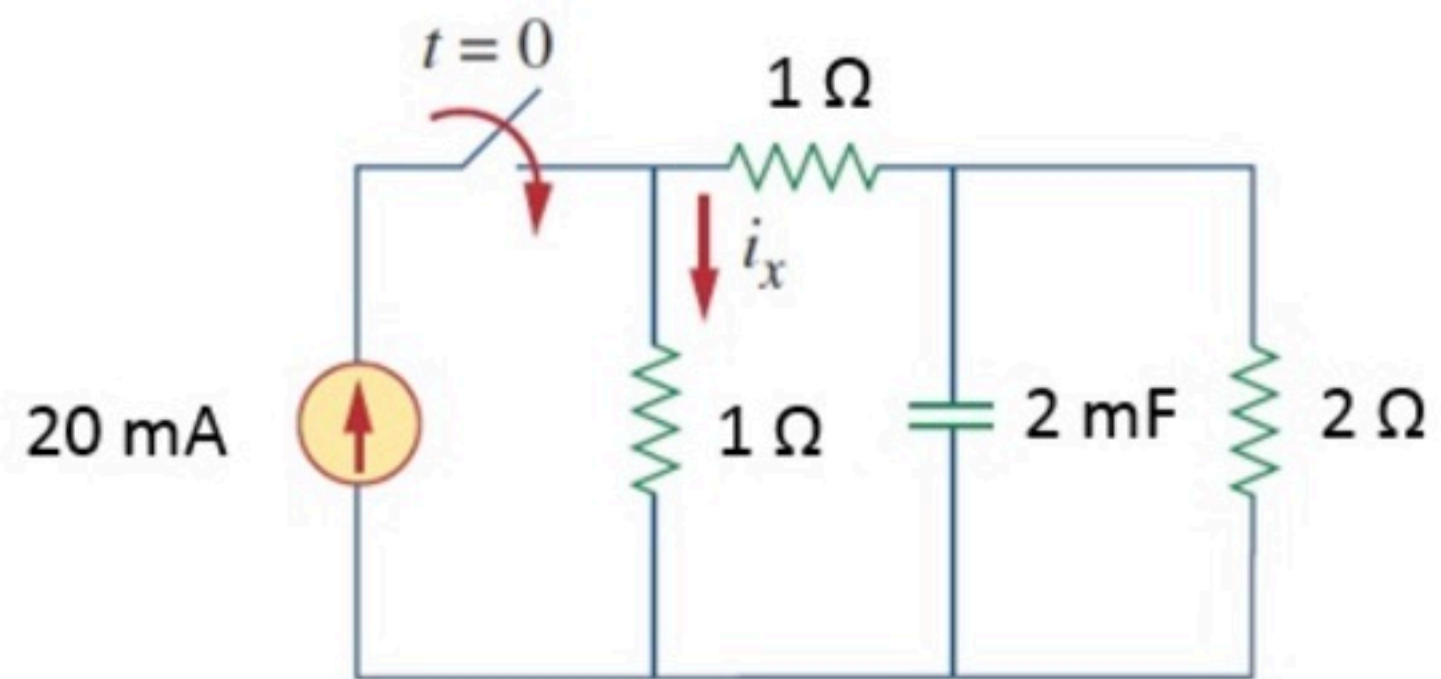Find  $i_x(t) = D$  for  $t = 0^-$   
 $= A \cdot e^{-t/\tau} + B$  for  $t > 0$



Given Variables:

...

Calculate the following:

D (mA) :

0

✓

A (mA) :

-5

✓

B (mA) :

15

✓

$\tau$  (ms) :

2

✓


Hint: What is the capacitor voltage right after the transition?

# PP First order circuits 007

Unlimited Attempts.

The switch has been open for a long time.  
At time  $t = 0$ , the switch is closed.

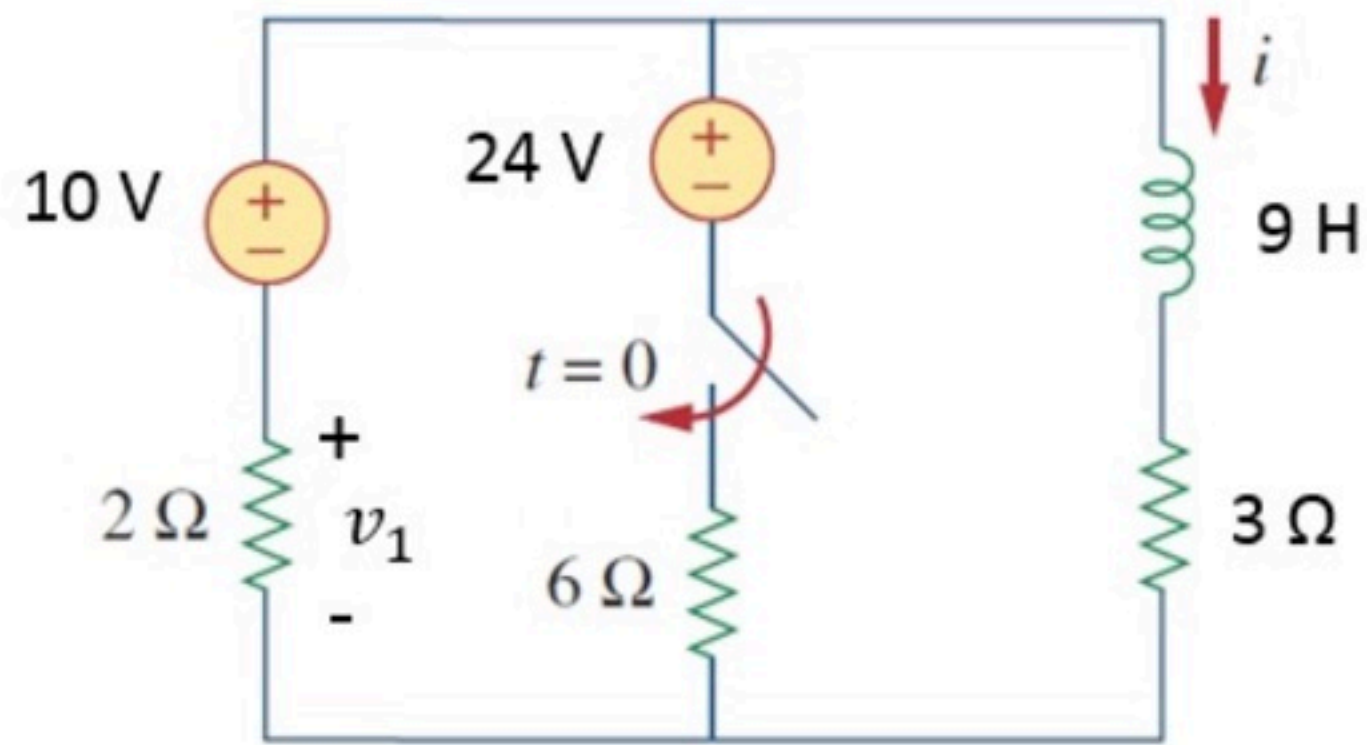Find  $v_1(t) = D$  for  $t = 0^-$   
 $= A \cdot e^{-t/\tau} + B$  for  $t > 0$



Given Variables:

...

Calculate the following:

D (V) :

-4



A (V) :

1.5



B (V) :

-1



$\tau$  (s) :

2



Hint: First find the inductor current just before the switch opens.




# PP First order circuits 008

Unlimited Attempts.

The switch has been in position A for a long time.  
At time  $t = 0$ , the switch moves to position B.

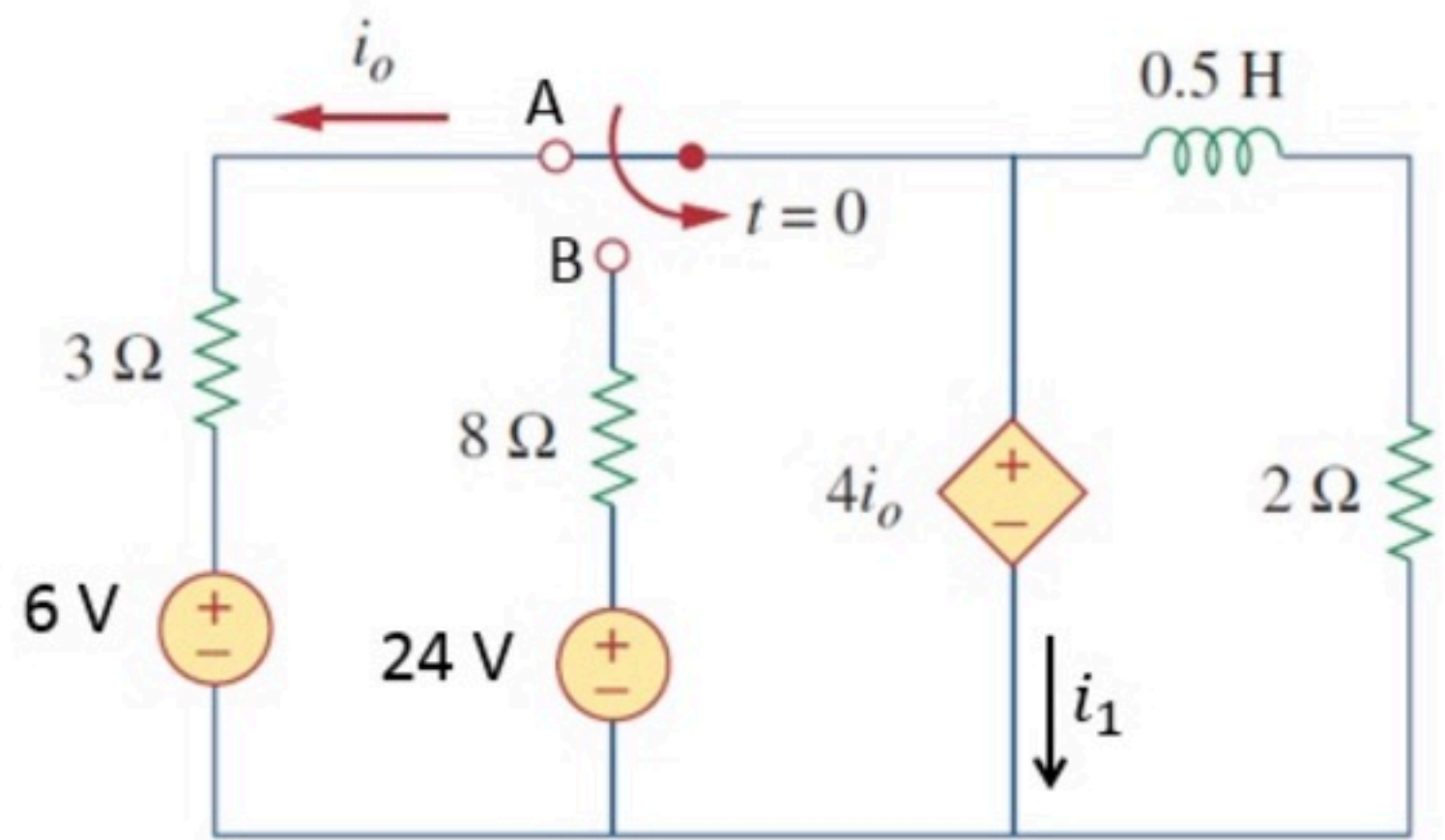Find  $i_1(t) = D$  for  $t = 0^-$   
 $= A \cdot e^{-t/\tau} + B$  for  $t > 0$



Given Variables:

...

Calculate the following:

D (A) :

-18

✓

A (A) :

-12

✓

B (A) :

3

✓

$\tau$  (s) :

0.25

✓

Hint: What is  $i_o$  after the switch opens?




# PP First order circuits 009

Unlimited Attempts.

The switch has been open for a long time.

At time  $t = 0$ , the switch is closed.

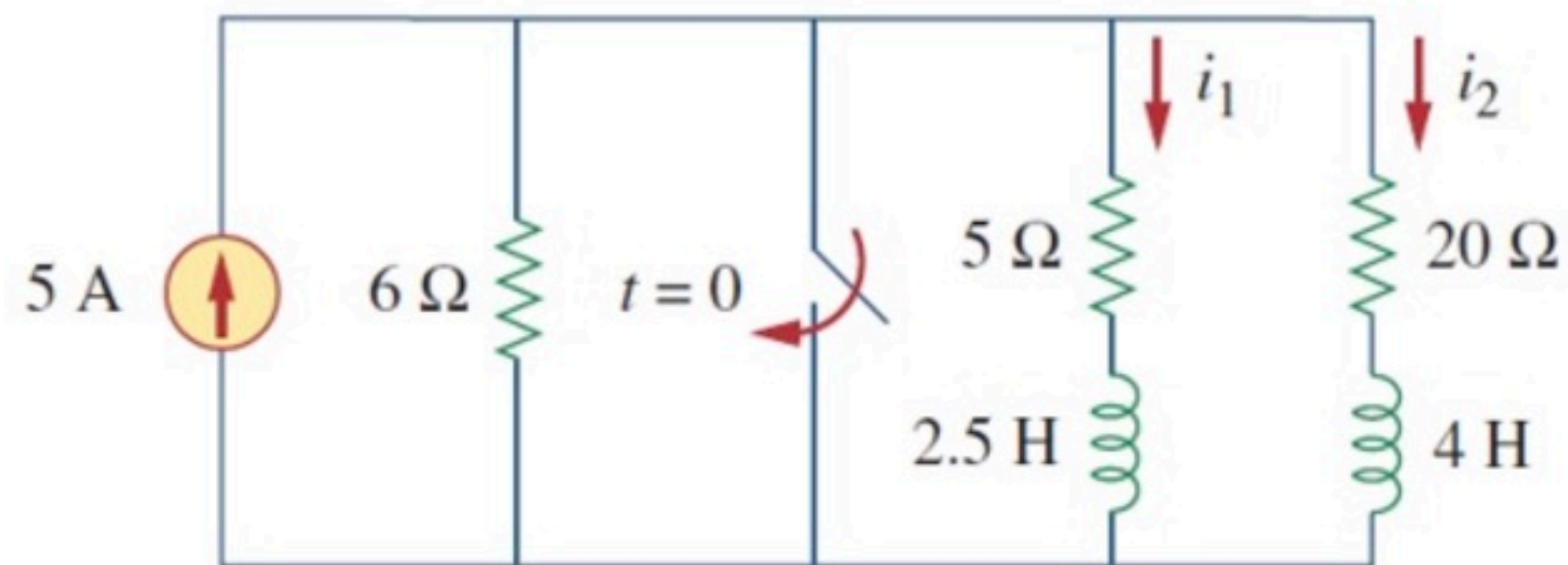Find  $i_1(t) = D$  for  $t = 0^-$   
 $= A \cdot e^{-t/\tau} + B$  for  $t > 0$



Given Variables:

...

Calculate the following:

D (A) :

2.4

✓

A (A) :

2.4

✓

B (A) :

0

✓

$\tau$  (s) :

0.5

✓

Hint: After the switch closes, do the two inductors influence each other?


# PP First order circuits 010

Unlimited Attempts.

The current source behaves as shown (and assume it has been zero for a long time for  $t < 0$ ).

Find  $v(t) = D$  for  $t = 2^- \text{ ms}$   
 $= A \cdot e^{-(t-2 \text{ ms})/\tau} + B$  for  $t > 2 \text{ ms}$

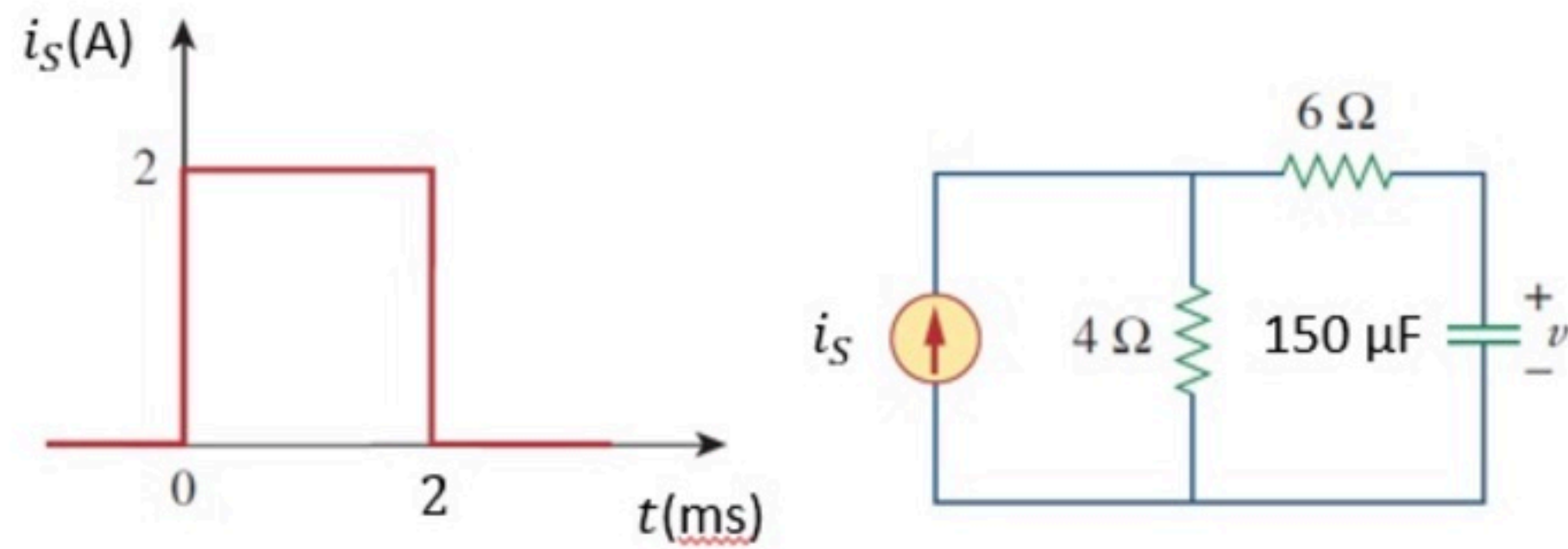Note, for your calculations, use:  $e^{-1/1.5} \approx 0.5$



Given Variables:

...

Calculate the following:

D (V) :

6

✓

A (V) :

6

✓

B (V) :

0

✓

$\tau$  (ms) :

1.5

✓

Hint: Find the result of the first transition first.


# PP Second order circuits 001

Unlimited Attempts.

Find  $i_1 = i(0^-)$  and  $v_1 = v(0^-)$

Find  $i_2 = i(0^+)$  and  $v_2 = v(0^+)$

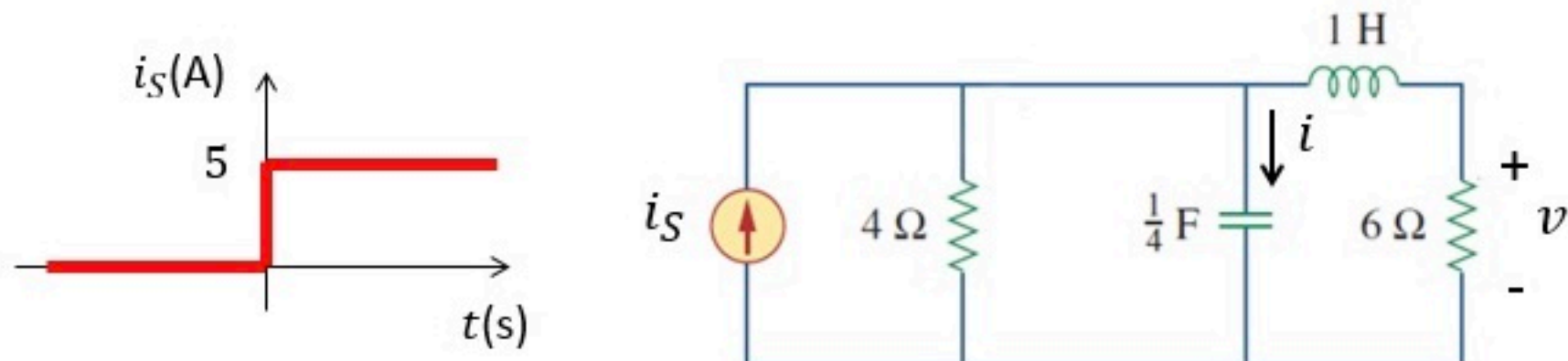Find  $i_3 = i(\infty)$  and  $v_3 = v(\infty)$



Given Variables:

. . .

Calculate the following:

$i_1$  (A) :

0

✓

$v_1$  (V) :

0

✓

$i_2$  (A) :

5

✓

$v_2$  (V) :

0

✓

$i_3$  (A) :

0

✓

$v_3$  (V) :

12

✓

Hint: Capacitors and inductors in steady state behave as opens and shorts.




# PP Second order circuits 002

Unlimited Attempts.

Find  $i_1 = i(0^-)$  and  $v_1 = v(0^-)$

Find  $i_2 = i(0^+)$  and  $v_2 = v(0^+)$

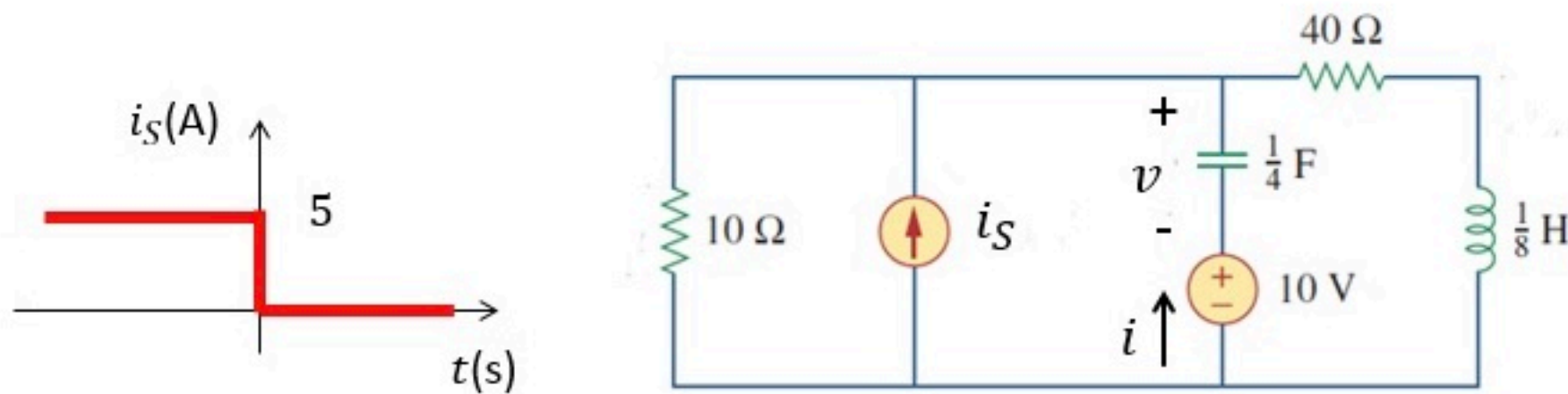Find  $i_3 = i(\infty)$  and  $v_3 = v(\infty)$



Given Variables:

. . .

Calculate the following:

$i_1$  (A) :

0

✓

$v_1$  (V) :

30

✓

$i_2$  (A) :

5

✓

$v_2$  (V) :

30

✓

$i_3$  (A) :

0

✓

$v_3$  (V) :

-10

✓

Hint: Capacitors and inductors in steady state behave as opens and shorts.