
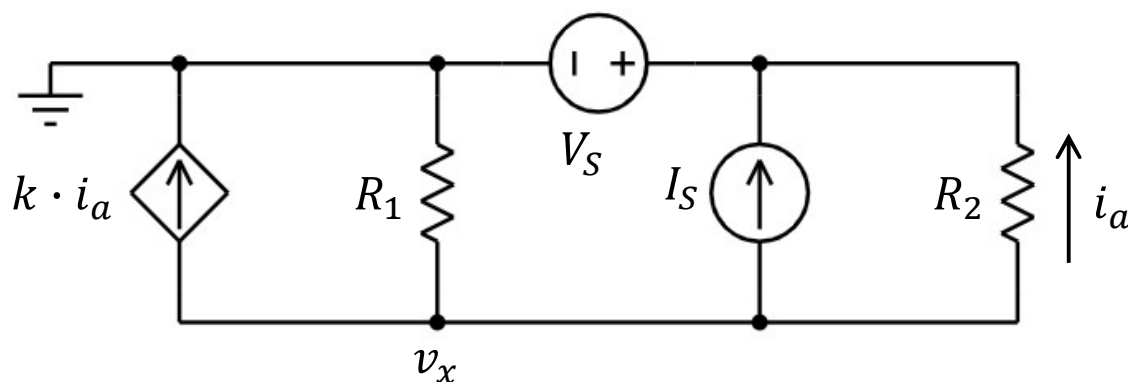


Q1

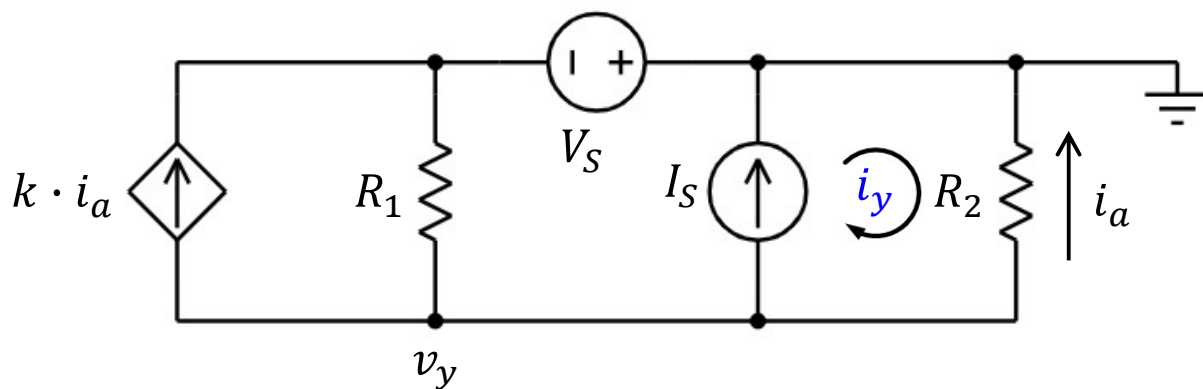- a. For the circuit below, find the node voltage v_x . You can use any technique. Write your equations symbolically first and only then plug in numbers.



- b. For the circuit below (which is identical to the one above, but with the ground moved to a new location), find the node voltage v_y .
- c. For the circuit below, find the mesh current i_y .




| | |
|------------------|------------|
| R1: | 2 Ω |
| R2: | 2 Ω |
| k: | 2 |
| V _S : | 2 V |
| I _S : | 1 A |

Q2

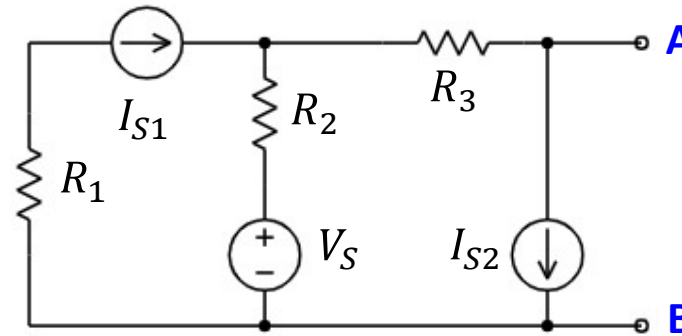- a. Consider the circuit on the right. The independent sources have the following values: $V_S = X$, $I_{S1} = Y$ and $I_{S2} = Z$, but you are not told what X , Y and Z are.

Find the Thevenin equivalent resistance between A and B.



| | |
|-----|------------|
| R1: | 1 Ω |
| R2: | 1 Ω |
| R3: | 2 Ω |
| I1: | 2 A |
| I2: | 2 A |

- b. We now add voltage source V_x to the circuit, as shown below. You are also told:

- If $V_S = 0$ V, $I_{S1} = Y$, $I_{S2} = 0$ A and $V_x = 10$ V, we find $i_x = I_1$.
- If $V_S = X/2$, $I_{S1} = 0$ A, $I_{S2} = Z/2$ and $V_x = 0$ V, we find $i_x = I_2$.

Consider $V_S = X$, $I_{S1} = Y$, $I_{S2} = Z$ and $V_x = 10$ V. What is i_x in this case?

- c. What is i_x when $V_S = X$, $I_{S1} = Y$, $I_{S2} = Z$ and $V_x = 22$ V?
(Hint: you can solve this using part a and b)

