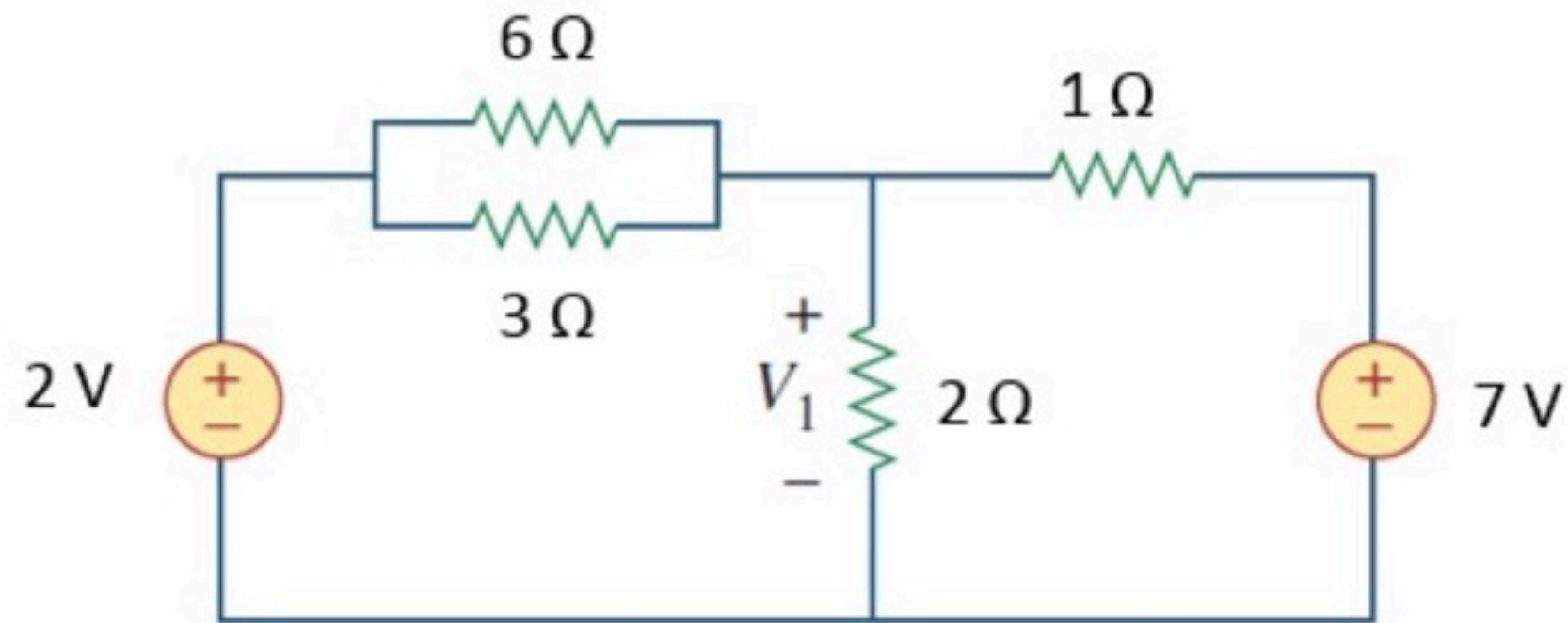


PP - Nodal Mesh 003

Problem has been graded.

Find V_1 . Solve using nodal analysis.

For extra practice: Afterwards solve again using mesh analysis.



Given Variables:

...

Calculate the following:

V_1 (V) :

4



Hint: Choose GND strategically