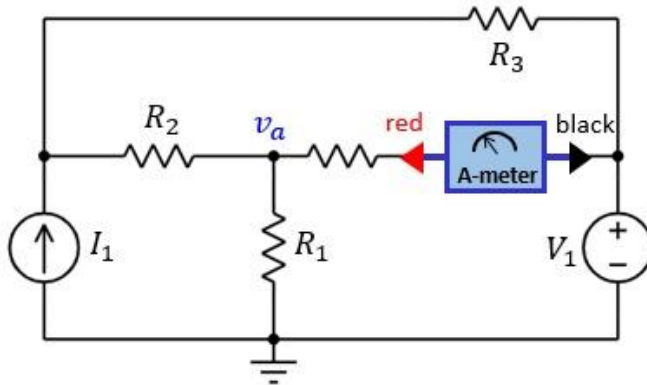


### Q1

Consider the circuit below. For one of the resistors, you are not given its value. The ammeter is ideal.


- The ammeter reading is  $X$ . Find the node voltage  $v_a$ .
- We flip the direction of both  $I_1$  and  $V_1$  and keep all the other circuit elements the same. What is  $v_a$  now?



R1:	2 Ω
R2:	1 Ω
R3:	2 Ω
V1:	6 V
I1:	1 A
X:	1 A
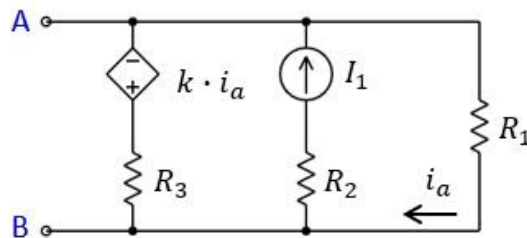
### Q2

- Consider the circuit below. Find the Thevenin equivalent resistance  $R_{Th}$  between A and B.



R1:	3 Ω
R2:	2 Ω
R3:	6 Ω
I1:	5 A
k:	3 V/A

- We double the value of  $I_1$  and all other circuit elements remain the same. Find the value of  $R_L$  to be connected between A and B such that the power received by  $R_L$  is maximized.