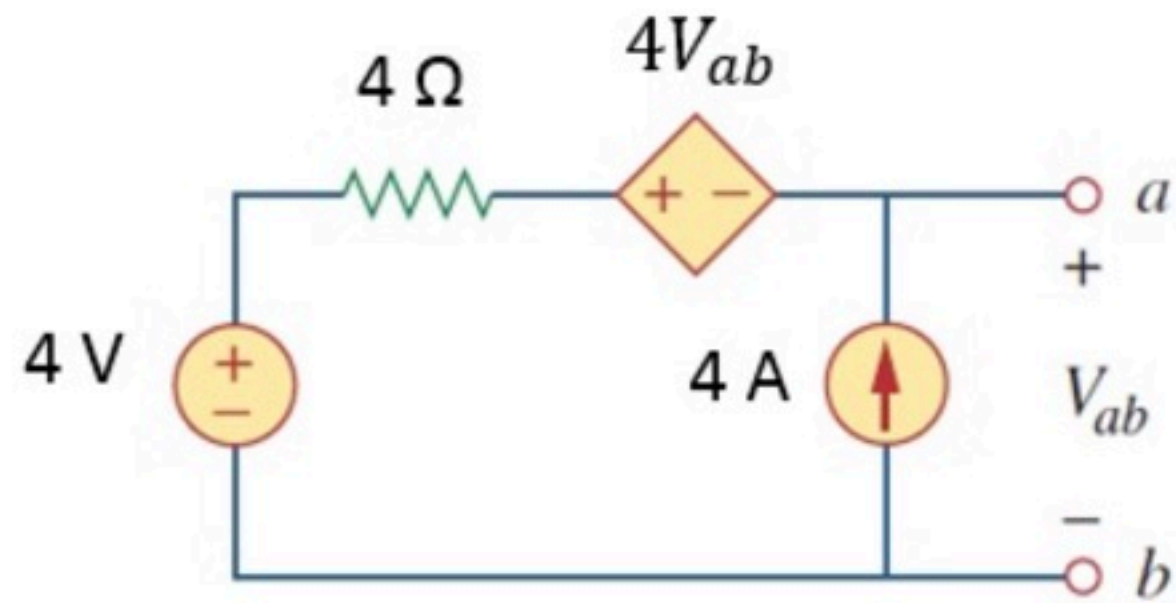


# PP Circuit theorems 005

Unlimited Attempts.

Use superposition to find  $V_{ab}$ .



Given Variables:

...

Calculate the following:

$V_{ab}$  (V) :

4



Hint: Always keep the dependent source.