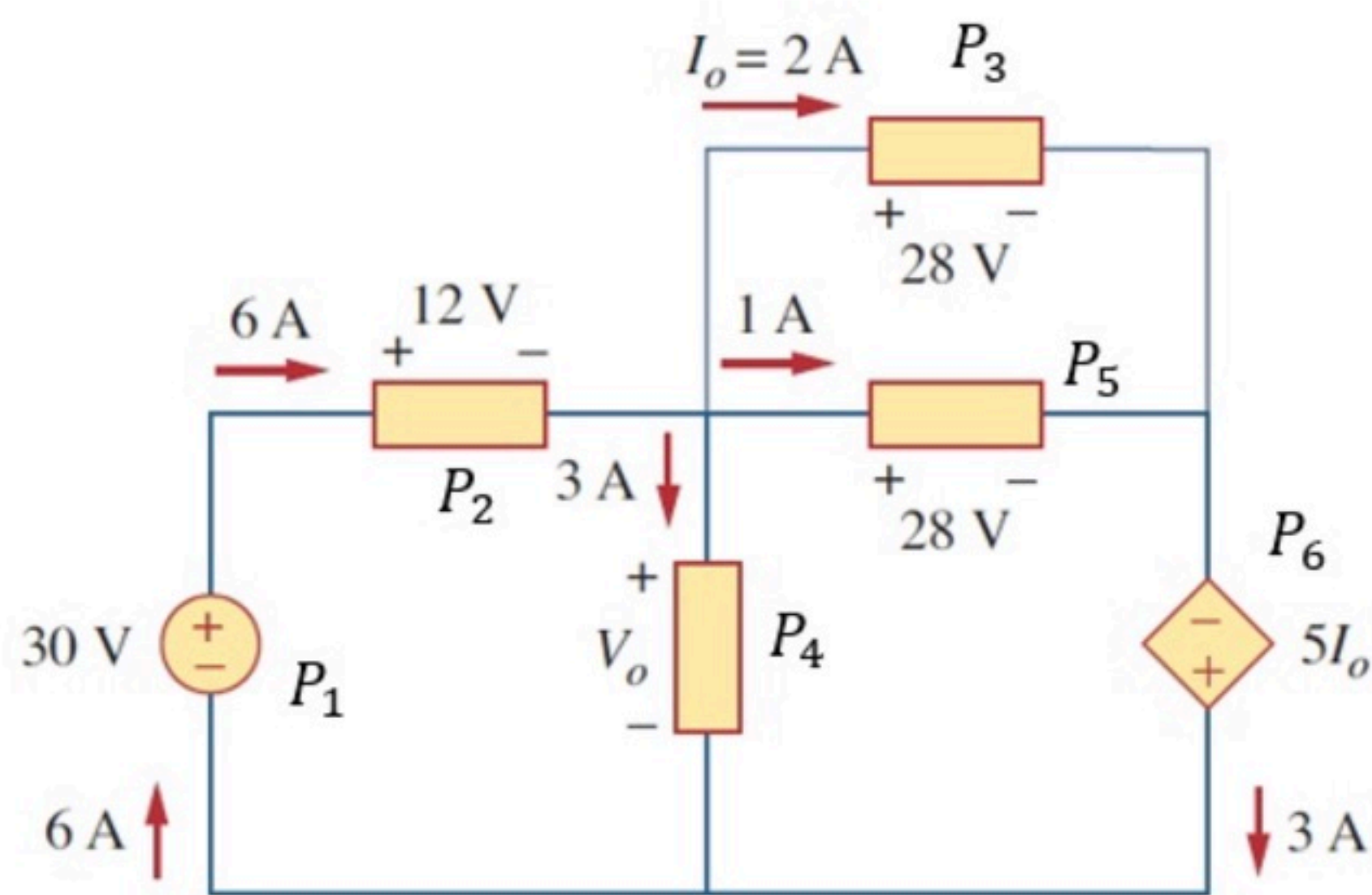


PP - Basic concepts 011

Problem has been graded.

Find the power received by each of the elements.



Given Variables:

...

Calculate the following:

P1 (W) :

-180



P2 (W) :

72



P3 (W) :

56



P4 (W) :

54



P5 (W) :

28



P6 (W) :

-30

