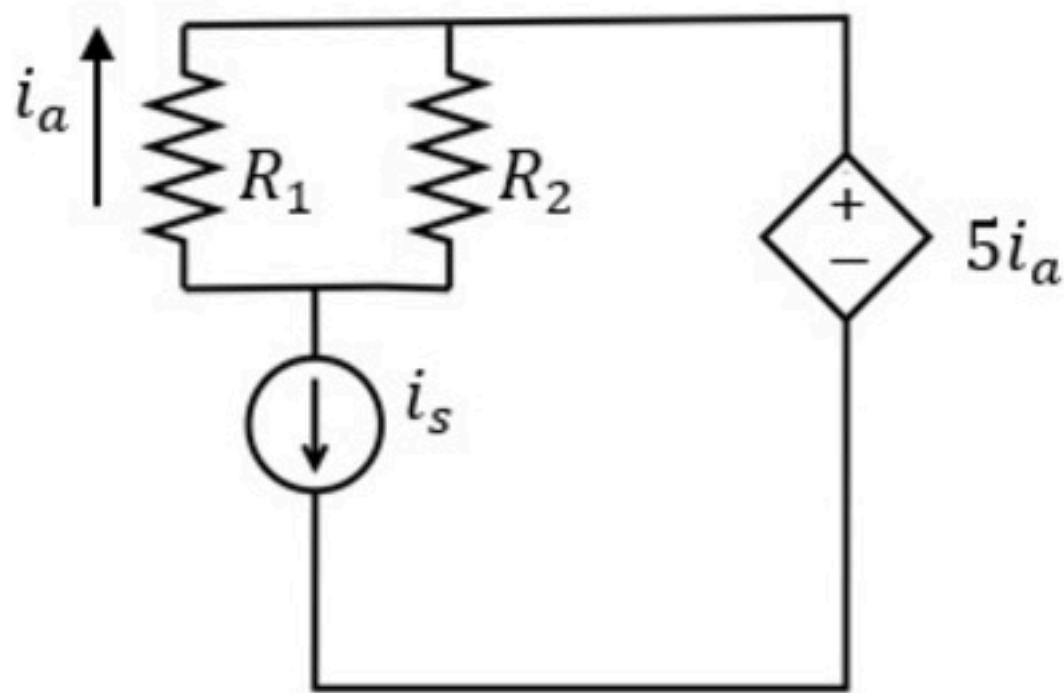


Basic analysis 005

Problem has been graded.

Find the power supplied by the dependent source.



Given Variables:

R_1 : 5 ohm

R_2 : 20 ohm

i_s : 5 A

Calculate the following:

P (W) :

Hint: Use current divider