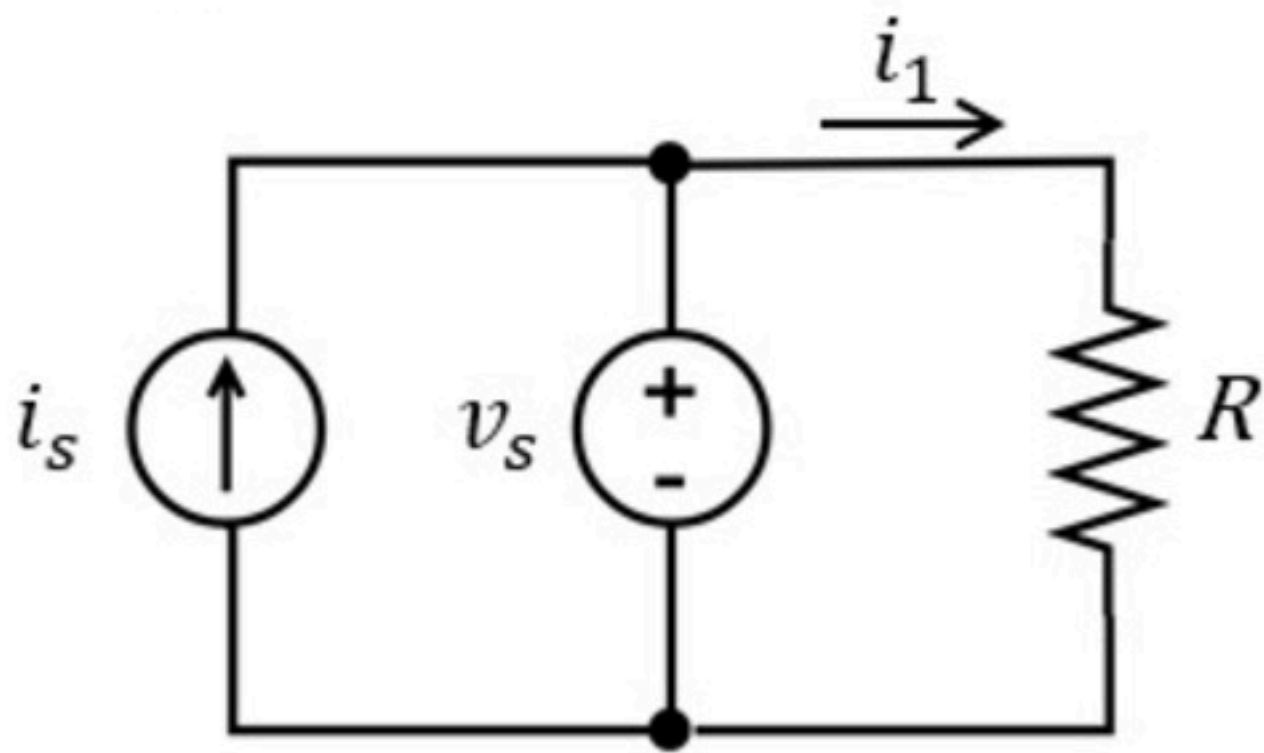


# Basic concepts 006

Problem has been graded.

Find the current  $i_1$  and the power  $P_1$  received by the resistor.

Then change the current source to 5A. Recalculate the current  $i_1$  (renaming it to  $i_2$ ) and the power  $P_2$  received by the resistor.



Given Variables:

$v_s$  : 16 V

$i_s$  : 4 A

$R$  : 8 ohm

Calculate the following:

$i_1$  (A) :

$P_1$  (W) :

$i_2$  (A) :

$P_2$  (W) :

Hint: The voltage across a current source can be non-zero


Find the current  $i_1$  and the power  $P_1$  received by the resistor.

$$V_s = 16 \text{ V}$$

Then change the current source to 5A. Recalculate the current  $i_1$  (renaming it to  $i_2$ ) and the power  $P_2$  received by the resistor.

$$I_s = 4 \text{ A}$$

$$R = 16 \Omega$$

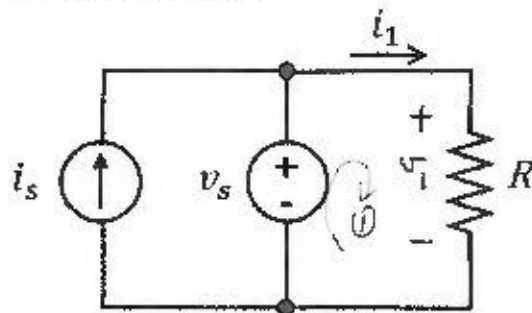

$$\text{KVL } \textcircled{1} : v_s = v_1 \Rightarrow v_1 = 16 \text{ V}$$

$$i_1 = \frac{v_1}{R} = \frac{16}{16} \Rightarrow \boxed{i_1 = 1 \text{ A}}$$

$$P_1 = i_1^2 \cdot R = 1^2 \cdot 16 \Rightarrow \boxed{P_1 = 16 \text{ W}}$$

received

When  $I_s = 5 \text{ A}$

$$v_1 \text{ still the same. } v_1 = 16 \text{ V} \Rightarrow i_2 = \frac{v_1}{R}$$

$$\boxed{i_2 = 1 \text{ A}}$$

$$P_2 = i_2^2 R$$


$$\boxed{P_2 = 16 \text{ W}}$$

received

# Basic analysis 002

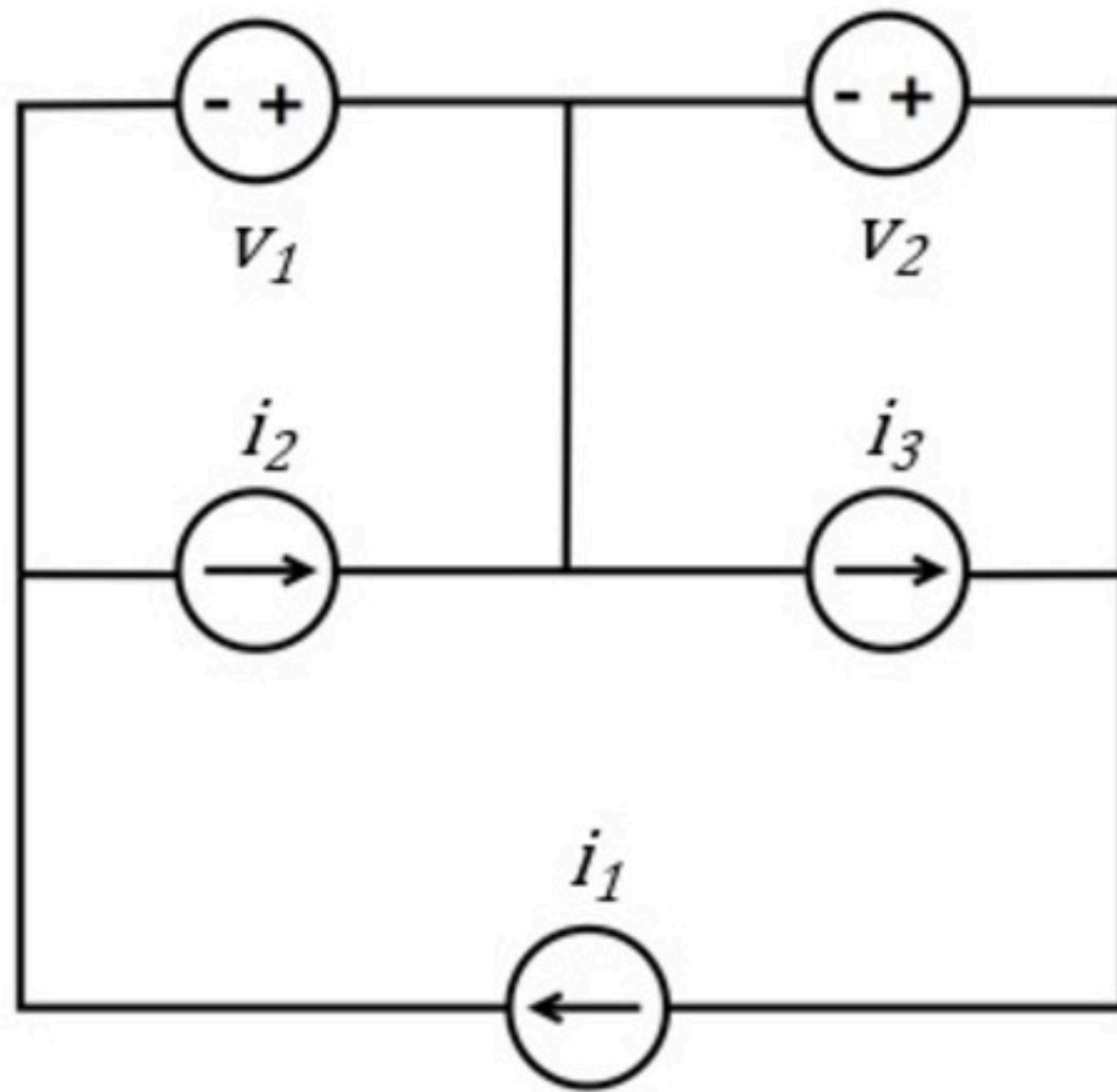Problem has been graded.

Determine the power  $P_1$  supplied by voltage source  $v_1$  and the power  $P_2$  supplied by voltage source  $v_2$ .



Given Variables:

$i_1$  : 4 A

$i_2$  : 2 A

$i_3$  : 3 A

$v_1$  : 3 V

$v_2$  : 4 V

Calculate the following:

$P_1$  (W) :

$P_2$  (W) :

Determine the power  $P_1$  supplied by voltage source  $v_1$  and the power  $P_2$  supplied by voltage source  $v_2$ .


$$i_1 = 4 \text{ A}$$

$$i_2 = 2 \text{ A}$$

$$i_3 = 3 \text{ A}$$

$$v_1 = 3 \text{ V}$$

$$v_2 = 4 \text{ V}$$

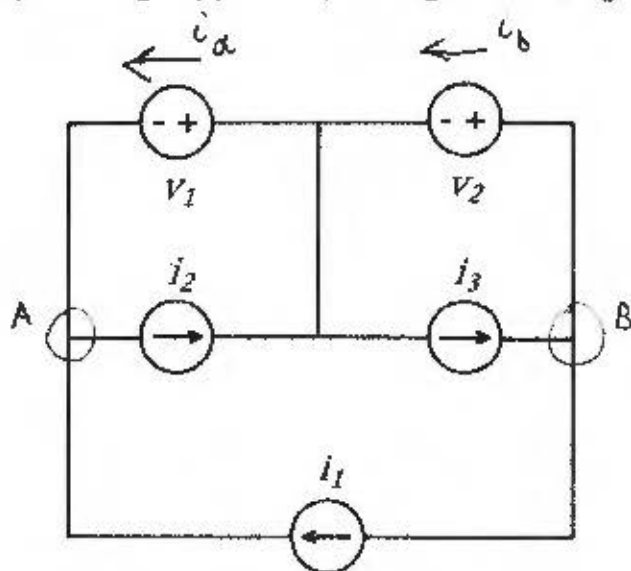

$$\text{KCL @ A: } i_1 + i_a = i_2 \Rightarrow i_a = 2 - 4 = -2 \text{ A}$$

$$P_1 = v_1 \cdot i_a = -6 \text{ W} \quad \text{RECEIVED} \quad \left( \text{PASSIVE SIGN CONVENTION} \right)$$

$$\boxed{P_1 = 6 \text{ W}} \quad \text{SUPPLIED}$$

$$\text{KCL @ B: } i_3 = i_b + i_1 \Rightarrow i_b = 3 - 4 = -1 \text{ A}$$


$$P_2 = v_2 \cdot i_b = -4 \text{ W} \quad \text{RECEIVED}$$

$$\boxed{P_2 = 4 \text{ W}} \quad \text{SUPPLIED}$$

# Basic analysis 003

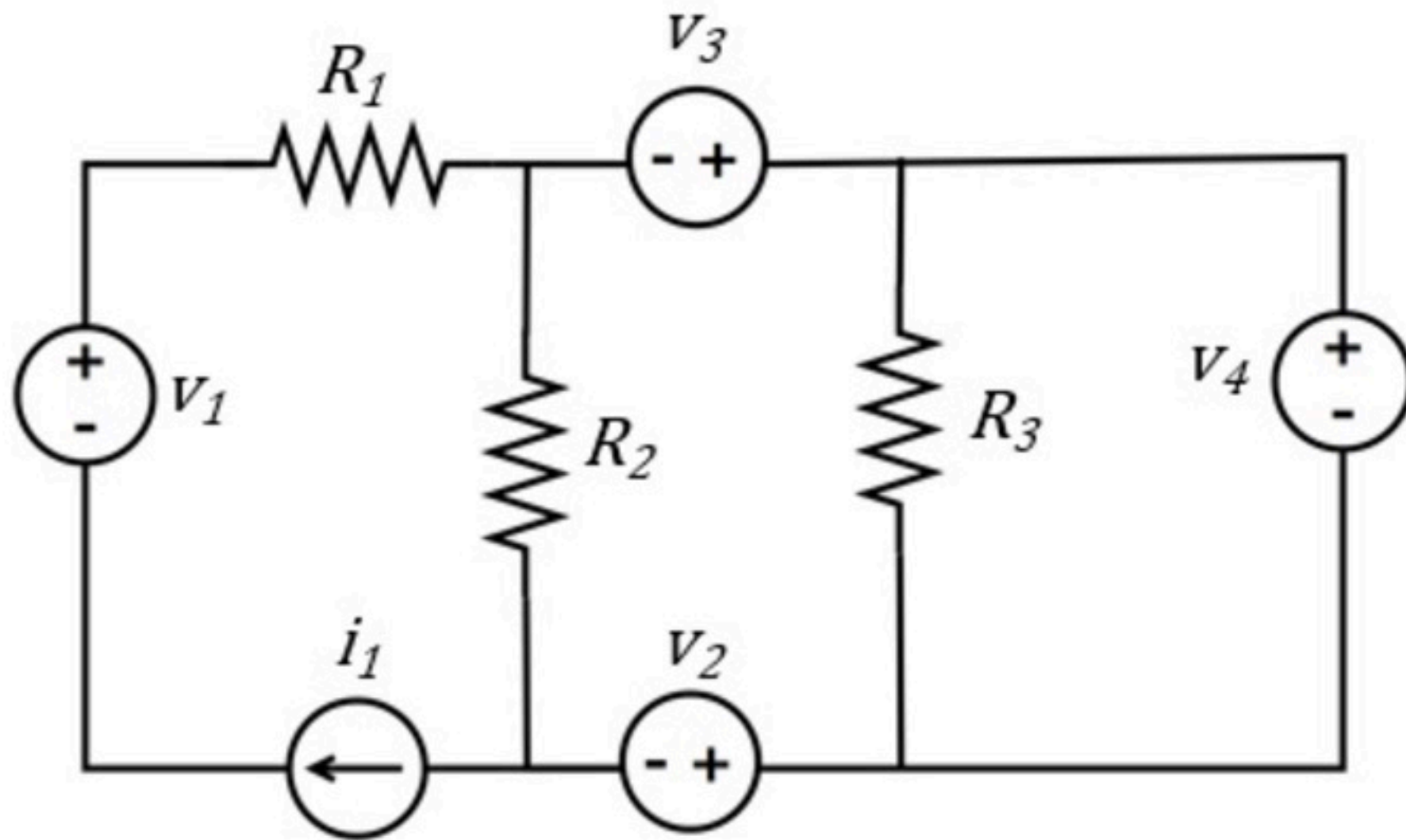Problem has been graded.

Determine the power received by each of the three resistors.



Given Variables:

$v_1$  : 3 V

$v_2$  : 5 V

$v_3$  : 1 V

$v_4$  : 2 V

$i_1$  : 1 A

$R_1$  : 2 ohm

$R_2$  : 3 ohm

$R_3$  : 4 ohm

Calculate the following:

$P_1$  (W) :

$P_2$  (W) :

$P_3$  (W) :

Hint: Find currents using KCL and KVL

Determine the power received by each of the three resistors.

$$v_1 = 2 \text{ V}$$

$$v_2 = 3 \text{ V}$$

$$v_3 = 4 \text{ V}$$


$$v_4 = 2 \text{ V}$$

$$i_1 = 4 \text{ A}$$

$$R_1 = 2 \Omega$$

$$R_2 = 1 \Omega$$

$$R_3 = 4 \Omega$$

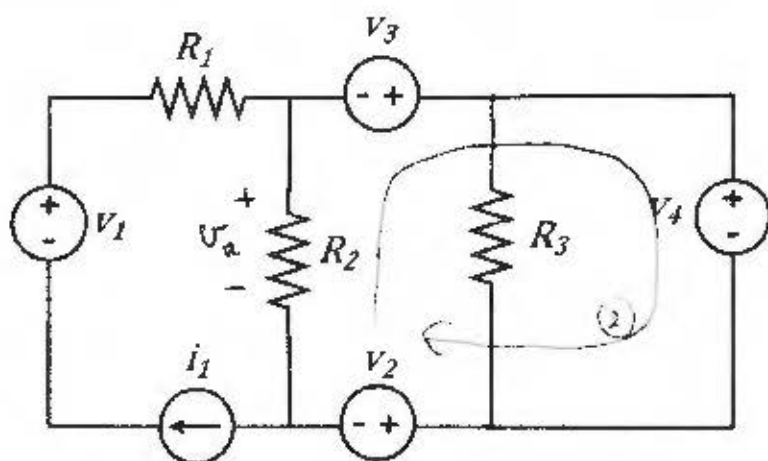

(a)  $R_1$  :  $P = R_1 \cdot i_1^2 = 2 \cdot 4^2$

$$P_{R_1} = 32 \text{ W}$$

(b)  $R_3$  :  $P = \frac{v_4^2}{R_3} = \frac{4}{4}$

$$P_{R_3} = 1 \text{ W}$$

(c) KVL in (2) :  $v_a + v_3 - v_4 - v_2 = 0$   
 $v_a = -4 + 2 + 3 = 1 \text{ V}$

$$P = \frac{v_a^2}{R_2} = \frac{1}{1}$$

$$P_{R_2} = 1 \text{ W}$$




# Basic analysis 011

Problem has been graded.

This circuit contains a capacitor (which we will cover in detail later in this course) with a voltage  $v_C$  across it. Voltage  $v_2$  and current  $i_1$  will satisfy the equations shown below (as we will also see later). Find the coefficients  $A$ ,  $D$  and  $E$ .

$$v_C = 10 - 10 \cdot e^{-20t} \text{ V}$$
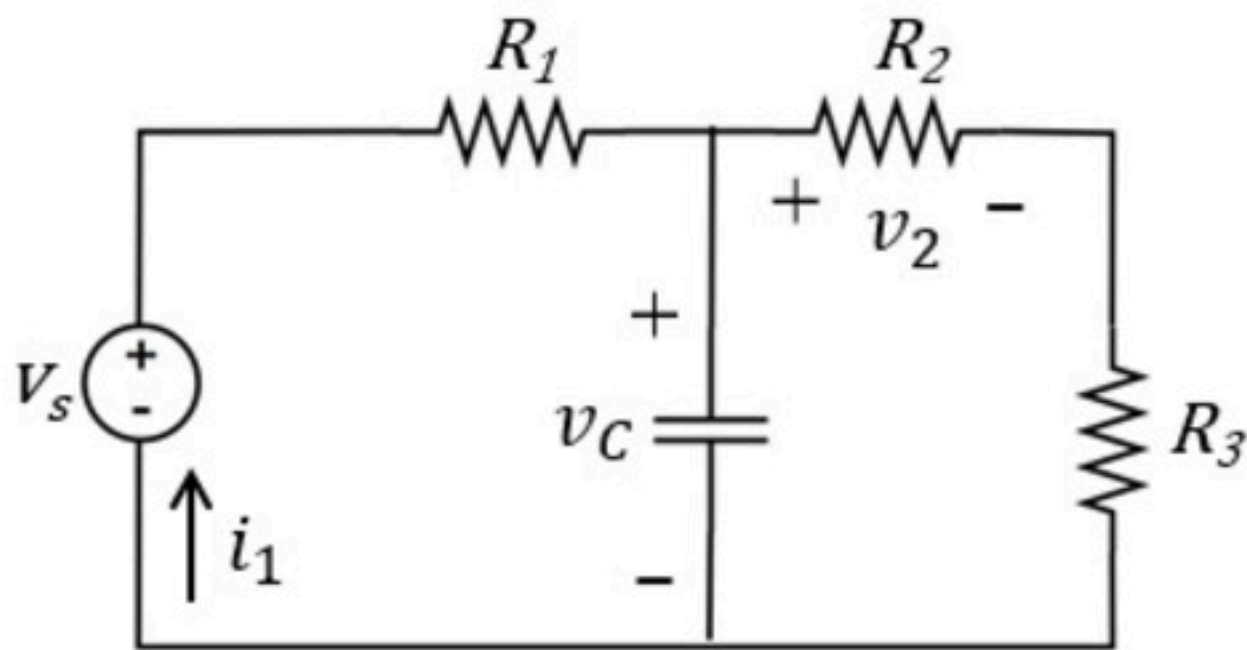
$$v_2 = A + B \cdot e^{-20t} \text{ V} \quad i_1 = D + E \cdot e^{-20t} \text{ A}$$



Given Variables:

$v_s$  : 20 V

$R_1$  : 20 ohm

$R_2$  : 7 ohm

$R_3$  : 13 ohm

Calculate the following:

$A$  (.):

$B$  (.):

$D$  (.):

$E$  (.):

This circuit contains a capacitor (which we will cover in detail later in this course) with a voltage  $v_C$  across it. Voltage  $v_2$  and current  $i_1$  will satisfy the equations shown below (as we will also see later). Find the coefficients  $A$ ,  $D$  and  $E$ .

$$V_s = 15 \text{ V}$$


$$R_1 = 10 \, \Omega$$

$$R_2 = 15 \, \Omega$$

$$R_3 = 5 \, \Omega$$

$$v_C = 10 - 10 \cdot e^{-20t} \text{ V}$$
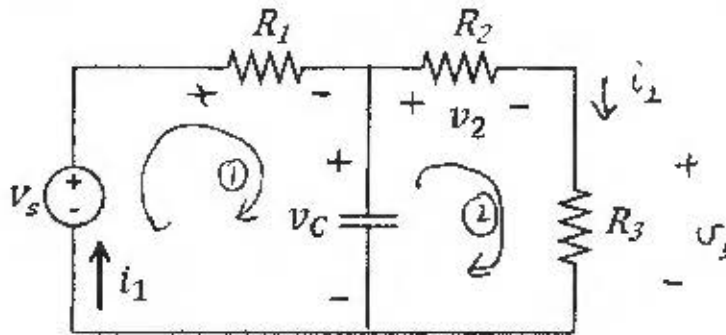
$$v_2 = A + B \cdot e^{-20t} \text{ V} \quad i_1 = D + E \cdot e^{-20t} \text{ A}$$



$$\text{KVL in } \textcircled{1} : v_s - v_{R_1} - v_C = 0 \quad v_{R_1} = i_1 \cdot R_1$$

$$\Rightarrow i_1 = \frac{1}{R_1} \cdot (v_s - v_C) = \frac{1}{10} \left( 15 - 10 + 10 e^{-20t} \right)$$

$$= \frac{1}{10} \left( 5 + 10 e^{-20t} \right)$$

$$\boxed{D = 0.5} \quad \boxed{E = 1}$$

$$\text{KVL in } \textcircled{2} : v_C - v_2 - v_3 = 0$$

$$v_2 = i_2 \cdot R_2$$

$$v_3 = i_2 \cdot R_3$$

$$\Rightarrow v_C = v_2 + v_3 = i_2 (R_2 + R_3)$$

$$\Rightarrow v_2 = R_2 \cdot i_2 = v_C \cdot \frac{R_2}{R_2 + R_3}$$

$$= v_C \cdot \frac{15}{20}$$

$\leadsto$  THIS COULD ALSO BE FOUND DIRECTLY WITH VOLTAGE DIVIDER

$$\Rightarrow v_2 = 7.5 - 7.5 e^{-20t}$$

$$\boxed{A = 7.5} \quad \boxed{B = -7.5}$$




# Basic analysis 013

No more attempts left.

Find  $v_a$ .

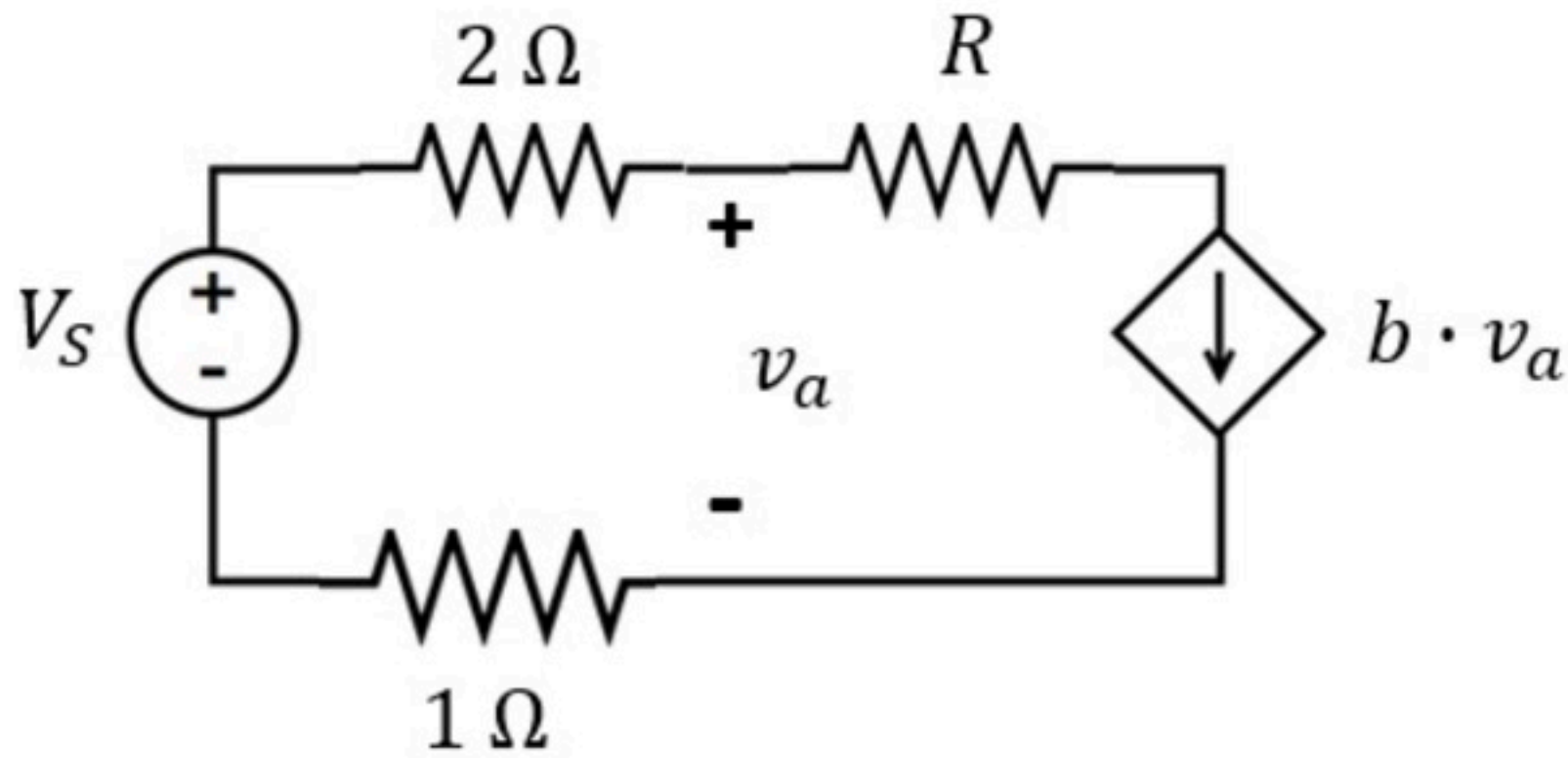What is the power  $P$  received by the dependent source?



Given Variables:

$V_s$  : 7 V

$R$  : 2 ohm

$b$  : 2 A/V

Calculate the following:

$v_a$  (V) :

$P$  (W) :

Hint: KVL also works when the voltage drop is not across an element.


Find  $v_a$ .

What is the power  $P$  received by the dependent source?

$$V_s = 7 \text{ V}$$

$$R = 2 \Omega$$

$$b = 2 \text{ A/V}$$

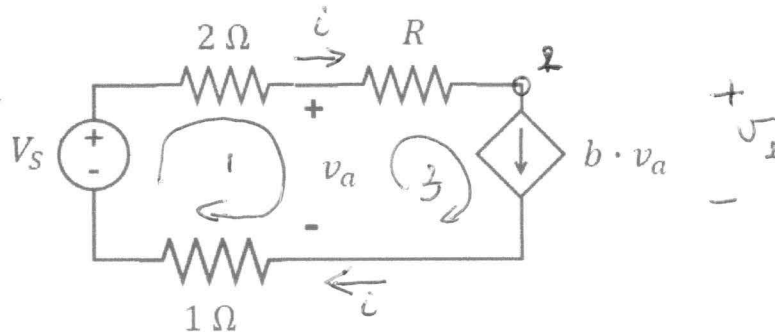


$$\text{KVL 1: } V_s = 2 \cdot i + v_a + 1 \cdot i \Rightarrow V_s = 3i + v_a \quad (1)$$

$$\text{KCL 2: } i = b v_a \quad (2)$$

$$(2) \text{ in } (1): V_s = 3b v_a + v_a = 7 \cdot v_a \Rightarrow \boxed{v_a = 1 \text{ V}}$$

$$\stackrel{(2)}{\Rightarrow} i = 2 \cdot v_a = 2 \text{ A}$$
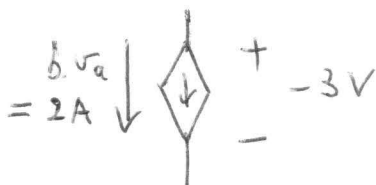
$$\text{KVL 3: } v_a = R \cdot i + v_2 \Rightarrow v_2 = 1 - 2 \cdot i = -3 \text{ V}$$



PASSIVE SIGN CONVENTION

$$P = (-3) \cdot 2 = -6$$

$$\boxed{P = -6 \text{ W RECEIVED}}$$