

ECE 65: Components & Circuits Lab

Lecture 6

Diode waveform shaping circuits

Rectifier circuits


Reference notes: sections 2.9

Sedra & Smith (7th Ed): sections 4.4-4.6

Saharnaz Baghdadchi

Course map




2. Diodes

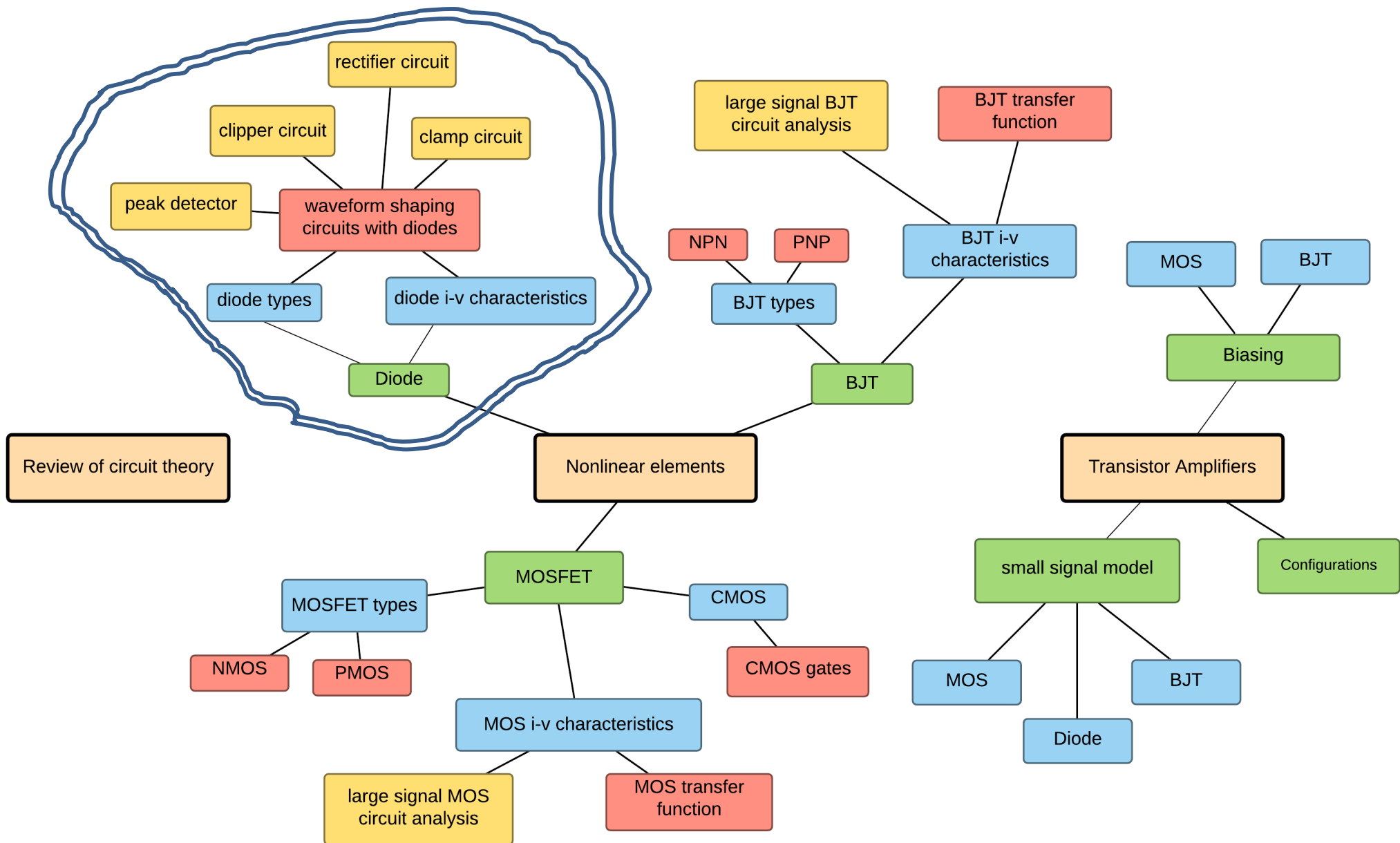

Diodes Waveform shaping Circuits

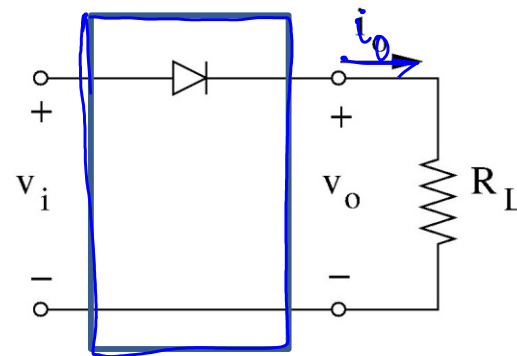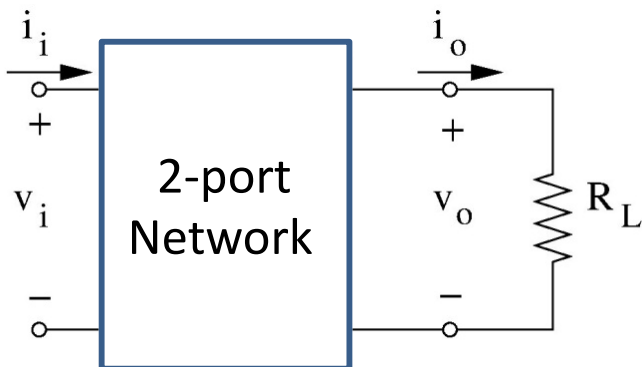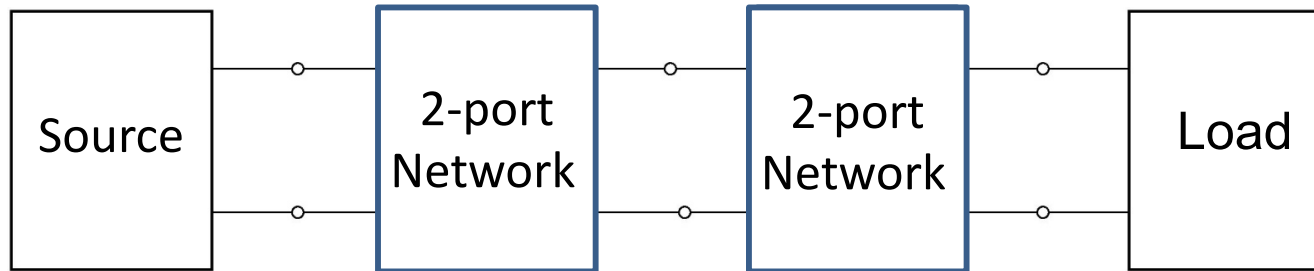- 1. Rectifier Circuit**
- 2. Clipper Circuit**
- 3. Peak Detector**
- 4. Clamp Circuit**

Diode waveform shaping circuits as two-port networks



We would like to find the transfer function, v_o vs v_i


“Open-loop” Transfer function is v_o vs v_i when $R_L \rightarrow \infty$ or $i_o = 0$.

Rectifier Circuit

$$\text{KVL: } \underline{v_i = v_D + v_o} \rightarrow v_o = v_i - v_D$$

$$\text{Ohm's law: } i_D = v_o / R_L$$

$$i_D = i_o$$

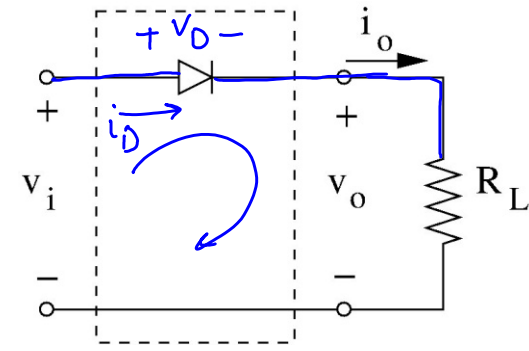

Diode OFF: $i_D = 0$ & $v_D < V_{D0}$

$$v_o = R_L i_D = 0$$

$$v_i = v_D + v_o \Rightarrow v_i = v_D < V_{D0} \rightarrow v_i < V_{D0}$$

Diode ON: $v_D = V_{D0}$ & $\underline{i_D \geq 0}$

$$v_o = v_i - V_{D0}$$



$$i_D = \frac{v_i - V_{D0}}{R} \geq 0 \rightarrow v_i \geq V_{D0}$$

Rectifier Circuit


Transfer Function is non-linear:

For $v_i \geq V_{D0}$, $v_o = v_i - V_{D0}$ (Diode is ON)

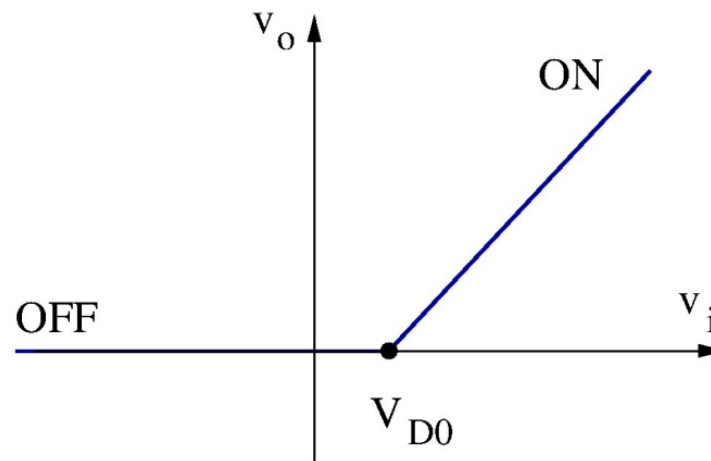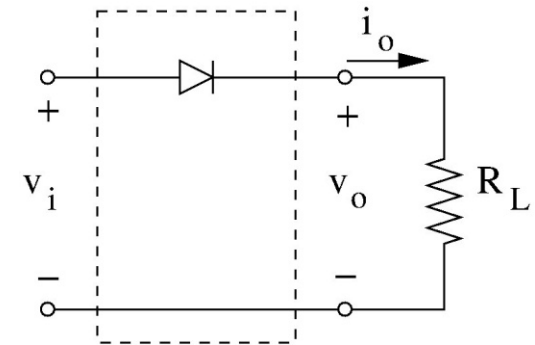For $v_i < V_{D0}$, $v_o = 0$ (Diode is OFF)



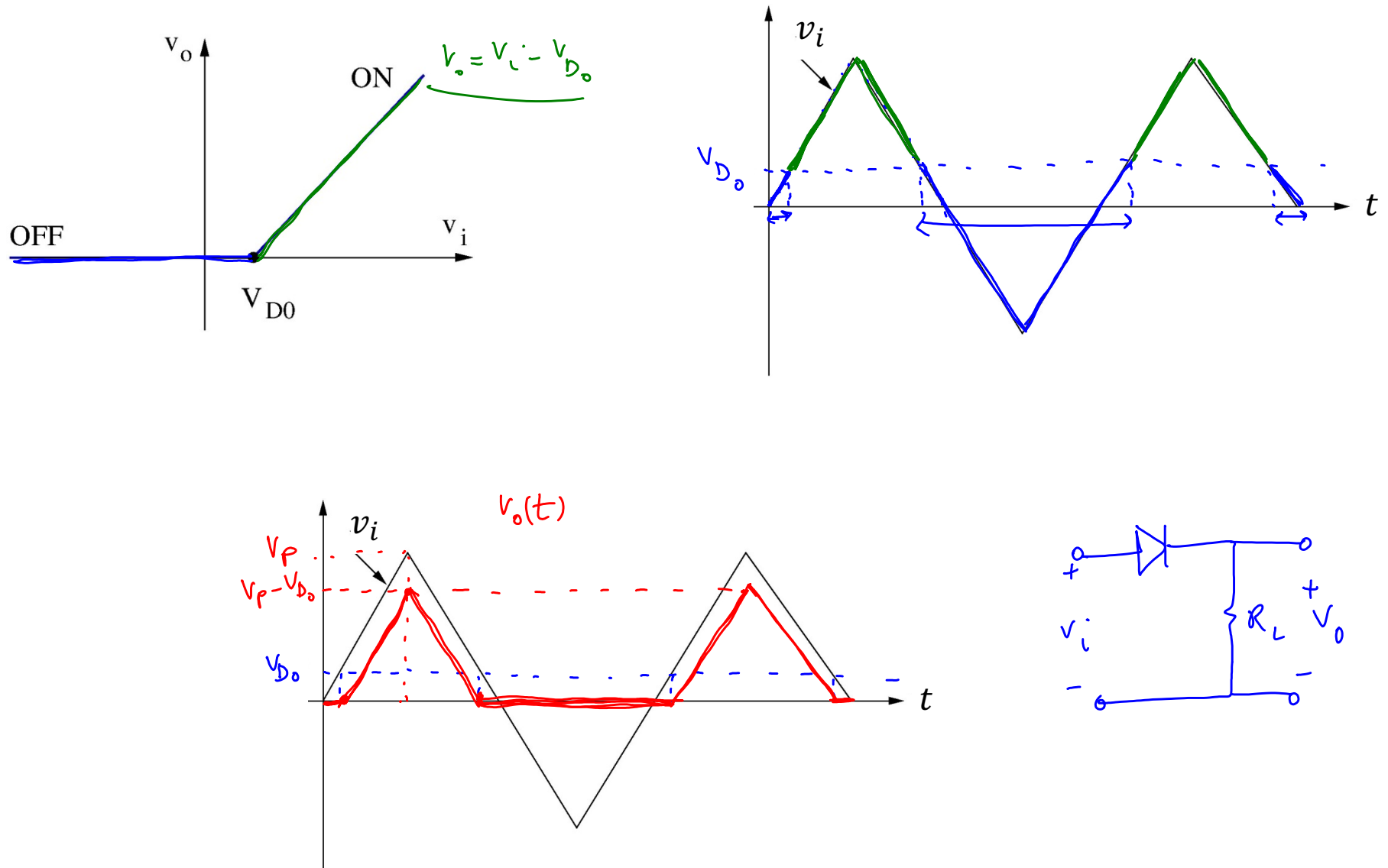Rectifier Circuit: example input - output waveforms




Rectifier Circuit for the negative part of v_i

Transfer Function is non-linear:

For $v_i \leq -V_{D0}$, $v_o = v_i + V_{D0}$ (Diode is ON)

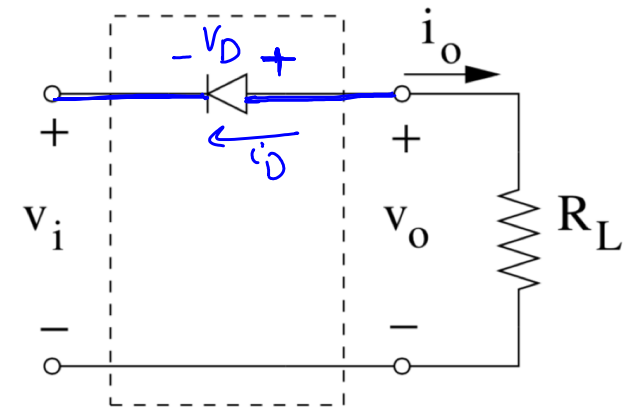For $v_i > -V_{D0}$, $v_o = 0$ (Diode is OFF) $\rightarrow i_D = 0$



Diode ON: $i_D \geq 0$, $V_D = V_{D0}$


KVL:

$$v_i = -V_D - R_L i_D$$

$$\rightarrow i_D = \frac{-V_D - v_i}{R_L}$$



$$i_D = \frac{-V_{D0} - v_i}{R_L} \geq 0$$

$$\rightarrow v_i \leq -V_{D0}$$


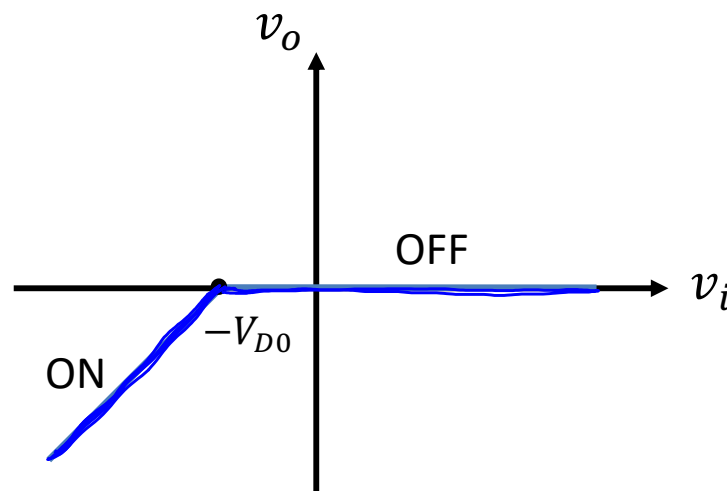


Application of Rectifier Circuit: AC to DC convertor for power supply




Half-wave rectifier

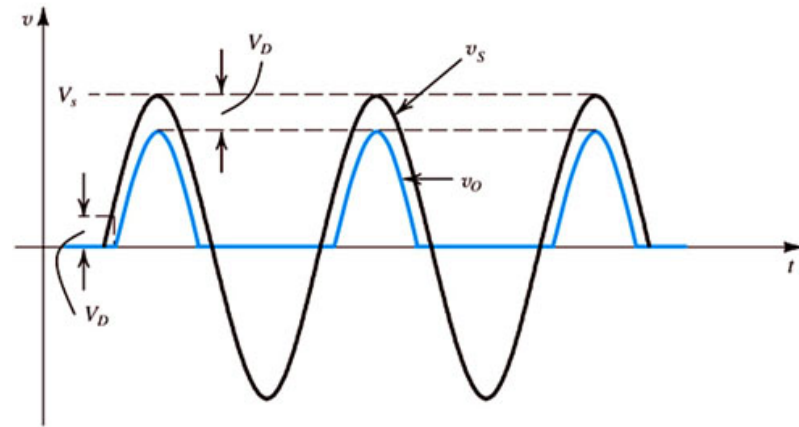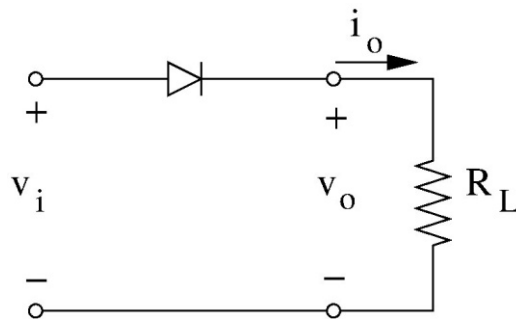

Full-wave rectifier

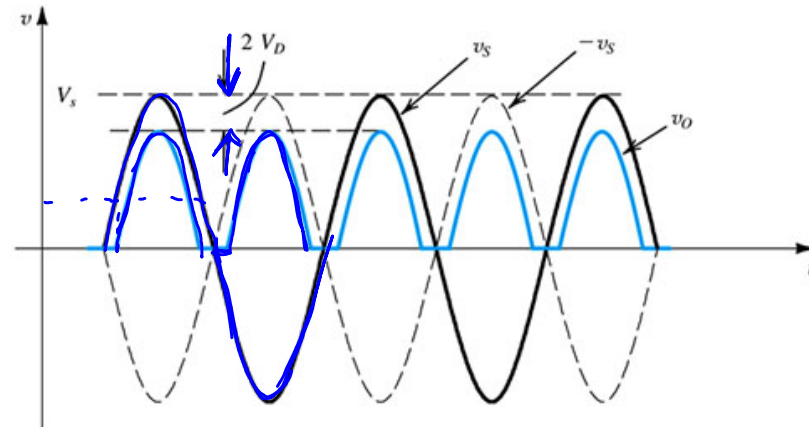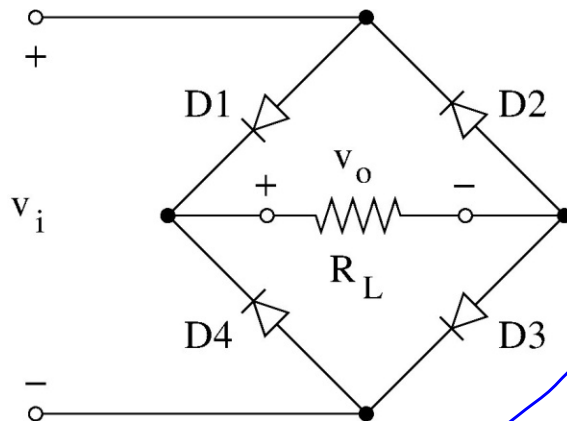

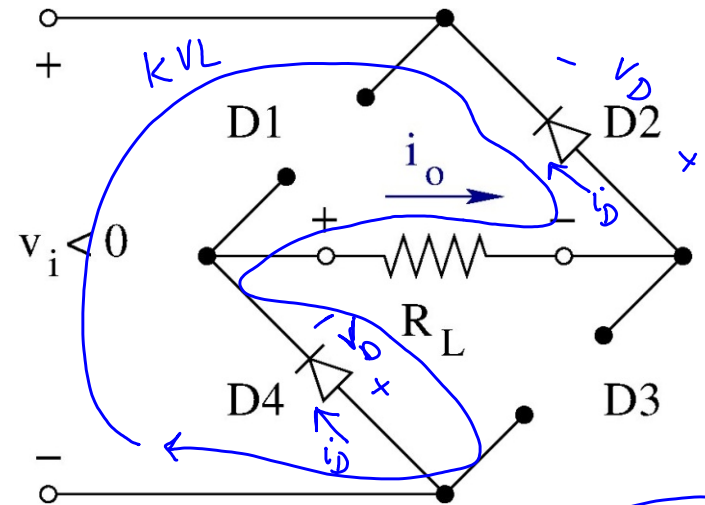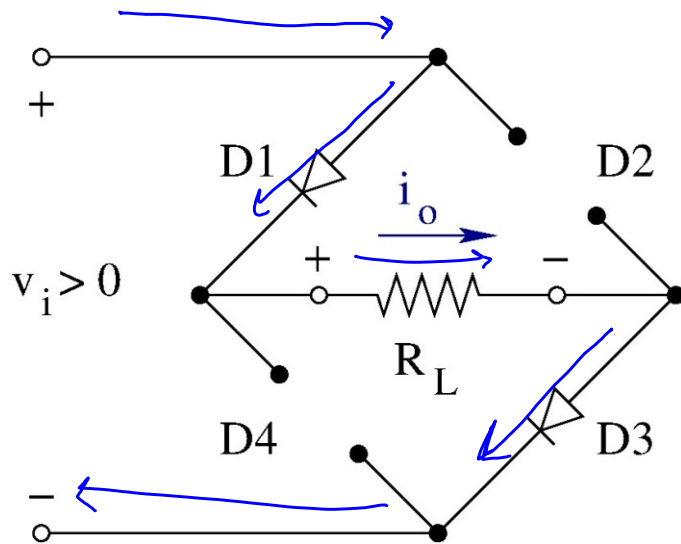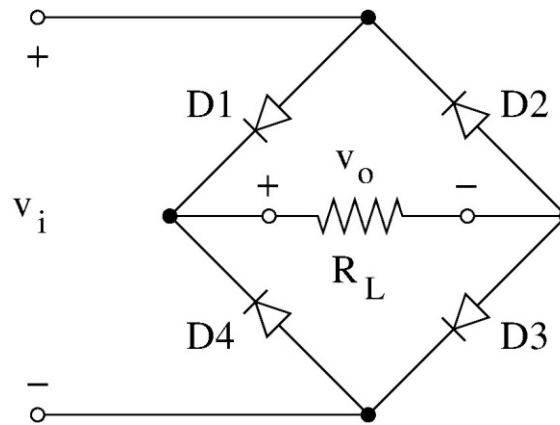Each pair of diodes conduct only for half of the cycle





$$-v_i - v_{D_0} - v_o - v_{D_0} = 0 \rightarrow v_o = -v_i - 2v_{D_0}$$



$$v_i \leq -2v_{D_0}$$

Lecture 6 reading quiz

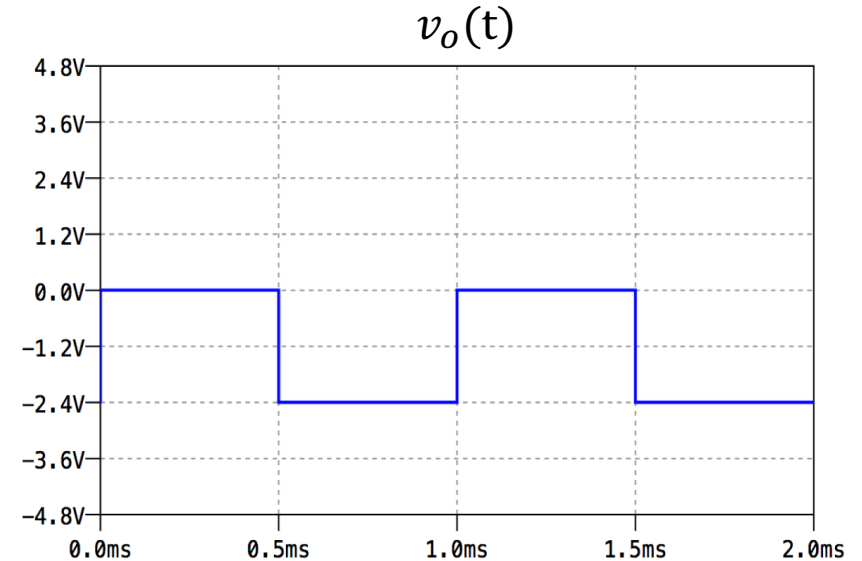
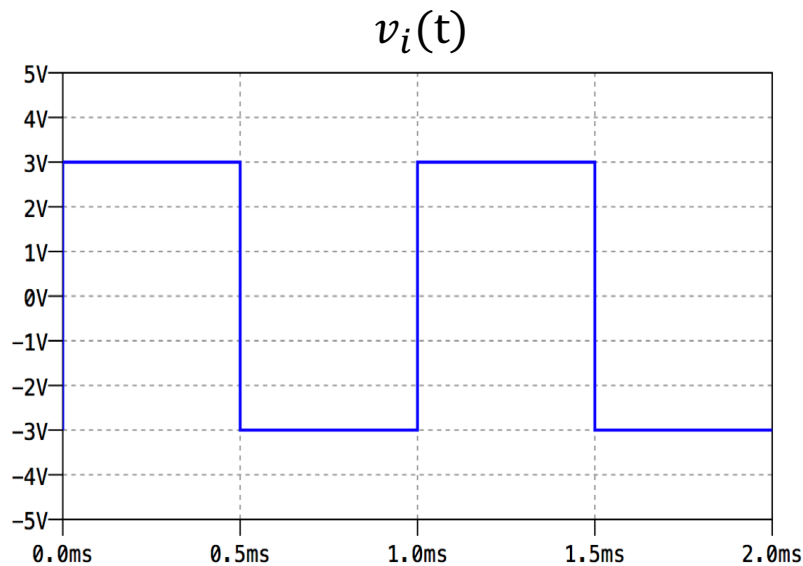
Which one of the circuits in the provided options could produce the shown output waveform for the given input signal?


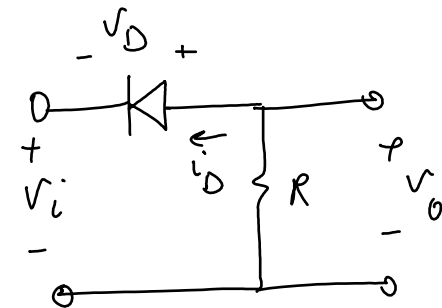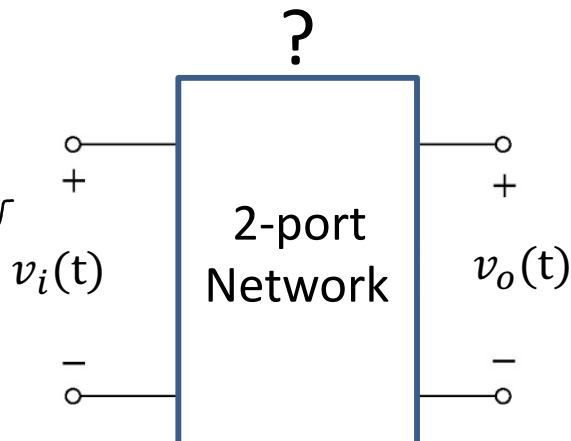
$$\left\{ \begin{array}{l} \text{for } v_i = +3\text{V} \rightarrow v_o = 0 \\ \text{for } v_i = -3\text{V} \rightarrow v_o = v_i + 0.6\text{V} \end{array} \right.$$




Block Diagram of a DC Power Supply

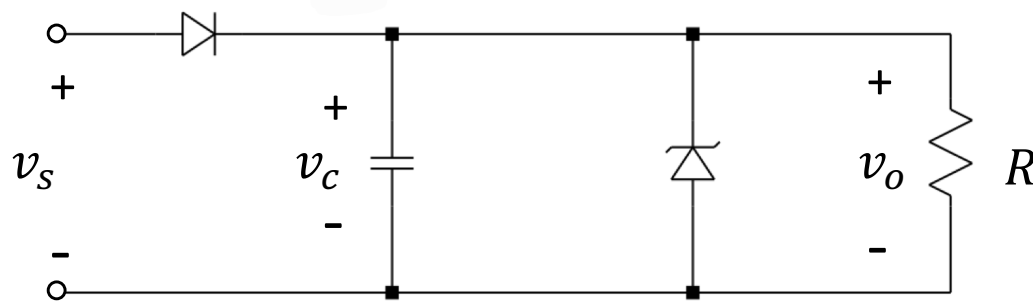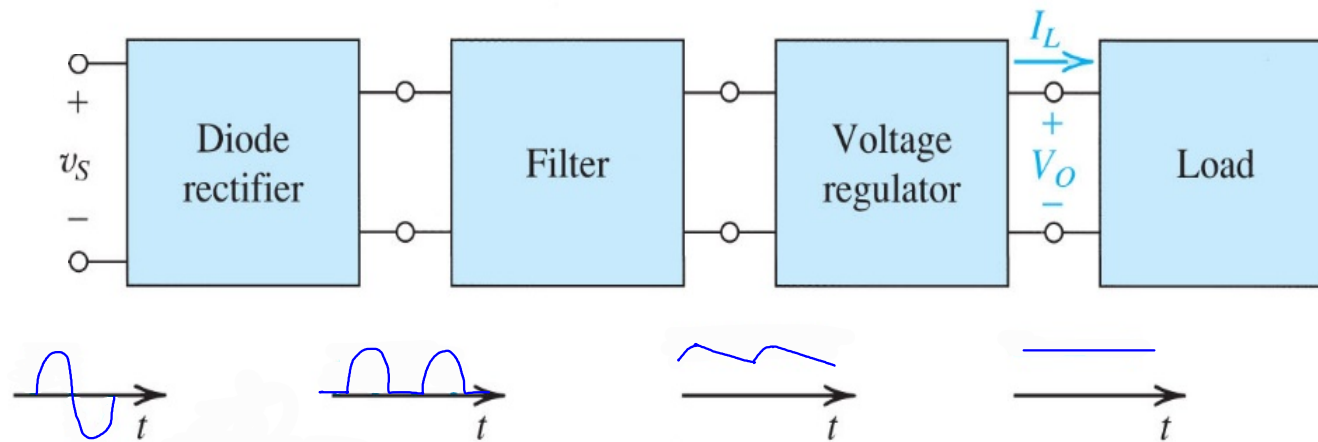

Discussion question 1.

Plot the transfer function of the following circuit. Find v_o for different ranges of v_i and plot a graph that shows the relationship between v_i and v_o . Assume $V_{D0} = 0.7\text{ V}$, $V_Z = 4\text{ V}$.

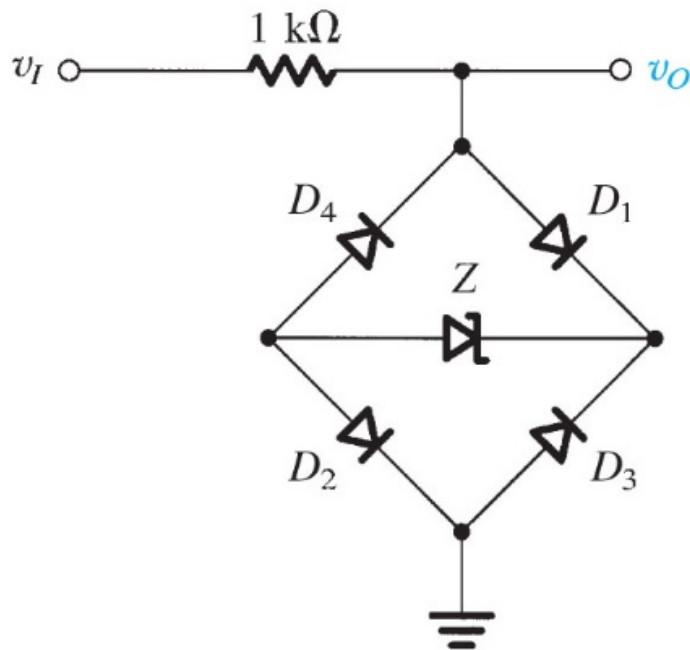

Case 1:

D_1 and D_2 ON, D_5 in the Zener mode, D_3 and D_4 off

Case 2:

D_1 and D_2 Off, D_5 in the Zener mode, D_3 and D_4 ON

Case 3:


D_1 , D_2 , D_5 , D_3 , and D_4 all off

Extra activity:

Draw the output voltage waveform if $v_i = 2 \sin(\omega t)$.

There are three possible cases for the operation of the diodes:

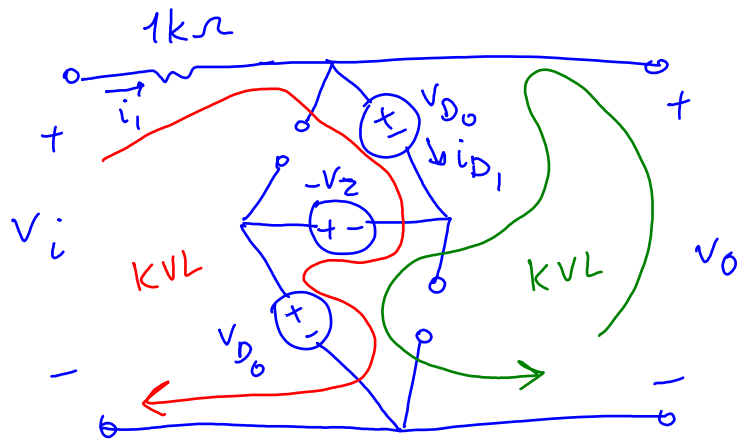Case 1: D_1 and D_2 are ON and D_5 is in Zener region. D_3 and D_4 are off



$$\text{KVL: } -V_i + 1k\Omega \times i_1 + V_{D_0} - (-V_Z) + V_{D_0} = 0$$

$$i_1 = i_{D_1}$$

$$D_1 \text{ is ON} \rightarrow i_{D_1} \geq 0$$

$$\rightarrow i_{D_1} = \frac{V_i - 2V_{D_0} - V_Z}{R} \geq 0$$

$$\Rightarrow V_i \geq 2V_{D_0} + V_Z$$

KVL:


$$-V_o + V_{D_0} - (-V_Z) + V_{D_0} = 0$$

$$\Rightarrow V_o = 2V_{D_0} + V_Z$$

Case 2:

D_3 and D_4 are ON and D_5 is in Zener region.

D_1 and D_2 are off

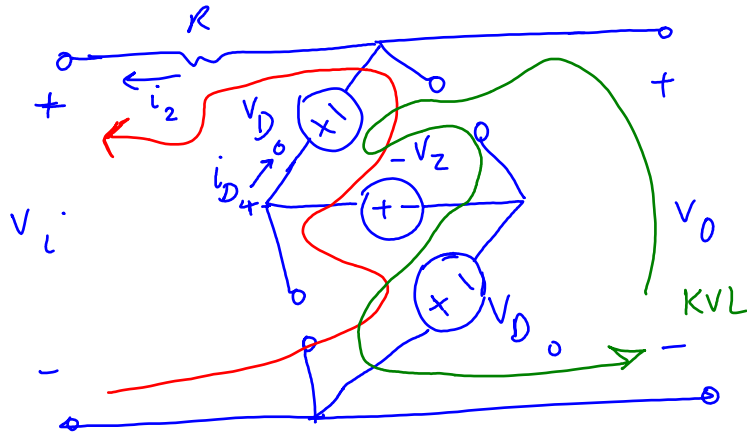

KVL: $+V_{D_6} - (-V_Z) + V_{D_6} + R i_2 + V_i = 0$

$$i_2 = i_{D_4}$$

$$D_4 \text{ is ON} \rightarrow i_{D_4} \geq 0$$

$$\rightarrow i_{D_4} = \frac{-V_i - 2V_{D_0} - V_Z}{R} \geq 0$$

$$\Rightarrow V_i \leq -2V_{D_0} - V_Z$$

KVL:

$$-V_o - V_{D_0} + (-V_Z) - V_{D_0} = 0$$



$$V_o = -2V_{D_0} - V_Z$$

Case 3:

All the diodes are off. $i = 0$

$$V_o = -R i + V_i \rightarrow V_o = V_i$$
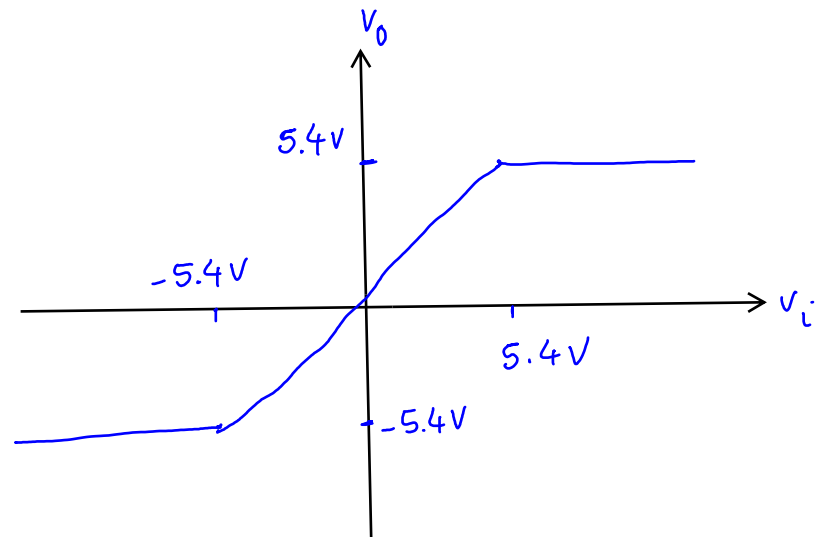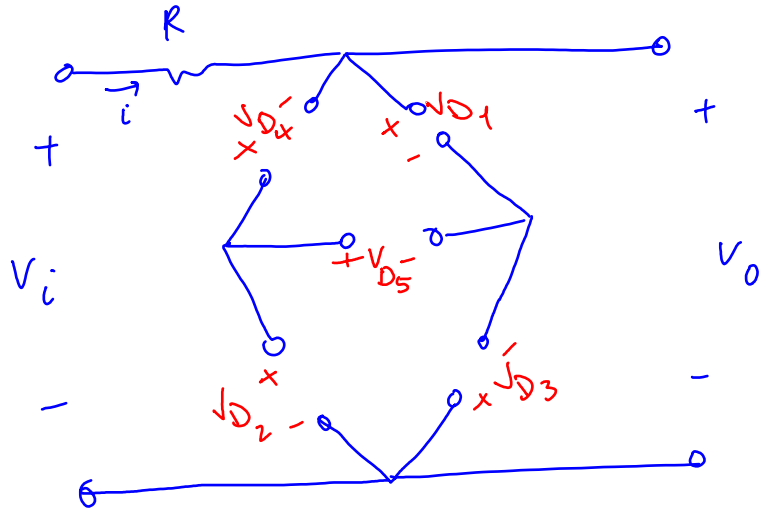
$$-2V_{D_0} - V_Z < V_i < 2V_{D_0} + V_Z$$



We will use the transfer function to draw the output of the circuit for

$$v_i(t) = 2 \sin(\omega t)$$

Amplitude of v_i changes between $+2V$ and $-2V$

$$\Rightarrow V_o = 2 \sin(\omega t)$$

