
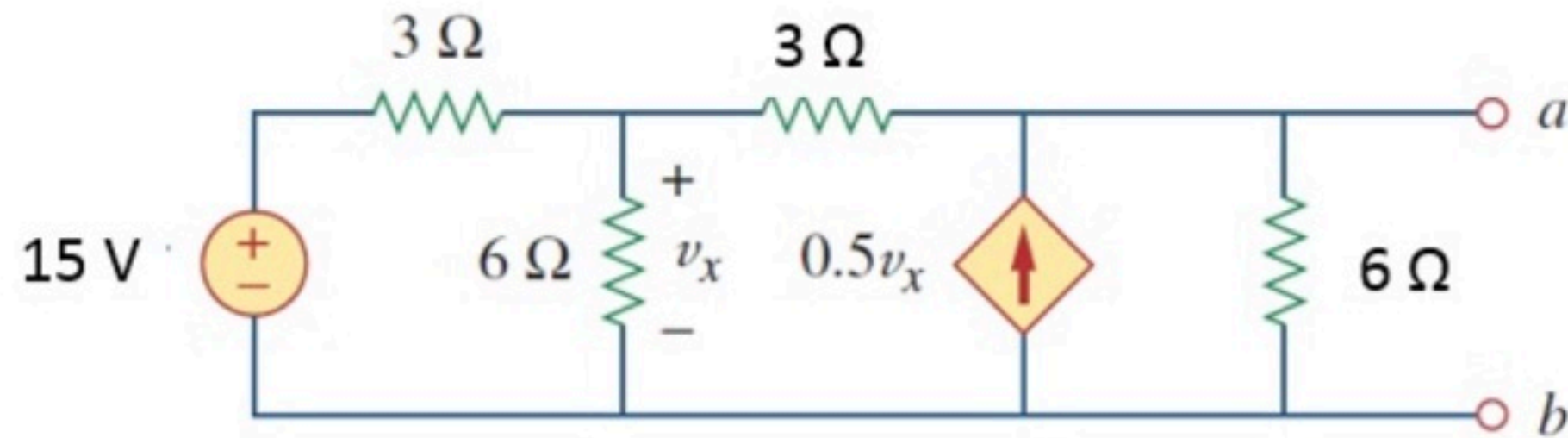


PP Circuit theorems 022

Unlimited Attempts.

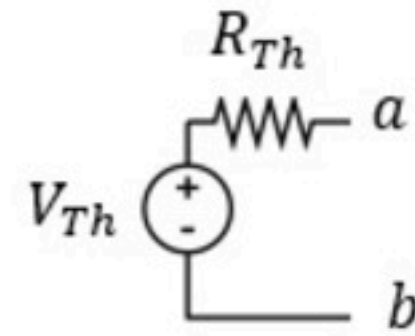Find the Thevenin equivalent model of this circuit, as seen between a and b.



Given Variables:

...

Calculate the following:

V_{th} (V) :

30



R_{th} (ohm) :

6



Hint: Find I_{sc} and V_{oc} .