

# Phasors 005

Unlimited Attempts.

Each voltage-current pair below is the voltage across an element and the current through that element, adhering to the passive sign convention ( $\omega$  is in units of rad/s).

$$v_1(t) = A_1 \cdot \cos(400t + 25^\circ) \quad i_1(t) = B_1 \cdot \sin(400t + 25^\circ)$$

$$v_2(t) = A_2 \cdot \sin(500t + 70^\circ) \quad i_2(t) = B_2 \cdot \sin(500t + 160^\circ)$$

$$v_3(t) = A_3 \cdot \cos(700t + 30^\circ) \quad i_3(t) = B_3 \cdot \sin(700t + 120^\circ)$$

For each element:

- Indicate the type of element. Enter 1 for resistor, 2 for inductor, and 3 for capacitor.
- Find the value of the element. Assume the units are  $\text{m}\Omega$ ,  $\text{mH}$  or  $\text{mF}$  respectively.

Given Variables:

A1 : 12 V

B1 : 3 A

A2 : 20 V

B2 : 4 A

A3 : 2 V

B3 : 4 A

Calculate the following:

Type 1 (.) :

2



Value 1 (.) :

10



Type 2 (.) :

3



Value 2 (.) :

0.4



Type 3 (.) :

1



Value 3 (.) :

500



Each voltage-current pair below is the voltage across an element and the current through that element, adhering to the passive sign convention.

$$v_1(t) = A_1 \cdot \cos(400t + 25)$$

$$i_1(t) = B_1 \cdot \sin(400t + 25)$$

$$v_2(t) = A_2 \cdot \sin(500t + 70)$$

$$i_2(t) = B_2 \cdot \sin(500t + 160)$$

$$v_3(t) = A_3 \cdot \cos(700t + 30)$$

$$i_3(t) = B_3 \cdot \sin(700t + 120)$$

$$A1 : 16 V$$

$$B1 : 2 A$$

$$A2 : 32 V$$

$$B2 : 8 A$$

$$A3 : 3 V$$

$$B3 : 30 A$$

For each element:

- a) Indicate the type of element. Enter 1 for resistor, 2 for inductor, and 3 for capacitor.

- b) Find the value of the element. Assume the units are  $m\Omega$ ,  $mH$  or  $mF$  respectively.

$$\sin(\alpha) = \cos(\alpha - 90^\circ)$$

$$V = Z \cdot I$$

$$Z_L = j\omega L \Rightarrow \angle Z = 90^\circ$$

$$Z_C = \frac{1}{j\omega C} \Rightarrow \angle Z = -90^\circ$$

$$Z_R = R \Rightarrow \angle Z = 0^\circ$$

$$(1) \quad V_1 = 16 e^{j25^\circ} \quad I_1 = 2 e^{j(25^\circ - 90^\circ)}$$

$$\angle Z_1 = \angle V_1 - \angle I_1 = 25^\circ - (25^\circ - 90^\circ) = 90^\circ$$

$$|Z_1| = \frac{|V_1|}{|I_1|} = \frac{16}{2} = \omega L \Rightarrow L = \frac{16}{2\pi f} \cdot \frac{1}{400}$$

INDUCTOR

L = 20 mH

$$(2) \quad V_2 = 32 e^{j(70^\circ - 90^\circ)} \quad I_2 = 8 e^{j(160^\circ - 90^\circ)}$$

$$\angle Z_2 = \angle V_2 - \angle I_2 = (70^\circ - 90^\circ) - (160^\circ - 90^\circ) = -90^\circ$$

$$|Z_2| = \frac{|V_2|}{|I_2|} = \frac{32}{8} = \frac{1}{\omega C} \Rightarrow C = \frac{1}{500} \cdot \frac{8}{32}$$

CAPACITOR

C = 0.5 mF

$$(3) \quad V_3 = 3 e^{j30^\circ} \quad I_3 = 30 e^{j(120^\circ - 90^\circ)}$$

$$\angle Z_3 = \angle V_3 - \angle I_3 = 30^\circ - (120^\circ - 90^\circ) = 0^\circ \Rightarrow$$

RESISTOR

$$|Z_3| = \frac{|V_3|}{|I_3|} = \frac{3}{30} = R \Rightarrow R = \frac{1}{10}$$

R = 100 m\Omega


# Phasors 006

Problem has been graded.

Find the steady-state currents  $i_1(t)$  and  $i_2(t)$ .

$$i_1(t) = A_1$$
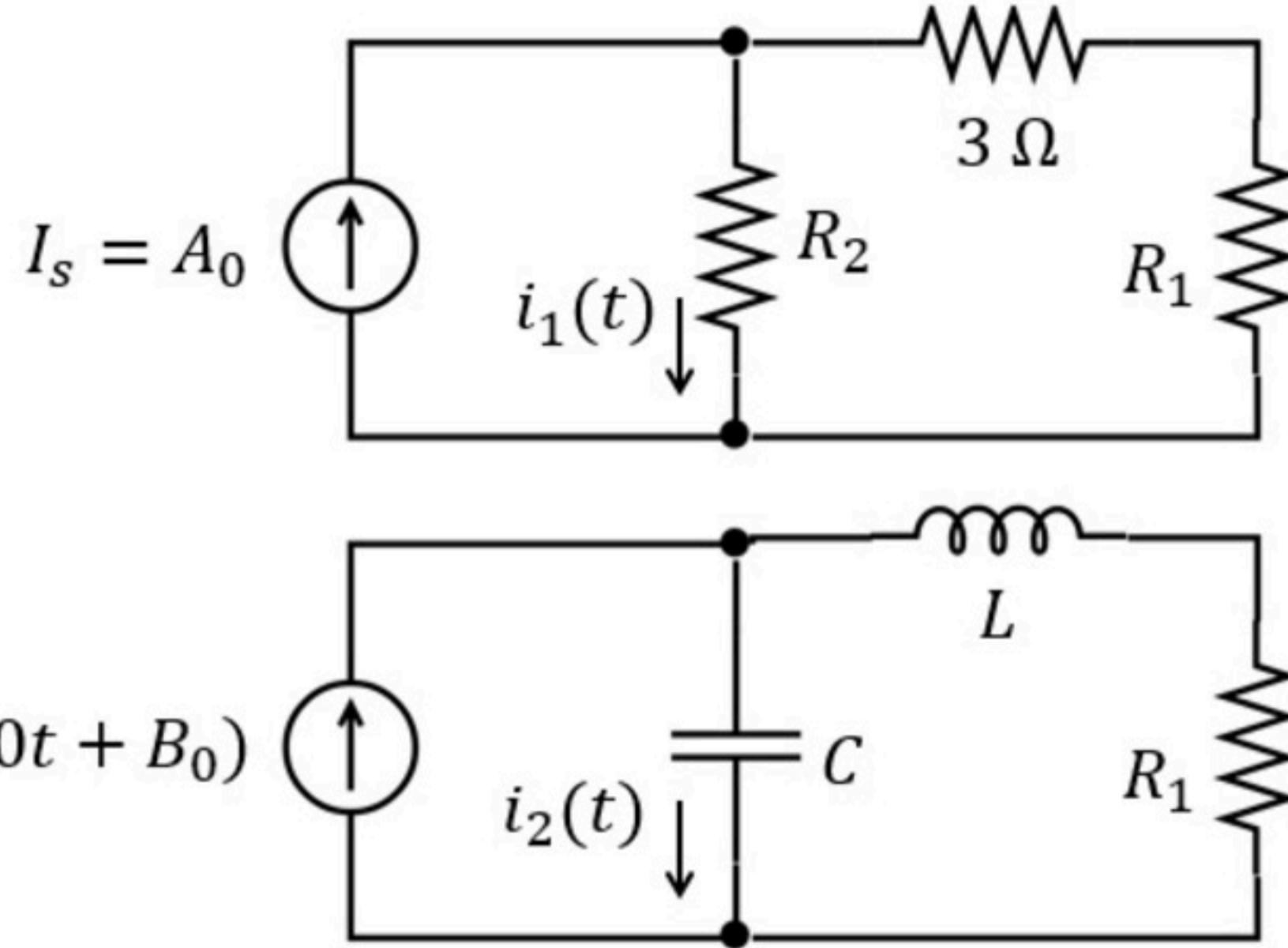
$$i_2(t) = A_2 \cos(1000t + B_2) \quad \text{with } -180^\circ < B_2 \leq 180^\circ$$



Given Variables:

A0 : 2 A

B0 : 25 degrees

C : 200 uF

L : 3 mH

R1 : 6 ohm

R2 : 3 ohm

Calculate the following:

A1 (A) :

1.5



A2 (A) :

1.5



B2 (degrees) :

70



Find the steady-state currents  $i_1(t)$  and  $i_2(t)$ .


A0 : 2 A

$$i_1(t) = A_1$$


B0 : 20 degrees

$$i_2(t) = A_2 \cos(1000t + B_2) \quad \text{with } -180^\circ < B_2 \leq 180^\circ$$

C : 250  $\mu\text{F}$

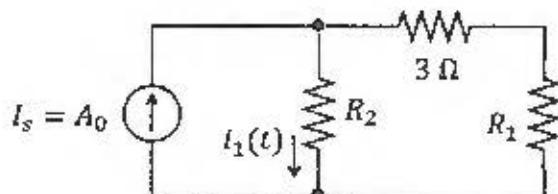

L : 4 mH

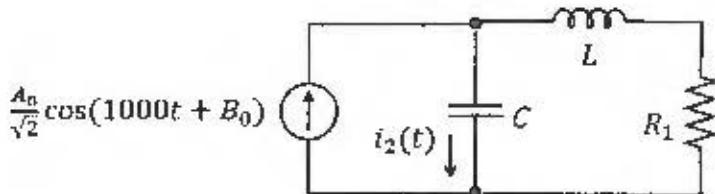


R1 : 4 ohm

R2 : 3 ohm

$$\textcircled{1} \text{ CURRENT DIVIDER. } I_1 = 2 \cdot \frac{3+4}{3+4+3} = \frac{14}{10}$$

$$A_1 = 1.4 \text{ A}$$

\textcircled{2}

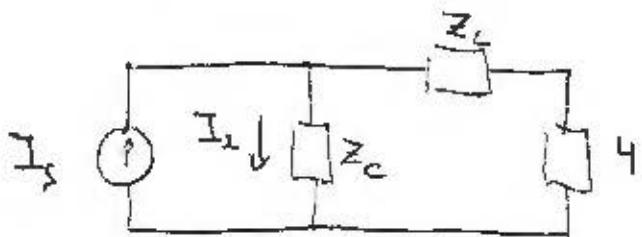

$$Z_L = j\omega L = j 1000 \cdot 4 \cdot 10^{-3} \\ = 4j$$

$$Z_C = \frac{1}{j\omega C} = \frac{1}{j 1000 \cdot 250 \cdot 10^{-6}} \\ = -4j$$

$$I_2 = I_s \cdot \frac{4j+4}{4j+4-4j} = I_s \cdot \frac{4(1+j)}{4} = \frac{2}{\sqrt{2}} e^{j20^\circ} \sqrt{2} e^{j45^\circ}$$

$$I_2 = 2 e^{j65^\circ}$$

$$i_2(t) = 2 \cos(1000t + 65^\circ)$$

$$A_2 = 2 \text{ A}$$

$$B_2 = 65^\circ$$

# Phasors 007


Problem has been graded.

$$v_s(t) = A_1 \sqrt{2} \cdot \cos(W_1 t + B_1)$$

$$i_s(t) = 2 \cdot \cos(W_1 t - 90^\circ) \quad \text{A}$$

Find steady state voltage
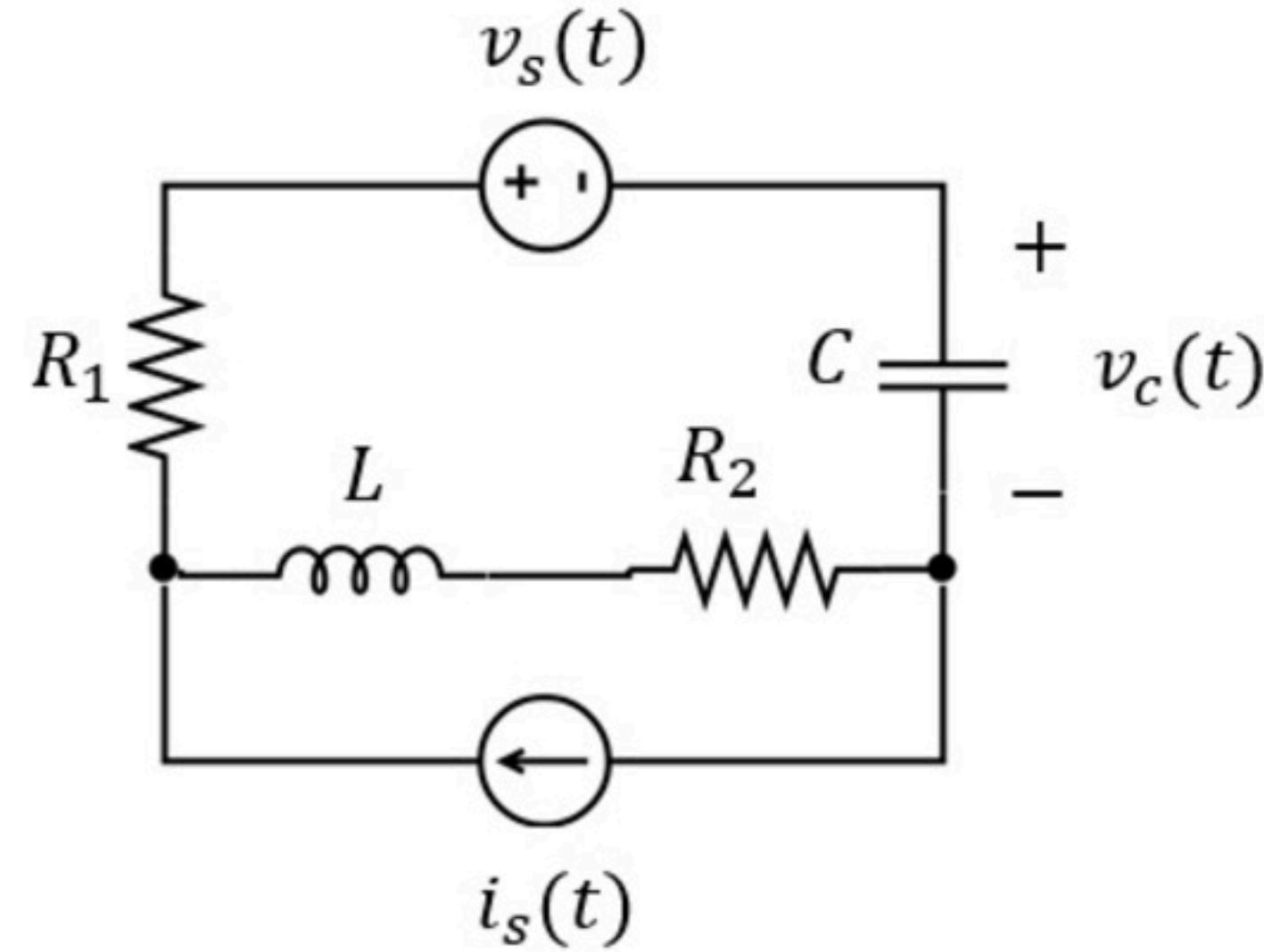
$$v_c(t) = A_2 \sqrt{2} \cdot \cos(W_2 t + B_2) \quad \text{with } -180^\circ < B_2 \leq 180^\circ$$



Given Variables:

A1 : 14 V

B1 : -45 degrees

W1 : 2000 (1/s)

C : 125 uF

L : 2 mH

R1 : 4 ohm

R2 : 4 ohm

Calculate the following:

A2 (V) :

3



B2 (degrees) :

45



W2 (1/s) :

2000



Hint: We do not need to use superposition, but we could if we wanted to.

$$v_s(t) = A_1 \sqrt{2} \cdot \cos(W_1 t + B_1)$$

A1 : 32 V

$$i_s(t) = 2 \cdot \cos(W_1 t - 90^\circ) \quad A$$


B1 : -45 degrees

Find steady state voltage

W1 : 2000 1/s

$$v_c(t) = A_2 \sqrt{2} \cdot \cos(W_2 t + B_2) \quad \text{with } -180^\circ < B_2 \leq 180^\circ$$


C : 125  $\mu F$

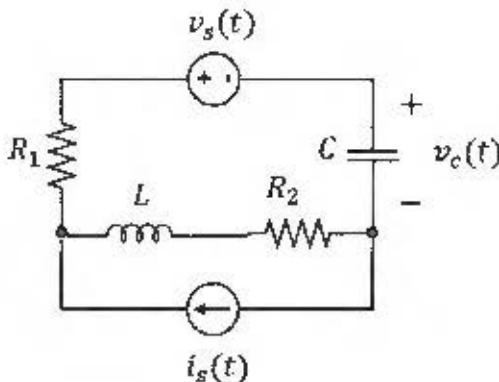

L : 2 mH

R1 : 4 ohm

R2 : 4 ohm

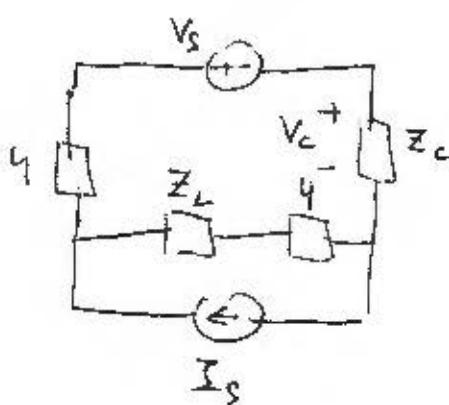

$$Z_C = \frac{1}{j\omega C} = \frac{10^6}{j2000 \cdot 125} = -4j$$

$$Z_L = j\omega L = j2000 \cdot 2 \cdot 10^{-3} = 4j$$

$$V_s = 32\sqrt{2} e^{-j45^\circ} = 32V_1 \left( \frac{\sqrt{2}}{2} - j \frac{\sqrt{2}}{2} \right) \\ = 32 - 32j$$

$$I_S = 2 e^{-j90^\circ} = -2j$$

$$\textcircled{1} \quad \underline{\text{ONLY } V_s} \quad V_{c_1} = -V_s \cdot \frac{Z_C}{Z_C + Z_L + 4 + 4} = \frac{(-32 + 32j) \cdot (-4j)}{-4j + 4j + 4 + 4} = \frac{-32 + 32j}{8} \\ = 16 + 16j$$

$$\textcircled{2} \quad \underline{\text{ONLY } I_S} : \quad V_{c_2} = I_S \cdot \frac{Z_L + 4}{Z_L + 4 + Z_C + 4} Z_C = (-2j) \frac{4 + 4j}{4 - 4j + 4j + 4} \cdot (-4j) \\ = -\frac{8(4 + 4j)}{8} = -4 - 4j$$

$$\textcircled{3} \quad \underline{\text{SUPERPOSITION}} : \quad V_c = V_{c_1} + V_{c_2} = 16 + 16j = 16\sqrt{2} e^{j45^\circ}$$

$$V_c(t) = 16\sqrt{2} \cos(2000t + 45^\circ)$$

$A_2 = 12V$
$B_2 = 45^\circ$

$W_2 = 2000 \frac{1}{s}$
--------------------------


# Phasors 008

Unlimited Attempts.

$$v_s(t) = A_1 \cdot \cos(1000t)$$

Find steady state voltage
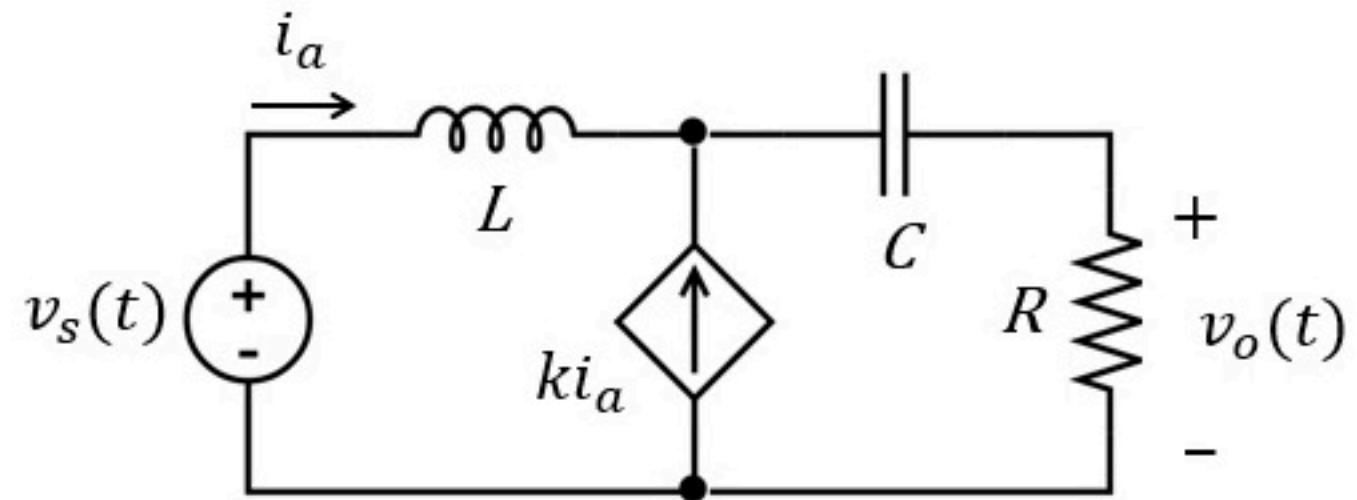
$$v_o(t) = A_2 \sqrt{2} \cdot \cos(1000t + B_2) \quad \text{with } -180^\circ < B_2 \leq 180^\circ$$



Given Variables:

A1 : 5 V

L : 20 mH

C : 20 uF

R : 45 ohm

k : 3 A/A

Calculate the following:

A2 (V) :

2.5



B2 (degrees) :

45



$$v_s(t) = A_1 \cdot \cos(1000t)$$

$$A_1 : 2 \text{ V}$$

Find steady state voltage


$$v_o(t) = A_2 \sqrt{2} \cdot \cos(1000t + B_2) \quad \text{with } -180^\circ < B_2 \leq 180^\circ$$

$$L : 150 \text{ mH}$$


$$C : 20 \mu\text{F}$$

$$R : 25 \text{ ohm}$$

$$k : 1 \text{ A/A}$$

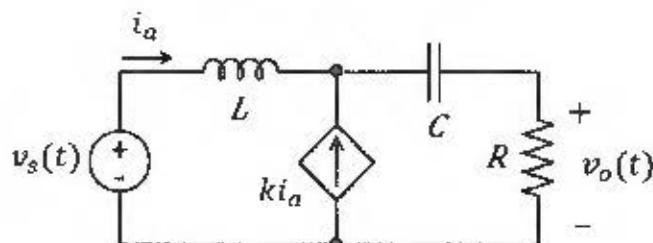

$$I_i = I_a + I_a = 2 I_a$$

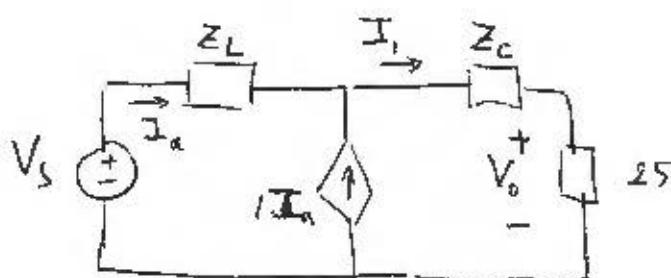

$$Z_L = j\omega L = j 150$$

$$Z_c = \frac{1}{j\omega C} = -j 50$$

$$V_s = 2$$

$$\underline{\text{KVL}}: V_s - I_a \cdot Z_L = I_i (Z_c + 25) = 2 I_a (Z_c + 25)$$

$$\Rightarrow I_a = \frac{V_s}{Z_L + 2 Z_c + 50} = \frac{V_s}{150j - 100j + 50} = \frac{V_s}{50 + 50j}$$

$$V_o = I_i \cdot 25 = 2 I_a \cdot 25 = \frac{50 \cdot V_s}{50 + 50j} = \frac{2}{1+j}$$

$$= \frac{2}{\sqrt{2}} e^{-j45^\circ} = \sqrt{2} e^{-j45^\circ}$$

$$v_o(t) = \sqrt{2} \cos(1000t - 45^\circ)$$

$$A_2 = 1 \text{ V}$$

$$B_2 = -45^\circ$$

# Phasors 009


0 of 5 attempts made

$$i_s(t) = A_1 \cdot \cos\left(1000t + \frac{\pi}{2}\right) + A_2 \cdot \cos\left(2000t - \frac{\pi}{2}\right)$$

Assume the system is in steady state. Find the current  $i_a$  at times

$$t_1 = 4\pi \text{ ms: } i_a(t_1) = B_1$$
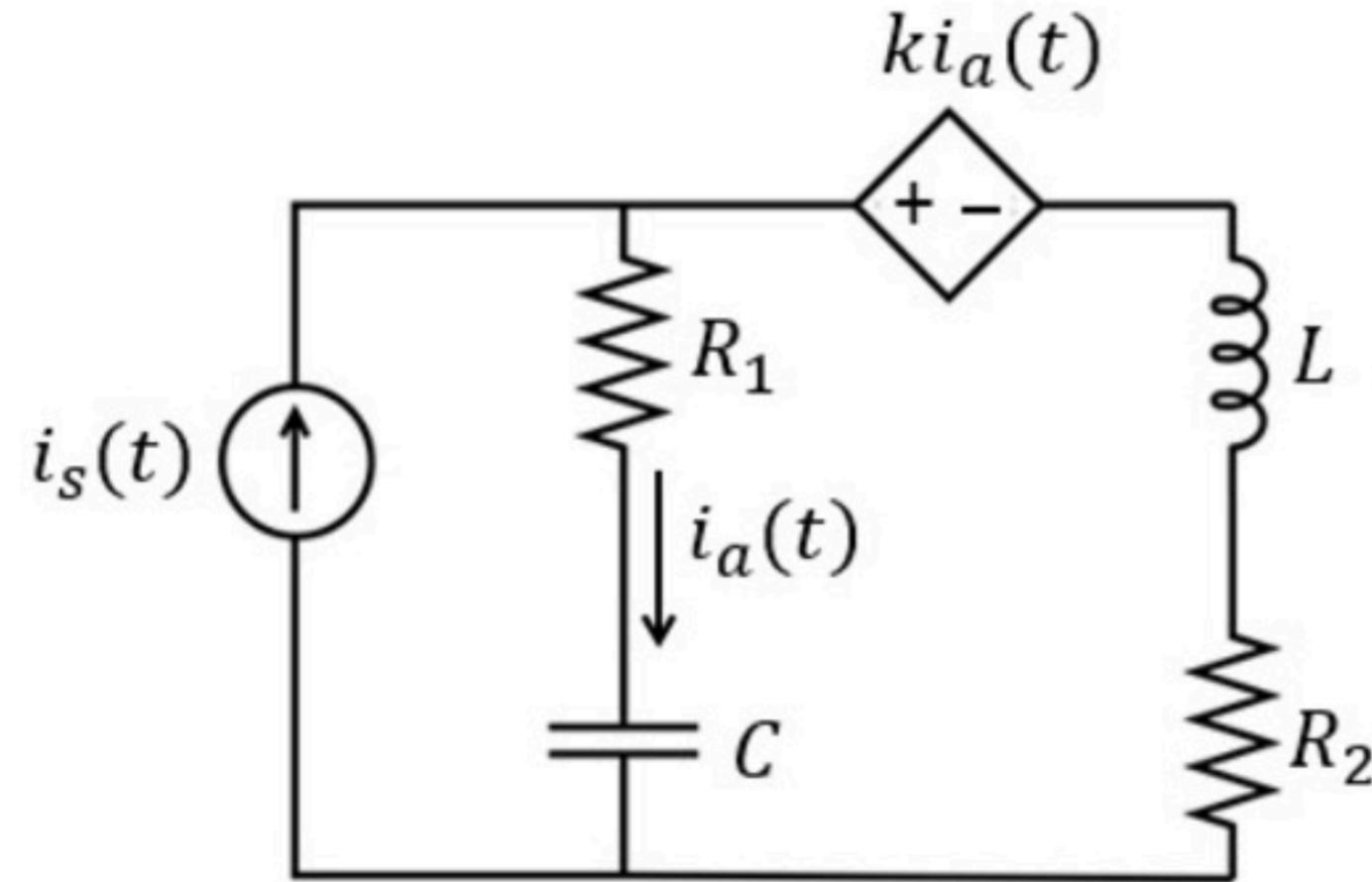
$$t_2 = 5\pi \text{ ms: } i_a(t_2) = B_2$$



Given Variables:

A1 : 1 A

A2 : 1 A

L : 1 mH

C : 250 uF

R1 : 1 ohm

R2 : 2 ohm

k : 4 V/A

Calculate the following:

B1 (A) :

-2.5



B2 (A) :

-1.5



$$i_s(t) = A_1 \cdot \cos(1000t + 90^\circ) + A_2 \cdot \cos(2000t - 90^\circ)$$

A1 : 6 A

Assume the system is in steady state. Find the current  $i_a$  at times


A2 : 9 A

$$t_1 = 4\pi \text{ ms}: i_a(t_1) = B_1$$

L : 1 mH

$$t_2 = 5\pi \text{ ms}: i_a(t_2) = B_2$$

C : 250 μF

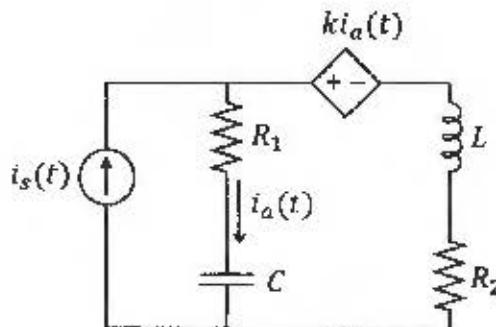

2 DIFFERENT  $\omega$  !

WE NEED TO  
USE SUPERPOSITION

R1 : 8 ohm

R2 : 2 ohm

k : 1 V/A

$$\underline{\omega = 1000}, \quad Z_L = j \cdot 1000 L = j$$


$$Z_C = \frac{1}{j \omega C} = -4j$$

$$I_s = 6 e^{j\frac{\pi}{2}} = 6j$$

$$Z_L = j 2000 L = 2j$$

$$Z_C = \frac{1}{j 2000 C} = -2j$$

$$I_s = 9 e^{-j\frac{\pi}{2}} = -9j$$

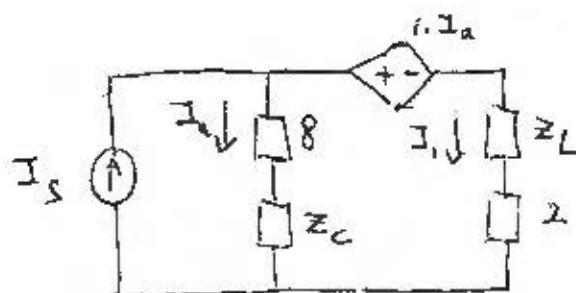

$$\underline{\omega = 2000}$$

$$I_a = I_s - I_{a_1} \Rightarrow I_a (8 + Z_C) = 1 \cdot I_{a_1} + (I_s - I_{a_1})(2 + Z_L)$$

$$\Rightarrow I_{a_1} = I_s - \frac{2 + Z_L}{9 + Z_C + Z_L}$$

$$\textcircled{1} \quad \underline{\omega = 1000}: \quad I_{a_1} = 6j \frac{(2+j)}{(9-4j+j)} = \frac{6(-1+2j)}{3(3-j)(3+j)} = \frac{2}{10} (-5+5j) = -1+j$$

$$i_{a_1}(t) = \sqrt{2} \cos(1000t + 135^\circ)$$

$$\textcircled{2} \quad \underline{\omega = 2000}: \quad I_{a_1} = (-9j) \frac{2+2j}{9+3j-1} = 2(1-j) \Rightarrow i_{a_1}(t) = 2\sqrt{2} \cos(2000t - 45^\circ)$$

$$\textcircled{3} \quad i_a(t) = i_{a_1}(t) + i_{a_2}(t) = \sqrt{2} \cos(1000t + \frac{3\pi}{4}) + 2\sqrt{2} \cos(2000t - \frac{\pi}{4})$$

$$\textcircled{4} \quad E = 4\pi \cdot 10^{-3} \quad i_a = \sqrt{2} \cos(4\pi + \frac{3\pi}{4}) + 2\sqrt{2} \cos(8\pi - \frac{\pi}{4}) = \sqrt{2} \cos(\frac{11\pi}{4}) + 2\sqrt{2} \cos(-\frac{\pi}{4}) \\ = \sqrt{2} \left(-\frac{\sqrt{2}}{2}\right) + 2\sqrt{2} \left(\frac{\sqrt{2}}{2}\right) = -1 + 2 = 1 \quad \boxed{B_1 = 1 \text{ A}}$$

$$E = 5\pi \cdot 10^{-3}, \quad i_a = \sqrt{2} \cos(5\pi + \frac{3\pi}{4}) + 2\sqrt{2} \cos(10\pi - \frac{\pi}{4}) = \sqrt{2} \cos(-\frac{\pi}{4}) + 2\sqrt{2} \cos(-\frac{\pi}{4})$$

$$= \sqrt{2} \left(\frac{\sqrt{2}}{2}\right) + 2\sqrt{2} \left(\frac{\sqrt{2}}{2}\right) = 1 + 2 = 3$$

$$\boxed{B_2 = 3 \text{ A}}$$


# Phasors 010

Problem has been graded.

$$v_s(t) = A_1 \cdot \cos(100t) \quad \text{and} \quad i_s(t) = A_2$$

Find  $i_a(t) = A_3\sqrt{2} \cdot \cos(100t + B_3) + A_4$

with  $-180^\circ < B_3 \leq 180^\circ$

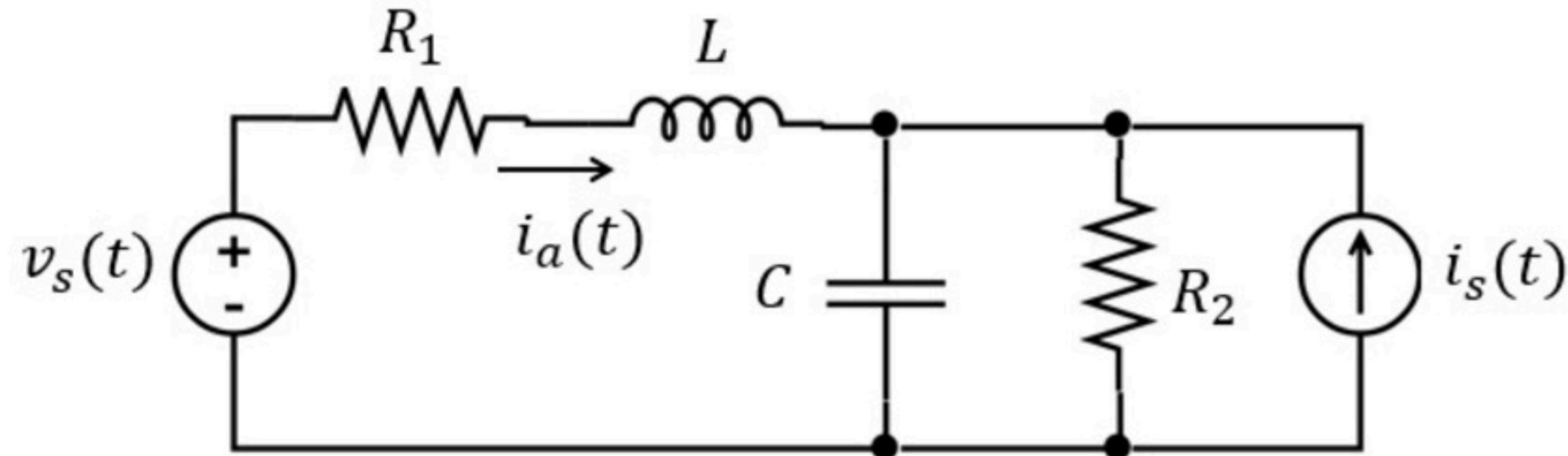

Given Variables:

A1 : 100 V

A2 : 6 A

C : 0.1 mF

L : 1.5 H

R1 : 50 ohm

R2 : 100 ohm

Calculate the following:

A3 (A) :

0.5



B3 (degrees) :

-45



A4 (A) :

-4



Hint: Use superposition

$$v_s(t) = A_1 \cdot \cos(100t) \quad \text{and} \quad i_s(t) = A_2$$

A1 : 100 V

$$\text{Find } i_a(t) = A_3 \sqrt{2} \cdot \cos(100t + B_3) + A_4$$

$$\text{with } -180^\circ < B_3 \leq 180^\circ$$


A2 : 6 A

C : 0.1 mF

L : 1.5 H

R1 : 50 ohm

R2 : 100 ohm

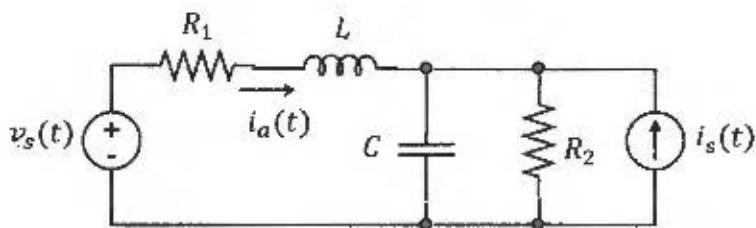


DIFFERENT  $\omega$  ! WE NEED TO USE SUPERPOSITION

①  $i_s(t)$  ONLY :  $\omega = 0$  DC  $\Rightarrow$  L SHORT / C OPEN



$$E_{u_1} = -\frac{100}{100+50} \cdot 6 = -4 \text{ A}$$

②  $v_s(t)$  ONLY :  $\omega = 100$

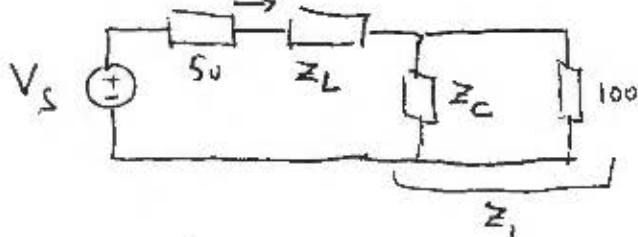

$$Z_L = j 100 L = 150 j$$

$$Z_C = \frac{1}{j 100 C} = -100 j$$

$$V_s = 100$$

$$Z_i = \frac{1}{\frac{1}{100} + \frac{1}{-j 100}} = \frac{100}{1+j} = 50(1-j)$$

$$I_u = \frac{V_s}{Z_i + 50 + Z_L} = \frac{100}{50 - 50j + 50 + 150j} = \frac{100}{100 + 100j} = \frac{\sqrt{2}}{2} e^{-j45^\circ}$$

$$i_{a_2} = \frac{\sqrt{2}}{2} \cos(100t - 45^\circ)$$

$$③ i_a(t) = i_{a_1} + i_{a_2} = \frac{\sqrt{2}}{2} \cos(100t - 45^\circ) - 4$$

$A_3 = 0.5 \text{ A}$
-----------------------

$B_3 = -45^\circ$
-------------------


$A_4 = -4 \text{ A}$
----------------------

# Phasors 011

Unlimited Attempts.

In the circuit below,  $v_s(t) = A_1 \cdot \cos(25 \cdot 10^4 \cdot t)$ .

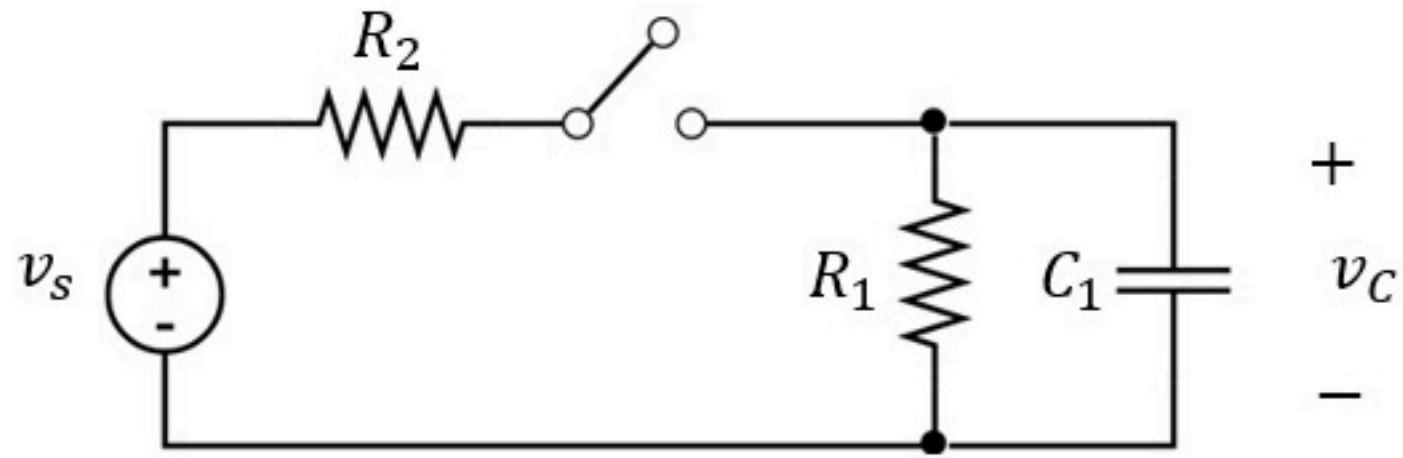The switch is closed for  $t < 0$ , and opens at time  $t = 0$  s.



Find these voltages:

$$v_1 = v_C(0^+) \quad v_2 = v_C(t_0)$$

Note, for your calculations, use:  $e^{-1/1.5} \approx 0.5$

Solve without a calculator

Given Variables:

R1 : 6 kohm

R2 : 12 kohm

C1 : 1 nF

A1 : 12 V

t0 : 8 us

Calculate the following:

v1 (V) :

2



v2 (V) :

0.5




In the circuit below,  $v_s(t) = A_1 \cdot \cos(25 \cdot 10^4 \cdot t)$ .

R1 : 6 kohm

The switch is closed for  $t < 0$ , and opens at time  $t = 0$  s.

R2 : 12 kohm

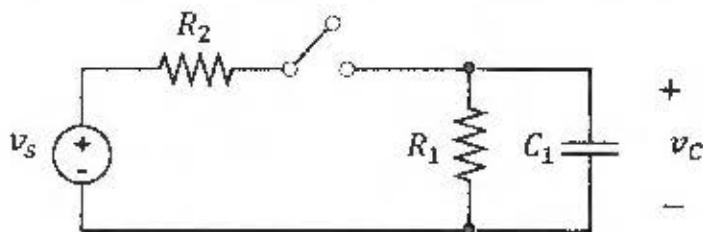

C1 : 1 nF

A1 : 12 V

t0 : 8 us


Find these voltages:

$$v_1 = v_c(0^+) \quad v_2 = v_c(t_0)$$

Note, for your calculations, use:  $e^{-1/1.5} \approx 0.5$

Solve without a calculator

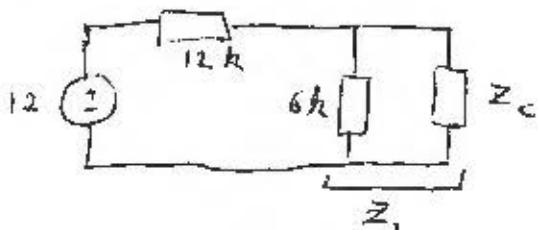①  $t < 0$  ASSUME STEADY STATE ②  $t = 0^-$



$$Z_C = \frac{1}{j 25 \cdot 10^4 \cdot 10^{-9}} = -(4k) \cdot j$$

$$Z_1 = \frac{1}{\frac{1}{6k} + \frac{j}{4k}} = \frac{24k}{4+6j} = \frac{12k}{2+3j}$$

$$V_C = V_S \frac{Z_1}{Z_1 + R_2} = 12 \cdot \frac{12}{12 + 12(2+3j)} = \frac{12}{3+3j} = \frac{4}{1+j} = \frac{4}{\sqrt{2}} e^{-j45^\circ}$$

$$v_c(t) = \frac{4}{\sqrt{2}} \cos(25 \cdot 10^4 t - \frac{\pi}{4}) \Rightarrow v_c(0^-) = \frac{4}{\sqrt{2}} \cos(-\frac{\pi}{4}) = \frac{4}{\sqrt{2}} \cdot \frac{\sqrt{2}}{2} = 2V$$

$$\textcircled{2} \quad \underline{t = 0^+} \quad v_c(0^+) = v_c(0^-) = 2V \Rightarrow \boxed{v_1 = 2V}$$

③  $t > 0$ : TRANSIENT RESPONSE OF RC CIRCUIT

$$v_c(0^+) = 2V \quad R_{TH} = R_1 \Rightarrow Z = R_1 \cdot C$$

$$v_c(\infty) = 0V$$

$$= (6k) \cdot (1n) = 6 \text{ m}\Omega$$

$$v_c(t) = 2 e^{-\frac{t}{6m\Omega}} \quad \text{FOR } t > 0$$

$$v_c(t_0) = v_c(8 \mu s) = 2 e^{-\frac{8}{6}} = 2 \left( e^{-\frac{4}{3}} \right)^2 = \frac{2}{4} = \frac{1}{2}V$$

$$\boxed{v_2 = 0.5V}$$

# Phasors 016


2 of 5 attempts made

The AC circuit below is in steady-state, and you are not told the  $\omega$  of the source. The phasor diagram shows the phasors of  $i_s$  and  $i_a$ .

The rectangular boxes represent two circuit elements. One of them is an inductor  $L_1$  (but you don't know if it corresponds to  $i_a$  or  $i_b$ ). The other can be a resistor  $R_2$ , a capacitor  $C_2$  or an inductor  $L_2$ .

You are also told that the maximum value of  $i_a(t)$  is  $A_1$  and the maximum value of  $i_s(t)$  is  $A_2$ .

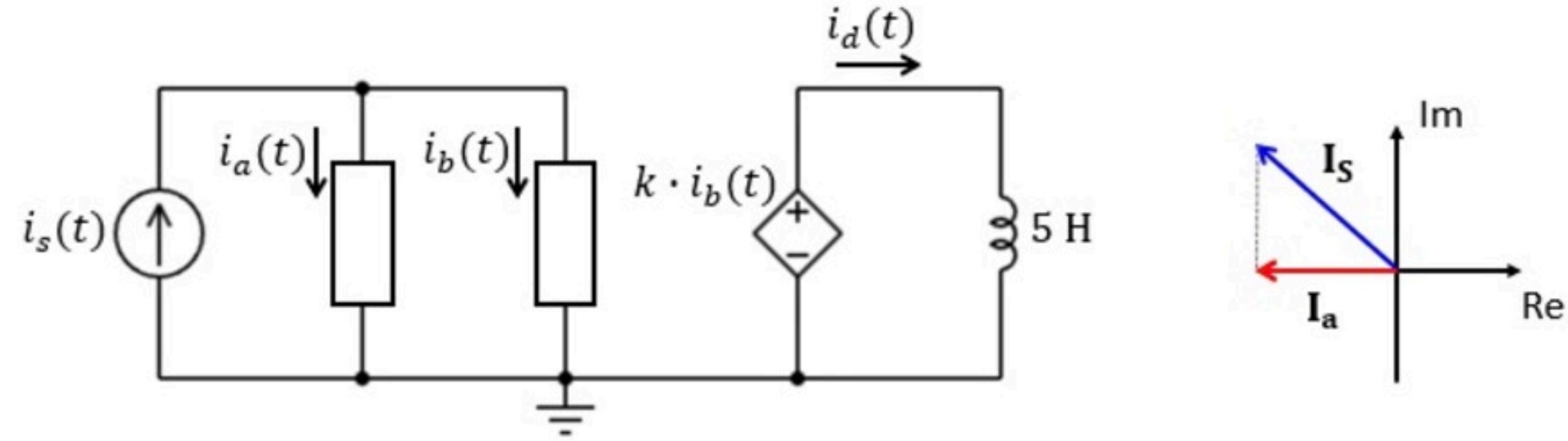- What is the maximum value of the  $i_b(t)$  waveform,  $i_{bmax}$ ?
- With  $i_d(t)$  expressed as  $A \cdot \cos(\omega t + B_1)$ , what is  $B_1$ ? Constraints:  $A > 0$  and  $-180^\circ < B_1 \leq 180^\circ$ .
- What is the value of  $\omega$ ?



Given Variables:

$A_1 : 4 \text{ A}$

$A_2 : 5 \text{ A}$

$L_1 : 2 \text{ mH}$

$R_2 : 3 \text{ ohm}$

$C_2 : 10 \text{ mF}$

$L_2 : 3 \text{ mH}$

$k : -5 \text{ V/A}$

Calculate the following:

$i_{bmax} (\text{A}) :$

3



$B_1 (\text{degrees}) :$

180



$\omega (\text{rad/s}) :$

2000



The AC circuit below is in steady-state, and you are not told the  $\omega$  of the source. The phasor diagram shows the phasors of  $i_s$  and  $i_a$ .



The rectangular boxes represent two circuit elements. One of them is an inductor  $L_1$  (but you don't know if it corresponds to  $i_a$  or  $i_b$ ). The other can be a resistor  $R_2$ , a capacitor  $C_2$  or an inductor  $L_2$ .

You are also told that the maximum value of  $i_a(t)$  is  $A_1$  and the maximum value of  $i_s(t)$  is  $A_2$ .

a. What is the maximum value of the  $i_b(t)$  waveform,  $i_{b,\max}$ ?

b. With  $i_d(t)$  expressed as  $A \cdot \cos(\omega t + B_1)$ , what is  $B_1$ ? Constraints:  $A > 0$  and  $-180^\circ < B_1 \leq 180^\circ$ .

c. What is the value of  $\omega$ ?

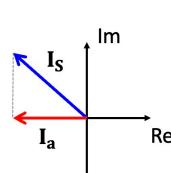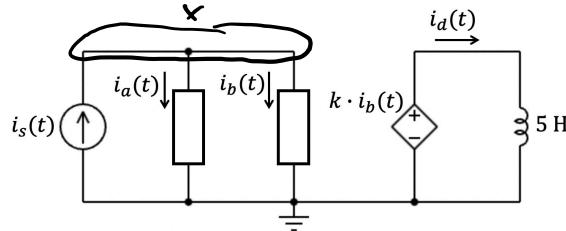

$$A_1 = 4 \text{ A}$$

$$A_2 = 5 \text{ A}$$

$$L_1 = 2 \text{ mH}$$

$$R_2 = 3 \Omega$$


$$C_2 = 10 \text{ mF}$$

$$L_2 = 3 \text{ mH}$$

$$k = -5 \frac{\text{V}}{\text{A}}$$

a. The max value of a sinusoidal waveform is its amplitude  $\Rightarrow i_{b,\max} = |I_b|$
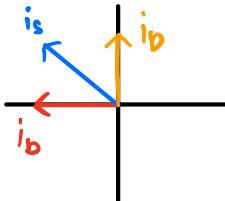
$$\text{KCL at } X : i_s = i_a + i_b \Rightarrow$$



$$\Rightarrow |I_s|^2 = |I_a|^2 + |I_b|^2$$

$$|I_b| = \sqrt{|I_s|^2 - |I_a|^2} = \sqrt{5^2 - 4^2} = \sqrt{25 - 16} = \sqrt{9} = 3 \Rightarrow i_{b,\max} = 3 \text{ A}$$

b. We can see that  $I_d = \frac{k \cdot I_b}{j\omega S}$

from part a,  $|I_b| = 3 \Rightarrow I_b = 3e^{j\frac{\pi}{2}}$

$$I_d = \frac{-S \cdot 3e^{j\frac{\pi}{2}}}{j\omega S} = \frac{-3e^{j\pi/2}}{j\omega} = -\frac{3}{\omega} = \frac{3}{\omega} e^{j\pi} \Rightarrow i_d(t) = \frac{3}{\omega} \cos(\omega t + \pi) \Rightarrow B_1 = 180^\circ$$

c. Assume  $Z_a$  is a resistor and  $Z_b$  is the known inductor ( $I_a$  goes through  $Z_a$ ,  $I_b$  goes through  $Z_b$ )

Define  $V_a$  as voltage across  $Z_a$ , and  $V_b$  across  $Z_b \Rightarrow V_a = V_b$  since they are in parallel

Plot the phasors roughly and see if assumption holds


We can see that the resistor current is in phase with the voltage and inductor voltage is ahead of the current

$\Rightarrow$  our assumption is correct ✓

$$\left. \begin{array}{l} Z_a = R_2, Z_b = j\omega L_1 \\ V_a = R_2 I_a, V_b = j\omega L_1 I_b \end{array} \right\} \quad V_a = V_b \Rightarrow 3 \cdot 4 e^{j\pi} = j\omega \cdot (2 \times 10^{-3}) \cdot 3 e^{j\pi/2}$$

$$\omega = \frac{3 \cdot 4}{(2 \times 10^{-3}) \cdot 3}$$

$$\omega = 2000 \text{ rad/s}$$

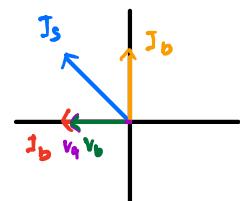


# Phasors 017

Problem has been graded.

The circuit below represents an AC circuit in steady-state in the phasor domain (for the complex numbers, you may assume units are V, A, Ω, etc. as appropriate). Both sources in the circuit have the same  $\omega$ , but you are not told the value of  $\omega$ . Each box represents the impedance of a single circuit element (a resistor, capacitor or inductor).

- What are the maximum values of waveforms  $v_S(t)$  and  $i_S(t)$ ? Enter your answers as  $Y_1$  and  $Y_2$ , with  $Y_1 = \frac{v_{Smax}}{\sqrt{2}}$  and  $Y_2 = i_{Smax}$ .
- We now double  $\omega$  of both sources but keep everything else the same (such as the capacitor, inductor and resistor values; the amplitude and phase of the sources, etc.). Find the new value of all complex numbers in the circuit (the new value of  $a_1$  is called  $a_2$ , etc.) as well as the new magnitude of the current source  $|I_S| = X_2$ .

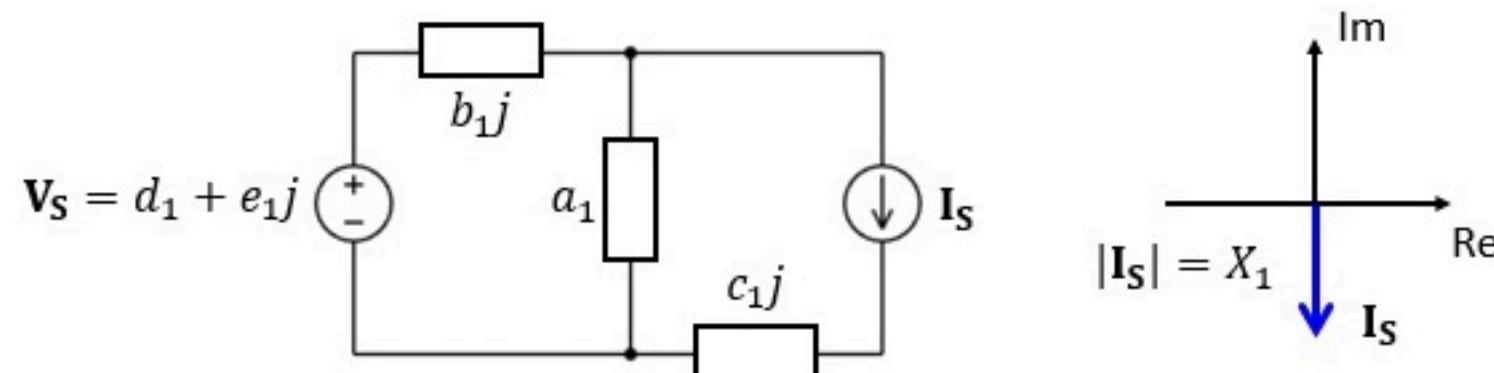

Given Variables:

$a1 : 30$

$b1 : -10$

$c1 : 5$

$d1 : 6$

$e1 : 6$

$X1 : 5 \text{ A}$

Calculate the following:

$Y1 (\text{V}) :$

5.999999999999999



$Y2 (\text{A}) :$

5



$a2 :$

30



$b2 :$

-5



$c2 :$

10



$d2 :$

6



$e2 :$

6




$X2 (\text{A}) :$

5



The circuit below represents an AC circuit in steady-state in the phasor domain (for the complex numbers, you may assume units are V, A, Ω, etc. as appropriate). Both sources in the circuit have the same ω, but you are not told the value of ω. Each box represents the impedance of a single circuit element (a resistor, capacitor or inductor).

- What are the maximum value of  $v_S(t)$  and  $i_S(t)$ , called  $v_{Smax}$  and  $i_{Smax}$  respectively?  
For  $v_{Smax}$ , find  $Y_1$  such that  $v_{Smax} = Y_1 \sqrt{2}$ .
- We now double ω of both sources but keep everything else the same (such as the capacitor, inductor and resistor values; the amplitude and phase of the sources, etc.). Find the new value of all complex numbers in the circuit (the new value of  $a_1$  is called  $a_2$ , etc.) as well as the new magnitude of the current source  $|I_S| = X_2$ .

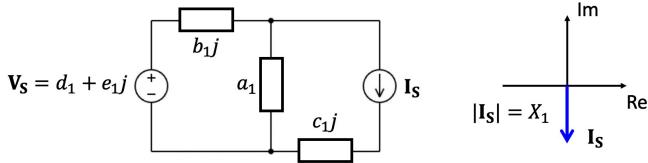

$$\begin{aligned}a_1 &= 50 \\b_1 &= -20 \\c_1 &= 10 \\d_1 &= 1 \\e_1 &= 1 \\X_1 &= 5A\end{aligned}$$

- The max value of a sinusoidal waveform is its amplitude

$$v_{S,\max} = |V_S| = \sqrt{d_1^2 + e_1^2} = \sqrt{1^2 + 1^2} = \sqrt{2} \Rightarrow Y_1 = 1$$

$$i_{S,\max} = |I_S| = X_1 \Rightarrow i_{S,\max} = 5A$$

- Analyze which elements have a dependence on ω

$$a_1 \text{ is the impedance of a resistor } \Rightarrow Z_R = 50, \text{ this has no dependence on } \omega \text{ so if } \omega \rightarrow 2\omega, 50 \rightarrow 50 \Rightarrow a_2 = 50$$

$b_1 j \Rightarrow -20j$  is the impedance of a capacitor

$$Z_C = \frac{1}{j\omega C} \Rightarrow \text{if } \omega \rightarrow 2\omega, \text{ then } \frac{1}{j2\omega C} = \frac{1}{2(j\omega C)} = \frac{1}{2} \cdot \frac{1}{j\omega C} = \frac{1}{2} Z_C$$

$$\text{if } \omega \rightarrow 2\omega, \text{ then } -20j \rightarrow \frac{1}{2}(-20j) = -10j \Rightarrow b_2 = -10$$

$c_1 j \Rightarrow 10j$  is the impedance of an inductor

$$Z_L = j\omega L \Rightarrow \text{if } \omega \rightarrow 2\omega, \text{ then } j2\omega L = 2(j\omega L) = 2Z_L$$

$$\text{if } \omega \rightarrow 2\omega, \text{ then } 10j \rightarrow 2(10j) = 20j \Rightarrow c_2 = 20$$

$V_S = d_1 + e_1 j = 1 + j$  is the phasor for a source  $v_S(t) = \frac{\sqrt{2}}{2} \cos(\omega t + \frac{\pi}{4})$

$$\text{if } \omega \rightarrow 2\omega, \text{ then } v_S(t) = \frac{\sqrt{2}}{2} \cos(2\omega t + \frac{\pi}{4}) \Rightarrow V_S = \frac{\sqrt{2}}{2} e^{j\frac{\pi}{4}} = 1 + j \Rightarrow$$

$$\begin{aligned}d_2 &= 1 \\e_2 &= 1\end{aligned}$$

$\Rightarrow$  the phasor for a voltage waveform does not depend on ω

$$\text{Similarly, } i_S(t) = 5 \cos(\omega t - \frac{\pi}{2}) \text{ if } \omega \rightarrow 2\omega, i_S(t) = 5 \cos(2\omega t - \frac{\pi}{2}) \Rightarrow X_2 = 5A$$

# Phasors 018



0 of 5 attempts made

In the circuit below, the switch moves from position 1 to position 2 at time  $t = 0$ . For  $t < 0$  (switch in position 1), you may assume that the system is in steady state. The voltage source is sinusoidal with  $\omega = W_1$ .

The diagram shows two phasors, **A** and **B**. (Note that the phasors are not drawn to scale. Also, we show three diagrams to illustrate the situation depending on the value of  $a$  you were given. You need to select the diagram that corresponds to your given value.) In your diagram, one phasor represents the capacitor voltage  $v_C$  and the other the resistor voltage  $v_R$  (but you are not told which one is which).

- Find  $i_1 = i_R(0^-)$  (i.e., just before the switch moves to position 2).
- Find  $i_2 = i_R(0^+)$  (i.e., just after the switch moves to position 2).

$$|A| = X\sqrt{2}$$

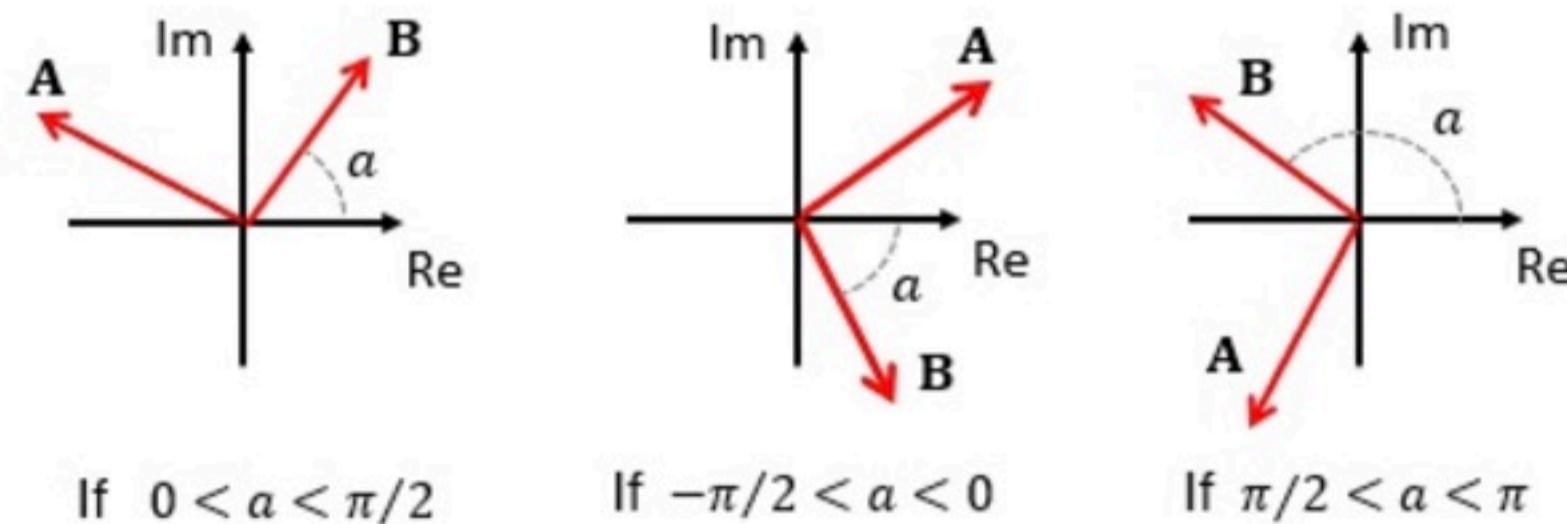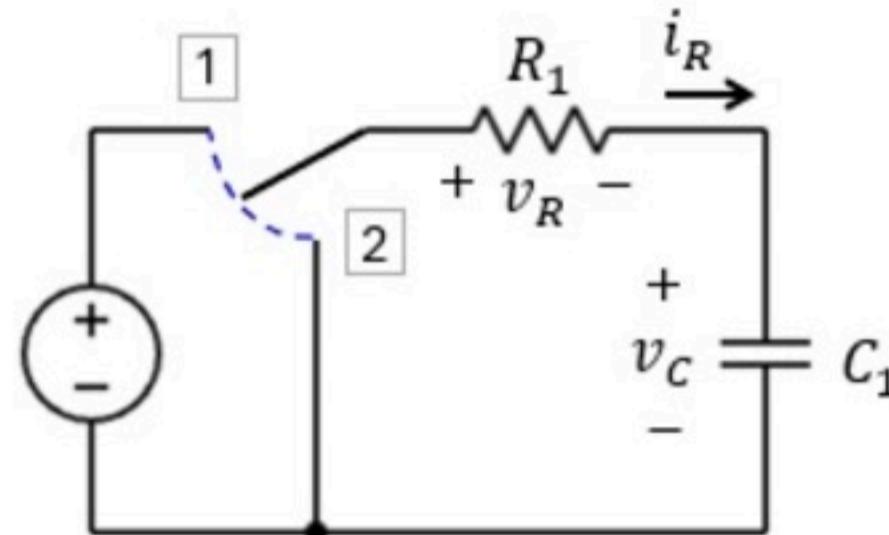

Given Variables:

$W_1 : 1 \text{ rad/s}$

$X : 25$

$a : -45 \text{ degrees}$

$R_1 : 5 \text{ ohm}$

$C_1 : 1 \text{ F}$

Calculate the following:

$i_1 (\text{A}) :$

5



$i_2 (\text{A}) :$

-1





In the circuit below, the switch moves from position 1 to position 2 at time  $t = 0$ . For  $t < 0$  (switch in position 1), you may assume that the system is in steady state. The voltage source is sinusoidal with  $\omega = W_1$ .

The diagram shows two phasors, **A** and **B**. (Note that the phasors are not drawn to scale. Also, we show three diagrams to illustrate the situation depending on the value of  $a$  you were given. You need to select the diagram that corresponds to your given value.) In your diagram, one phasor represents the capacitor voltage  $v_C$  and the other the resistor voltage  $v_R$  (but you are not told which one is which).

- Find  $i_1 = i_R(0^-)$  (i.e., just before the switch moves to position 2).
- Find  $i_2 = i_R(0^+)$  (i.e., just after the switch moves to position 2).

$$|A| = X\sqrt{2}$$

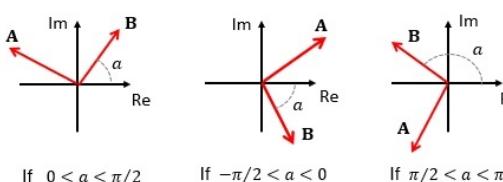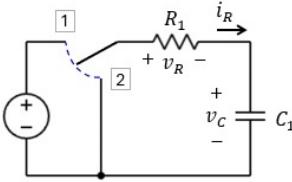

$$\omega_1 = 1 \text{ rad/s}$$

$$X = 10$$


$$q = 45^\circ$$

$$P_1 = 2 \text{ W}$$

$$C_1 = 1 \text{ F}$$

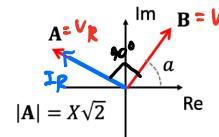a. Assume  $A = V_R$  and  $B = V_C$

We plot  $I_R$  such that it is in phase with  $V_R$



$I_R = I_C$  since the resistor is series with the capacitor

$\Rightarrow$  the capacitor current is ahead of the capacitor voltage  $\Rightarrow$  our assumption is correct ✓

At  $t = 0^-$

$$V_R = X\sqrt{2} e^{j(a + 90^\circ)} = 10\sqrt{2} e^{j135^\circ}$$

$$i_R = \frac{V_R}{R_1} = \frac{10\sqrt{2} e^{j135^\circ}}{2} = 5\sqrt{2} e^{j135^\circ}$$

$$i_R(t) = 5\sqrt{2} \cos(t + 135^\circ)$$

$$i_R(0^-) = 5\sqrt{2} \cos(0 + 135^\circ) = 5\sqrt{2} \cdot \left(-\frac{\sqrt{2}}{2}\right) \Rightarrow i_1 = -5\text{A}$$

b. At  $t = 0^+$ , the capacitor voltage cannot change instantaneously


$$Z_C = \frac{1}{j\omega_1 C_1} = \frac{1}{j(1)(1)} = -j$$

$$V_C = i_R \cdot Z_C = 5\sqrt{2} e^{j135^\circ} \cdot -j = 5\sqrt{2} e^{j45^\circ}$$

$$V_C(t) = 5\sqrt{2} \cos(t + 45^\circ)$$

$$V_C(0^+) = 5\sqrt{2} \cos(0 + 45^\circ) = 5\sqrt{2} \cdot \left(\frac{\sqrt{2}}{2}\right) = 5\text{V} \Rightarrow V_C(0^+) = 5\text{V}$$

at  $t = 0^+$

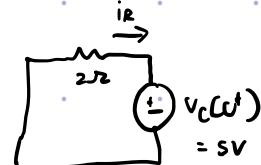

$$i_R(0^+) = \frac{-5}{2} \text{ A}$$



$$i_2 = -2.5 \text{ A}$$

# Phasors 019

0 of 5 attempts made

The AC circuit below has  $\omega = W_1$  and is in steady state. The phasor diagram shows the phasors of  $v_s$  and  $i_s$ . You are given the angle  $a$ , and vector lengths  $|I_s| = A_1$  and  $|V_s| = A_2\sqrt{b}$ . The diagram is not necessarily drawn to scale (but  $V_s$  is along the imaginary axis). The element in the center (rectangular box) is either an inductor or a capacitor but you are not told which.

- At what time does  $v_R$  reach its maximum value? Enter  $k = t_0 \cdot \frac{12}{\pi}$ , where  $t_0$  is the first time that the maximum is reached, for  $t_0 \geq 0$ . (Hint: convert  $a$  to radians first)
- We select the mystery element such that  $|I_a|$  is minimized (note that this is the current through the voltage source). What is the mystery element type (enter 1 for capacitor, 2 for inductor)? What is its value  $X$  (i.e., either the capacitance or the inductance value, in F or H respectively)?

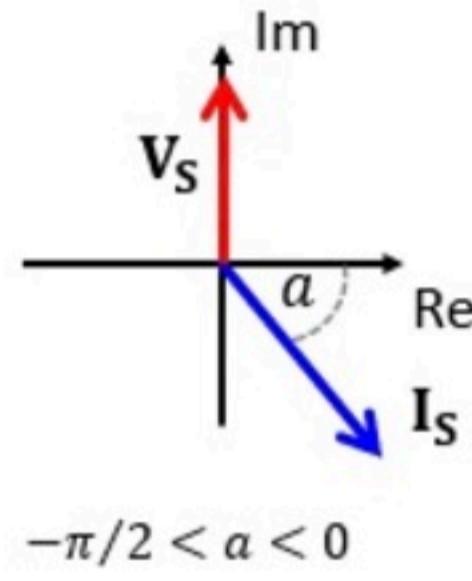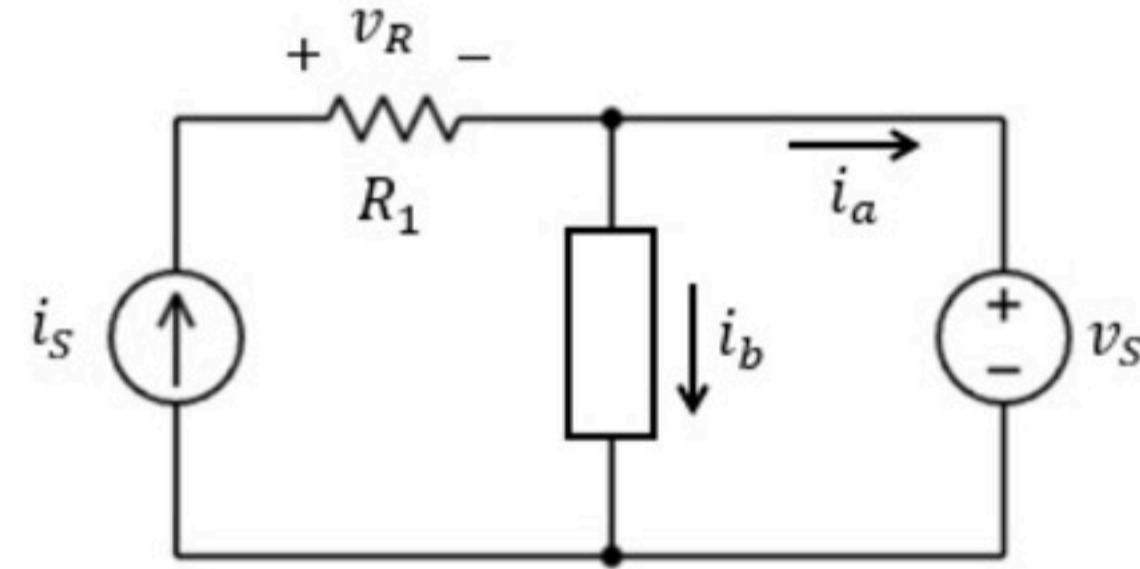

Given Variables:

W1 : 4 rad/s

a : -30 degrees

A1 : 1 A

A2 : 10 V

b : 3

R1 : 1 ohm

Calculate the following:

k (s) :

0.5



Type :

2





X :

5



The AC circuit below has  $\omega = W_1$  and is in steady state. The phasor diagram shows the phasors of  $v_s$  and  $i_s$ . You are given the angle  $a$ , and vector lengths  $|I_s| = A_1$  and  $|V_s| = A_2 \sqrt{b}$ . The diagram is not necessarily drawn to scale (but  $V_s$  is along the imaginary axis). The element in the center (rectangular box) is either an inductor or a capacitor but you are not told which.

- At what time does  $v_R$  reach its maximum value? Enter  $k = t_0 \cdot \frac{12}{\pi}$ , where  $t_0$  is the first time that the maximum is reached, for  $t_0 \geq 0$ . (Hint: convert  $a$  to radians first)
- We select the mystery element such that  $|I_a|$  is minimized (note that this is the current through the voltage source). What is the mystery element type (enter 1 for capacitor, 2 for inductor)? What is its value  $X$  (i.e., either the capacitance or the inductance value, in F or H respectively)?

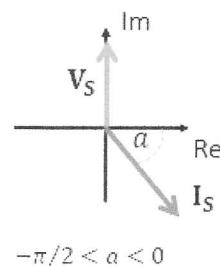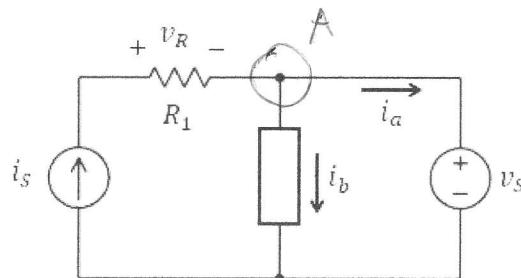

$$W_1 = 2 \text{ rad/s}$$

$$a = -30^\circ$$

$$A_1 = 2 \text{ A}$$

$$A_2 = 10 \text{ V}$$

$$b = 3$$

$$R_1 = 1 \Omega$$

$$\textcircled{a} \quad V_R = R_1 I_s = R_1 \cdot A_1 e^{j\alpha} = 2 e^{-j30^\circ}$$



$$V_{R\max} = |V_R| \quad V_R(t) = 2 \cos(2t - 30^\circ) \quad \text{MAX WHEN } \cos(\theta) = 1$$

$$\theta = 0 \Rightarrow 2t_0 - \frac{\pi}{6} = 0 \Rightarrow t_0 = \frac{\pi}{12} \Rightarrow k = t_0 \cdot \frac{12}{\pi} = 1 \quad \boxed{k=1}$$


$$\textcircled{b} \quad \text{KCL at A: } I_s = I_b + I_a$$

If the mystery element is a capacitor or inductor:  $I_b$  is perpendicular to  $V_s$

Let's look at different options

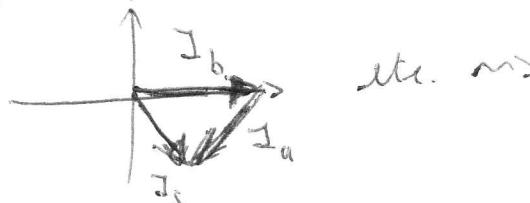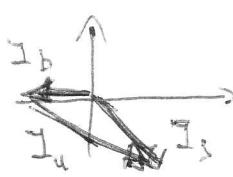

etc. and

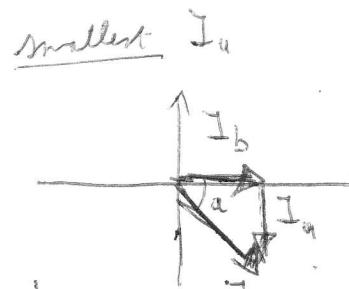

$$\cos(-\alpha) = \frac{|I_b|}{|I_s|} \Rightarrow \cos\left(\frac{\pi}{6}\right) = \frac{\sqrt{3}}{2} = \frac{|I_b|}{2}$$

$$|I_b| = \sqrt{3} \quad \text{on the real axis} \Rightarrow I_b = \sqrt{3}$$

$$\text{also: } V_s = Z \cdot I_b \Rightarrow Z = \frac{V_s}{I_b} = \frac{10\sqrt{3}}{\sqrt{3}} j = 10j$$

$$\text{This must be an inductor: } Z = j\omega L = 10j$$

$$\Rightarrow \omega L = 10 \Rightarrow L = \frac{10}{2} = 5 \text{ H}$$

$$\boxed{x=5}$$


# PP Phasors 021

Unlimited Attempts.

Find the Thevenin equivalent model between a and b, in phasor notation:

$$\mathbf{V}_{\text{Th}} = a + jb$$

$$\mathbf{Z}_{\text{Th}} = c + jd$$

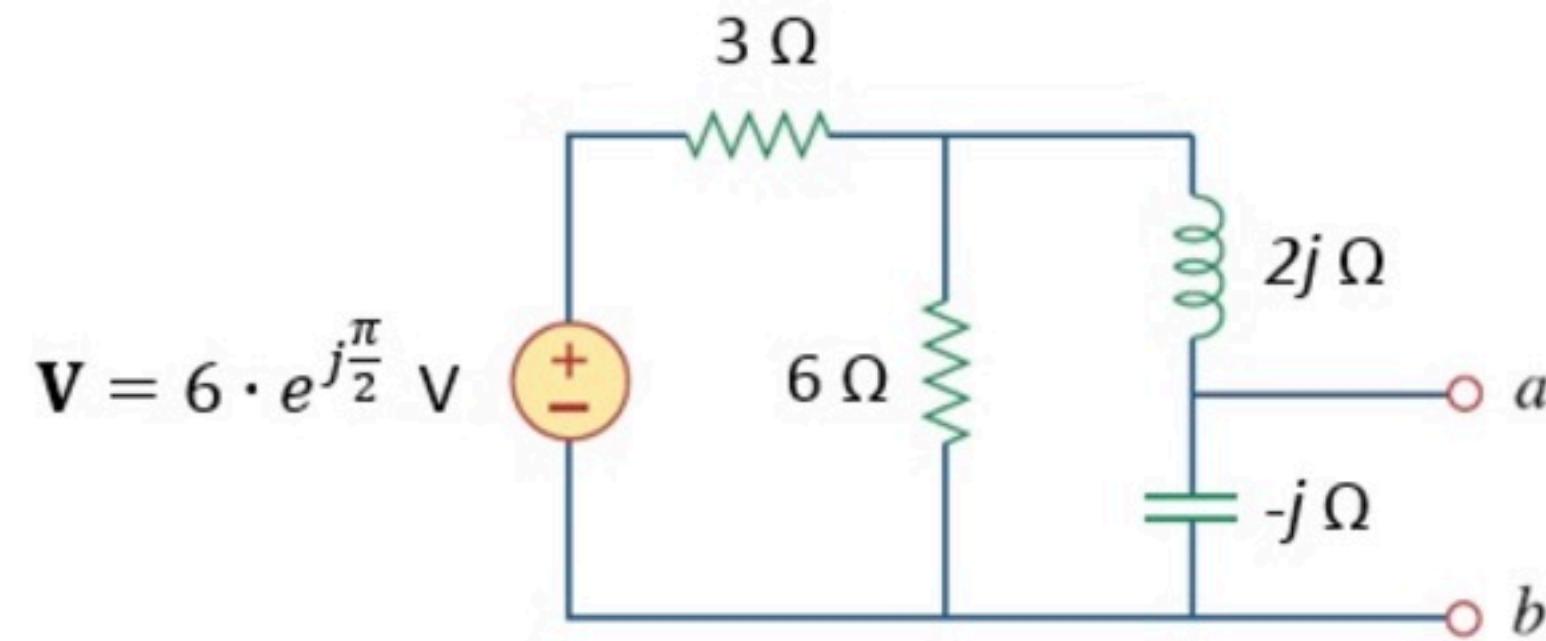

Given Variables:

...

Calculate the following:

a (V) :

1.6



b (V) :

-0.8



c (ohm) :

0.4




d (ohm) :

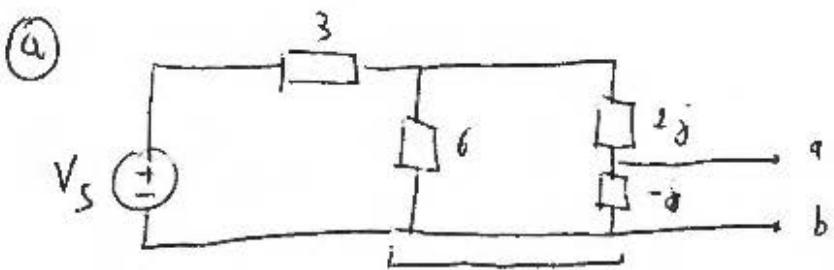-1.2



Hint: You can use voltage divider and series/parallel connections of impedances




$$\rightarrow Z_1 = 6 \parallel (2j - j) = 6 \parallel j = \frac{1}{\frac{1}{6} + \frac{1}{j}} = \frac{6j}{6+j}$$

$$V_{ab} = V_s \cdot \frac{Z_1}{Z_1 + 3} \cdot \frac{-j}{2j - j} = V_s \cdot \frac{6j}{6j + 3(6+j)} \cdot \frac{-j}{j} = -V_s \cdot \frac{6j}{18 + 9j}$$

$$= -\frac{6e^{j\frac{\pi}{2}} \cdot 6j}{9(2+j)} \cdot \frac{(2-j)}{(2-j)} = \frac{-6j \cdot 6j}{9} \cdot \frac{(2-j)}{(4+1)} = \frac{36}{9} \cdot \frac{2-j}{5} = \frac{4}{5}(2-j)$$
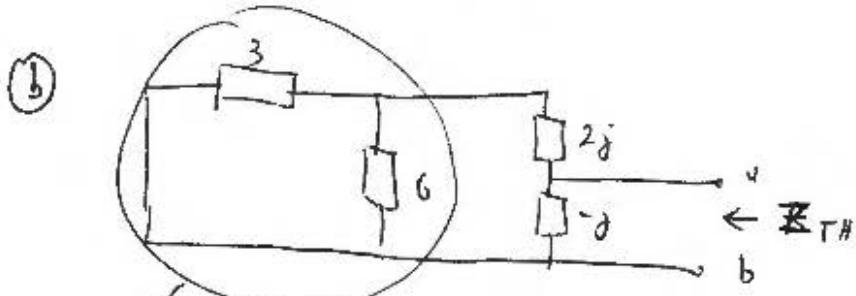
$$V_{TH} = V_{ab} = \frac{8}{5} - \frac{4}{5}j \quad \boxed{a = 1.6V} \quad \boxed{b = -0.8V}$$



$$3 \parallel 6 = \frac{1}{\frac{1}{3} + \frac{1}{6}} = \frac{6}{3} = 2 \Omega$$

$$Z_{TH} = (2+2j) \parallel (-j) = \frac{1}{\frac{1}{2+2j} + \frac{1}{-j}} = \frac{-j(2+2j)}{-j+2+2j} = \frac{2-2j}{2+j}$$

$$= \frac{(2-2j)(2-j)}{(2+j)(2-j)} = \frac{(4-2j-4j-2)}{5} = \frac{2}{5} - \frac{6}{5}j$$

$$Z_{TH} = \frac{2}{5} - \frac{6}{5}j \quad \boxed{c = 0.4 \Omega} \quad \boxed{d = -1.2 \Omega}$$