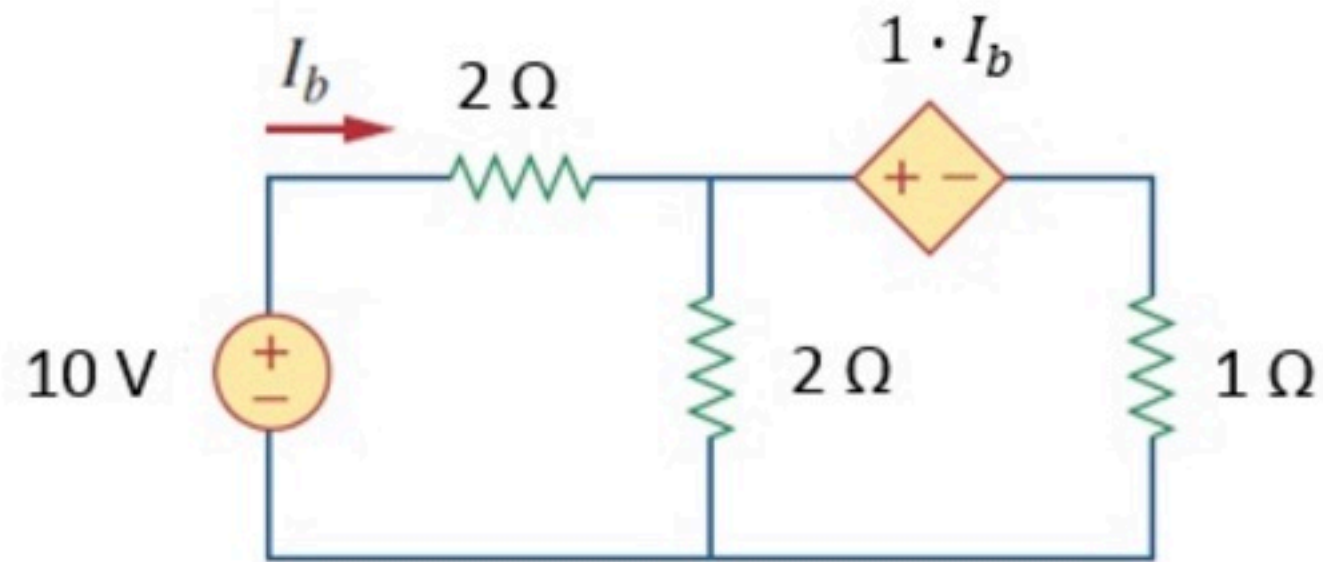


PP - Nodal Mesh 005

Problem has been graded.

Find I_b . Solve using nodal analysis.

For extra practice: Afterwards solve again using mesh analysis.



Given Variables:

...

Calculate the following:

I_b (A) :

3



Hint: Need to use a supernode