

# **ECE 65: Components & Circuits Lab**

## **Lecture 22**

### **Common collector amplifier parameters**


Reference notes: sections 6.1, 6.2

Sedra & Smith (7<sup>th</sup> Ed): sections 7.3




Saharnaz Baghdadchi

# Course map
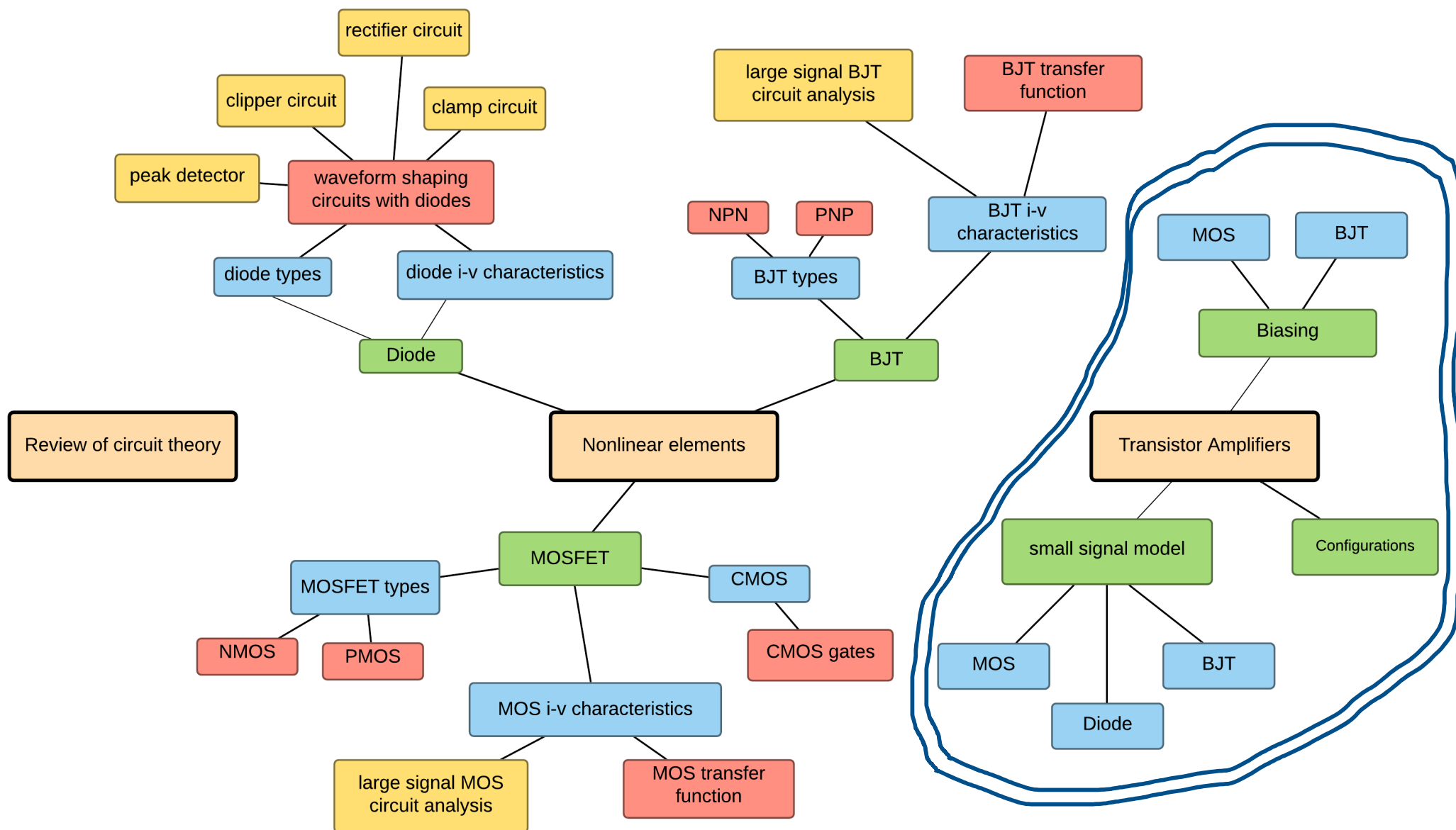
## 6. Transistor Amplifier Configurations


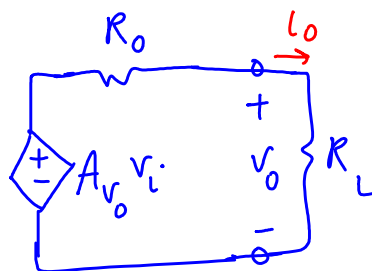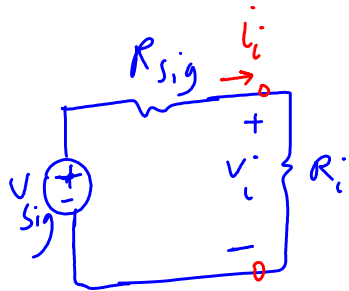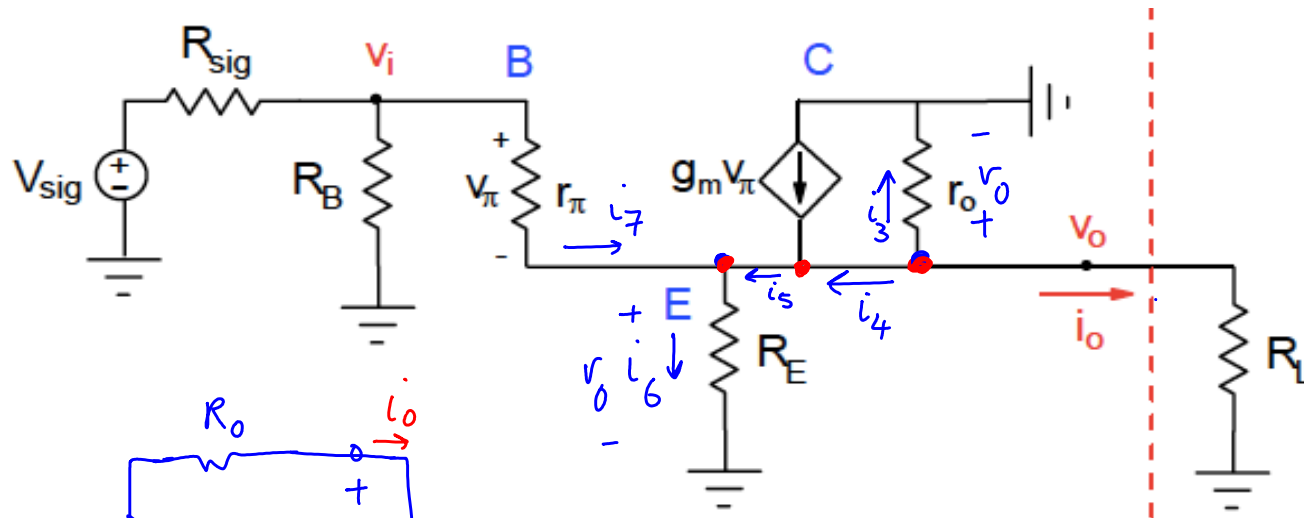
# Derivation of $A_{vo}$ , $R_o$ , $R_i$ for the common collector BJT amplifier




$$\underline{A_{v_o} v_i = v_o + R_o i_o}$$

$$i_3 = \frac{v_o}{r_o}, \quad i_4 + i_o + i_3 = 0 \quad \longrightarrow \quad i_4 = -\left(i_o + \frac{v_o}{r_o}\right)$$

$$g_m v_{\pi} + i_4 - i_5 = 0 \quad \longrightarrow \quad i_5 = i_4 + g_m v_{\pi} = -\left(i_o + \frac{v_o}{r_o}\right) + g_m v_{\pi}$$

$$i_5 + i_7 - i_6 = 0, \quad i_6 = \frac{v_o}{R_E}, \quad i_7 = \frac{v_i - v_o}{r_{\pi}}, \quad v_{\pi} = v_i - v_o$$
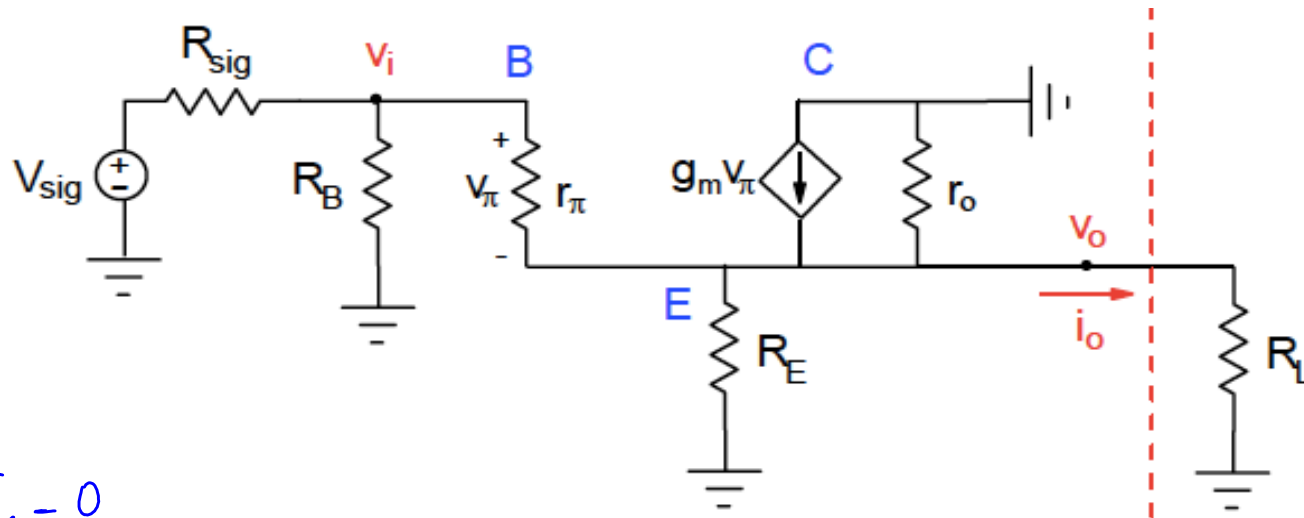
# Derivation of $A_{vo}$ , $R_o$ , $R_i$ for the common collector BJT amplifier



$$i_5 + i_7 - i_6 = 0$$

$$-\left(i_o + \frac{v_o}{r_o}\right) + g_m(v_i - v_o) + \frac{v_i - v_o}{r_\pi} - \frac{v_o}{R_E} = 0$$

$$\left(g_m + \frac{1}{r_\pi}\right)v_i = \left(g_m + \frac{1}{r_\pi} + \frac{1}{R_E} + \frac{1}{r_o}\right)v_o + i_o$$



$$A_{v_o} \left( \frac{1}{g_m + \frac{1}{r_\pi} + \frac{1}{R_E} + \frac{1}{r_o}} \right) \left( g_m + \frac{1}{r_\pi} \right) v_i = v_o + \left( \frac{1}{g_m + \frac{1}{r_\pi} + \frac{1}{R_E} + \frac{1}{r_o}} \right) i_o$$

$$A_{v_o} v_i = v_o + R_o i_o$$

$$g_m = \frac{1}{1/g_m}$$

$g_m$  has the units of  $A/V$
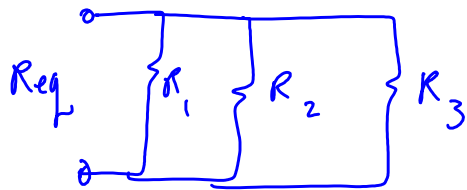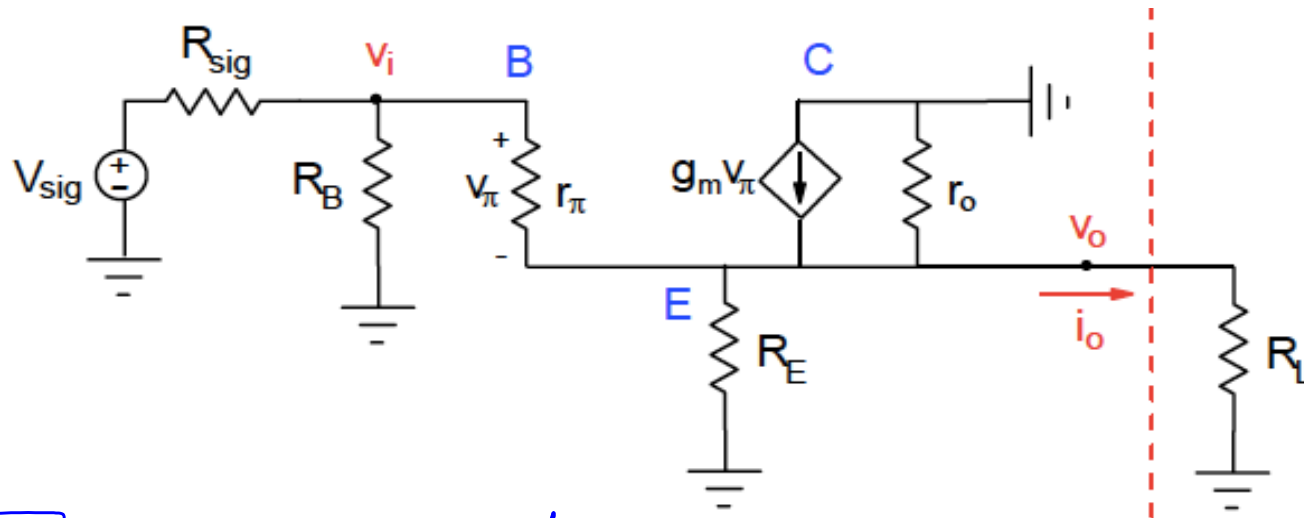
# Derivation of $A_{vo}$ , $R_o$ , $R_i$ for the common collector BJT amplifier




$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

$$R_o = \left( \frac{1}{g_m} \right) \parallel r_{\pi} \parallel R_E \parallel r_o$$

$$A_{v_o} = \frac{\left( \frac{1}{g_m} \right) \parallel r_{\pi} \parallel R_E \parallel r_o}{\left( \frac{1}{g_m} \right) \parallel r_{\pi}}$$
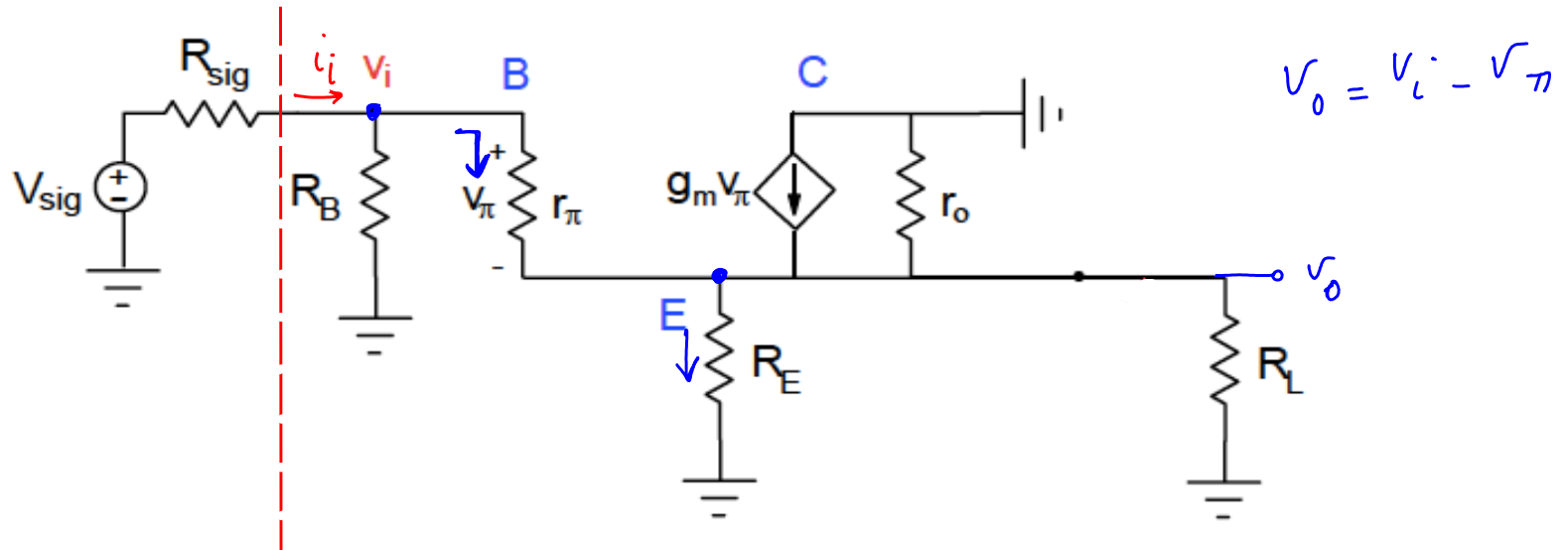
# Derivation of $A_{vo}$ , $R_o$ , $R_i$ for the common collector BJT amplifier




$$R_i = \frac{V_i}{i_i}$$

$$i_i = \frac{V_i}{R_B} + \frac{v_{\pi}}{r_{\pi}}$$

$$\frac{v_{\pi}}{r_{\pi}} + g_m v_{\pi} = \left( \frac{V_i - v_{\pi}}{R_E} \right) + \left( \frac{V_i - v_{\pi}}{r_o} \right) + \frac{V_i - v_{\pi}}{R_L}$$

$$g_m = \frac{\beta}{r_{\pi}} \quad \longrightarrow \quad (\beta + 1) \frac{v_{\pi}}{r_{\pi}} = \frac{V_i - v_{\pi}}{R_E \parallel r_o \parallel R_L}$$


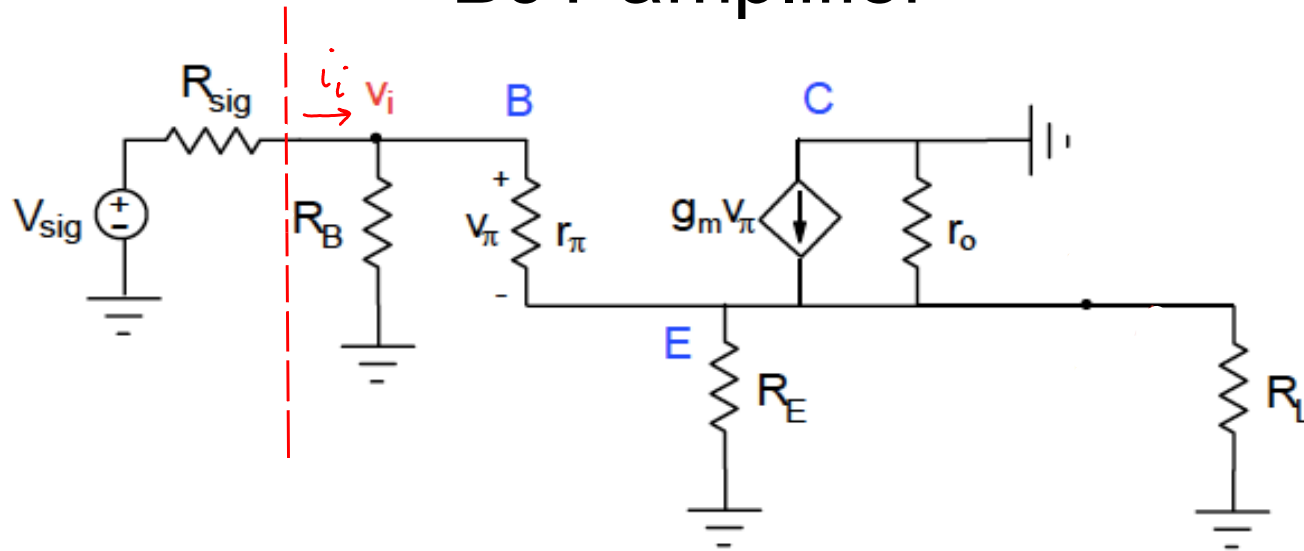
# Derivation of $A_{vo}$ , $R_o$ , $R_i$ for the common collector BJT amplifier





$$i_i = \frac{v_i}{R_B} + \frac{v_i}{r_{\pi} + (\beta + 1)(R_E \parallel r_o \parallel R_L)}$$

$$R_i = \frac{v_i}{i_i} \rightarrow R_i = R_B \parallel \left[ r_{\pi} + (\beta + 1)(R_E \parallel r_o \parallel R_L) \right]$$

# Common-Darin MOS amplifier parameters

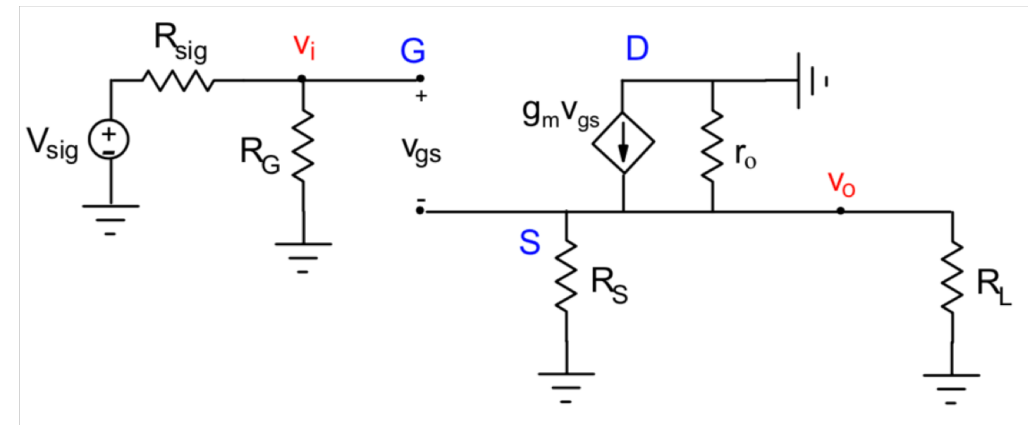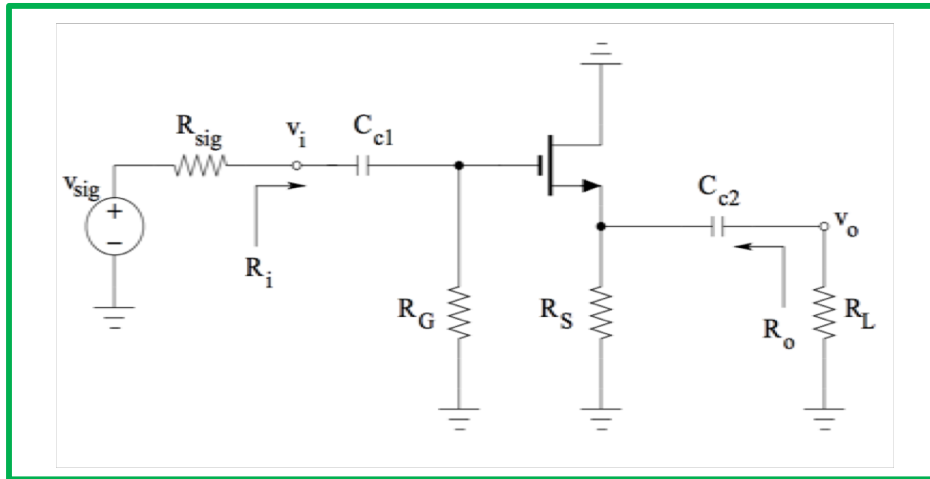

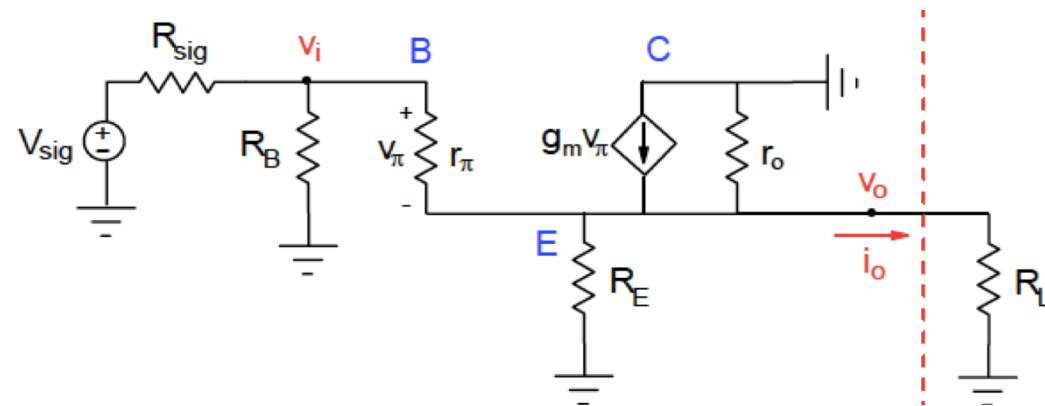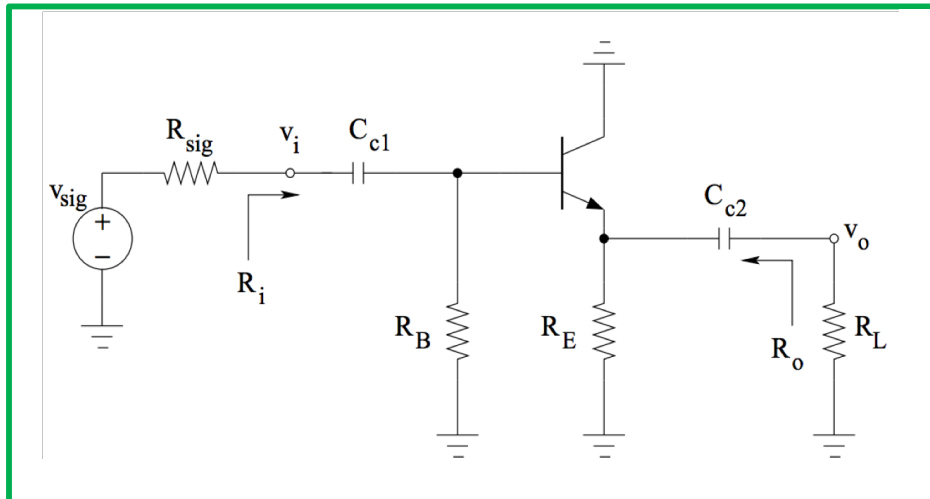
Compare it with the signal circuit for a common collector BJT amplifier:




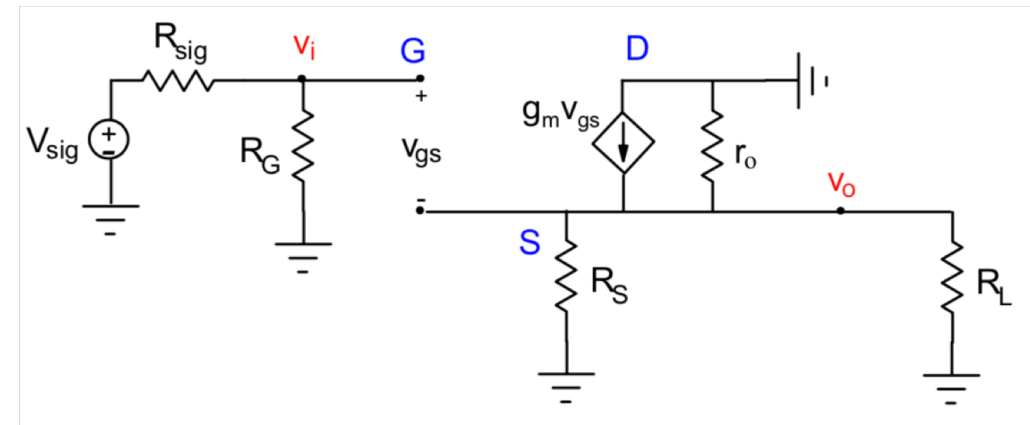
# Common-Darin MOS amplifier parameters

In the derived equations for the common-collector BJT amplifier, replace  $R_B$  with  $R_G$ ,  $R_E$  with  $R_S$ , and  $r_\pi \rightarrow \infty$ .




**common collector BJT amplifier:**

$$A_{vo} = \frac{g_m(R_S \parallel r_o)}{1 + g_m(R_S \parallel r_o)}$$

$$R_o = (1/g_m) \parallel R_S \parallel r_o$$

$$R_i = R_G$$

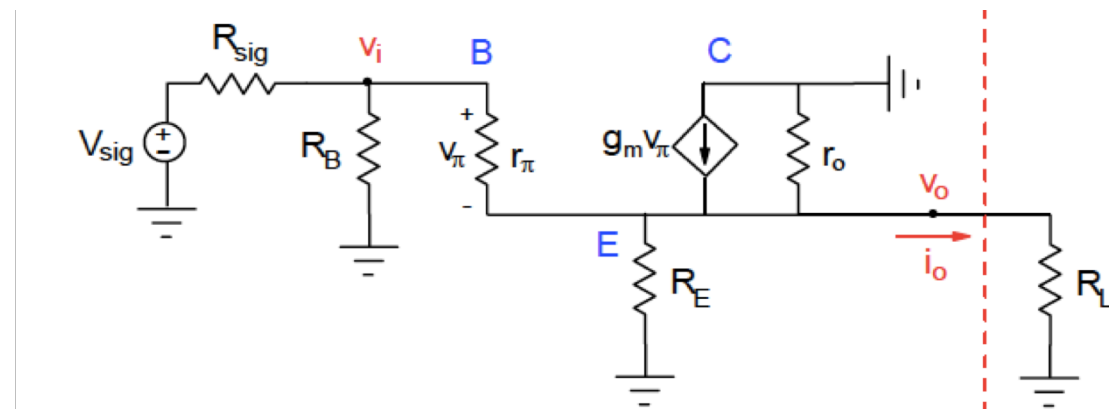

## Some notes on *source follower* and *emitter follower* amplifiers:

- They have a voltage gain of lower than but close to unity.
- They have a low output resistance and a high input resistance.
- They are usually used as a voltage buffer.

### *source follower*

$$A_{vo} = \frac{g_m(R_S \parallel r_o)}{1 + g_m(R_S \parallel r_o)}$$

$$R_o = (1/g_m) \parallel R_S \parallel r_o$$

$$R_i = R_G$$

### *emitter follower*

$$A_{vo} = \frac{g_m(R_E \parallel r_o)}{1 + g_m(R_E \parallel r_o)}$$


$$R_o = (1/g_m) \parallel r_\pi \parallel R_E \parallel r_o$$

$$R_i = R_B \parallel [r_\pi + (\beta + 1)(r_o \parallel R_E \parallel R_L)]$$
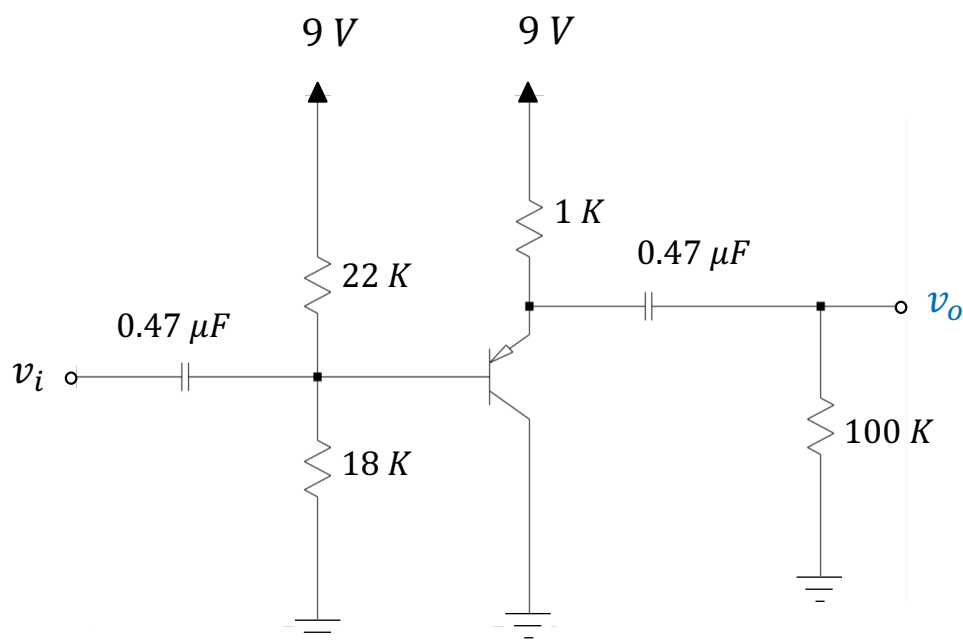
## Lecture 22 reading quiz


In the following circuit, find the amplifier parameters,  $R_o$ ,  $R_i$ ,  $A_{v_o}$ .

Let  $\beta = 100$ ,  $V_T = 25 \text{ mV}$ ,  $V_A = 150 \text{ V}$ . Ignore the early effect in bias calculations.



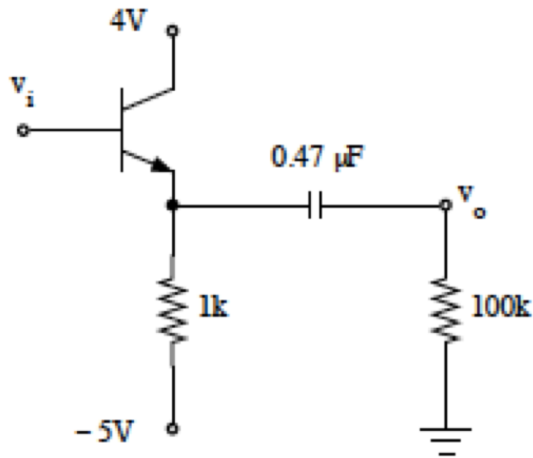
## Discussion question 1

Write the  $A_{vo}$ ,  $R_o$ ,  $R_i$  equations for the following circuit by comparing it to the prototype circuit and using the derived equations.



The prototype common-collector circuit:

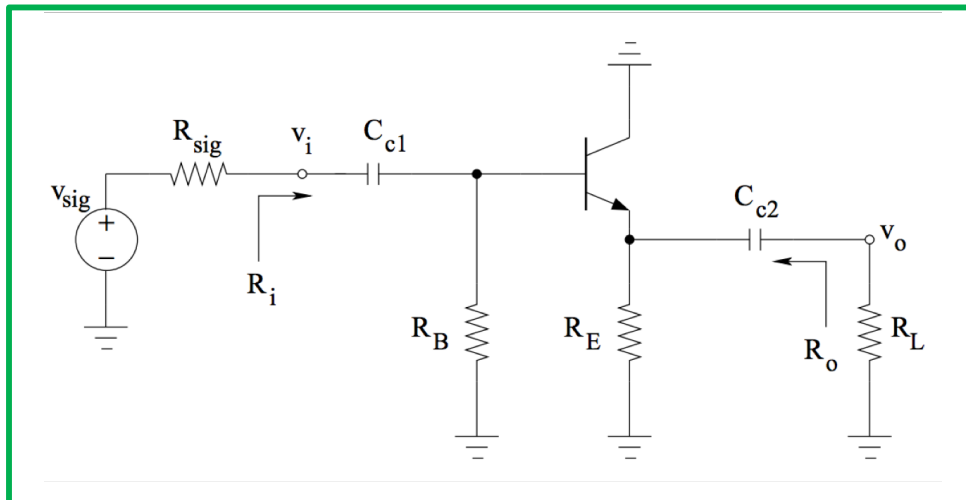


$$A_{vo} = \frac{g_m(R_E \parallel r_o)}{1 + g_m(R_E \parallel r_o)}$$

$$R_o = (1/g_m) \parallel r_\pi \parallel R_E \parallel r_o$$

$$R_i = R_B \parallel [r_\pi + (\beta + 1)(r_o \parallel R_E \parallel R_L)]$$
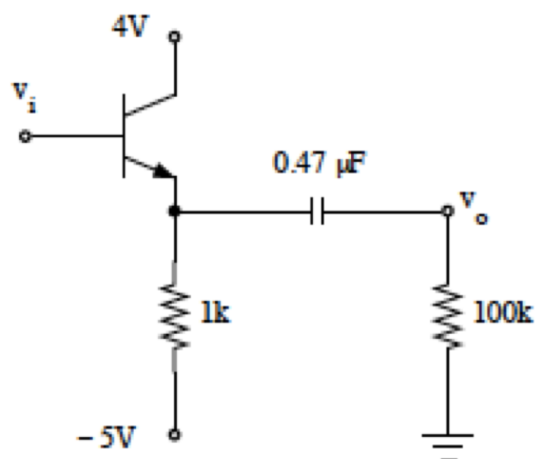
## Discussion question 1

Write the  $A_{vo}$ ,  $R_o$ ,  $R_i$  equations for the following circuit by comparing it to the prototype circuit and using the derived equations.




- Start with the equation of the input resistance. Look at the given circuit in the problem and find what  $R_E$ ,  $R_L$ ,  $R_B$  are. Do all of them exist in the given circuit. If not how should you modify the equation of the input resistance to take that into account?

- Note that  $r_{\pi}$ ,  $r_o$ , and  $g_m$  are small signal parameters and will be calculated after solving the bias circuit, so in the modified equations, they will not be removed or changed.

- Do we need to change the equations of  $A_{vo}$  and  $R_o$ ?

The prototype common-collector circuit:

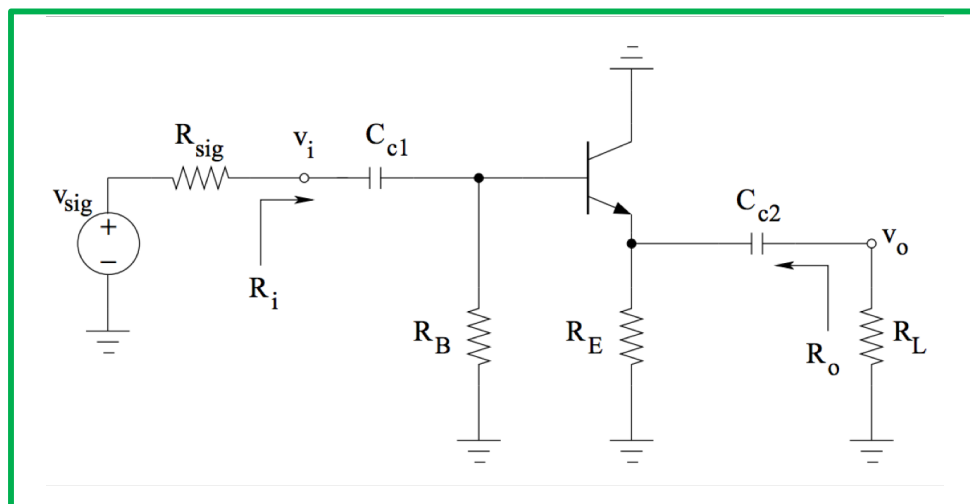


$$A_{vo} = \frac{g_m(R_E \parallel r_o)}{1 + g_m(R_E \parallel r_o)}$$

$$R_o = (1/g_m) \parallel r_{\pi} \parallel R_E \parallel r_o$$


$$R_i = R_B \parallel [r_{\pi} + (\beta + 1)(r_o \parallel R_E \parallel R_L)]$$
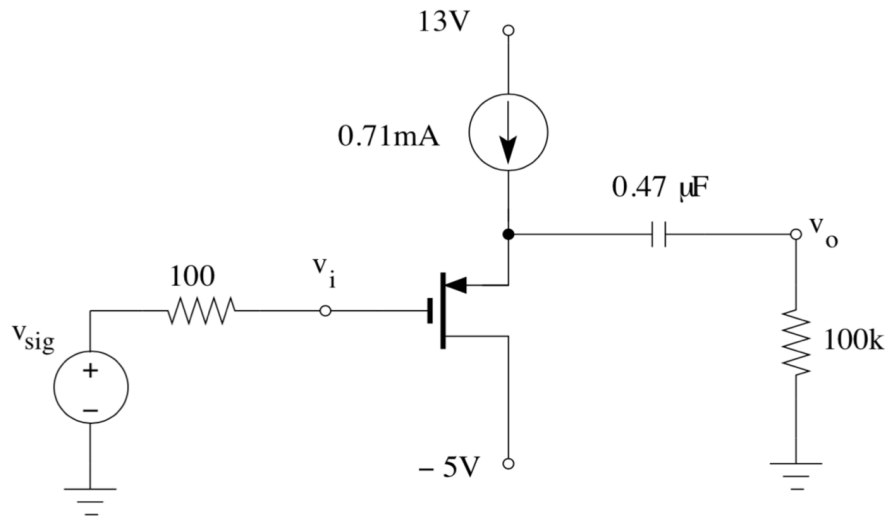
## Discussion question 2.

Write the  $A_{vo}$ ,  $R_o$ ,  $R_i$  equations for the following circuit by comparing it to the prototype circuit and using the derived equations.



The prototype common-drain circuit:

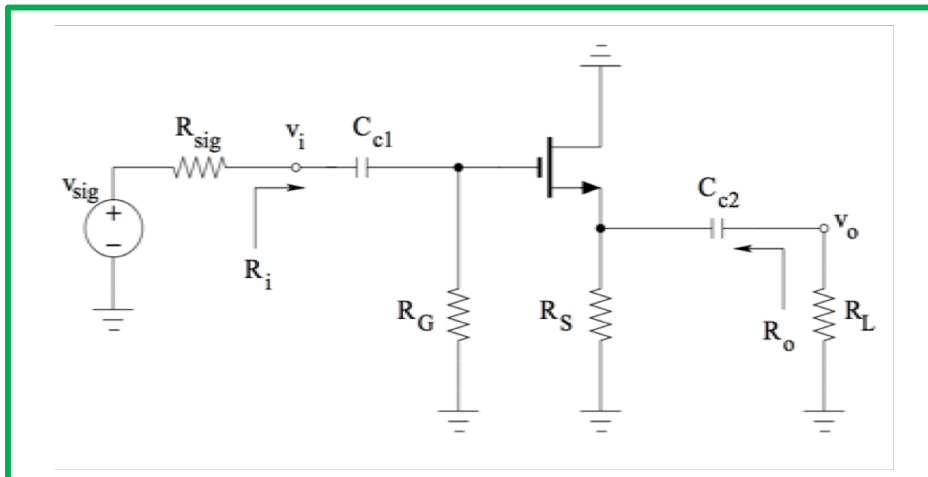


$$A_{vo} = \frac{g_m(R_S \parallel r_o)}{1 + g_m(R_S \parallel r_o)}$$

$$R_o = (1/g_m) \parallel R_S \parallel r_o$$

$$R_i = R_G$$
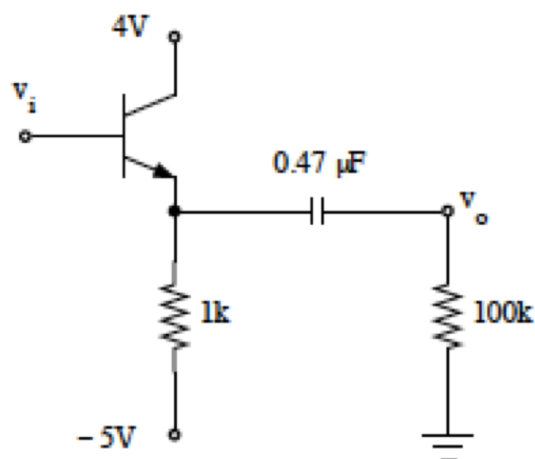
## Discussion question 1

Write the  $A_{vo}$ ,  $R_o$ ,  $R_i$  equations for the following circuit by comparing it to the prototype circuit and using the derived equations.




- Start with the equation of the input resistance. Look at the given circuit in the problem and find what  $R_E$ ,  $R_L$ ,  $R_B$  are. Do all of them exist in the given circuit. If not how should you modify the equation of the input resistance to take that into account?

- Note that  $r_{\pi}$ ,  $r_o$ , and  $g_m$  are small signal parameters and will be calculated after solving the bias circuit, so in the modified equations, they will not be removed or changed.

- Do we need to change the equations of  $A_{vo}$  and  $R_o$ ?

The prototype common-collector circuit:

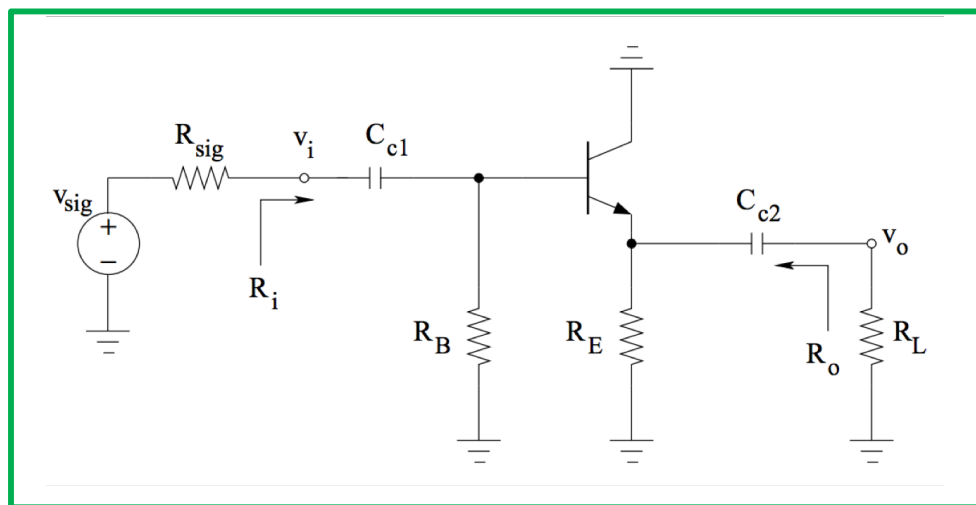

$$A_{vo} = \frac{g_m(R_E \parallel r_o)}{1 + g_m(R_E \parallel r_o)}$$


$$R_o = (1/g_m) \parallel r_{\pi} \parallel R_E \parallel r_o$$

$$R_i = R_B \parallel [r_{\pi} + (\beta + 1)(r_o \parallel R_E \parallel R_L)]$$

### Discussion question 3.

The NMOS in the below amplifier has  $V_{tn} = 0.7\text{ V}$  and  $V_A = 50\text{ V}$ . Neglecting the early effect, verify that the transistor is in saturation with  $I_D = 0.5\text{ mA}$  and  $V_{OV} = 0.3\text{ V}$ . What must the MOSFET's  $k_n$  be? What is the DC voltage at the drain?

Find  $R_i$  and  $A_v$ .

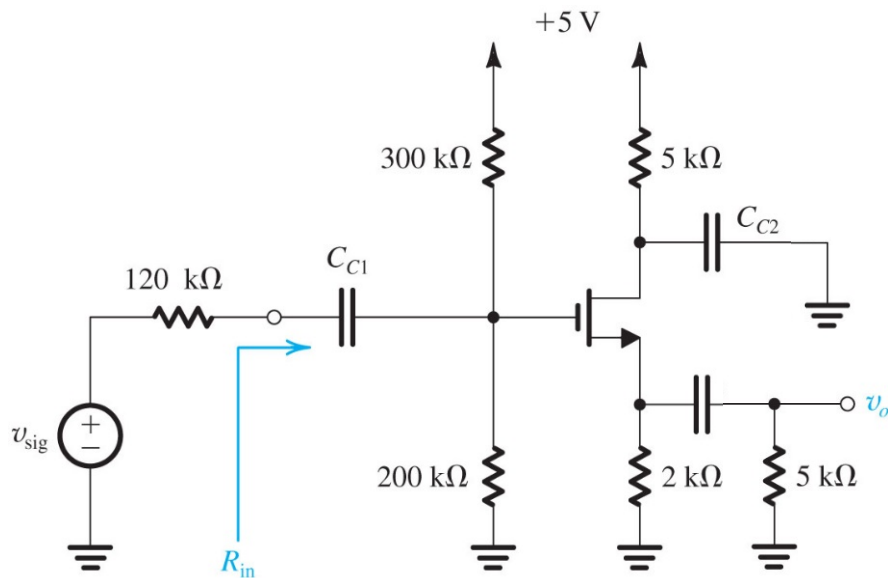




## Discussion question 3.

The NMOS in the below amplifier has  $V_{tn} = 0.7\text{ V}$  and  $V_A = 50\text{ V}$ . Neglecting the early effect, verify that the transistor is in saturation with  $I_D = 0.5\text{ mA}$  and  $V_{OV} = 0.3\text{ V}$ . What must the MOSFET's  $k_n$  be? What is the DC voltage at the drain?

Find  $R_i$  and  $A_v$ .

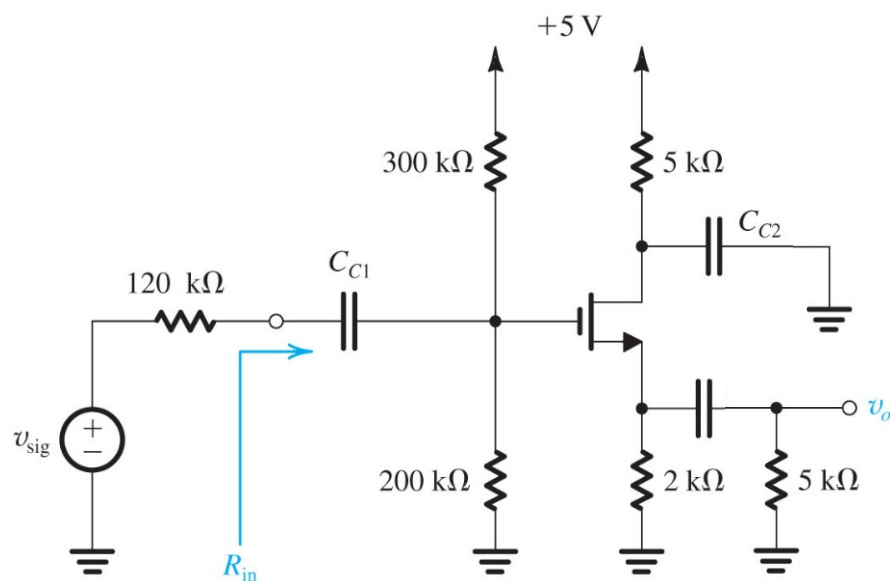

- What is the condition of MOSFET operating in the saturation region?
- Draw and solve the bias circuit and verify that NMOS is in saturation.
- Use the characteristic drain current equation to find  $k_n$ .
- Identify the MOSFET amplifier type, and using the related set of equations, find  $R_i$  and  $A_v$ .