

Phasors 005

Unlimited Attempts.

Each voltage-current pair below is the voltage across an element and the current through that element, adhering to the passive sign convention (ω is in units of rad/s).

$$v_1(t) = A_1 \cdot \cos(400t + 25^\circ)$$
$$v_2(t) = A_2 \cdot \sin(500t + 70^\circ)$$
$$v_3(t) = A_3 \cdot \cos(700t + 30^\circ)$$

$$i_1(t) = B_1 \cdot \sin(400t + 25^\circ)$$
$$i_2(t) = B_2 \cdot \sin(500t + 160^\circ)$$
$$i_3(t) = B_3 \cdot \sin(700t + 120^\circ)$$

- For each element:
- a)

Indicate the type of element. Enter 1 for resistor, 2 for inductor, and 3 for capacitor.
- b)

Find the value of the element. Assume the units are $\text{m}\Omega$, mH or mF respectively.

Given Variables:

A1 : 12 V
B1 : 3 A
A2 : 20 V
B2 : 4 A
A3 : 2 V
B3 : 4 A

Calculate the following:

Type 1 (.) :

2

✓

Value 1 (.) :

10

✓

Type 2 (.) :

3

✓

Value 2 (.) :

0.4

✓

Type 3 (.) :

1

✓

Value 3 (.) :

500

✓