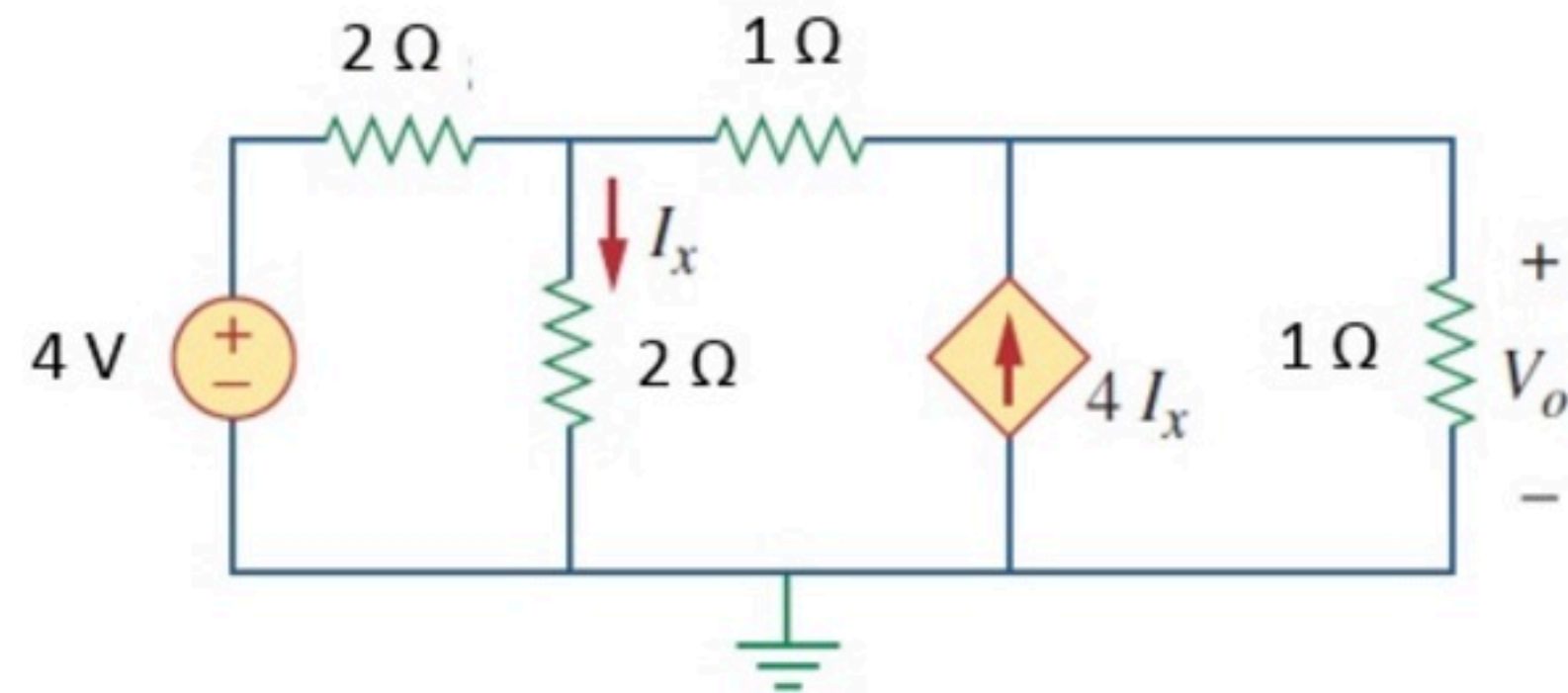


PP - Nodal Mesh 004

Problem has been graded.

Find V_o . Solve using nodal analysis.

For extra practice: Afterwards solve again using mesh analysis.



Given Variables:

...

Calculate the following:

V_o (V) :

6



Hint: Express I_x as a function of node voltages