
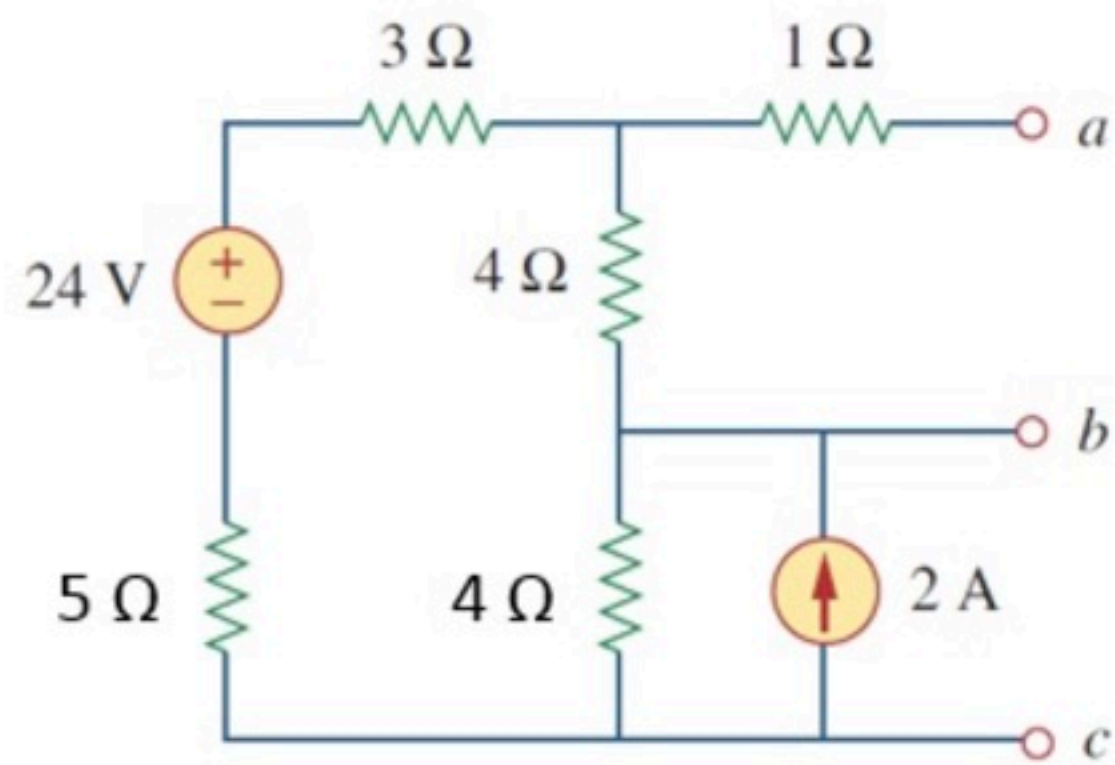


PP Circuit theorems 019

Unlimited Attempts.

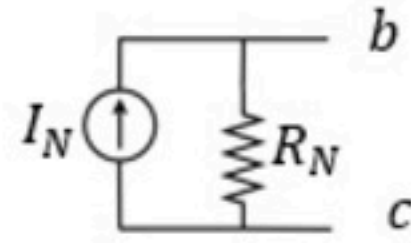Find the Norton equivalent model of this circuit, as seen between b and c.



Given Variables:

...

Calculate the following:

I_N (A) :

4



R_N (ohm) :

3



Hint: Does the 1 ohm resistor impact your calculations?