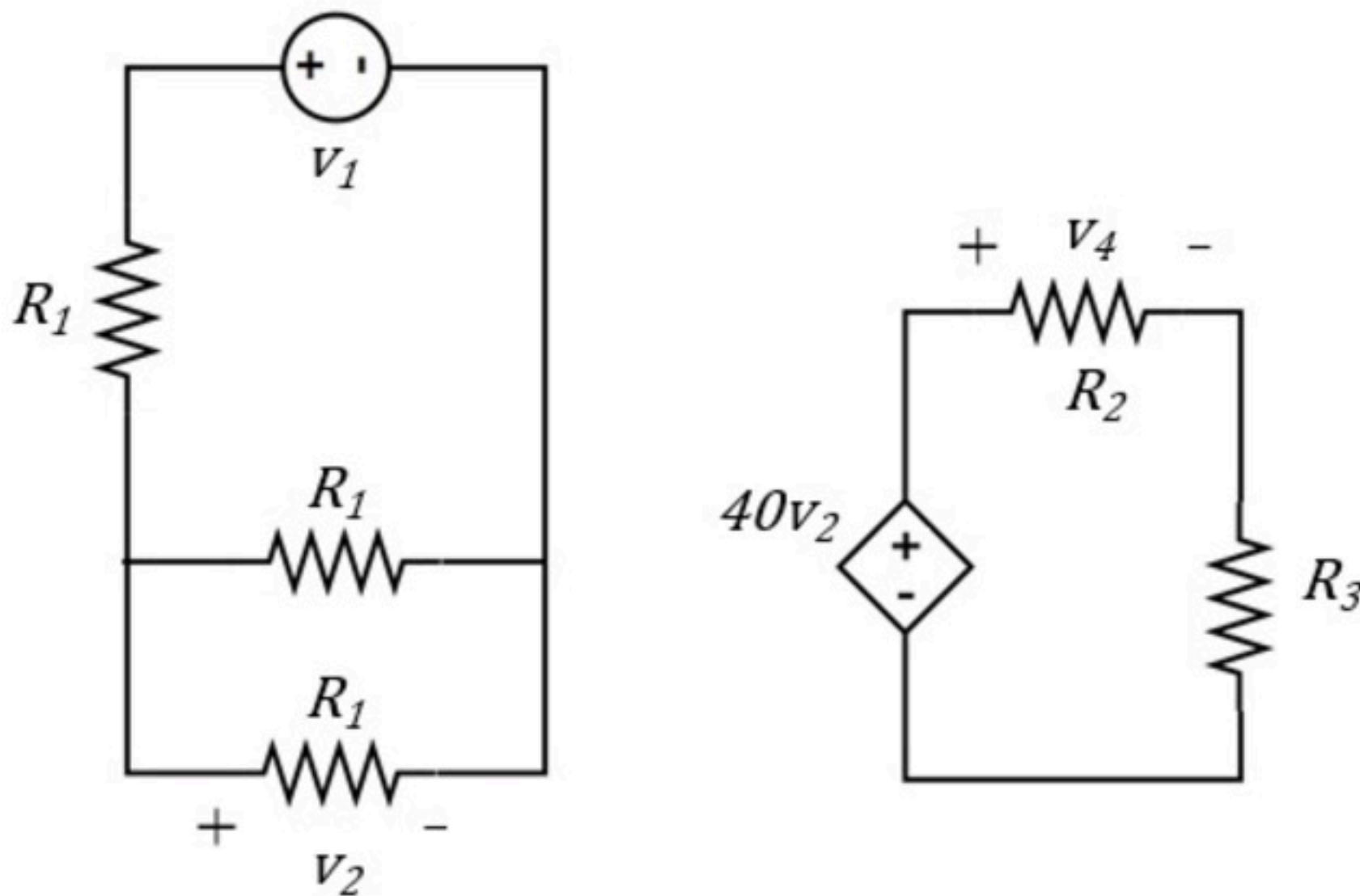


Basic analysis 007

Problem has been graded.

In this circuit, v_1 is an input, but you don't know what its value is. Find v_4 as a function of v_1 .

More specifically, find $X = \frac{v_4}{v_1}$.



Given Variables:

R_1 : 10 ohm

R_2 : 3 ohm

R_3 : 5 ohm

Calculate the following:

X (V/V) :