

Lecture 7: Blocking and Non-blocking Assignments

UCSD ECE 111

Prof. Farinaz Koushanfar

Fall 2024

Important announcements (Details in Canvas)

- **Prof office hours next week:** Tues 10/22 from 12-2pm or by email appointment
- **TA office hours:** are now MWF 9-11am for Fall'24
 - Zoom Meeting ID: 948 6397 0932; Passcode 004453
 - <https://ucsd.zoom.us/j/94863970932?pwd=iXcQXbLYjOaAQTdOJlrmglCYMSyeir.1>
- **TA Discussion session:** Wed 4-4:50PM (in person) Location: CNTRE 214
- **Oct 15:** Homework 3 was posted on Canvas
 - Due on Wed Oct 23, **10/23/24**
 - **Late homework policy:** Max of 2 late days, with 20% grade reduction per day

Homework 3 overview

- You will learn how to:
 - Create synthesizable SystemVerilog code
 - Learn about primary ports
 - Better learn how to use testbenches
 - Design functional SystemVerilog code that can post synthesis.
- There will be two parts for this homework:
 - **Homework-3a:** Developing a Synthesizable SystemVerilog Model for a 4-bit Johnson Counter
 - **Homework-3b:** Developing a synthesizable SystemVerilog model of a 4-bit Universal Shift Register.

Review

Review: System Verilog Data

- SystemVerilog data can be specified using two properties : (i) Kind and (ii) Type
 - Data kind refers to usage as net or variable
 - Data type refers to possible values a data kind can take (e.g. integer, float etc.)


- Any data can be declared using the syntax:

<data_kind> <data_type> <literal_name>

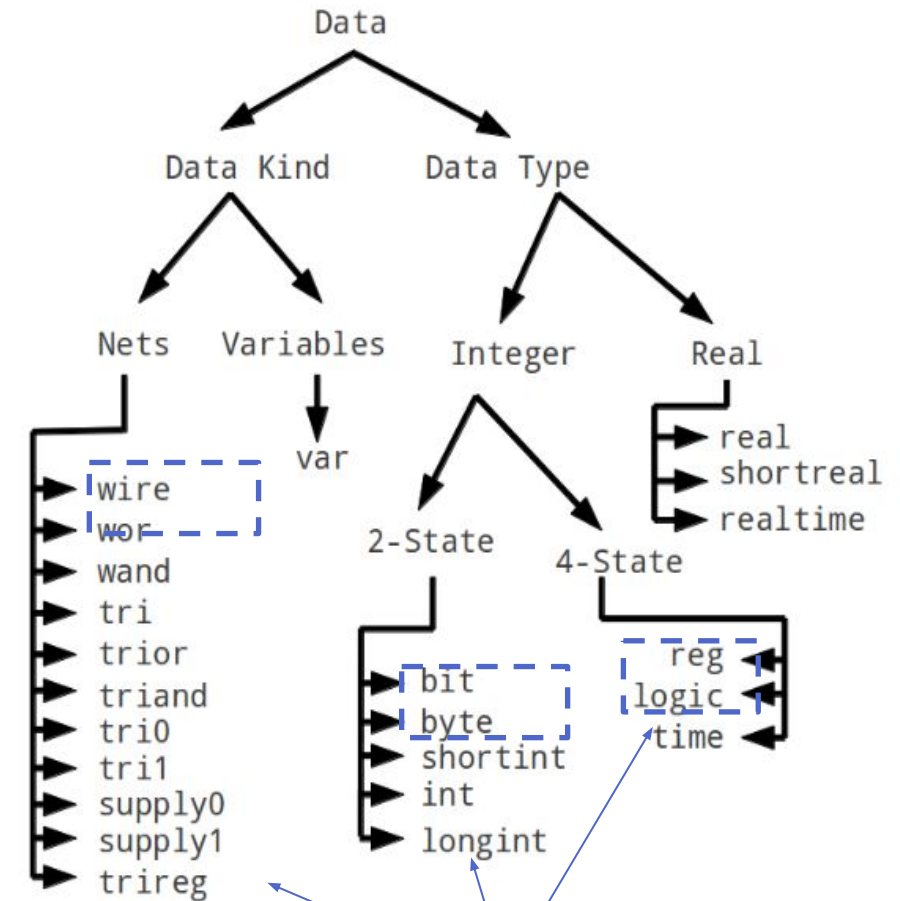example: `var logic carry_out;`
`wire logic [2:0] sum;`

Here :

- carry_out is declared as a variable which can store 4-state values
- sum is declared as a net which can store 4-state values
- logic specification after wire is optional (`wire [2:0] sum;`)



Synthesizable

Truth Table for Some Net Types

Wire/tri

	0	1	x	z
0	0	x	x	0
1	x	1	x	1
x	x	x	x	x
z	0	1	x	z

Wand/triand

	0	1	x	z
0	0	0	0	0
1	0	1	x	1
x	0	x	x	x
z	0	1	x	z


Wor/trior

	0	1	x	z
0	0	1	x	0
1	1	1	1	1
x	x	1	x	x
z	0	1	x	z


tri0

	0	1	x	z
0	0	x	x	0
1	x	1	x	1
x	x	x	x	x
z	0	1	x	0

Wand Data Type Example

 

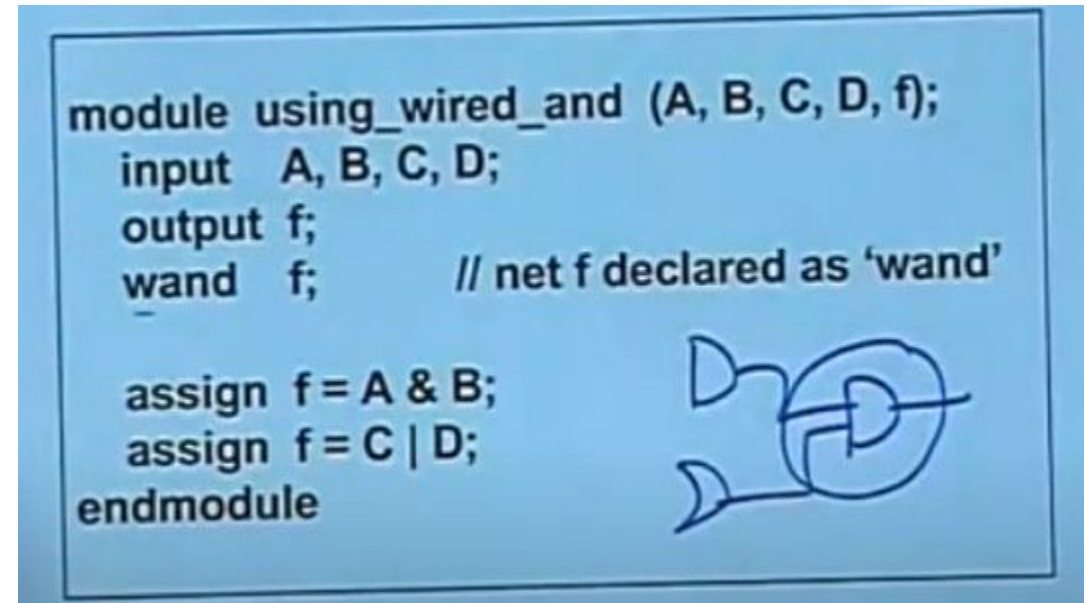Synthesis tool will give design Error
where wire 'f' is assigned from two
continuous assign statements !



Synthesis tool will connect output of
OR and AND gate and explicitly
add AND gate at the output.

Use of 2-State Variables with Caution

- Avoid all 2-state data types in RTL modeling
 - 2-state data types can hide design bugs !
 - It can lead to simulation vs synthesis mismatches
 - Synthesis treats bit, byte, shortint, int and longint 2-state data types as a 4-state reg variable. Simulation treats as 2-State variable.
 - Simulation might start with a value 0 in each bit whereas synthesized implementation might power-up with each bit a 0 or 1.
 - Any x or z driven values on 2-state variables, are converted to 0. These data types are initialized to 0 at the start of simulation and may not trigger an event for active low signals.
 - **Exception** : use 2-state int data type variable for the iterator variable in for-loops where x and z is not required.

Verilog Vs. SystemVerilog Data Types

Verilog


- For synthesizable variables supports only 4-state (0,1,X,Z) variables

SystemVerilog


- Synthesizable 2-state (0,1) data type added
- 2-state variable can be used in testbench code where X,Z are not required
- 2-state variable in RTL Model improves simulation performance and 50% reduced memory usage as compared to 4-state variables

Blocking and Non-Blocking Statements

Combinational Vs. Sequential Circuits

 

 - Output solely depends on current input values
- Does not require memory elements or clock signals
- Behavior defined by a set of output functions
- E.g.: Mux, Full adder, comparator, decoder etc.



- Output depends on current input values and state (i.e. determined by the sequence of past inputs)
- Requires clock signal and memory elements for storing the 'state'
- Behavior defined by a set of output functions and next state function
- E.g.: Flip-flop, latch, shift register, etc.

Overview

- Today's lecture applies to procedural blocks in SystemVerilog
- Two types of procedural blocks:
 1. Initial: execute only once at time zero
 2. Always: execute over and over again (always)

```
initial begin  
    <procedural statements>  
end
```

```
always@(<sensitivity list>) begin  
    <procedural statements>  
end
```

Overview of always Block

```
always@(<sensitivity list>) begin
  <procedural statements>
end
```

```
always@(a or b) begin
  c = a ^ b; // executes if value of 'a' or 'b' changes
end
```

- always procedural blocks are used to describe events that should happen under certain conditions
 - whenever any event in the sensitivity list occurs, the procedural statements are executed
 - sensitivity list can have one or more signals specified
 - **always block runs continuously throughout the simulation !**
- Event in sensitivity list can be specified in multiple different ways :
 - Edge (posedge, negedge)
 - Level (any change in value of signal)

```
// always block sensitive to
// posedge event of clock
always@(posedge clock) begin
  dout = din;
end
```

```
// always block sensitive to
// negedge event of clock
always@(negedge clock) begin
  dout = din;
end
```

```
// always block is sensitive to both
// posedge and negedge event of
// interrupt
always@(interrupt) begin
  abort = 1;
end
```

Overview of always Block

- Always procedure can be used to model :
 - Combinational logic
 - Sequential logic
 - Edge-sensitive sequential logic (such as flipflops)
 - Level-sensitive sequential logic (such as latches)

```
module flop (  
  input logic clk, d,  
  output logic q);  
  
  always@(posedge clk)  
  begin  
    q <= d;  
  end  
endmodule
```

Sequential Logic

```
module comb (  
  input logic inv, input logic [3:0] data,  
  output logic [3:0] result);  
  
  always@(inv, data) begin  
    if(inv) result = ~data;  
    else    result = data;  
  end  
endmodule
```

Combinational Logic

Posedge and Negedge Events

Positive edge (posedge) defines a rising edge of a signal


Posedge event triggers when a signal transitions from:

- 0 to 1
- 0 to X
- X to 1
- 0 to Z
- Z to 1

Negative edge (negedge) defines a falling edge of a signal

Negedge event triggers when a signal transitions from:

 - 1 to 0
- 1 to X
- X to 0
- 1 to Z
- Z to 0



System Verilog Procedural Assignments: Blocking and Non Blocking

- SystemVerilog has two types of procedural assignments to model combinational and sequential circuits/logic
 - **Blocking Assignments** represented with equal sign (=) to model **combinational** logic
 - Syntax : LHS Variable_Name = [delay or event control] RHS_Expression;
 - Example: `sum = a + b;`
 - `sum = #5 a + b;`
 - **Non-Blocking Assignments** represented with less-than-equal (<=) to model **sequential** logic, such as flip flops, latches, shift registers, etc
 - Syntax : LHS Variable_Name <= [delay or event control] RHS_Expression;
 - Example: `sum <= a + b;`

Blocking and Non Blocking Statements

Blocking

```
sum = a + b;  
prod = sum * c;
```

- Evaluation and assignment in a single step
 - Expression on RHS of (=) assignment is evaluated and the variable on LHS is updated immediately before the next sequential statement in the procedural block is evaluated and executed
- Each blocking assignment statement executes sequentially in the order it is specified in a procedural block
 - Order matters!
- Used to model combinational logic

Non-blocking

```
sum <= a + b;  
prod <= sum * c;
```

- Evaluation and assignment in two separate steps
 - Expression on RHS of (=) assignment is evaluated but the LHS variable is update is postponed till all the statements in the procedural block are evaluated and executed
- Each blocking assignment statement executes concurrently (i.e., in parallel) without blocking each other
 - Order does not matter!
- Used to model sequential logic

Blocking and Non Blocking Statements

Blocking

```
integer a, b, c, sum, prod;  
initial begin  
    a=5; b=10; c=4; sum=2; prod=8;  
    sum = a + b;  
    prod = sum * c;  
end
```

Simulation Result

- Initial values of a=5, b=10, c=4, sum=2, prod=8
- sum becomes $(5 + 10) = 15$
- prod becomes $(15 * 4) = 60$

Non-Blocking

```
integer a, b, c, sum, prod;  
initial begin  
    a=5; b=10; c=4; sum=2; prod=8;  
    sum <= a + b;  
    prod <= sum * c;  
end
```

Simulation Result

- At 1st step, a=5, b=10, c=4, sum=2, prod=8
 - Compute next sum value: $(5 + 10) = 15$
 - Compute next prod value: $(2 * 4) = 8$
- At 2nd step,
 - sum becomes 15
 - prod becomes 8

Blocking and Non Blocking Statements

```
module blocking_assignment (  
    input logic clock, a,  
    output logic b  
);  
always@(posedge clock)  
begin  
    a = 1;  
    // a is '1'  
    b = a;  
    // b is now '1' as well  
end  
endmodule
```

- Value is assigned immediately
- Process waits until the first assignment is complete, it blocks progress

```
module non_blocking_assignment (  
    input logic clock, a,  
    output logic b  
);  
always@(posedge clock)  
begin  
    a <= 1;  
    b <= a;  
    // all assignments are made  
    // b is not yet '1'  
end  
endmodule
```

- Values are assigned at the end of the block
- All assignments are made in parallel, process flow is not-blocked

Quiz: Blocking / Non Blocking Statements?

```
module blocking_assignment (  
  input logic clock  
  output logic [2:0] a=0,b=0,c=0  
);  
  
always@(posedge clock)  
begin  
  a = #5 2;  
  b = #5 4;  
  c = #10 5;  
end  
endmodule
```

```
module non_blocking_assignment (  
  input logic clock,  
  output logic [2:0] a=0,b=0,c=0  
);  
  
always@(posedge clock)  
begin  
  a <= #5 2;  
  b <= #5 4;  
  c <= #10 5;  
end  
endmodule
```

Draw the timing waveforms for when a, b, and c values change?

System Verilog Modeling and Verification

Events Scheduling Flow


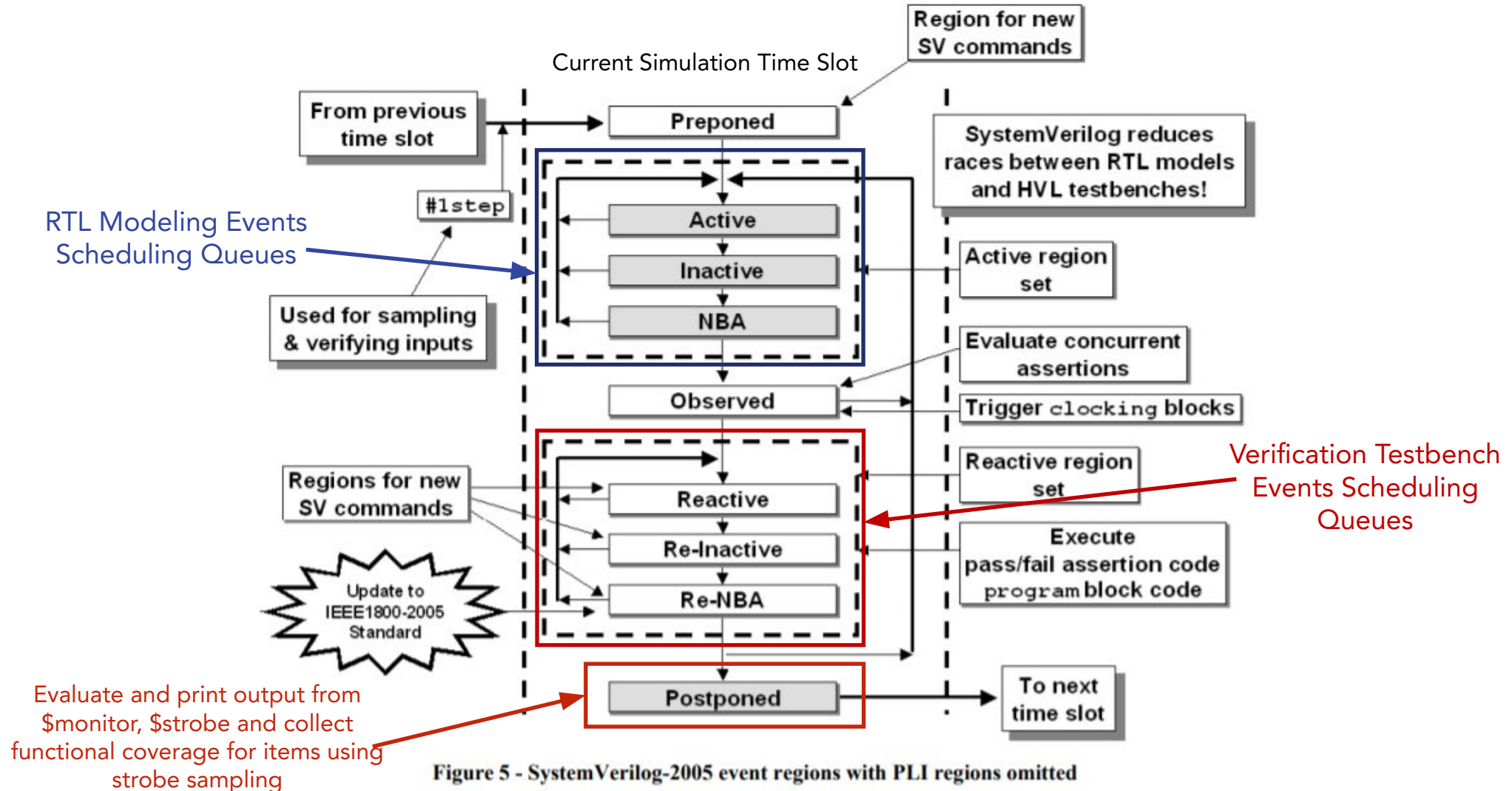


Figure 5 - SystemVerilog-2005 event regions with PLI regions omitted
Credit : Sunburst design, Clifford E. Cummings and Synopsys Arturo Salz

System Verilog RTL Modeling Schedule Flow

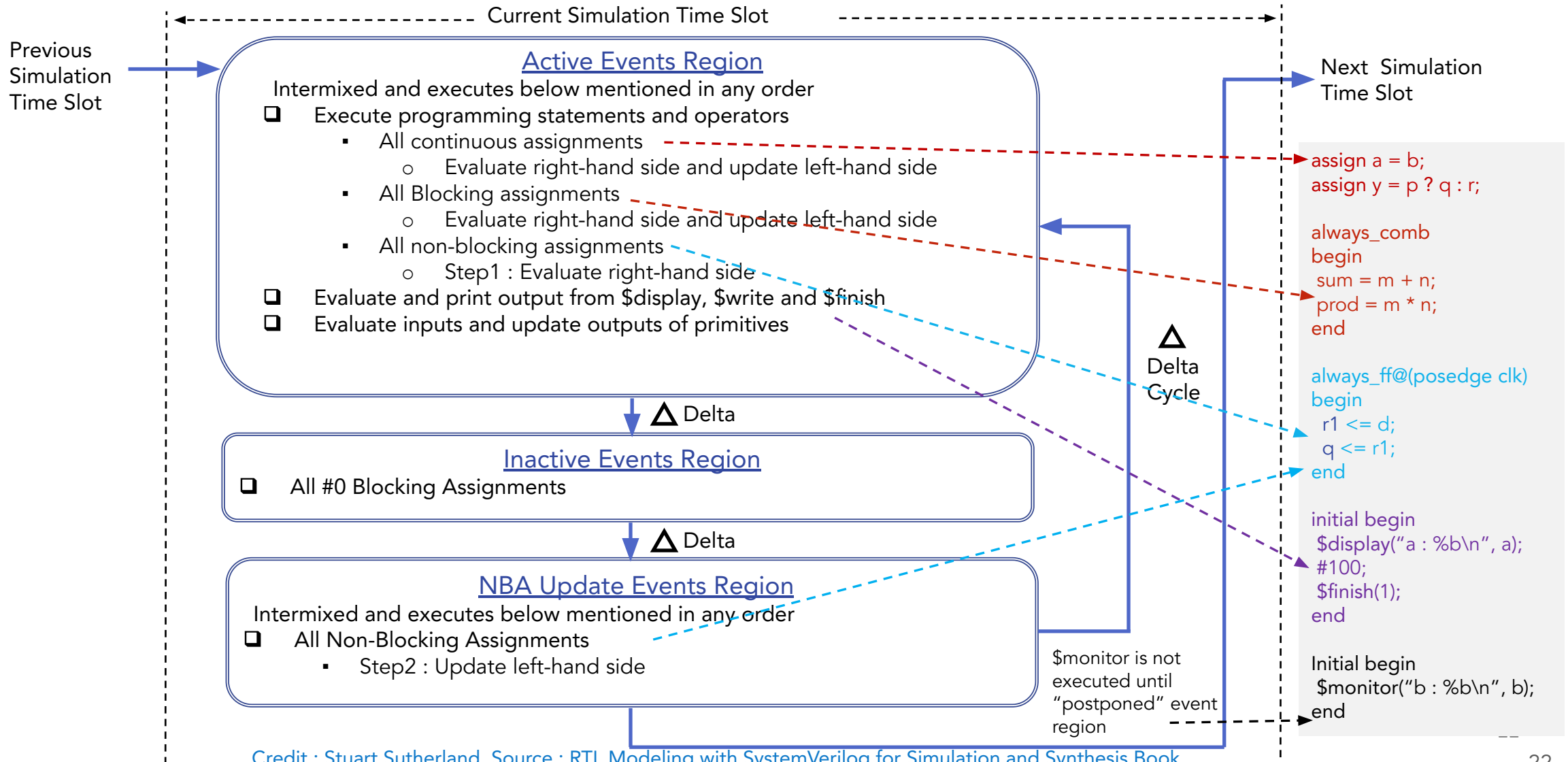

Blocking Vs. Non Blocking Assignment

```
module blocking_assignment (  
    input logic clock, a,  
    output logic b  
);  
always@(posedge clock)  
begin  
    a = 1;  
    // a is '1'  
    b = a;  
    // b is now '1' as well  
end  
endmodule
```

- Value is assigned immediately
- Process waits until the first assignment is complete, **it blocks progress**

```
module non_blocking_assignment (  
    input logic clock, a,  
    output logic b  
);  
always@(posedge clock)  
begin  
    a <= 1;  
    b <= a;  
    // all assignments are made  
    // b is not yet '1'  
end  
endmodule
```



- Values are assigned at the end of the block
- All assignments are made in parallel, **process flow is not-blocked**

Which Code Will Swap a_swap and b_swap?

```
module blocking_assignment (  
    input logic clock, rst, a, b,  
    output logic a_swap, b_swap  
);  
  
always@(posedge rst, posedge clock)  
begin  
    if (rst == 1) begin  
        a_swap = a;  
        b_swap = b;  
    end  
    else begin  
        a_swap = b_swap;  
        b_swap = a_swap;  
    end  
end  
endmodule
```


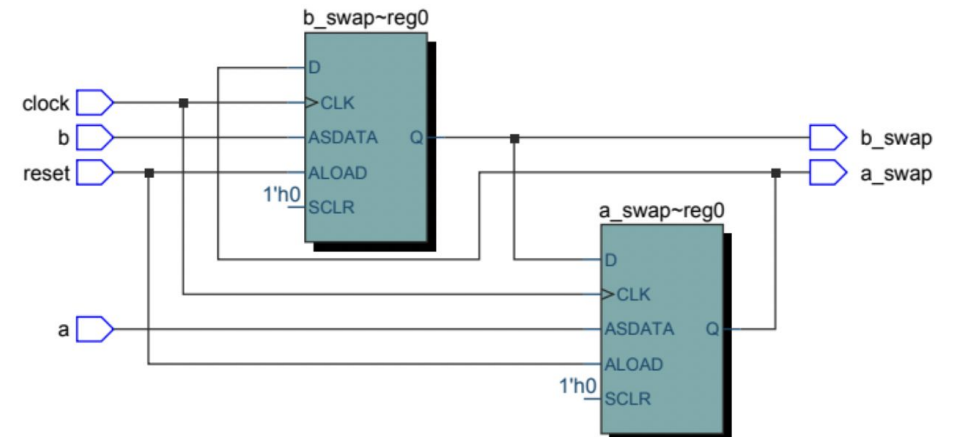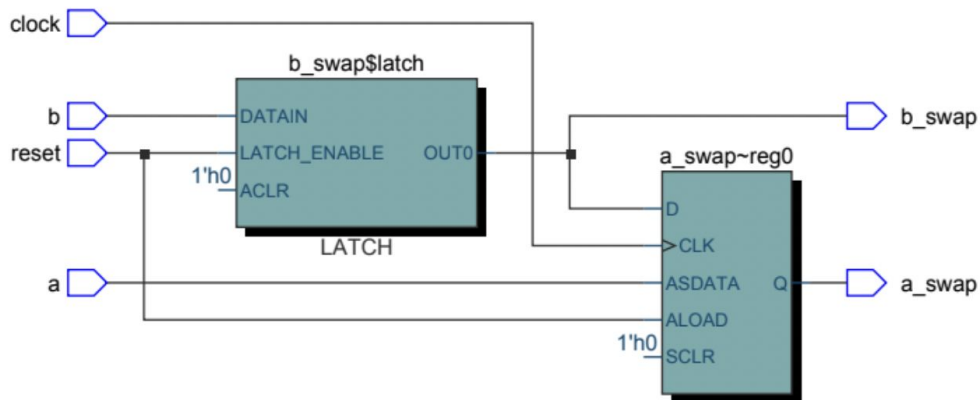
```
module non_blocking_assignment (  
    input logic clock, rst, a, b,  
    output logic a_swap, b_swap  
);  
  
always@(posedge rst, posedge clock)  
begin  
    if (rst == 1) begin  
        a_swap <= a;  
        b_swap <= b;  
    end  
    else begin  
        a_swap <= b_swap;  
        b_swap <= a_swap;  
    end  
end  
endmodule
```



The Final (p,q) Values at the Next Clock Edge...

- Assume Initial Value of $p=5$ and $q=8$

```
always@ (posedge clock) begin
    p = q;
end
always@ (posedge clock) begin
    q = p;
end
```

Both always blocks will execute concurrently and there is a **race condition** between two always procedural assignments

Two possibilities:

1. $p=8$ and $q=8$
2. $p=5$ and $q=5$

No swapping of values of p and q in either case!

```
always@(posedge clock) begin
    p = q;
    q = p;
end
```

Simulator will execute $p = q$ statement first and then execute the statement $q = p$

One possibility:

- $p=8$ and $q=8$

No swapping of values of p and q !

```
always@(posedge clock) begin
    tmp1 = p;
    tmp2 = q;
    p = tmp2;
    q = tmp1;
end
```

Simulator will execute four statements in order: (i) $tmp1 = p$, (ii) $tmp2 = q$, (iii) $p = tmp2$, (iv) $q = tmp1$.

One possibility:

- $p=8$ and $q=5$

Swapping of values of p and q happens!

The Final (p,q) Values at the Next Clock Edge...

- Assume Initial Value of $p=5$ and $q=8$

```
always@ (posedge clock) begin
    #0 p = q;
end
always@ (posedge clock) begin
    q = p;
end
```

$q=p$ statement will always execute before the $p=q$ statement as the #0 delay pushes the first statement to the "Inactive Region"

Single possibility:

1. $p=5$ and $q=5$

No swapping of values of p and q in either case!

Quiz: What Would the Synthesis Tool do?

```
module parallel_registers (  
  input logic clk, d, // clk is a clock  
  output logic q1, q2  
);  
always @(posedge clk)  
begin  
  q1 = d;  
  q2 = q1;  
end  
endmodule
```

q1 is not connected to q2
and both q1 and q2 will get
same value of d in same
clock cycle

Synthesis compiler will create two registers in parallel

```
module shift_register (  
  input logic clk, d, // clk is a clock  
  output logic q1, q2  
);  
always @(posedge clk)  
begin  
  q1 <= d;  
  q2 <= q1;  
end  
endmodule
```


q1 is serially connected to
q2. New value of d is first
propagated to q1 and one
clock cycle later it will
propagate to q2

Example of blocking vs non-blocking assignment

```
module parallel_registers (  
  input logic clk, d, // clk is a clock  
  output logic q1, q2  
);  
always @(posedge clk)  
begin  
  q1 = d;  
  q2 = q1;  
end  
endmodule
```

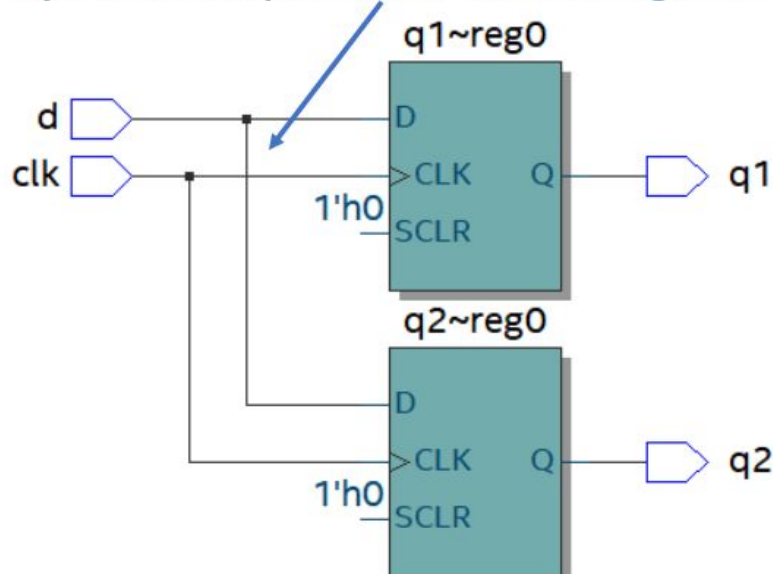q1 is not connected to q2
and both q1 and q2 will get
same value of d in same
clock cycle

Synthesis compiler will create two registers in parallel



```
module shift_register (  
  input logic clk, d, // clk is a clock  
  output logic q1, q2  
);  
always @(posedge clk)  
begin  
  q1 <= d;  
  q2 <= q1;  
end  
endmodule
```

q1 is serially connected to
q2. New value of d is first
propagated to q1 and one
clock cycle later it will
propagate to q2

Synthesis compiler will create two serially chained registers
and circuit will behave as a two bit shift register

