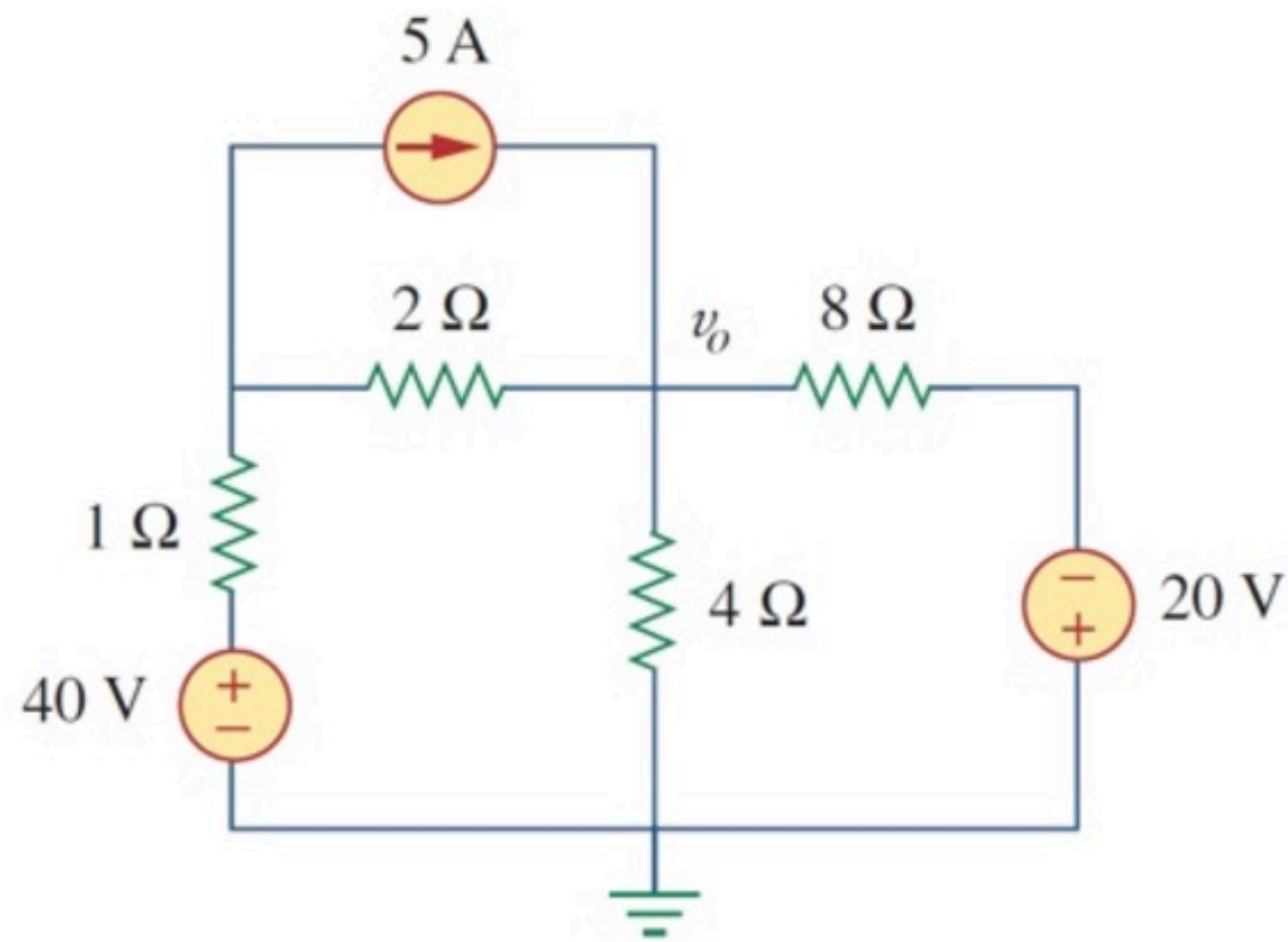


# PP Nodal Mesh 020

Unlimited Attempts.

Find the voltage  $v_o$ . Solve using mesh analysis.

For extra practice: Afterwards solve again using nodal analysis.



Given Variables:

...

Calculate the following:

$v_o$  (V) :

20



Hint: Can we find a mesh current directly?