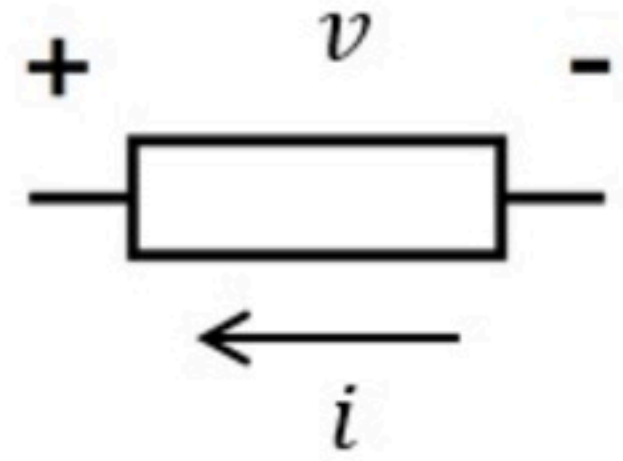



# PP - Basic concepts 005

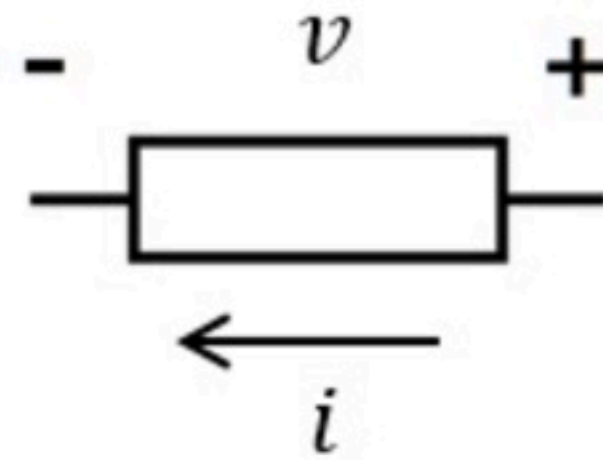Problem has been graded.


Find the power  $P_1$  received by this element:



Find the power  $P_2$  received by this element:



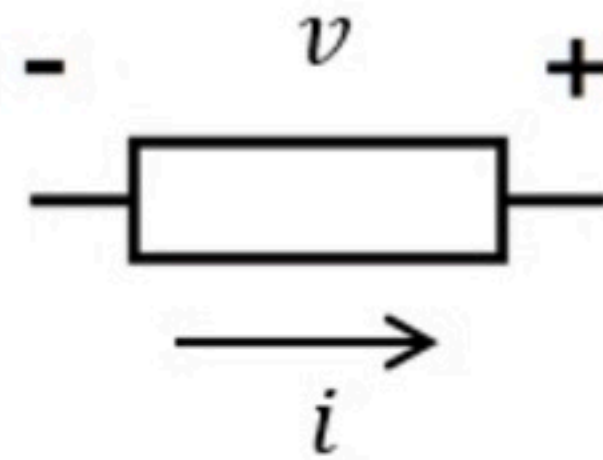Find the power  $P_3$  supplied by this element:



Given Variables:

$v : 2 \text{ V}$

$i : -3 \text{ A}$

Calculate the following:

$P_1 \text{ (W) :}$

6



$P_2 \text{ (W) :}$

-6



$P_3 \text{ (W) :}$

-6



Hint: Convert first to passive sign convention