
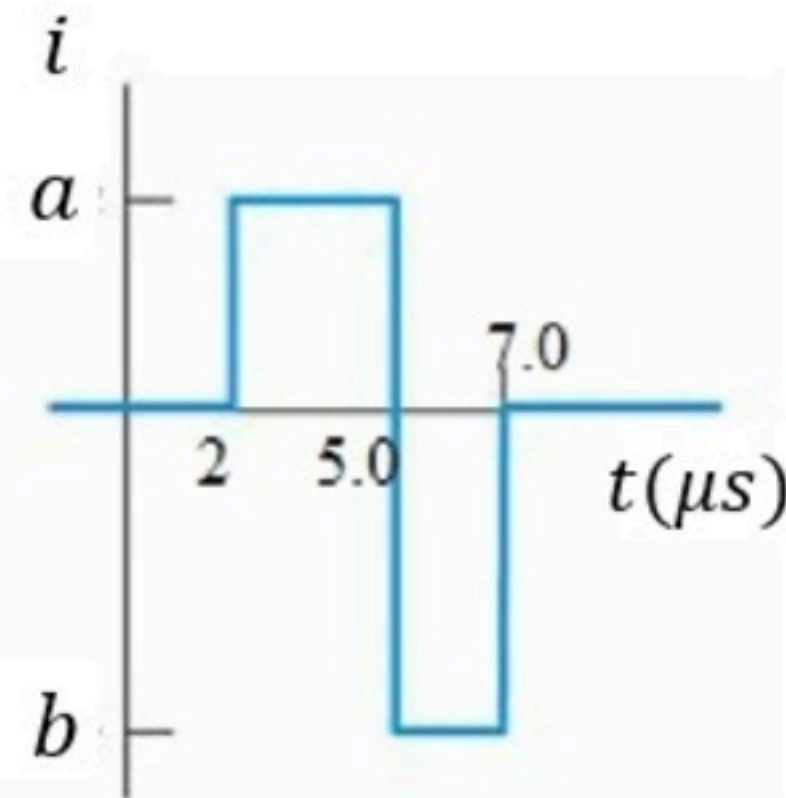
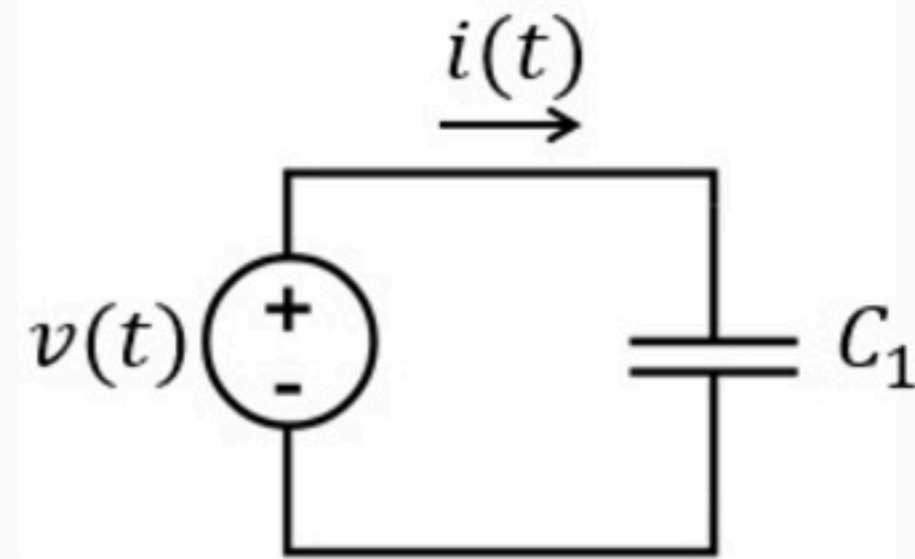


Capacitors Inductors 003

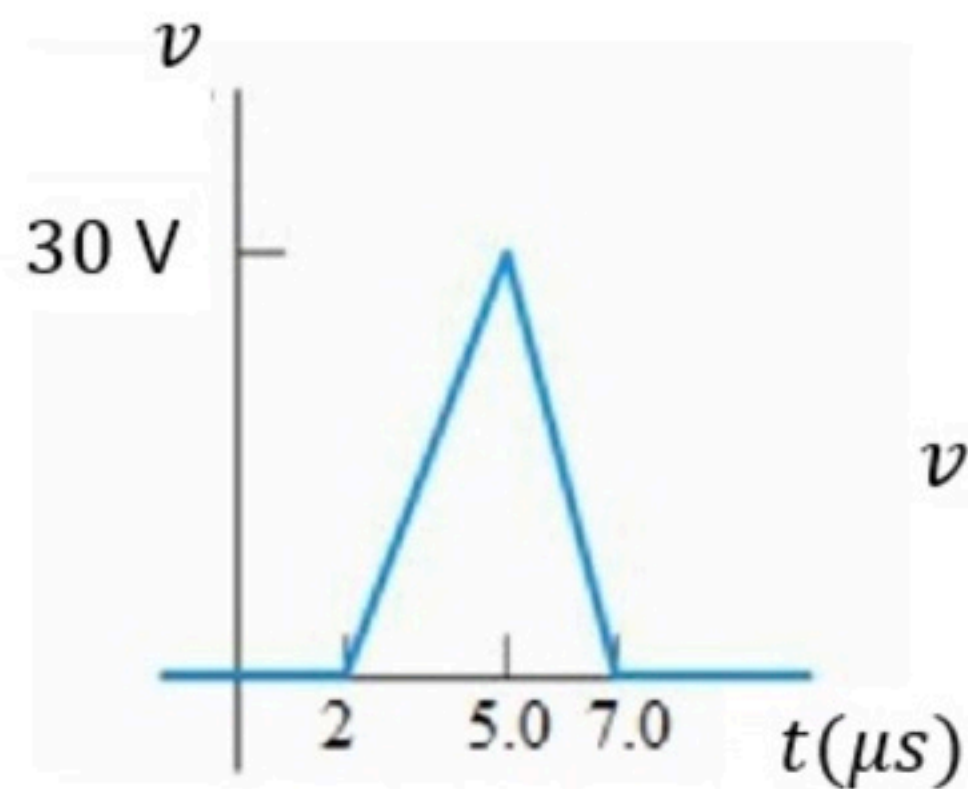Problem has been graded.

Given the two plots of the voltage and current of the capacitor.
Find the values of a and b labeled on the graph.



Given Variables:

$C_1 : 8 \text{ nF}$

Calculate the following:

$a \text{ (A)} :$

0.08



$b \text{ (A)} :$

-0.12

