

Lecture 13: Finite State Machines II

UCSD ECE 111

Prof. Farinaz Koushanfar

Fall 2024

Important announcements (Details in Canvas)

- **Prof office hours next week:** Tues 11/12 from 12-2pm or by email appointment
- **TA office hours:** are now MWF 9-11am for Fall'24
 - Zoom Meeting ID: 948 6397 0932; Passcode 004453
 - <https://ucsd.zoom.us/j/94863970932?pwd=iXcQXbLYjOaAQTdOJlrmglCYMSyeir.1>
- **TA Discussion session:** Wed 4-4:50PM (in person) Location: CNTRE 214
- **Nov 5:** Homework 6 posted on Canvas
 - Due on Wed Nov **11/13/24**
 - **Late homework policy:** Max of 2 late days, with 20% grade reduction per day


Homework 6 overview

- Design of a synthesizable SystemVerilog code for a Vending Machine (Moore and Mealy), and Synchronous FIFO, and design a system for UART communication protocol by implementing Rx-Tx communication system and a UART controller.
- You will learn how to:
 - Create synthesizable SystemVerilog code
 - Better learn how to use testbenches
 - Design functional SystemVerilog code that can compile post synthesis.
- There will be three parts for this homework:
 - **Homework-6a:** Developing a Synthesizable SystemVerilog model for a of a Vending Machine (Moore and Mealy FSM).
 - **Homework-6b:** Developing a synthesizable SystemVerilog model of a synchronous FIFO.
 - **Homework-6c:** Developing a synthesizable SystemVerilog model of a UART communication system with a Receiver, Transmitter, and a UART controller.

Recap

Finite State Machines (FSMs)


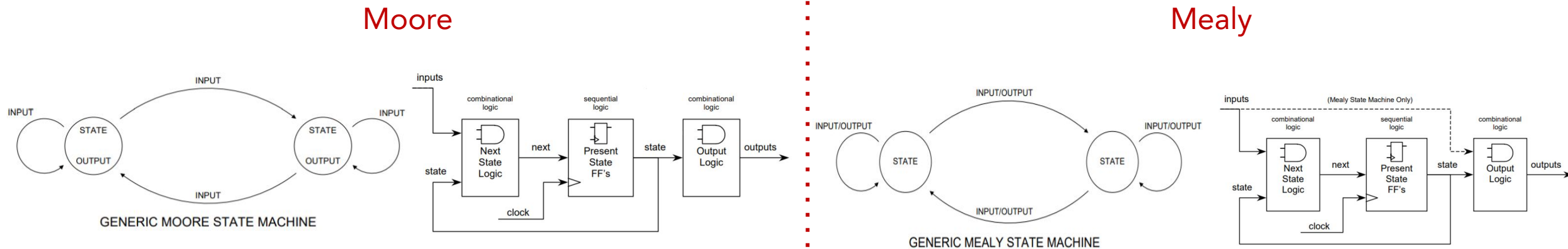
- Moore FSM:
 - 2 always block
 - 3 always block
 - 1 always block (delayed output)
- Mealy FSM:
 - 2 always block approach



True or False?

The FSMs corresponding to the following two state diagrams are equivalent

- ☐ True
- ☐ False

  


Multiple Choice Questions

Select which of the following mentioned statements are true for Moore and Mealy finite state machines. Select **all** statements which are true :

- ☐ Output from Moore FSM depends only on current state
- ☐ Moore FSM output reacts to input immediately
- ☐ Registering Mealy FSM output is equivalent to Moore FSM output
- ☐ Output from Mealy FSM depends on both present state and inputs

Registering Mealy Machine = Moore Machine!

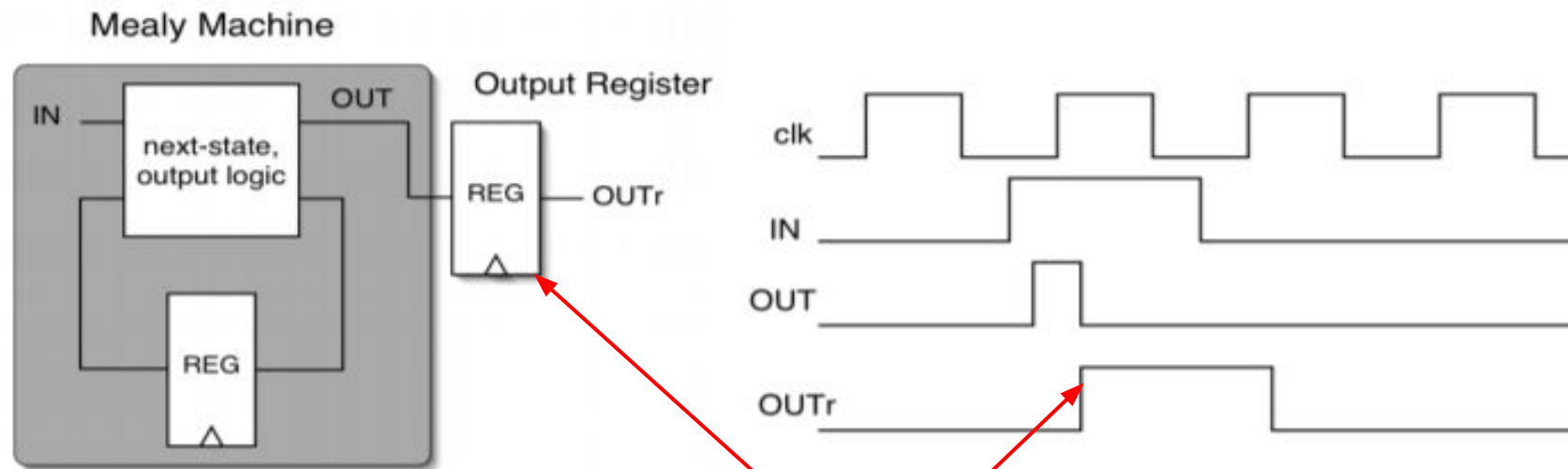- The output timing behavior of the Moore machine can be achieved in a Mealy machine by “**registering**” the Mealy output values i.e., by having a **flipflop** at the output signal



Registered output of Mealy matches the output timing behavior of Moore machine

State Encoding

State Encoding

- States in FSM are represented by **encoded value**. There are many choices:

1. Binary encoding
2. One-hot encoding
3. Gray encoding
4. Johnson encoding
5. Etc.

Most common!



Binary and One-Hot Encoding

Binary encoding

- For **N** states, use **$\text{ceil}(\log_2 N)$** bits to encode the states, with each state represented by a unique combination of the bits
- Example (with 4 states):
 - **enum** logic [1:0] {**RESET** = 2'b00, **WAIT** = 2'b01, **LOAD** = 2'b10, **DONE** = 2'b11} next_state
- Tradeoffs:
 - Most **efficient use of state registers** (less number of Flipflops are required)
 - **Slower** and **more complicated** combinational logic to detect when in a particular state

One-hot encoding

- For **N** states, **N** bits to encode the states, with bit corresponding to the current state set 1 and all the other bits set to 0
- Example (with 4 states):
 - **localparam** **RESET** = 4'b0001, **WAIT** = 4'b0010, **LOAD** = 4'b0100, **DONE** = 4'b1000;
- Tradeoffs:
 - Usually leads to **simpler** and **faster** designs as there is much less combinational logic for state decoding (generally a good choice to optimize for speed and power)
 - **Costly** in terms of the number for Flipflops required for a large number of states => **more area!**

State Encoding Constants and Variable Declaration

1. Using enumeration

```
enum logic [1:0] {WAIT=2'b00, EDGE=2'b01}  
present_state, next_state;
```

2. Using parameter

```
parameter logic [1:0] WAIT = 2'b00, EDGE =  
2'b01;  
logic [1:0] present_state, next_state;
```


3. Using local parameter

```
localparam logic [1:0] WAIT = 2'b00, EDGE =  
2'b01;  
logic [1:0] present_state, next_state;
```

4. Using typedef (SystemVerilog only)

```
typedef enum logic [1:0] {WAIT=2'b00,  
EDGE=2'b01} e_states;  
e_states present_state, next_state
```


One-Hot FSM Implementation Example

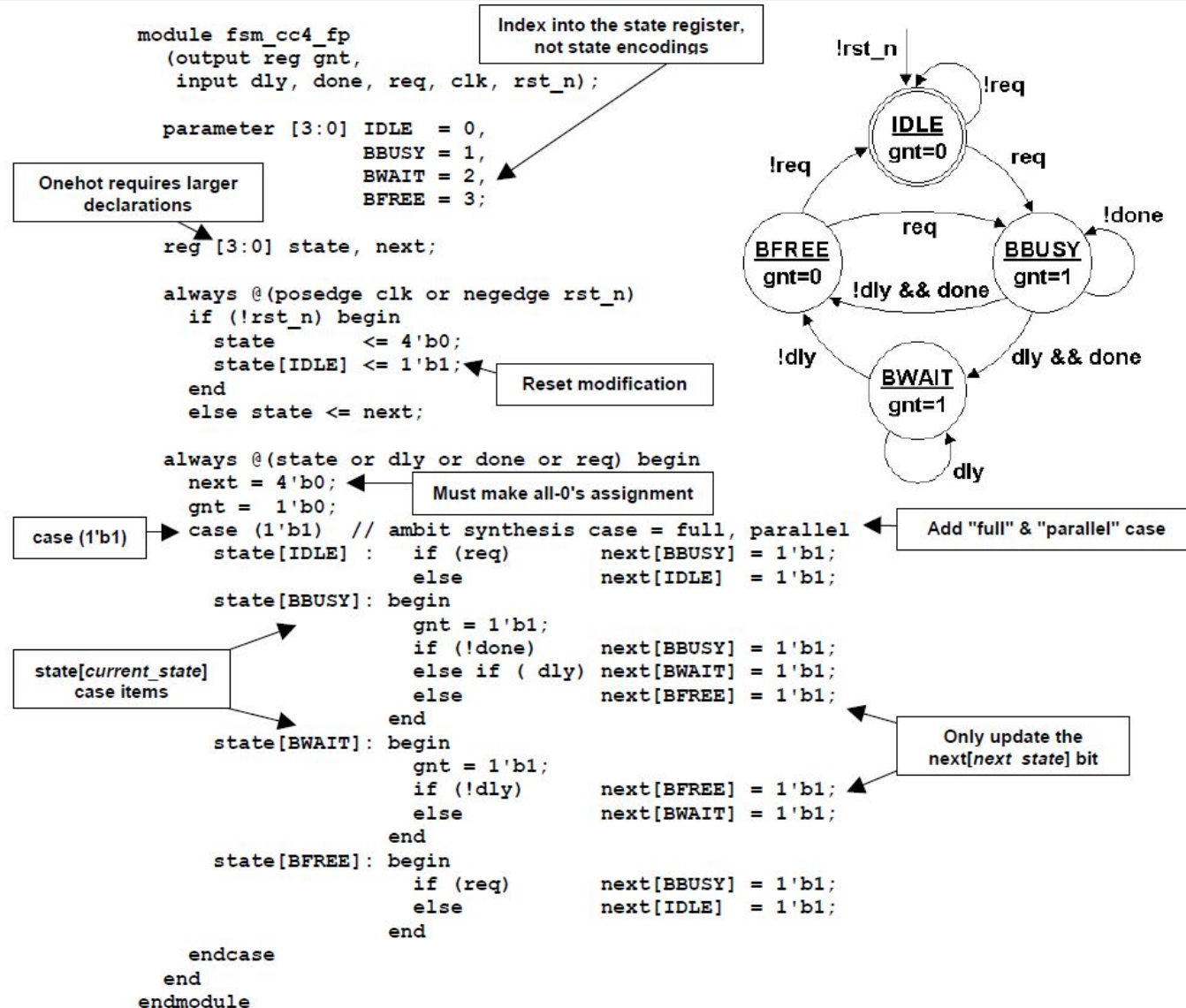

One-Hot State Encoding

- In case of **one-hot encoding style** FSM, Quartus Prime **will not auto-generate FSM state diagrams!**
 - **Example:** if sequence detector state machine state encoding is changed from binary counting to one hot encoding style as described below, no state machine diagram generated however it will still work as an FSM
 
```
parameter[3:0] IDLE=4'b0001, S1=4'b0010, S2=4'b0100, S3=1000;  
logic[3:0] present_state, next_state;
```



Sequence Detector State machine diagram will not be generated by Quartus Synthesizer
Functionally logic will still behave as a correct FSM !


FSM Design Steps

FSM Design Steps Using SystemVerilog

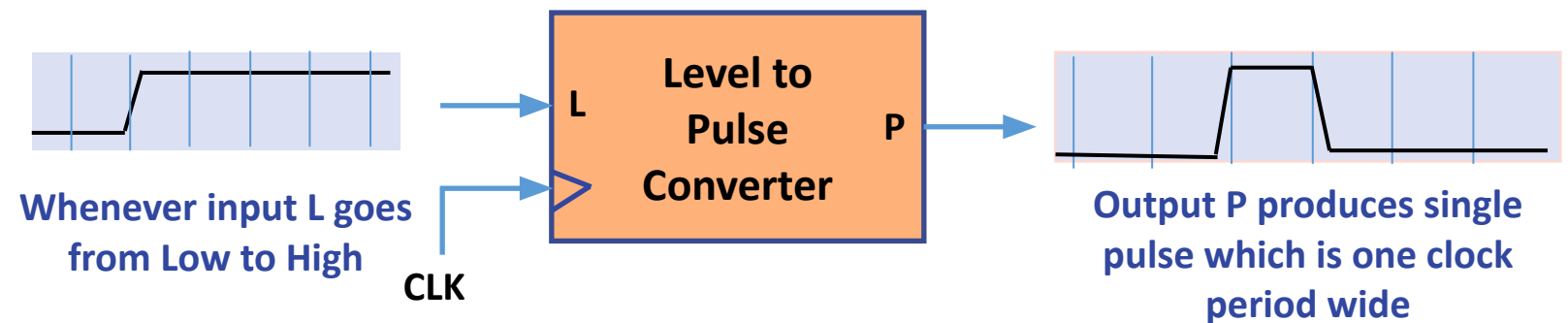1. Specify circuit **function**
2. Draw **state transition** diagram
3. **Minimize** number of states (later lecture!)
4. Derive **state transition** table
5. Determine **next state** and **output function**
 - For Moore style machine make outputs dependent only on state not dependent on inputs
6. Assign **encodings** (bit patterns) to symbolic states
7. **Implement** State Machine using SystemVerilog :
 - Use either of the **parameters/enum/localparam/typedef** to represent encoded states.
 - Use **separate always blocks** for next state register assignment and combinational logic blocks
 - Use **always_comb** for all combinational block specification
 - Use **case statements** within combinational block (including **default case** item expression to avoid latches) to assign all outputs and next state value based on inputs


Level to Pulse Converter

- **A level-to-pulse converter produces a single cycle pulse each time its input goes high**
 - It is also known as **synchronous rising edge detector**
 - Example use-case: pushing a button of a signal traffic light controller at pedestrian crossing; the pedestrian pressing the button for an arbitrary period of time should generate a single-cycle enable signal for counters in traffic light controller system



Level to Pulse Converter : Moore and Mealy State Diagrams


Moore State Transition Diagram

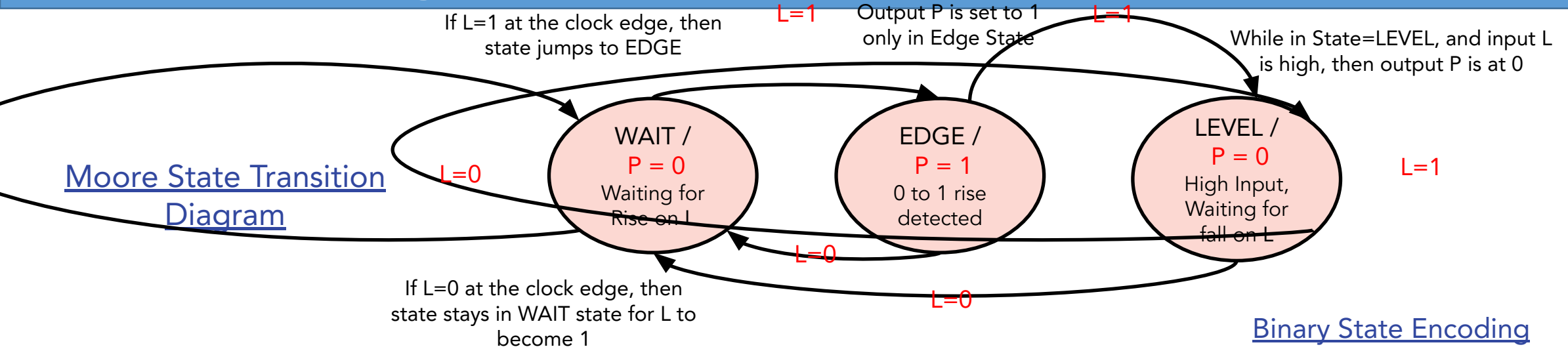

Binary State Encoding

- WAIT (2'b00) : Input is '0', wait for '1'
- EDGE (2'b01) : '0' to '1' edge detected on Input
- LEVEL (2'b11): Input is stable at '1'

Mealy State Transition Diagram

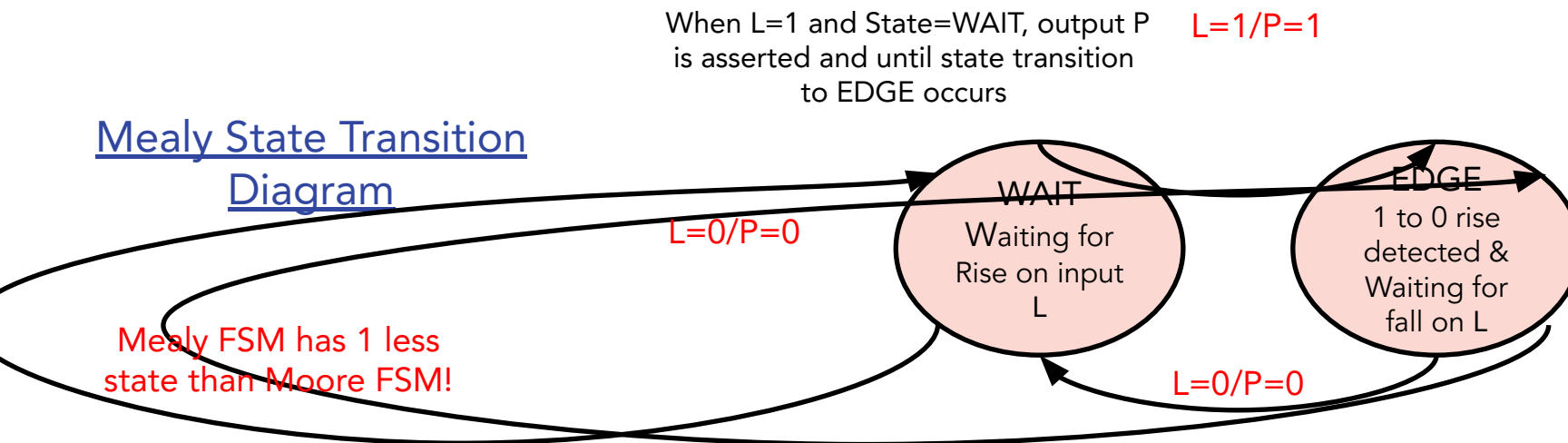

Mealy FSM has 1 less state than Moore FSM!

While in State=EDGE, and input L is high, then output P is at 0

Level to Pulse Converter (Moore FSM)


```
module level_to_pulse_converter_moore(  
    input logic clk, rstn,  
    input logic L,  
    output logic P);  
  
    // FSM state encodings and state registers declaration  
    enum logic[1:0] {WAIT=2'b00,  
                    EDGE=2'b01,  
                    LEVEL=2'b11} present_state, next_state;  
  
    // Sequential Logic for present state  
    always_ff@(posedge clk) begin  
        if(!rstn)  
            present_state <= WAIT;  
        else  
            present_state <= next_state;  
        end  
    end
```

(continued....)

```
    // Combination Logic for Next State and Output  
    always_comb begin  
        case(present_state)  
            WAIT: begin  
                P = 0;  
                if(L==1) next_state = EDGE;  
                else next_state = WAIT;  
            end  
            EDGE: begin  
                P = 1;  
                if(L==1) next_state = LEVEL;  
                else next_state = WAIT;  
            end  
            LEVEL: begin  
                P = 0;  
                if(L==1) next_state = LEVEL;  
                else next_state = WAIT;  
            end  
            default: begin  
                P = 0; next_state = WAIT;  
            end  
        endcase  
    end  
endmodule: level_to_pulse_converter_moore
```


Level to Pulse Converter Simulation and Synthesis Results (Moore FSM)

Post Synthesis RTL Netlist Schematic

 

Resource	Usage
Estimated ALUTs Used	2
-- Combinational ALUTs	2
-- Memory ALUTs	0
-- LUT_REGS	0
Dedicated logic registers	2

Moore State Diagram

 


Mealy State Transition Table

	Source State	Destination State	Condition
1	EDGE	LEVEL	(L).(rstn)
2	EDGE	WAIT	(!L) + (L).(!rstn)
3	LEVEL	LEVEL	(L).(rstn)
4	LEVEL	WAIT	(!L) + (L).(!rstn)
5	WAIT	WAIT	(!L) + (L).(!rstn)
6	WAIT	EDGE	(L).(rstn)

2 Flipflops to represent three states WAIT EDGE, LEVEL

Simulation Waveform

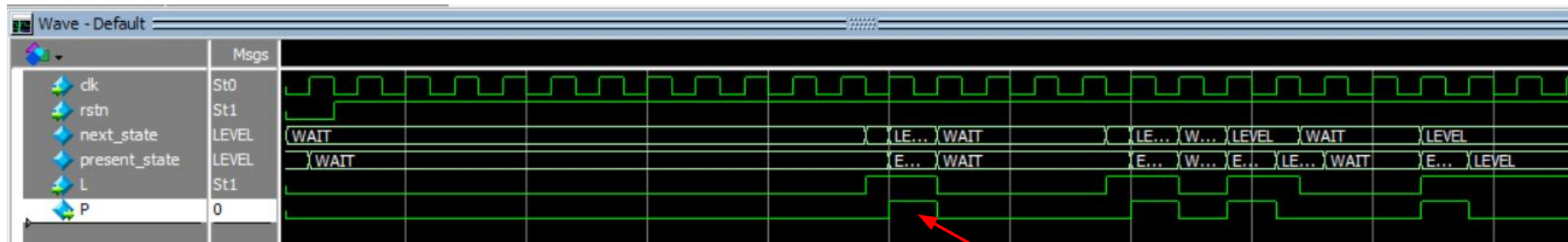

Output P is a single cycle pulse, available sometime after there is a rising edge on input L


Level to Pulse Converter (Mealy FSM)

```
module level_to_pulse_converter_mealy(  
    input logic clk, rstn,  
    input logic L,  
    output logic P);  
  
    // FSM state encodings and state registers declaration  
    enum logic[1:0] WAIT=2'b00,  
                    EDGE=2'b01 present_state,  
    next_state;  
  
    // Sequential Logic for present state  
    always_ff@(posedge clk) begin  
        if(!rstn)  
            present_state <= WAIT;  
        else  
            present_state <= next_state;  
        end  
  
    (continued....)
```


```
    // Combination Logic for Next State and Output  
    always_comb begin  
        case(present_state)  
            WAIT: begin  
                if(L==1) begin  
                    next_state = EDGE; P = 1;  
                end  
                else begin  
                    next_state = WAIT; P = 0;  
                end  
            end  
            EDGE: begin  
                if(L==1) begin  
                    next_state = EDGE; P = 0;  
                end  
                else begin  
                    next_state = WAIT; P = 0;  
                end  
            end  
            default: begin P = 0; next_state = WAIT; end  
        endcase  
    end  
endmodule: level_to_pulse_converter_mealy
```

Level to Pulse Converter Simulation and Synthesis Results (Mealy FSM)

Post Synthesis RTL Netlist Schematic

 

Moore State Diagram

 

Mealy State Transition Table


	Source State	Destination State	Condition
1	EDGE	EDGE	(L).(rstn)
2	EDGE	WAIT	(!L) + (L).(!rstn)
3	WAIT	EDGE	(L).(rstn)
4	WAIT	WAIT	(!L) + (L).(!rstn)

Resource	Usage
▼ Estimated ALUTs Used	2
-- Combinational ALUTs	2
-- Memory ALUTs	0
-- LUT_REGS	0
Dedicated logic registers	1

1 Flipflop to represent two states WAIT and EDGE.

1 less D-flipflop required in Mealy compared to Moore FSM

Simulation Waveform

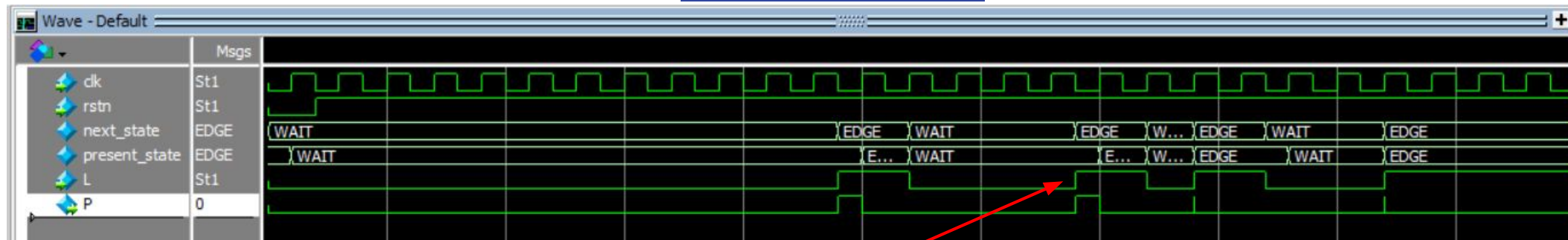

Output P is available as soon as input L changed from '0' to '1'. However output P pulse is not stable for 1 cycle. Which does not meet design requirement for P to be 1 cycle pulse!

Level to Pulse Converter (Mealy FSM + Registered output)

```
module level_to_pulse_converter_mealy(  
    input logic clk, rstn,  
    input logic L,  
    output logic P);  
  
// FSM state encodings and state registers declaration  
enum logic[1:0] {WAIT=2'b00,  
                 EDGE=2'b01} present_state, next_state;  
  
logic r_P; // local variable declaration  
  
// Sequential Logic for present state  
always_ff@(posedge clk) begin  
    if(!rstn) begin  
        present_state <= WAIT;  
        P <= 0;  
    end  
    else begin  
        present_state <= next_state;  
        P <= r_P; ←  
    end  
end  
(continued....)
```


Synthesizer will create D-flipflop to provide registered output P. Output P is registered to ensure P is at least 1 cycle pulse

```
// Combination Logic for Next State and Output  
always_comb begin  
    case(present_state)  
        WAIT: begin  
            if(L==1) begin  
                next_state = EDGE; r_P = 1;  
            end  
            else begin  
                next_state = WAIT; r_P = 0;  
            end  
        end  
        EDGE: begin  
            if(L==1) begin  
                next_state = EDGE; r_P = 0;  
            end  
            else begin  
                next_state = WAIT; r_P = 0;  
            end  
        end  
        default: begin r_P = 0; next_state = WAIT; end  
    endcase  
end  
endmodule: level_to_pulse_converter_mealy
```


Output is assigned to local variable r_P

Level to Pulse Converter Simulation and Synthesis Results (Moore FSM)

Post Synthesis RTL Netlist Schematic

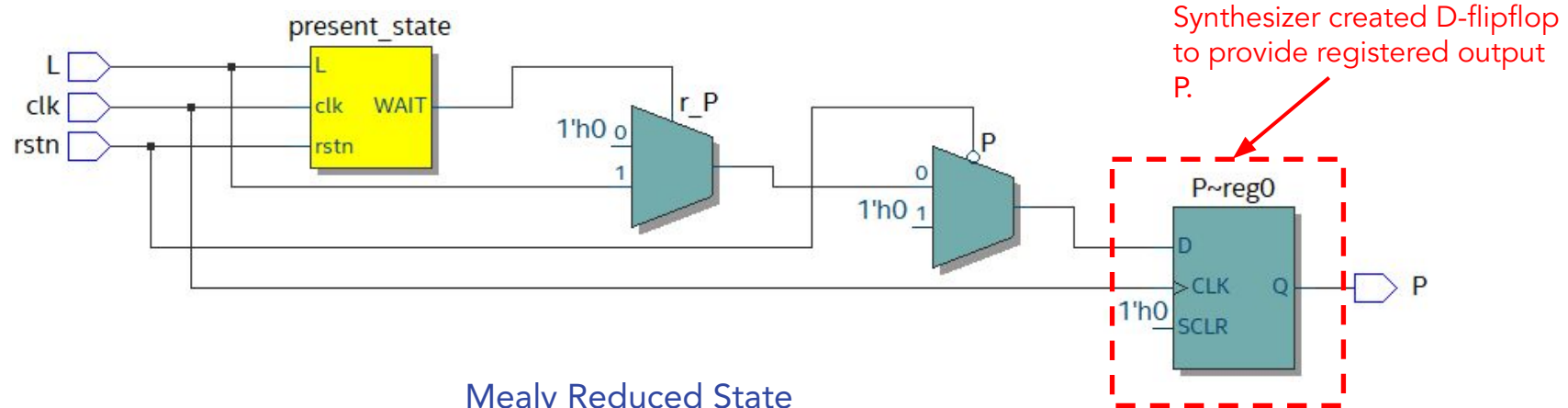

Mealy Reduced State Diagram

 

Only 2 states in Mealy FSM compared to Moore which has 3 States

Mealy Reduced State Transition Table

	Source State	Destination State	Condition
1	EDGE	WAIT	$(!L) + (L).(!rstn)$
2	EDGE	EDGE	$(L).(rstn)$
3	WAIT	WAIT	$(!L) + (L).(!rstn)$
4	WAIT	EDGE	$(L).(rstn)$


Post Synthesis Resource Utilization

Resource	Usage
Estimated ALUTs Used	2
-- Combinational ALUTs	2
-- Memory ALUTs	0
-- LUT_REGS	0
Dedicated logic registers	2

1 Flipflop for registering output P and 1 Flipflop for representing two states WAIT and EDGE

Level to Pulse Converter Simulation Result(Mealy FSM) : With Registered Output

Post Synthesis RTL Netlist Schematic

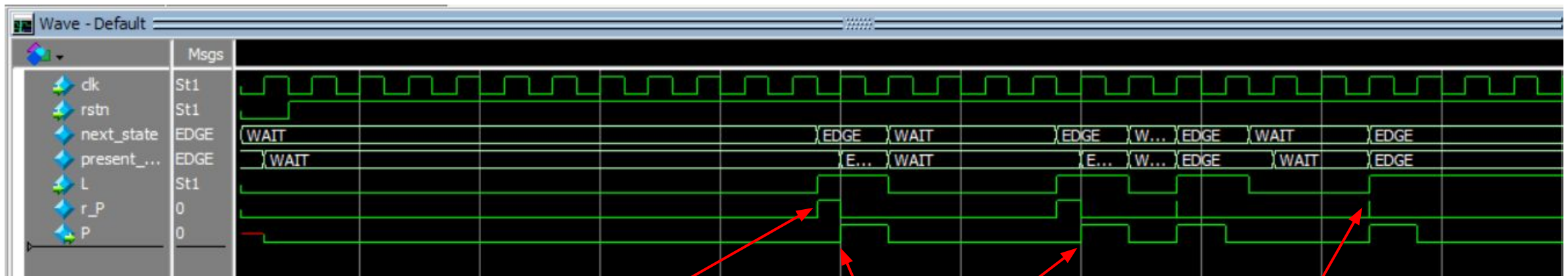

Unregistered output r_P is available as soon as input L changed from '0' to '1'

Registered Output P which is single cycle pulse when there is rising edge on L detected.

Glitches in simulation on unregistered output r_P

True or False?

Two or three always block approaches for Moore FSMs are equivalent

- ☐ True
- ☐ False

Example 1: Vending Machine


- Vending Machine: A soft drink dispenser
- Accepts Nickel (¢5), Dime (¢10), and Quarter (¢25)
- Dispenses a drink when receives ¢35
- Returns change



Ref: http://www.ece.uc.edu/~wjone/Digital/Drinking_machine.pdf


Diagram

- Inputs and outputs
- Other units

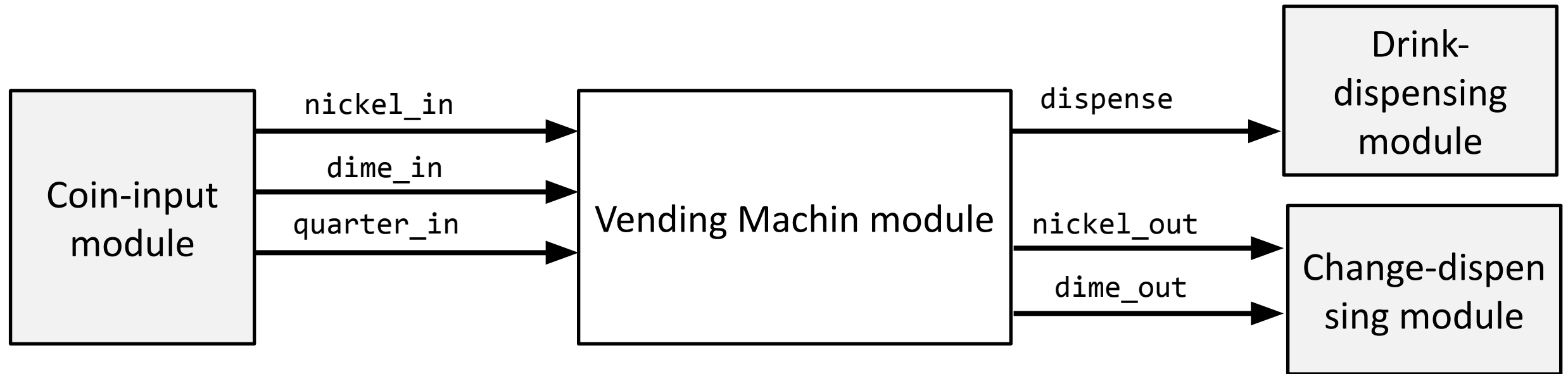


Vending Machine

 
- Let's draw a Mealy FSM
- The states represent sum of the inserted coins (do we need more?).




nickel_in

 

dime_in

 

quarter_in

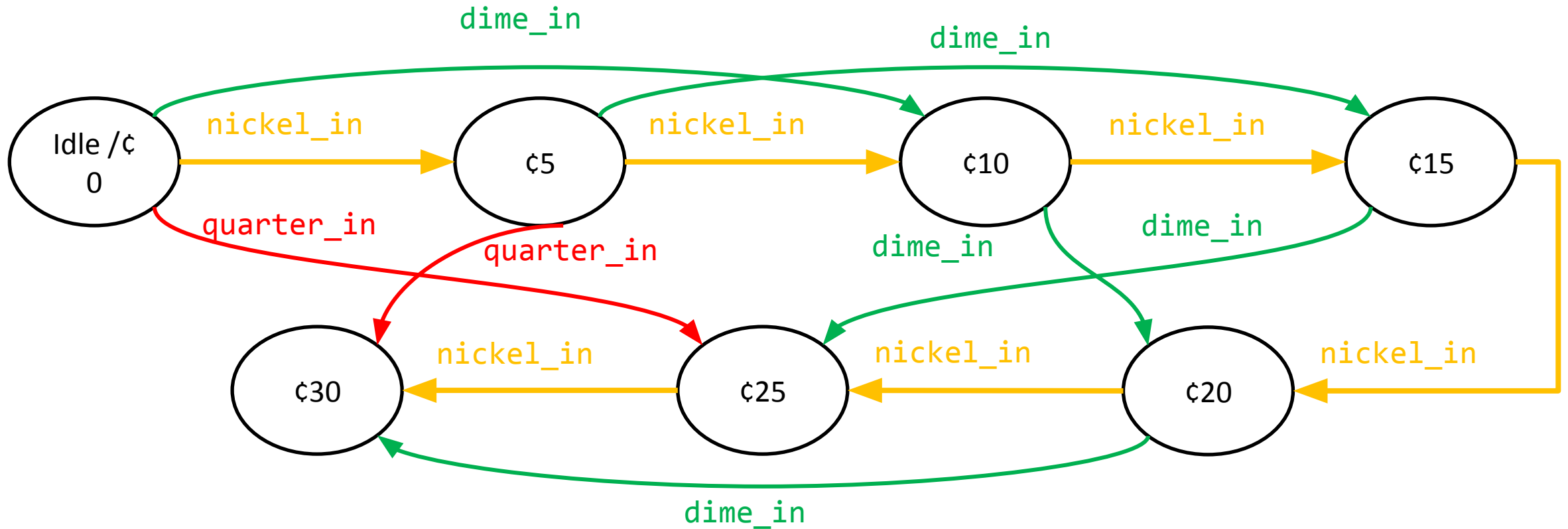


Output


- Output:
 - {dispense, nickel_out, dime_out}
 - E.g, output = 3'b110 (/110) means dispense and return a nickel.

Output/


quarter_in/100

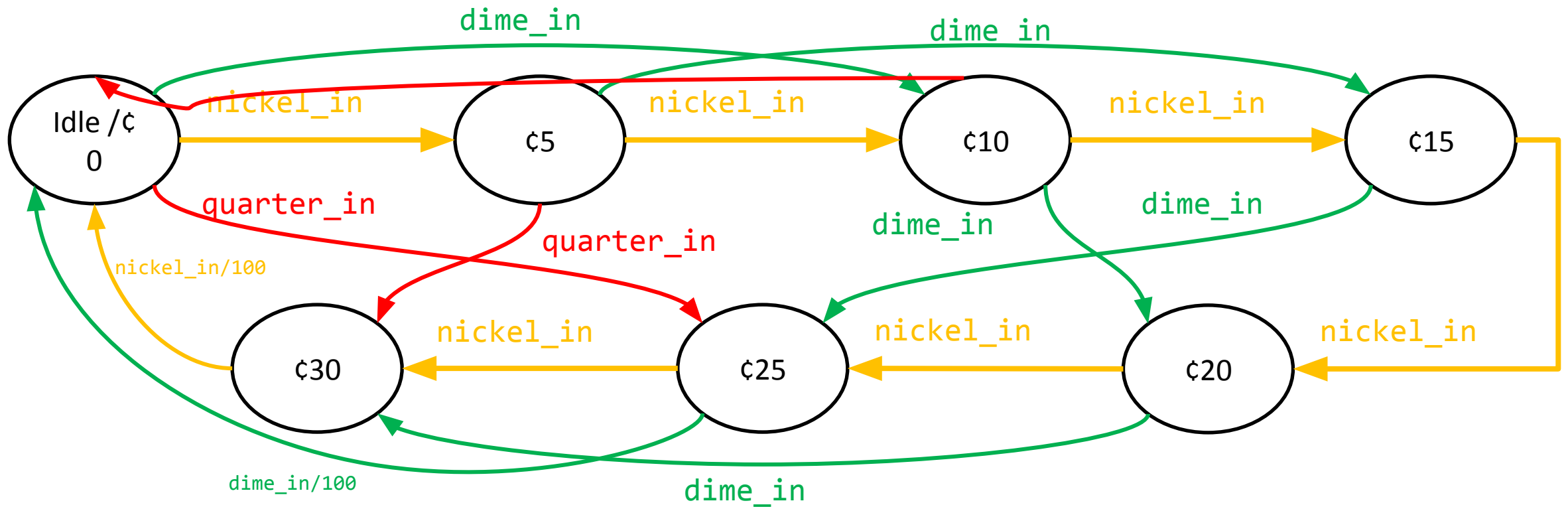

Change Dime

 


Change Quarter

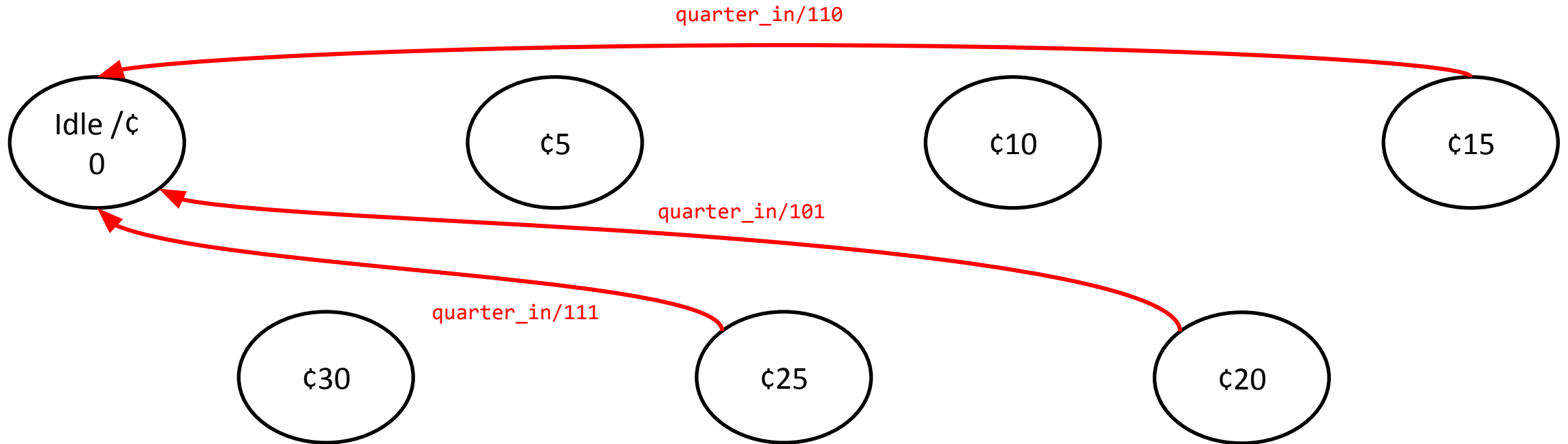

Ops! what about ¢30 with a quarter? $30+25 = 35 + 10 + 10$
We need one more state.

Owe ¢10

 

In -¢10, we owe the user ¢10.