Phasar:


$$X(t) = A \cos(\omega t + \theta)$$
 = Re { A e j \theta} e j w t }

amplitude angular freq phasar

$$Sin(w+\theta) = Cos(w+\theta-\frac{\pi}{2})$$

$$X(t) = 3 \sin(200 \pi t + \frac{\pi}{6}) = 3 \cos(200 \pi t + \frac{\pi}{6} - \frac{\pi}{2}) = 3 \cos(200 \pi t - \frac{\pi}{3}) \Rightarrow X = 3 e^{-j\frac{\pi}{3}}$$

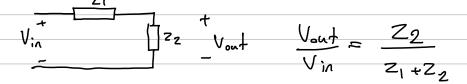
Inductor: 
$$V = L \stackrel{di}{dt} \longrightarrow V = jwL I \Rightarrow Z_L = jwL$$



Example:

$$I_{S}(t) = A \cos(\omega t)$$



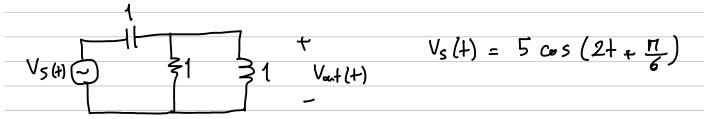

- b) How Vout will relate to Us in frequency domain?
- C) compute Vout (+)