

Name

PID

UNIVERSITY OF CALIFORNIA, SAN DIEGO

Electrical and Computer Engineering Department

ECE 65 – Fall 2021

Components and Circuits lab

Midterm Exam 1

Closed books, two double-sided cheat sheets, and calculators are allowed

Electronic devices are not allowed.

Please put all answers in the provided sheets.

Be sure to write your name and PID on **all pages**.

Please do not begin until told. **Show your work**. Good luck.

All electronic devices including cell phones must be turned off and stored away in a backpack or a purse. Anyone caught with such a device on their person during the exam will be charged with academic dishonesty.

There is only one problem on this exam.

Problem (15 points)

- a) Design a diode waveform shaping circuit that would have the below transfer characteristics.
- You can use PN junction diodes and Zener diodes with $V_{D0} = 0.7\text{ V}$, $V_Z = 4\text{ V}$, DC voltage sources, and resistors in your design.
 - **You must use a Zener diode in your design.**
 - In your circuit schematic, show v_i with the symbol of a voltage source. Clearly label the terminals that are used to measure the output.
- b) Write the possible cases of the operation of the diode(s) in your designed circuit, and for each case, include the calculation of finding v_o and the range of v_i .

Show your work.

- c) Sketch the output, $v_o(t)$, for $0 \leq t \leq 2\text{ ms}$, if the input is a 5V DC signal, $v_i(t) = 5\text{ V}$.

