

Second order circuits 001

Problem has been graded.


The switch opens at time $t = 2$ s. Before the switch opens, the system has reached steady state.

Find these voltages and currents (i.e., just before the switch opens):

$$i_{L1} = i_L(2^-) \quad v_{L1} = v_L(2^-) \quad i_{C1} = i_C(2^-) \quad v_{C1} = v_C(2^-)$$

Find these voltages and currents (i.e., just after the switch opens):
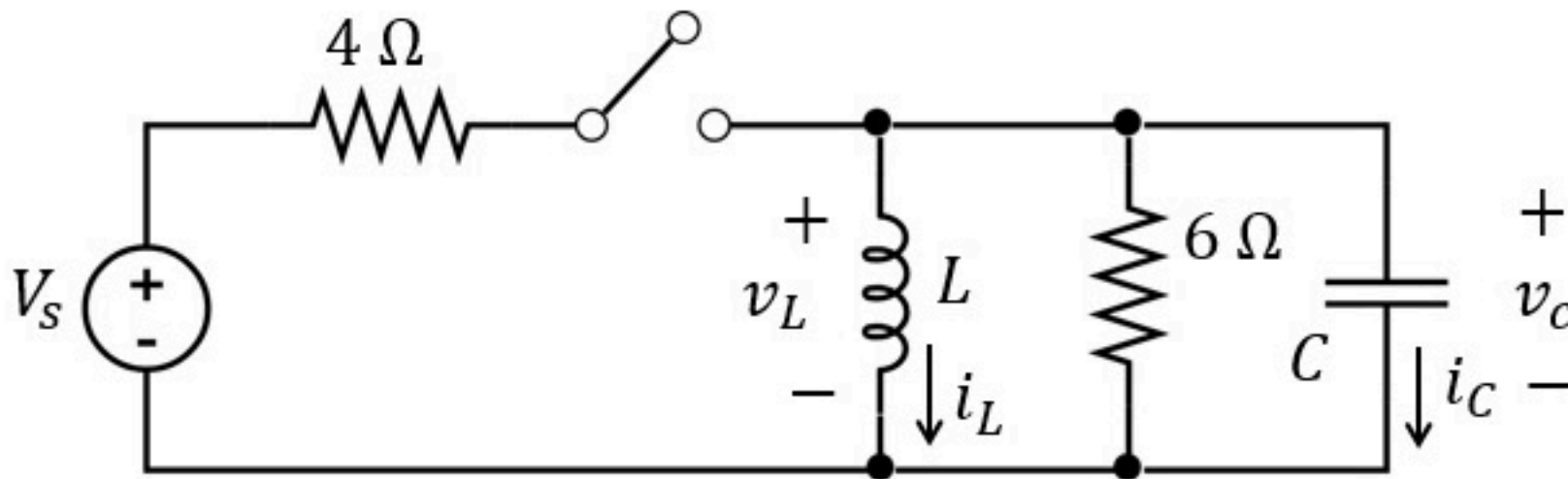
$$i_{L2} = i_L(2^+) \quad v_{L2} = v_L(2^+) \quad i_{C2} = i_C(2^+) \quad v_{C2} = v_C(2^+)$$



Given Variables:

V_s : 8 V

C : 2 nF

L : 2 mH

Calculate the following:

i_{L1} (A) :

2

✓

v_{L1} (V) :

0

✓

i_{C1} (A) :

0

✓

v_{C1} (V) :

0

✓

i_{L2} (A) :

2

✓

v_{L2} (V) :

0

✓

i_{C2} (A) :

-2

✓

v_{C2} (V) :

0

✓

Hint: In steady state, the capacitor and inductor behave as an open and short respectively.