

ECE 35, Winter 2019

Quiz 2

/ 12
------

Last name

First + middle  
name(s)


**PID**


**Instructions:**

- Read each problem completely and thoroughly before beginning.
- All calculations need to be done on these sheets.
- Write your answers in the answer boxes for each question. Make sure you list units!
- Answers without supporting calculations will receive zero credit.



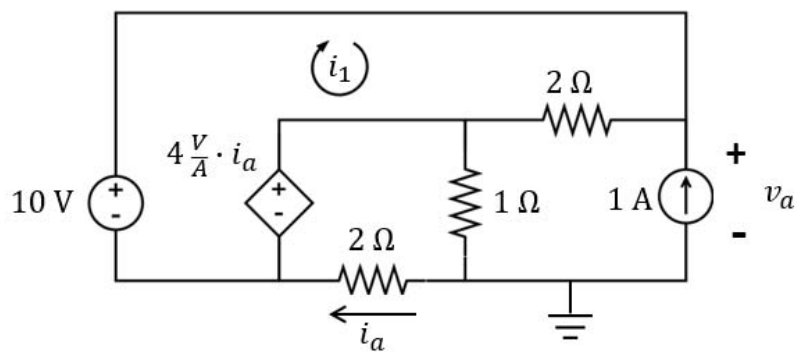(1) You must use nodal analysis to solve this problem. Find the value of voltage  $v_a$  and of mesh current  $i_1$ . (6 points)



$v_a$


$i_1$

- (2) (a) For figure (a) below, find the value of  $k$  such that the Thevenin equivalent resistance between  $a$  and  $b$  is equal to  $2\ \Omega$ .  
(3 points)


$k$

- (b) Someone chose a value of  $k$  that resulted in a Thevenin equivalent resistance of  $1\ \Omega$  between  $a$  and  $b$  for part (a). With this same value of  $k$ , what load resistance  $R_L$  should be attached between  $c$  and  $d$ , in figure (b), to get the maximum power dissipated in this  $R_L$ ? (3 points)

$R_L$

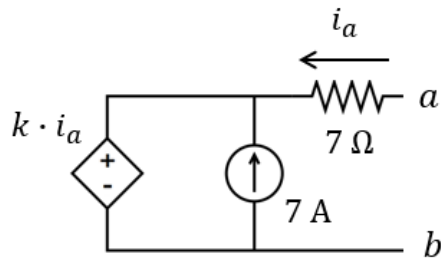

(a)

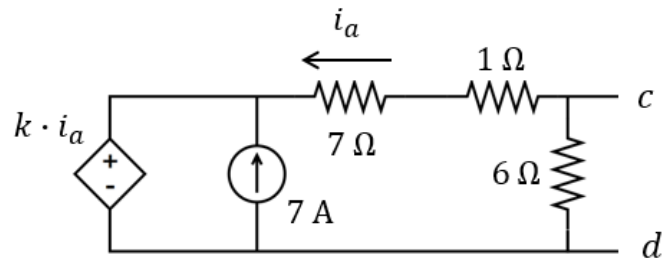

(b)