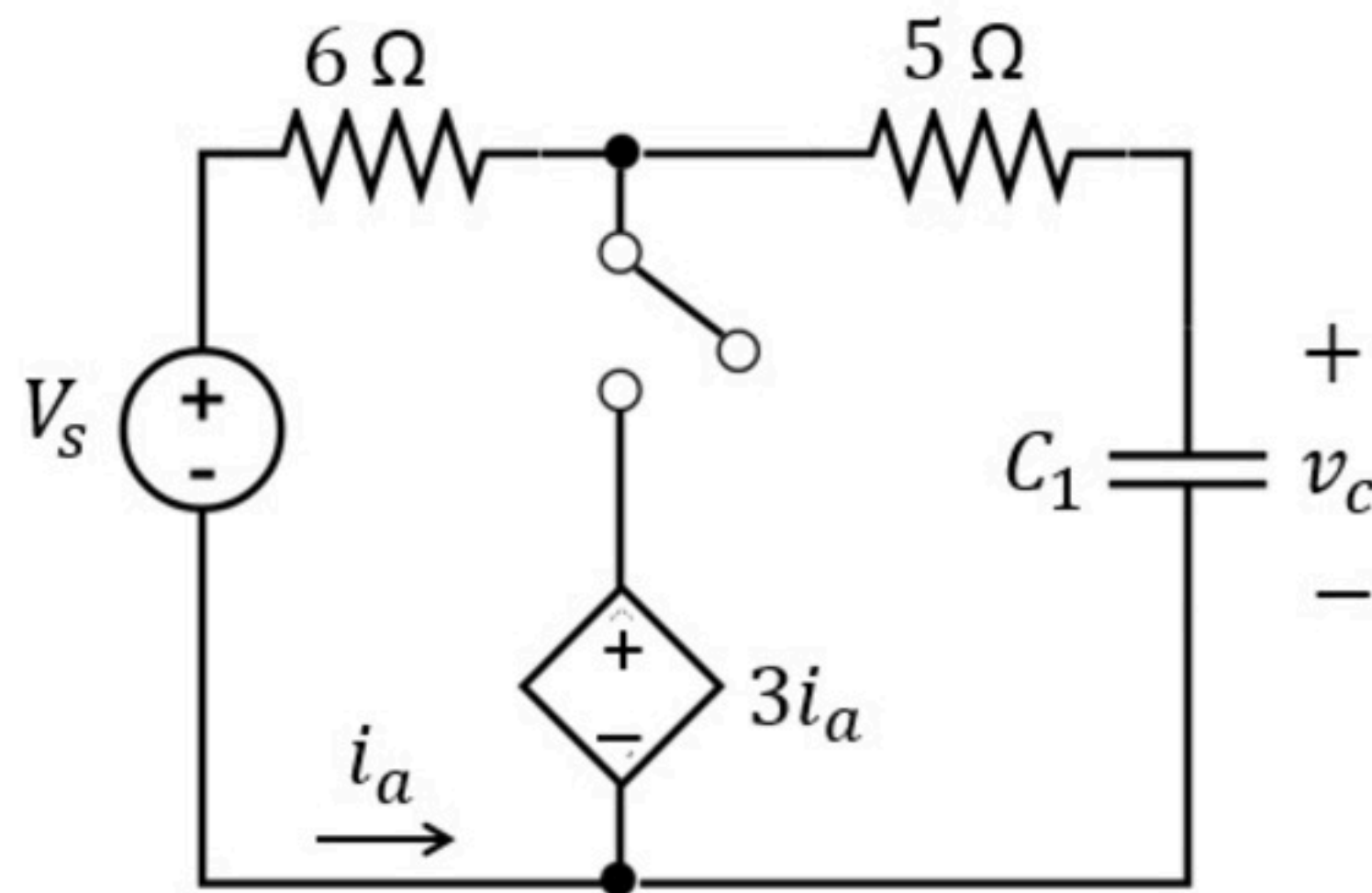


First order circuits 003

Problem has been graded.

The switch has been open for a long time before it closes at time $t = 0$.

Find the capacitor voltage $v_c = A + B \cdot e^{-t/\tau}$ for $t > 0$.



Given Variables:

V_s : 15 V

C_1 : 0.1 nF

Calculate the following:

A (V) :

-15



B (V) :

30



τ (ns) :

0.5



Hint: First find the capacitor voltage at $t = 0^-$. Note where A and B are.