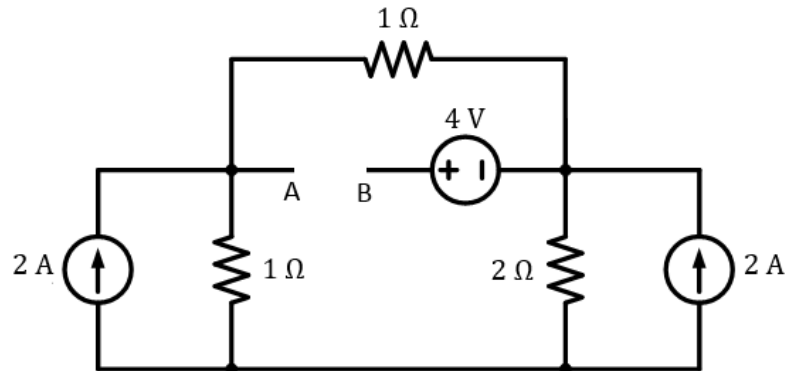



Practice Final

Problem 1




- Find the Thevenin equivalent model between A and B.
- If we were to place a $1.5\ \Omega$ resistor between A and B in the circuit above, what is the current through that resistor (measured from A to B)?

Problem 2

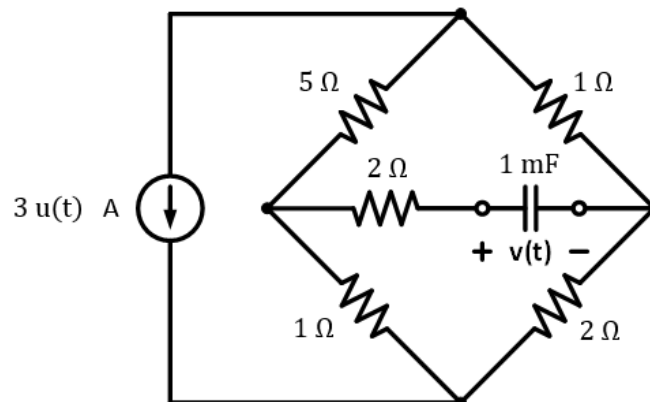


- Find $v(t)$ for $t \geq 0$.
- Sketch the waveform of $v(t)$ for $t \geq 0$.

Problem 3

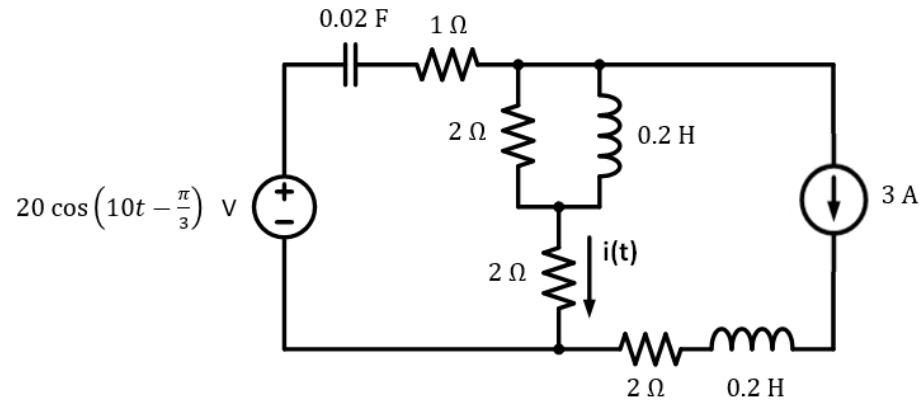


Find the steady-state response of $i(t)$.

Problem 4

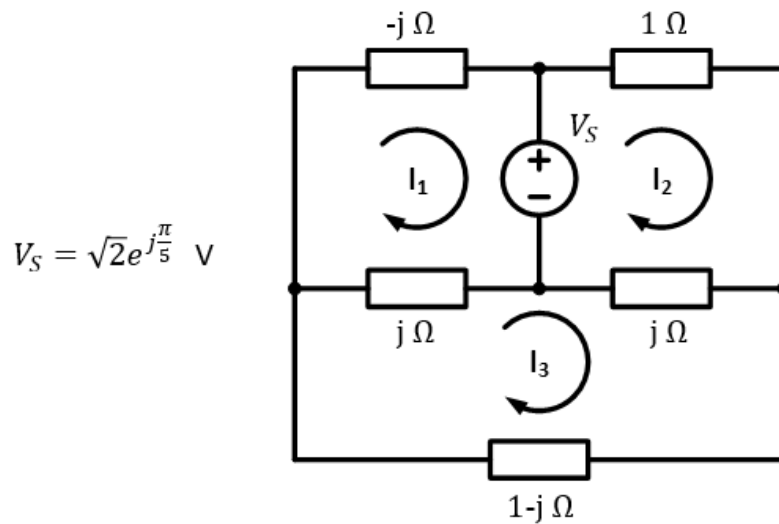

- Find the values of the mesh current phasors, I_1 , I_2 , and I_3 (in polar form).
- Find the complex power supplied by V_S .

Problem 5

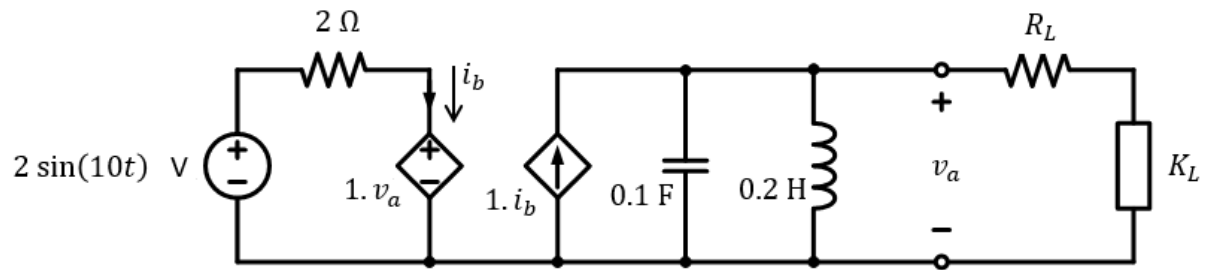

A load ($R_L + K_L$) is connected to a power distribution network consisting of a resistor, inductor, capacitor and AC voltage source. The load itself includes a resistor R_L in series with a mystery element K_L , where K_L is either a capacitor or an inductor. The goal is to maximize the average power delivered to the load.

- Determine the values of R_L and K_L for the circuit that cause maximum power transfer to the load.
- Determine the mystery element (a capacitor or an inductor; and its value).
- Calculate the maximum power transferred to the load.