

UNIVERSITY OF CALIFORNIA, SAN DIEGO

Electrical and Computer Engineering Department

ECE 65 – Spring 2019

Components and Circuits lab

Midterm Exam

Closed books, two double-sided cheat sheets, and calculators are allowed

Electronic devices are not allowed.

Please put all answers in the provided sheets.

Be sure to write your name and PID on **all pages**.

Please do not begin until told. Show your work. Good luck.

All electronic devices including cell phones must be turned off and stored away in a backpack or a purse. Anyone caught with such a device on their person during the exam will be charged with academic dishonesty.

Problem 1. (10 points)


Consider an op-amp connected in the inverting configuration to achieve a closed-loop gain of 40 dB (this is the absolute value of the voltage gain) using $1\text{ k}\Omega$ and $100\text{ k}\Omega$ resistors. A load resistance R_L is connected from the output to ground. A sine-wave signal of peak amplitude V_p is used as the input signal.

Assume an ideal op-amp with $V_{sat} = \pm 10\text{V}$ and $I_{out_{max}} = 20\text{ mA}$, and answer the following questions. Show your work.

- a) For $R_L = 400\ \Omega$, what is the maximum possible V_p while an undistorted output sinusoidal signal is obtained?
- b) If it is desired to obtain an output sinusoidal signal with a peak amplitude of 10V , What values of R_L are allowed?

Problem 2. (10 points)


In the following circuit, find the values of the collector, base and emitter currents and the collector, base and emitter node voltages. Assume $\beta = 100$, $V_{D0} = 0.7\text{ V}$, $V_{sat} = 0.2\text{ V}$.

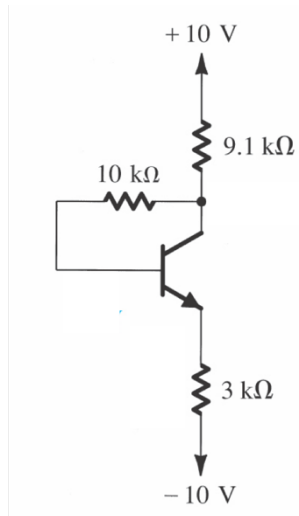

Problem 3. (10 points)

In the circuit below, $v_i(t) = 4 \sin(\omega t)$ where $\omega = 1000$ rad/s, $v_c(0) = 0$, $v_o(0) = 0$.

Use $V_{D0} = 0.7$ V, $V_Z = 2.3$ V.

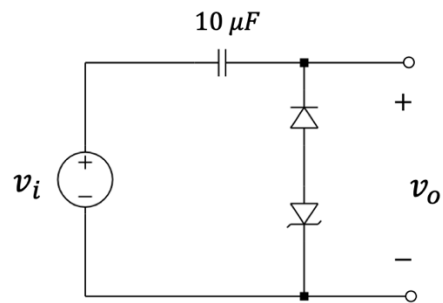

- a) What is the value of $v_o(t)$ at $t = 2$ ms?
- b) What is the value of $v_o(t)$ at $t = 6$ ms?